
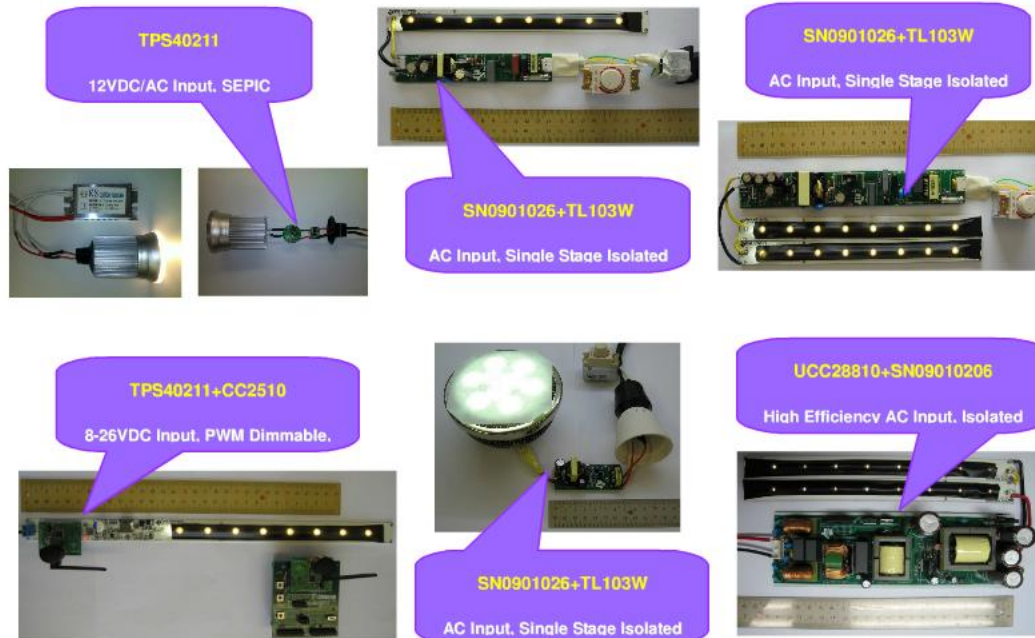


TI

LED Lighting Power Reference Designs

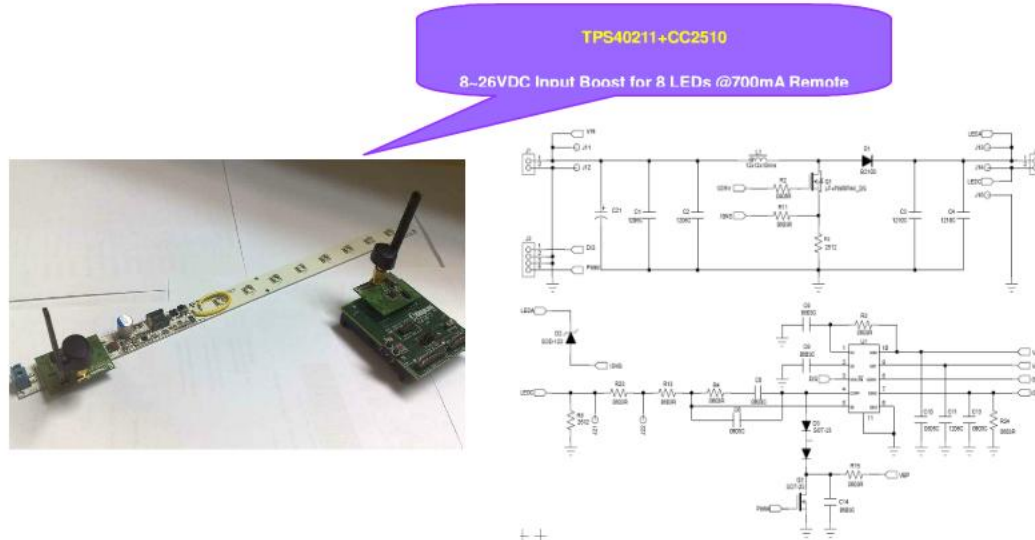


1. DC Boost LED Driver with Remote Control



2. Single Stage AC/DC Isolated LED Driver

Application	TI Parts	Output Power	Input Voltage	Output Current
AC/DC Isolated LED Driver with Front-End (TRIAC) Dimming Compatible	SN0109026+ TL103W	10W/ 25W/ 50W	90-265 Vrms	350mA~500mA Up to 700mA

Figure: Simplified Application

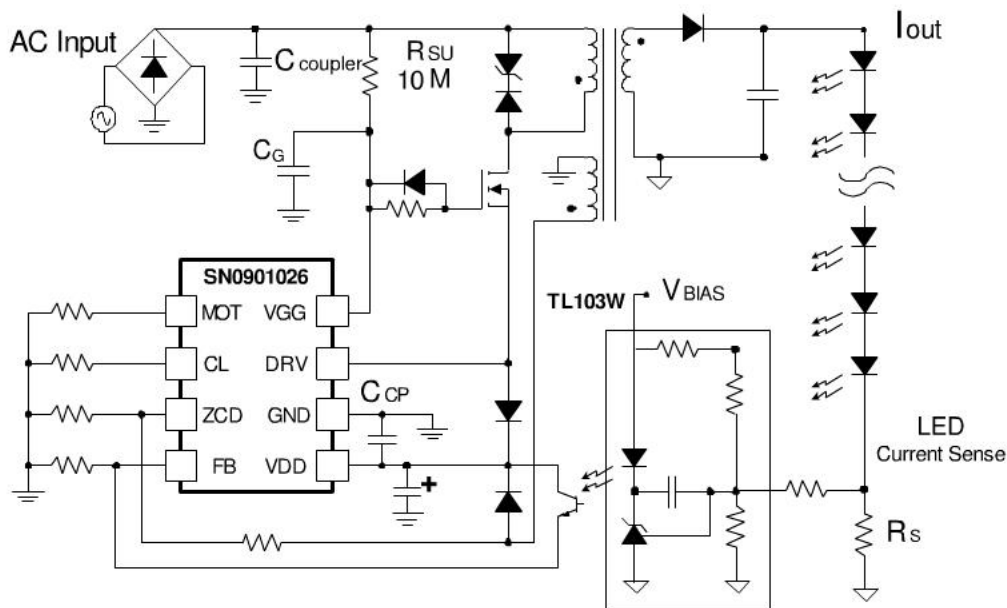

Key Features and Benefits:

- **Single Stage Design**
 - Requires only one Simple Power Converter
- **Phase-Angle “TRIAC” Dimmable**
 - Operates down to Minimum Input Setting
 - Can be used with Traditional Wall Dimmers
- **Natural PF Correction and Low THD**
 - Operates down to Minimum Input Setting
 - Can be used with Traditional Wall Dimmers
- **High Efficiency & Current Accuracy**
 - Minimizes thermal management
- **Isolated Design meets Safety Requirement**

3. 10W Design (SN0901026+TL103W)





10W Design SN0901026+TL103W

90V to 265VAC Input AC/DC for 9 LEDs @350mA

Vin	PF	Efficiency	THD	Iout
90V	0.998	79.7%	5.85%	353mA
110V	0.997	83.5%	5.02%	357mA
220V	0.985	84.5%	4.27%	356mA
240V	0.979	85.1%	4.31%	358mA
265V	0.968	85.3%	5.08%	358mA

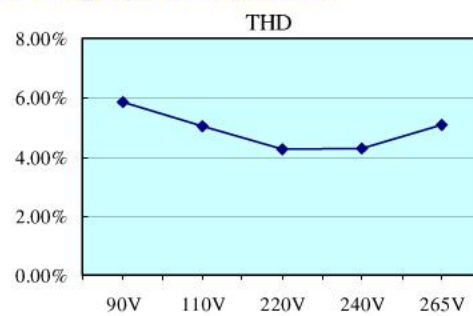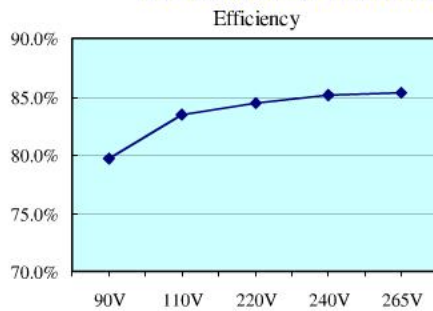Efficiency, THD, Power Factor Vs Line Voltage 9pcs LEDs at 350mA



4. 25W Design (SN0901026+TL103W)





25W Design SN0901026+TL103W

90V to 265VAC Input AC/DC for 10 LEDs @700mA

Vin	PF	Efficiency	THD	Iout
90V	0.998	77.4%	6.41%	696mA
110V	0.972	83.7%	5.41%	701mA
220V	0.974	85.1%	3.04%	706mA
240V	0.96	85.8%	4.03%	703mA
265V	0.939	86.5%	5.25%	700mA

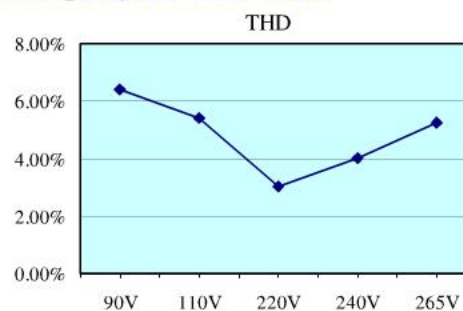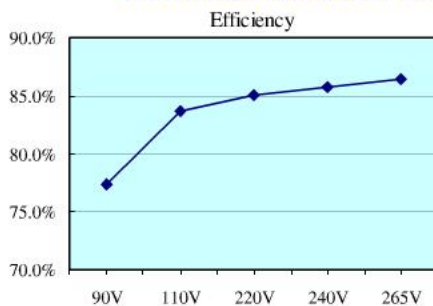
Efficiency, THD, Power Factor Vs Line Voltage 10pcs LEDs at 700mA



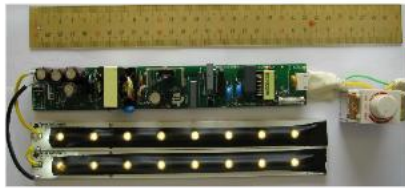5. 50W Design (SN0901026+TL103W)



50W Design SN0901026+TL103W

90V to 265VAC Input AC/DC for 20 LEDs @700mA




Vin	PF	Efficiency	THD	Iout
90V	0.999	84.6%	4.27%	700mA
110V	0.997	85.7%	4.36%	701mA
220V	0.965	86.6%	6.73%	700mA
240V	0.952	86.6%	7.93%	702mA
265V	0.931	86.3%	9.54%	701mA

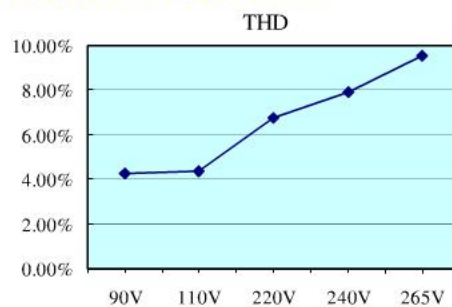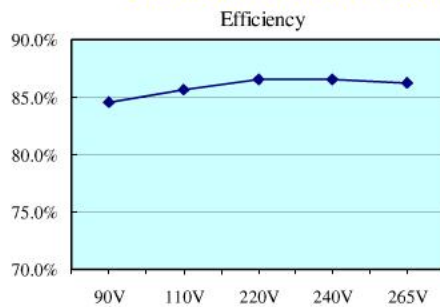Efficiency, THD, Power Factor Vs Line Voltage 20pcs LEDs at 700mA




6. 100W Non-Isolated PFC+ Buck LED Driver

Application	TI Parts	Output Power	Input Voltage	Output Current
PR788: High Efficiency AC Power Factor Corrected, Dimmable LED Driver	UCC28810/11	100 W	90-264 Vrms	Up to 1000 mA

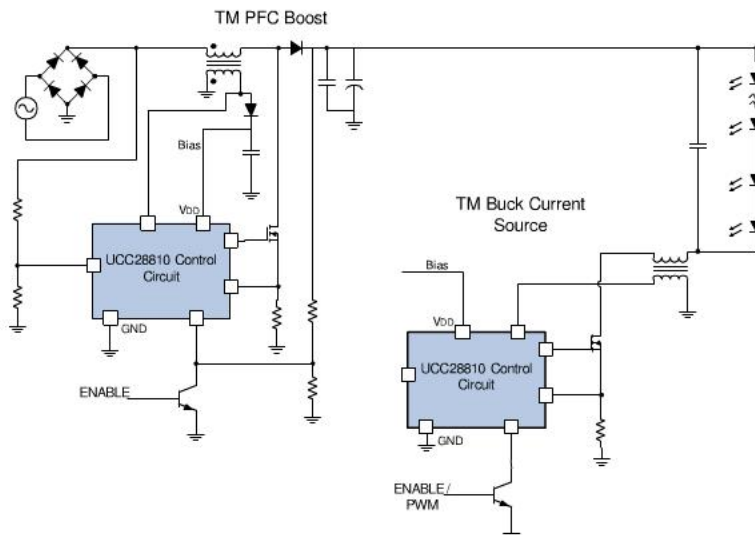

Benefits:


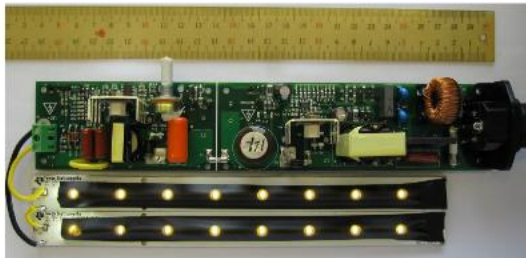
- **Extremely Robust**
- The LEDs are Well Protected
- **Extremely Simple to Use**
 - TM Buck Inherently Stable
 - No Compensation Required
- **High Efficiency**
 - High Power Density
- **Fast LED Current Response**
 - Well Suited for PWM Dimming



100W Non-Isolated Design (UCC28810+28811)


Parameter	Condition	Min	Typ	Max	Units
Vin RMS		90		264	VRMS
PFC Vout		235		415	VDC
PF	80-100W	0.95	0.97		
Pout, LED Dvr		45	80	100	W
Iavg, LED	Setpoint: No PWM Dimming	0.84	0.90	0.96	A
Iavg, LED Line Regulation	90-264VRMS			0.03	A
Shutdown Thresh	PFC: J8 Pin 1 Buck: J9 Pin 1 #	0.72		1.1	V
PWM Thresh		0.72		1.3	V
PWM Frequency	Input Signal J9 Pin 3	200		1K	Hz
Efficiency	(Typ-Full Load)	90	93		%

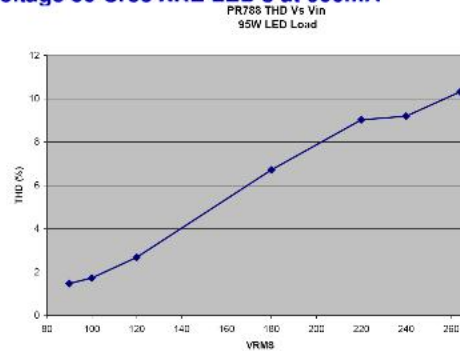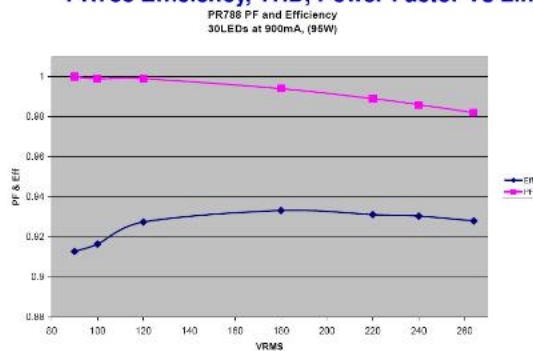PR788 Efficiency, THD, Power Factor Vs Line Voltage 30 Cree XRE LED's at 900mA



7. 100W Isolated PFC+ QR-Flyback LED Driver

Application	TI Parts	Output Power	Input Voltage	Output Current
High Efficiency AC/DC Isolated Factor Corrected, Dimmable Driver	UCC28810/11 + SN0901026	100 W	90-264 Vrms	Up to 700 mA

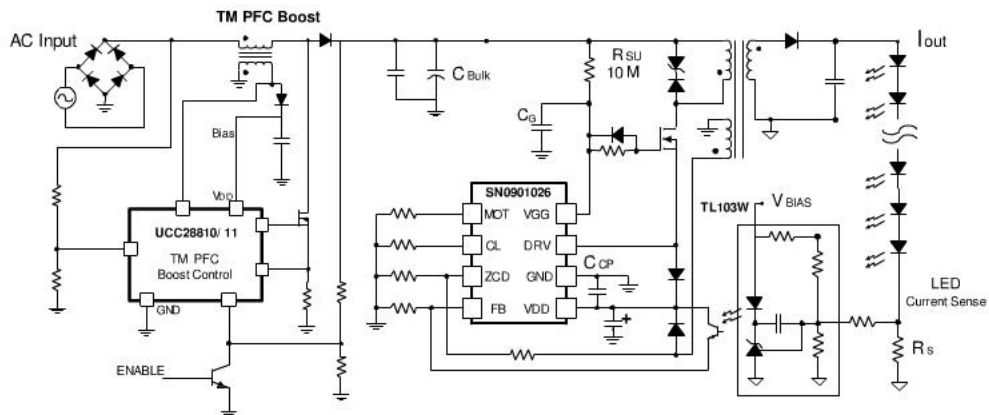

100W Design (UCC28810/11+SN0901026)





100W Design UCC28810+SN09010206


90V to 265VAC Input AC/DC for 40 LEDs @700mA

Vin	PF	Efficiency	THD	Iout
90V	0.999	88.5%	2.16%	701mA
110V	0.996	89.2%	3.91%	701mA
220V	0.951	90.2%	6.09%	702mA
240V	0.931	90.3%	6.78%	702mA
265V	0.91	90.4%	7.32%	702mA

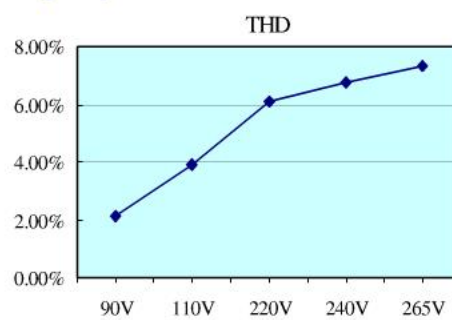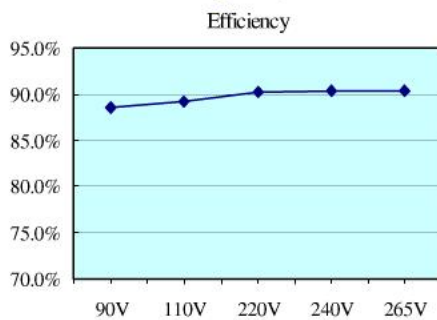Efficiency, THD, Power Factor Vs Line Voltage 40pcs LEDs at 700mA



8. 25W UCC28810 Design SCH

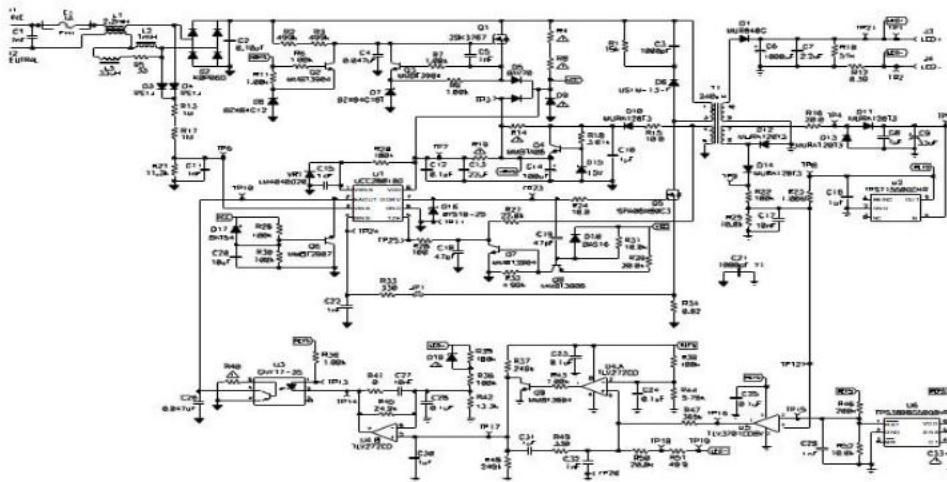

- 效率較高 > 0.8 (可以達到 0.85, 滿載時)
- 功率因素 > 0.9 (可以達到 0.97)
- 電流穩定性好
- 可實現 Triac 調光

