


CDCI6214: Low Oscillation Issue

LVDS driver

Current controlled by
diffbuf_ibias_trim bits


Controlled by 1.5V Ido

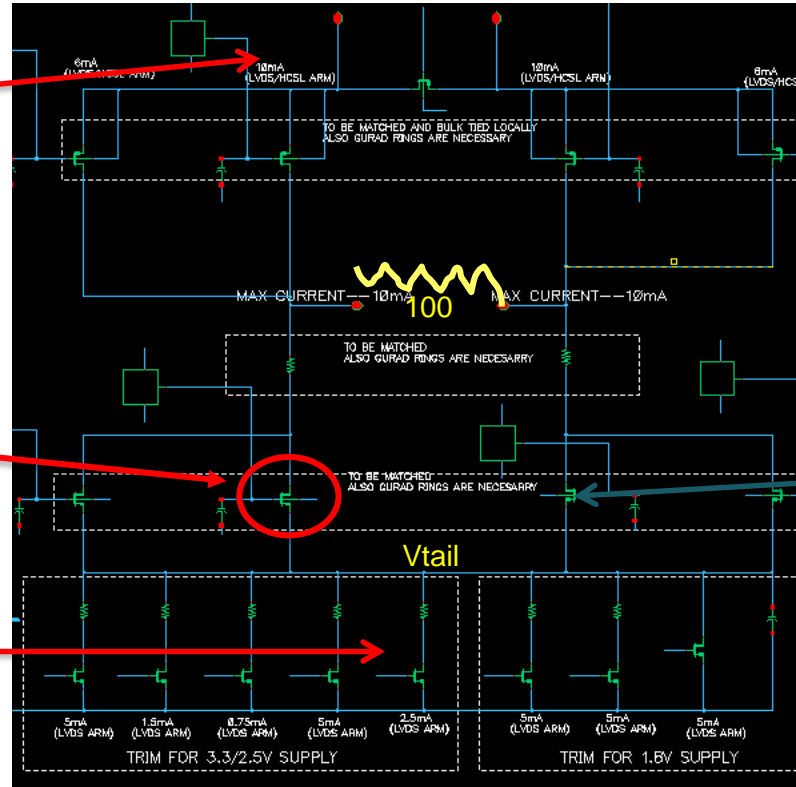These arms control
the CM voltage,
controlled by cmtrim



Higher common-mode voltage setting (which increases the tail resistance) along with higher bias current setting pushes the V_{tail} voltage higher and that pushes the NMOS into OFF state causing both V_{op} and V_{on} to go to supply rail and it will either not swing or swing less

Output LVDS Driver functionality

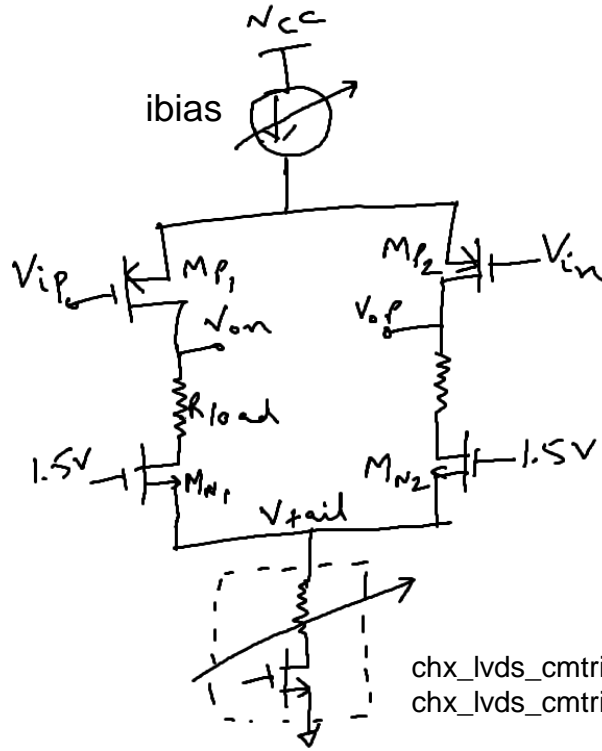


chx_lvds_cmtrim_dec reduces the tail resistance
chx_lvds_cmtrim_inv increases the tail resistance


- MP1 and MP2 are input pair
- MN1 and MN2 are protection transistors for bottom tail resistors (which decides the output CM voltage)
- For MN1 and MN2 to be ON, Vtail voltage needs to be lower than certain voltage otherwise it will turn OFF and Vop/Von will go close to Vcc and driver will not be functional
- For higher ibias setting (to get higher output swing), tail resistor needs to be reduced (chx_lvds_cmtrim_dec).

Simulation Results

net015 and net073 are
Vop and Vom nets

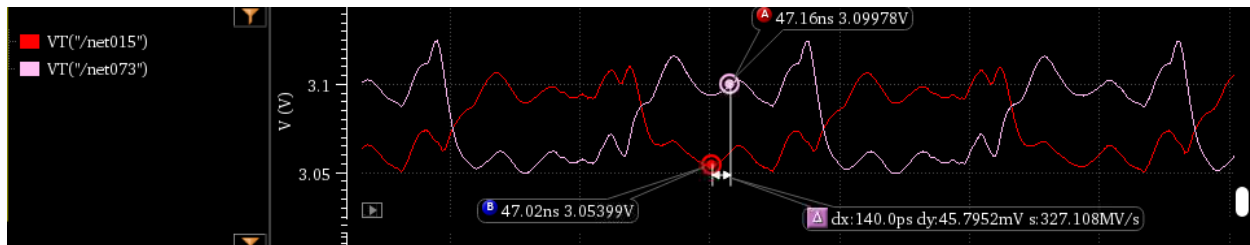

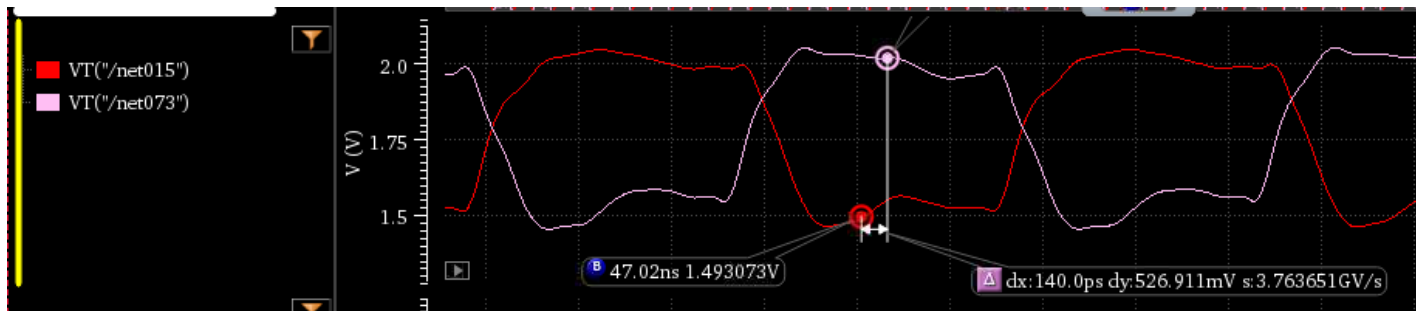Low swing with lvds_cmtrim_inc=10, diffbuf_ibias_trim=3h



Good swing with lvds_cmtrim_inc=00, diffbuf_ibias_trim=3h

LVDS driver recommended settings

- `chx_diffbuf_ibias_trim = 0`
- `chx_lvds_cmtrim_inc = 0`
- `chx_lvds_cmtrim_dec = 0`

If needed higher swing, use below:

- `chx_diffbuf_ibias_trim = 3`
- `chx_lvds_cmtrim_inc = 0`
- `chx_lvds_cmtrim_dec = 1, 2 or 3` depending on common-mode needs