

Operational Amplifier Stability

Part 6 of 15: Cap Load Stability: R_{iso}, High Gain & CF, Noise Gain

By Tim Green

Strategic Development Engineer, Burr-Brown Products from Texas Instruments

Part 6 of this series is the beginning of a new Electrical Engineering tune "There must be six ways to leave your capacitive load stable". The six ways are R_{iso}, High Gain & CF, Noise Gain, Noise Gain & CF, Output Pin Compensation, and R_{iso} w/Dual Feedback. Part 6 will focus on the first three of these stability techniques for capacitive loading on the output of an op amp. Parts 7 & 8 will cover the remaining techniques in detail. Each technique presented will use familiar tools from our stability analysis tool kit and each technique will be presented by first order analysis, confirmed through Tina SPICE loop stability simulation, checked by the V_{OUT}/V_{IN} AC transfer function analysis in Tina SPICE and finally sanity-checked by the Transient Real World Stability Test run in Tina SPICE. Each of the techniques has been confirmed to work as predicted in real-world, actually-built circuits at some time over the last 23 years. However, due to resource limitations, each circuit specifically presented here has not been built, but rather is left to the reader as an exercise or the application of each technique to his/her own individual application (i.e. analyze, synthesize, simulate, build and test).

Op Amp Examples and Computing R_o

Our op amp of the day for the stability examples in this part will be a high voltage, up to +/-40V, operational amplifier, the OPA452. Such a "Power Op Amp" is often used for driving piezo actuators which, as you may have guessed, are mostly purely capacitive in nature. A few key specifications for this amplifier are listed in Fig. 6.1. The one key parameter missing is R_o, the small signal AC open-loop output resistance, which is *EXTREMELY* key to simplifying stability analysis when driving capacitive loads. Since the data sheet does not have this parameter listed in any form we will need to extract the value for R_o through measurement. Since the SPICE model for this amplifier was built by W. K. Sands of Analog & RF Models (<http://www.home.earthlink.net/%7Ewksands/>) we are going to measure R_o using Tina SPICE. The W. K. Sands SPICE models have been proven time and time again to be very accurate to the data sheet specifications and, even more importantly, the actual silicon part!

OPA452

Supply: +/-10V to +/-40V

Slew Rate: +7.2V/us, -10V/us

V_{out} Saturation:

I_o=50mA, (V-)+5V, (V+)-5.5V

I_o=10mA, (V-)+2V, (V+)-2V



Fig. 6.1: OPA452 Key Specifications

In Fig. 6.2 we mark on Open Loop Gain and Phase vs Frequency plot of the OPA452 with the “operating point” for testing R_O . By testing for R_{OUT} at this “operating point” (a frequency and gain point where there is no loop gain) $R_{OUT} = R_O$ (see Part 3 of this series for a detailed discussion of R_O and R_{OUT}).

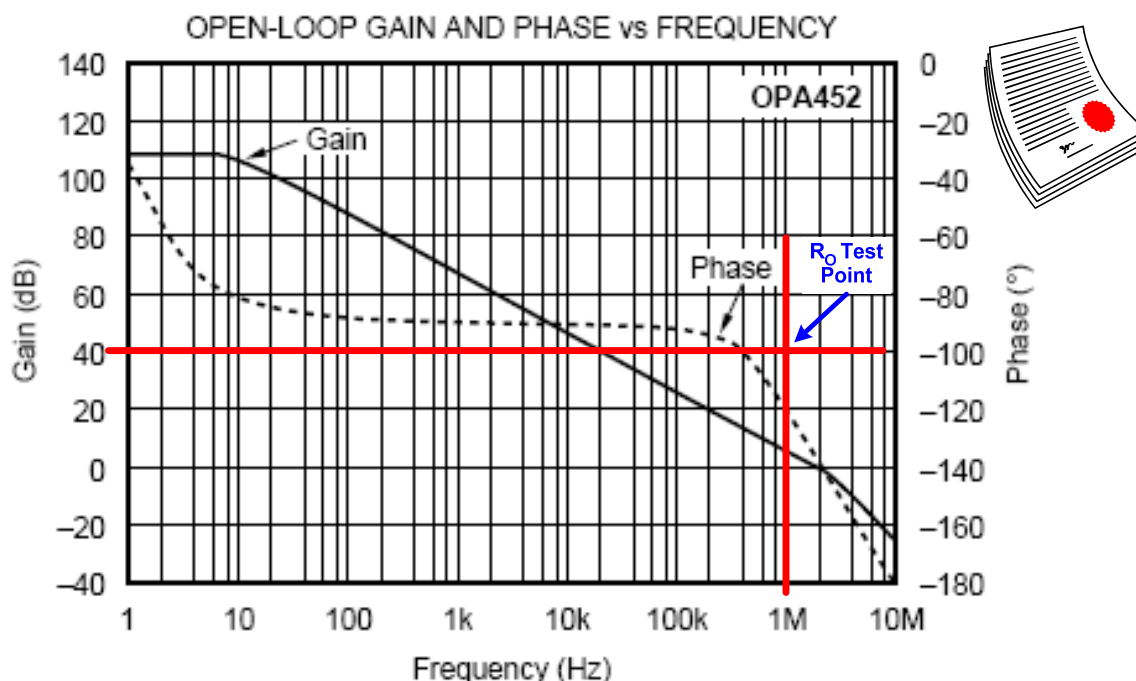


Fig. 6.2: OPA452 AoI Curve with R_O Measurement “Operating Point”

Since we are only testing for R_O in Tina SPICE there is a “yet to be introduced trick” that works well in SPICE as shown in Fig. 6.3. First we set the amplifier circuit to our selected gain point of 100. We AC couple our source through C1 and limit the maximum current driven into the op amp output through R3. Next a current meter (ammeter), A1, is inserted in series with our excitation source. By placing a voltage probe, VOA, on the output of the op amp we can easily calculate R_{OUT} , which is R_O in our test configuration. This is a variation on the “Measuring R_O – Drive Method” presented in Part 3 of this series.

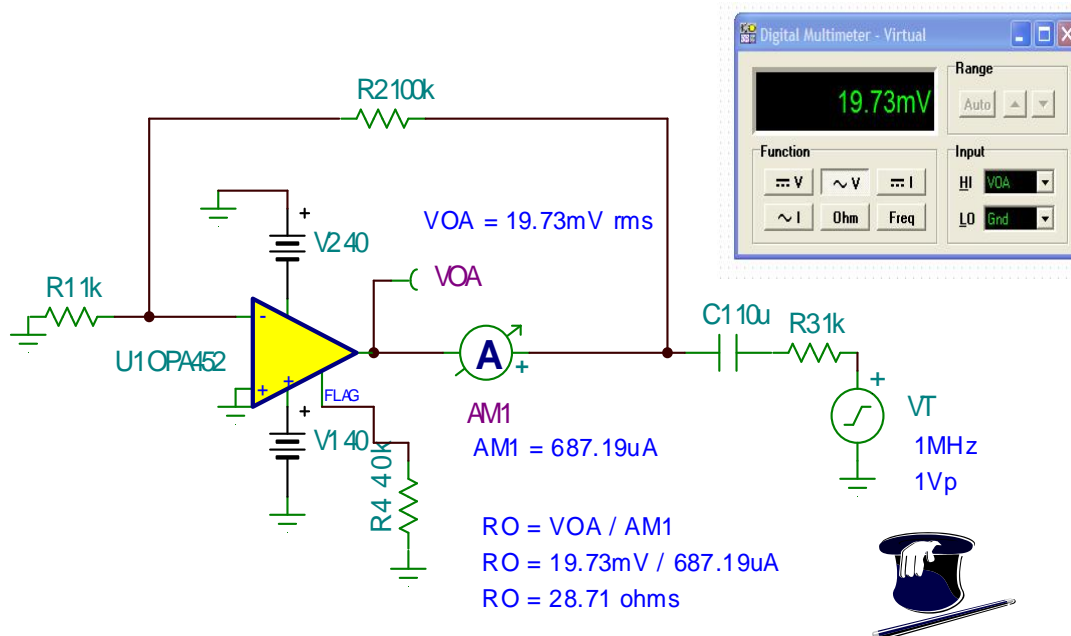


Fig. 6.3: Tina SPICE - R_O Test Technique 1

As a double check of our R_O measurement we will use the “Measuring R_O - Load Method” from Part 3 of this series to measure R_O as shown in Fig. 6.4. The trick we present here is that it can all be done in one SPICE run by using one AC signal source, VT, and two identical amplifiers, U1 and U2, with one amplifier, U1, unloaded and the other op amp, U2, loaded. The result shown of $R_O=28.67$ ohms agrees with our technique used for measuring R_O in Fig. 6.3. We will use $R_O=28.7$ ohms for the OPA452.

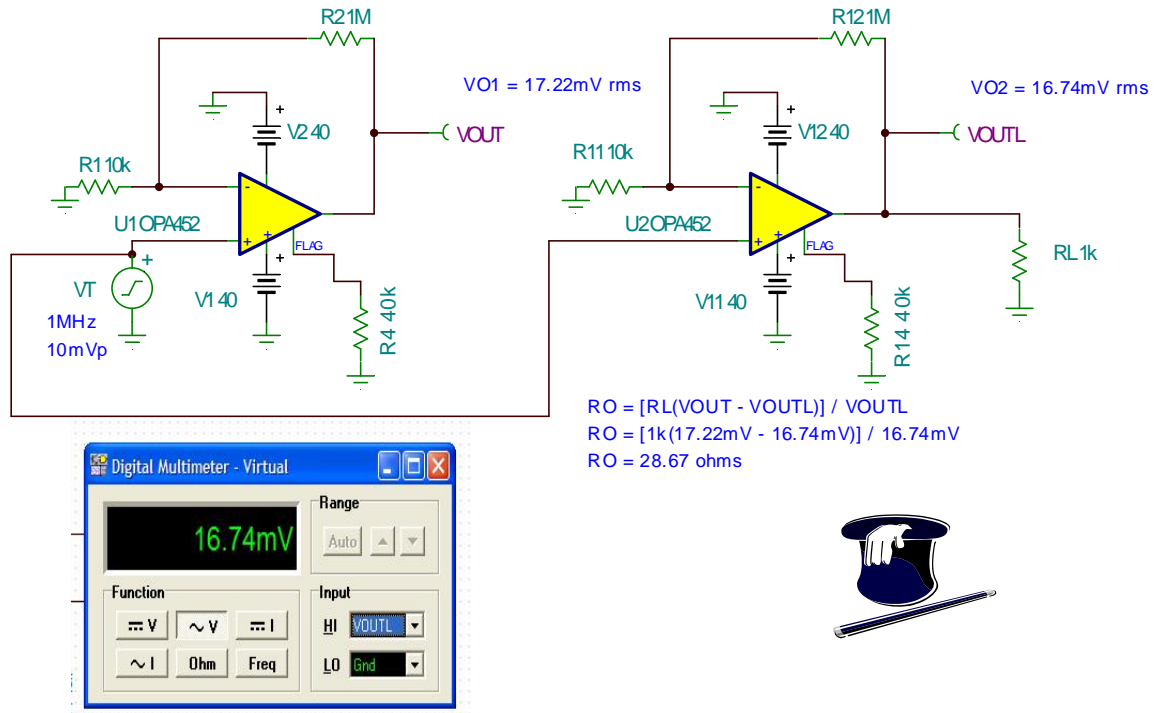


Fig. 6.4: Tina SPICE - R_O Test Technique 2

Modified Aol Model

Our stability analysis of the effects of capacitive loading on an op amp will be simplified by the introduction of the “Modified Aol Model”. As shown in Fig. 6.5 the data sheet Aol curve is followed by the op amp output resistance, R_O . The capacitive load, CL, in conjunction with R_O will form an additional pole in the Aol plot and may be represented by a new “Modified Aol” plot as shown in Fig. 6.6.

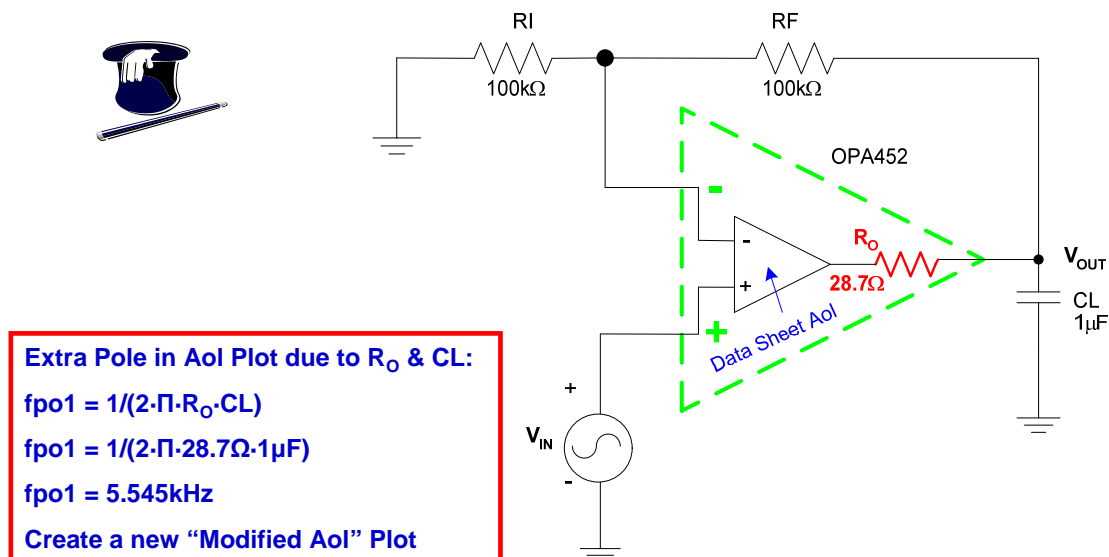


Fig. 6.5: Modified Aol Model with CL

A Bode plot showing the open-loop gain (Aol) of the OPA452 op-amp and its modified version due to a closed-loop (CL) feedback. The y-axis is Gain (dB) from -60 to 120. The x-axis is Frequency (Hz) on a log scale from 1 to 10M. The red line represents the OPA452 Aol, and the blue line represents the Modified Aol due to CL. The blue line has a steeper slope, indicated by a purple arc and the text '40dB/Decade Rate-Of-Closure'. A green line at 0 dB is labeled '1/β'. A red circle with 'STABLE' inside is shown. A vertical orange line marks the frequency 'fcl'. A small icon of a graduation cap and a pencil is in the top right corner.

Now we will check our first order analysis by using Tina SPICE. The circuit shown in Fig. 6.7 breaks the loop for a loop stability check by opening the loop for AC at the minus input of the op amp. This allows an easy way to plot the “Modified Aol” due to the CL load interacting with R_O .



In Fig. 6.8 we see that our first order analysis is vindicated. The actual second pole in the “Modified Aol” plot is at 5.6kHz. We had predicted a second pole due to CL at 5.45kHz from our first order analysis.

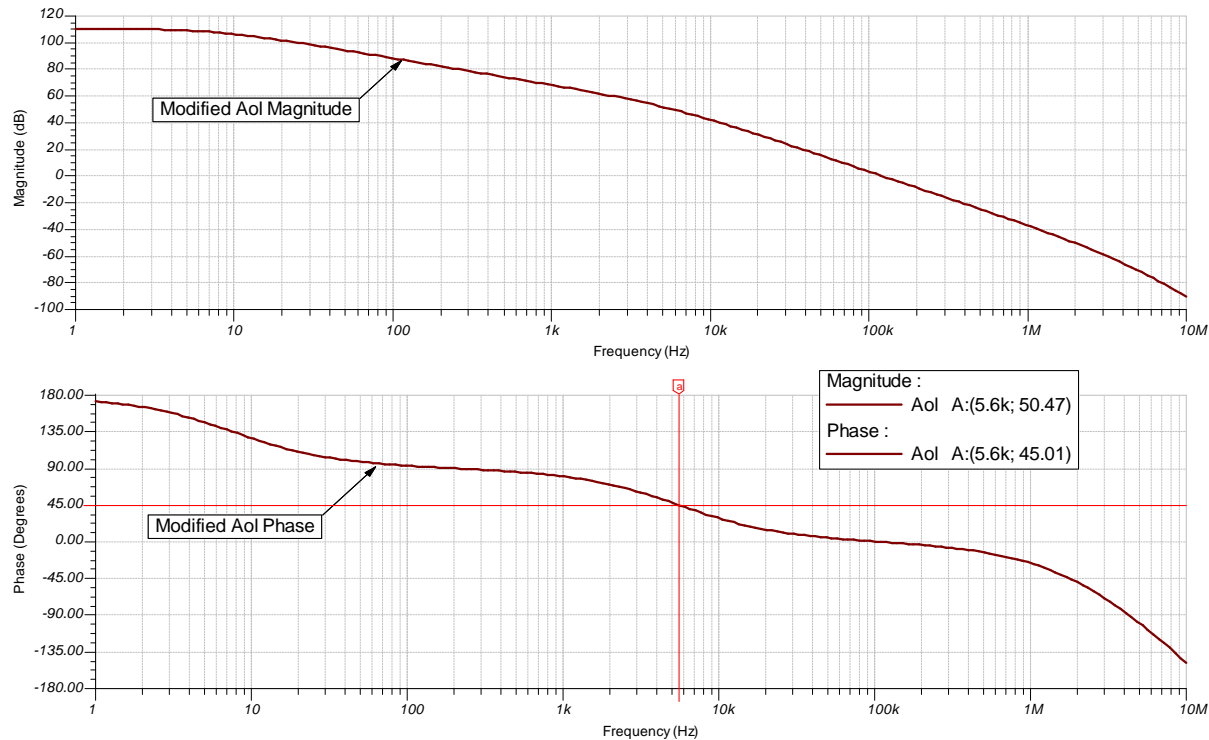


Fig. 6.8: Tina SPICE - Modified Aol Plots with CL

To enforce the idea that our first order analysis was right in predicting instability a loop gain analysis was performed as shown in Fig. 6.9. The loop gain phase clearly indicates we are headed for trouble since it hits zero at fcl.

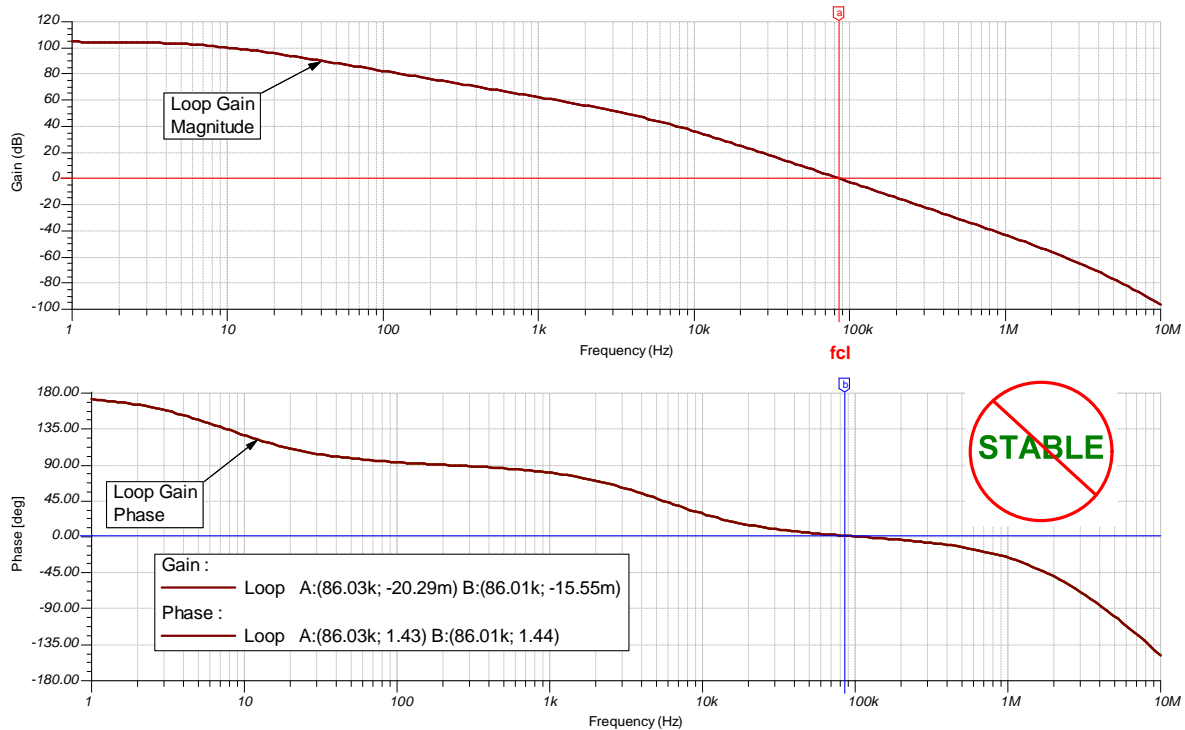


Fig. 6.9: Tina SPICE - Loop Gain Plots with CL

Fig. 6.10 details a Transient Real World Stability Test circuit we will run in Tina SPICE. Our loop gain plot predicts instability as did our first order analysis. For completeness we will look at the transient response of our circuit.

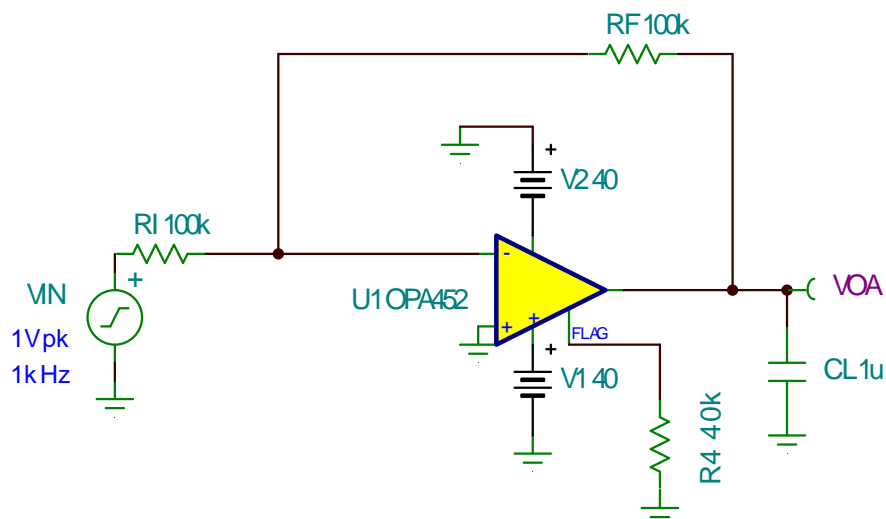


Fig. 6.10: Tina SPICE - Transient Test with CL

The results of our Transient Tina SPICE simulation in Fig 6.11 confirm that this circuit is in “stability jeopardy” if we do not do something to make it stable.

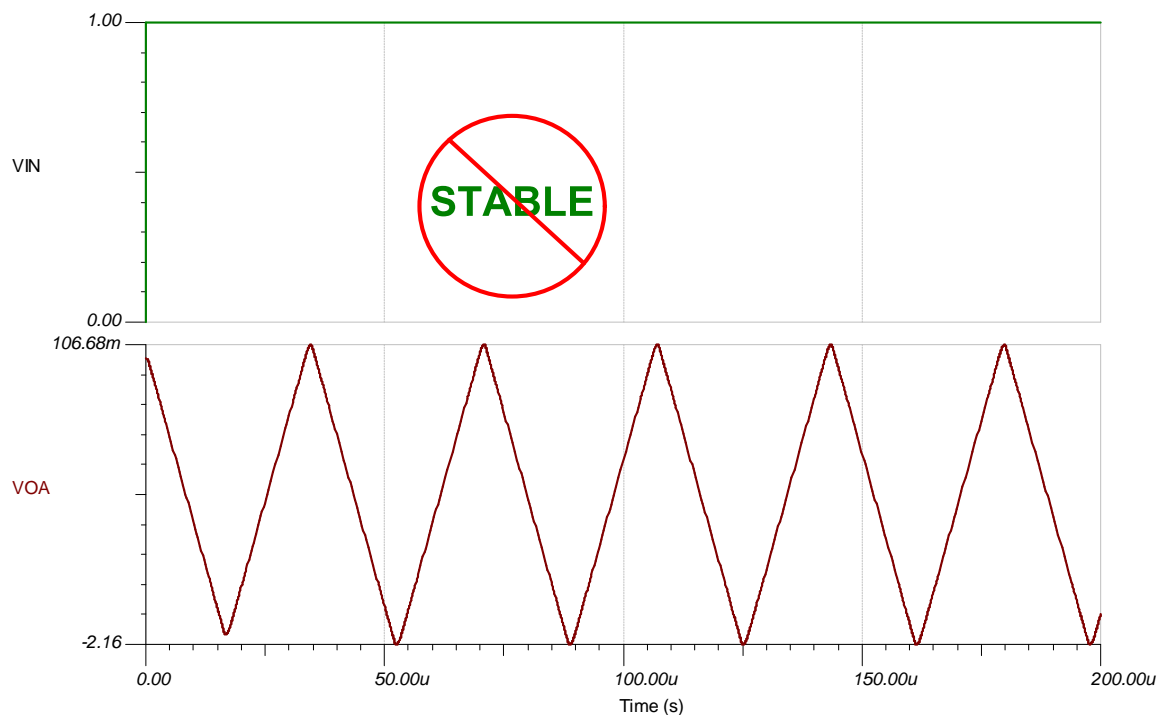


Fig. 6.11: Tina SPICE - Transient Test Results with CL

Before we try to compensate our unstable, capacitively loaded op amp circuit we should consider if the load resistance will affect the location of the second pole in our “Modified AoI” plot due to R_O and CL . As shown in Fig. 6.12 the effect of the load resistance, R_L , is to appear in parallel with the op amp output resistance, R_O , which increases the frequency location of the pole. The final pole location will be now determined by the parallel combination of R_O and R_L along with the load capacitance CL . From this we form a handy rule of thumb based on our favorite decade approach. If $R_L > 10R_O$ we can ignore the effect of R_L and the second pole will be predominantly determined by R_O and CL .

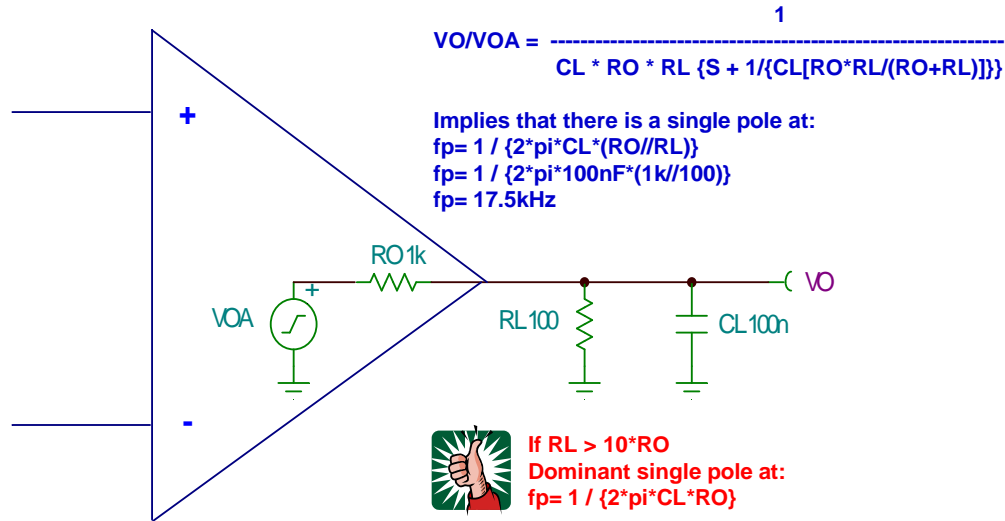


Fig. 6.12: Do We Need To Worry About R_L ?

Fig. 6.13 confirms our first order analysis that for the configuration of R_O , R_L and CL that the pole location is determined, as predicted, by the parallel combination of R_O and R_L in conjunction with CL .

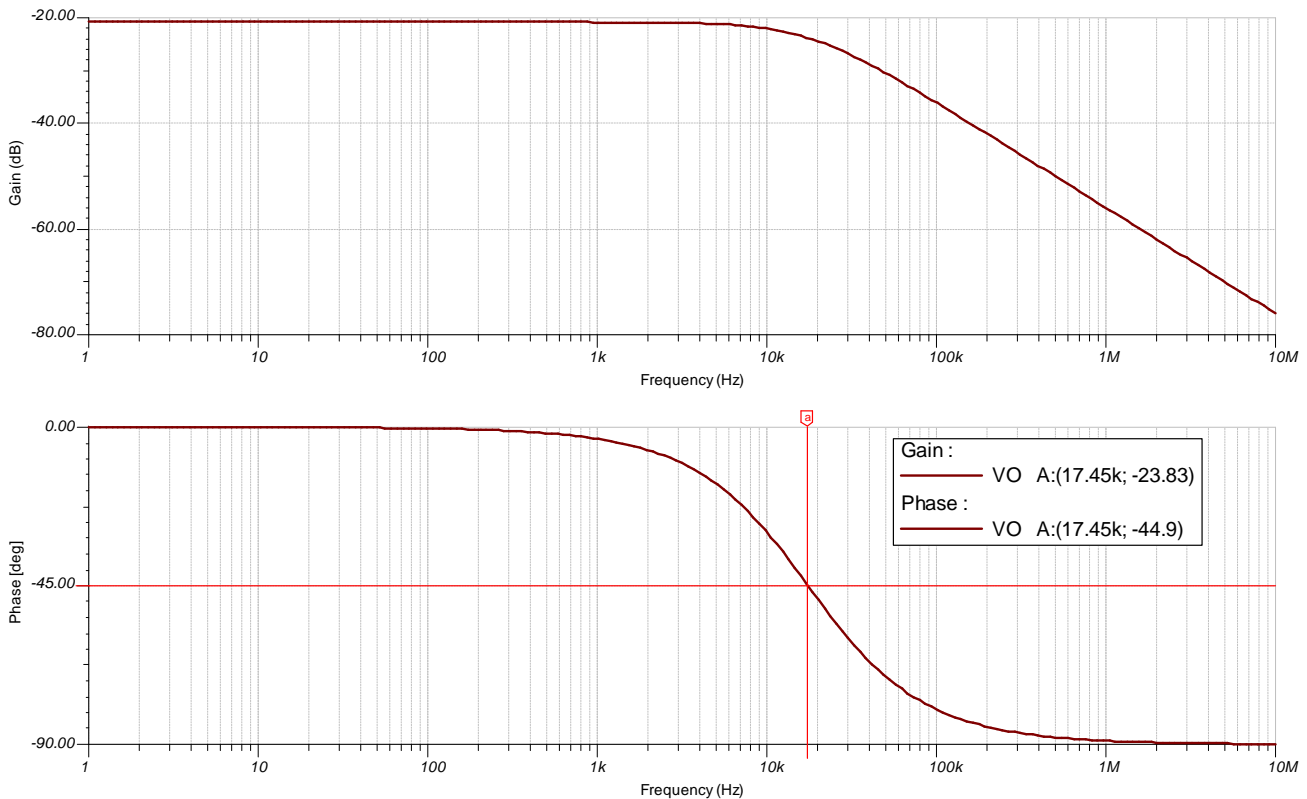


Fig. 6.13: Tina SPICE - R_O , R_L , CL Pole Plot

R_{ISO} & CL Compensation

Our first technique, as shown in Fig. 6.14, to stabilize an op amp driving a capacitive load is to use an isolation resistor, R_{ISO} , between the output of the op amp and the capacitive load, CL. Our point of feedback is taken directly at the output of the op amp. This will create for us, in the "Modified Aol" plot an additional pole and zero. One key consideration for this technique is the current flowing out of the op amp to the load through R_{ISO} . This current will cause an error in V_{OUT} compared with V_{OA} , which is the point of feedback for the op amp. A given application will determine if this error is acceptable.

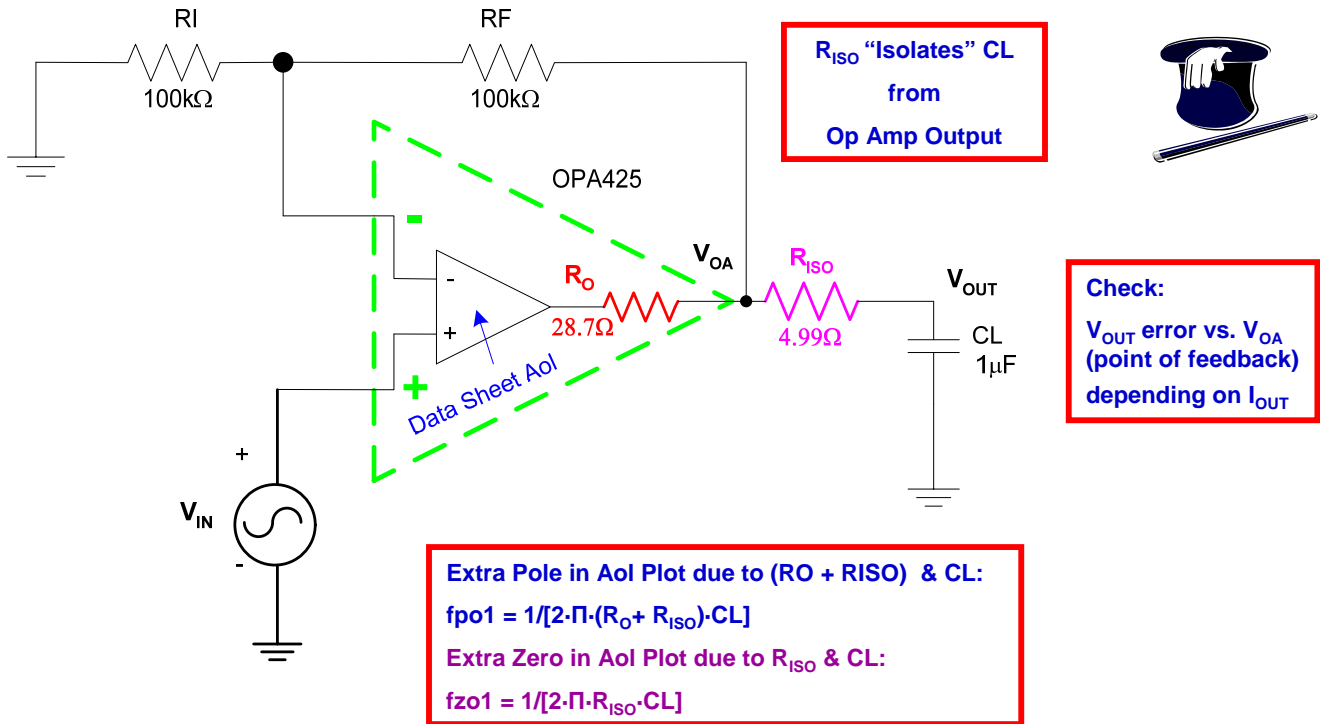


Fig. 6.14: R_{ISO} & CL Compensation

Fig 6.15 shows our first order analysis using the R_{ISO} & CL technique. As shown f_{po1} is determined by the total sum of the resistance of R_O and R_{ISO} interacting with CL. f_{zo1} is determined by the combination of R_{ISO} and CL. Now for a $1/\beta$ of 6dB we see that at f_{cl} the rate-of-closure is 20dB/decade and our first order analysis predicts stability.

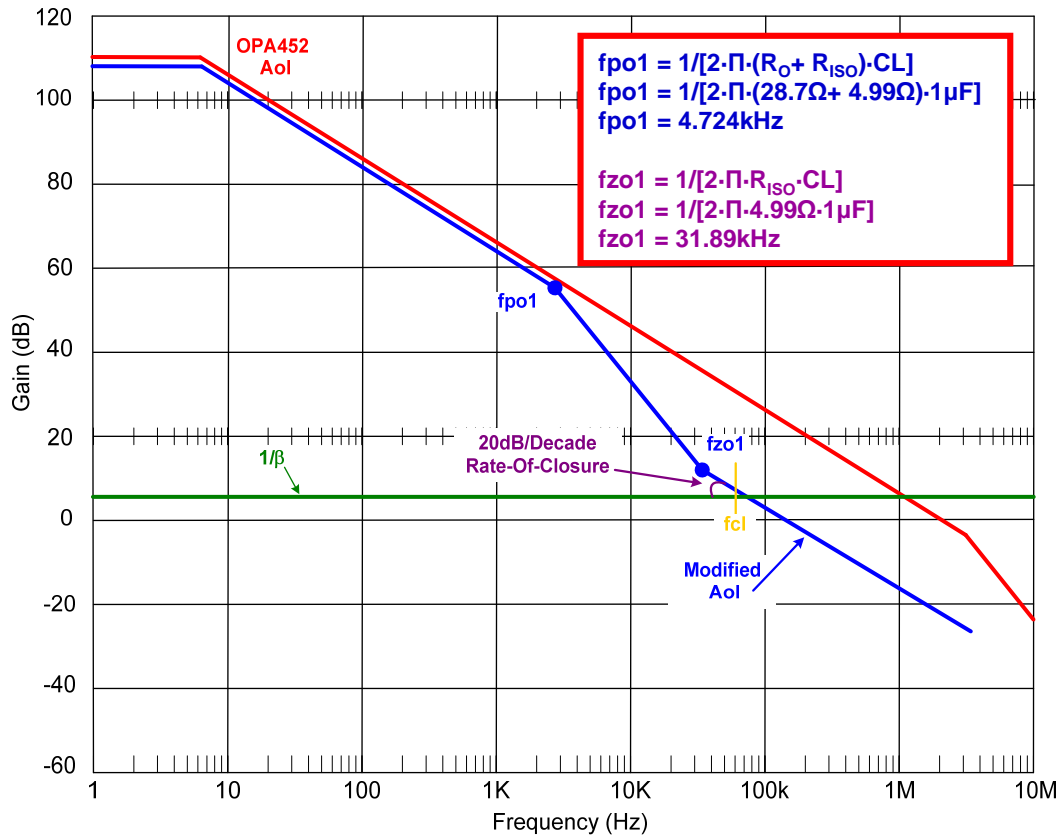


Fig. 6.15: First Order Analysis - R_{ISO} & CL Modified Aol

We will use the Tina SPICE circuit shown in Fig. 6.16 to confirm our first order analysis. Notice that we break the loop here at the minus input of the op amp which allows us to easily plot the “Modified Aol” curve and Loop Gain. $1/\beta$, by inspection will be x2 or 6dB.

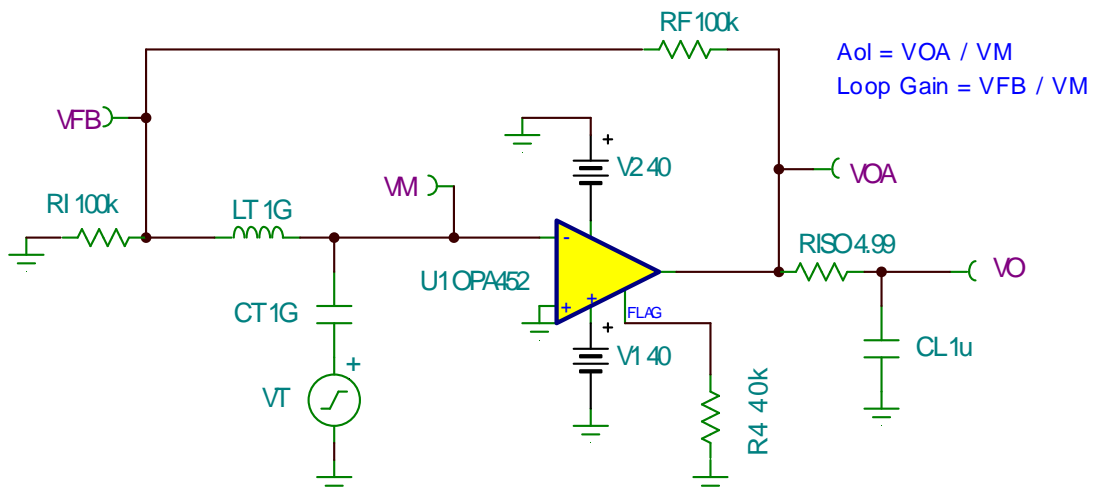


Fig. 6.16: Tina SPICE - R_{ISO} & CL Loop Circuit

The “Modified Aol” plot in Fig 6.17 shows poles and zeros close to our predicted $f_{p01}=4.724\text{kHz}$ and $f_{z01}=31.89\text{kHz}$.

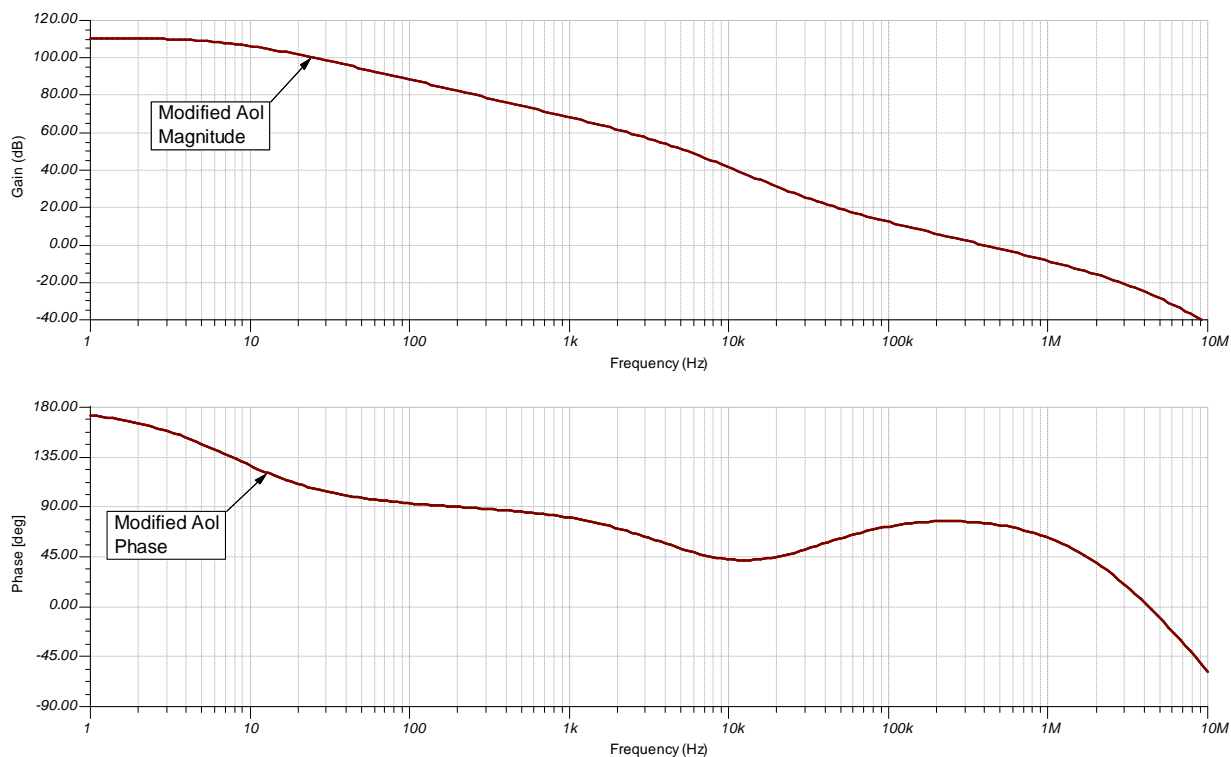


Fig. 6.17: Tina SPICE R_{ISO} & CL “Modified Aol”

The Loop Gain plots shown in Fig. 6.18 indicate good stability for the R_{ISO} & CL stability technique. From our synthesis rules-of-thumb we see phase margin never dipping below 45 degrees from DC to f_{cl} .


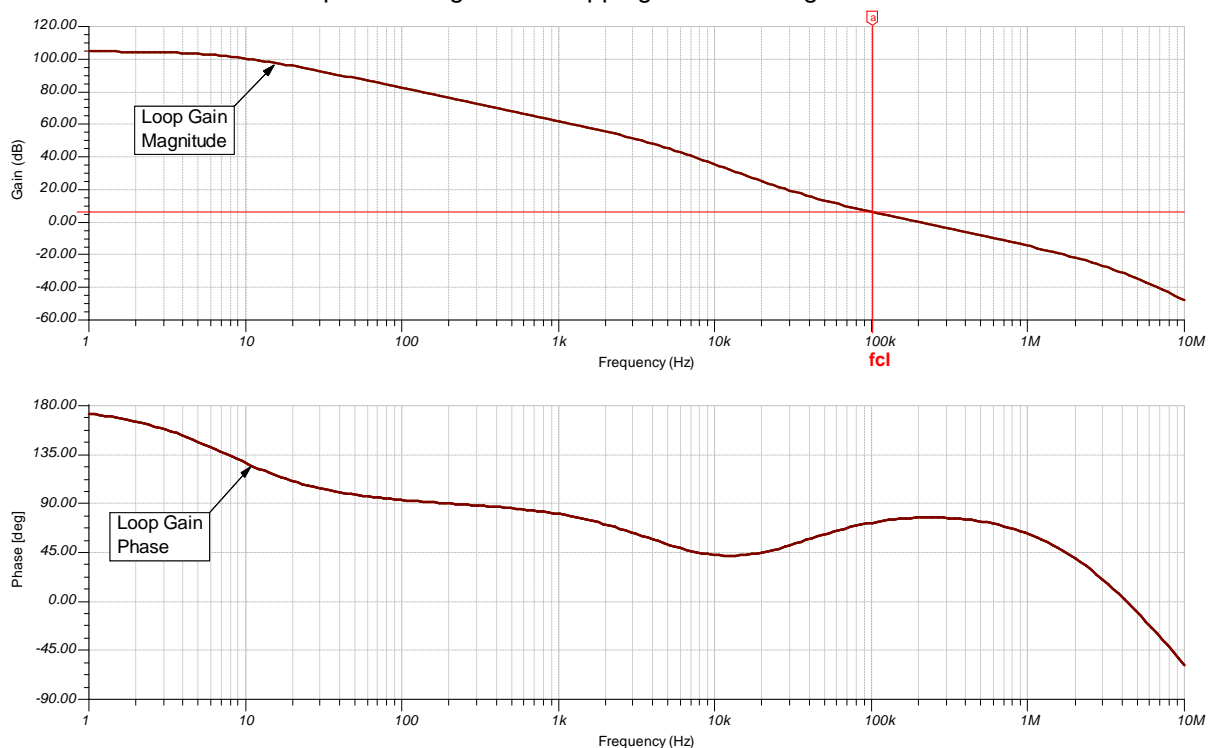


Fig. 6.18: Tina SPICE - R_{ISO} & CL Loop Gain

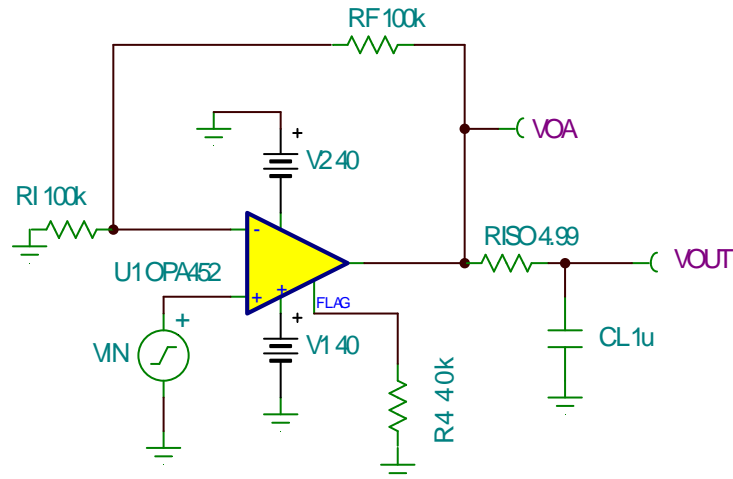The Tina SPICE circuit in Fig 6.19 will be used to run our AC V_{OUT}/V_{IN} transfer function and rerun with V_{IN} changed for our transient analysis.



AC Analysis: $V_{IN} = 1\text{Vpk}$

Transient Analysis $V_{IN} = 100\text{mVpk}$, 10kHz, 10nS rise/fall time

Fig. 6.19: Tina SPICE - R_{ISO} & CL V_{OUT}/V_{IN} Circuit

The V_{OUT}/V_{IN} AC transfer function for R_{ISO} & CL is a little bit tricky without some first order analysis to help us understand how the frequency behavior of this circuit works. As shown in Fig. 6.20 we need to consider the V_{OA}/V_{IN} AC transfer function along with the V_{OUT}/V_{IN} AC transfer function. The point of feedback for this circuit is from V_{OA} and therefore V_{OA}/V_{IN} will be flat until the $1/\beta$ curve intersects the Modified Aol plot. At fcl V_{OA}/V_{IN} will follow the Modified Aol curve on down since there is no loop gain left. V_{OUT}/V_{IN} will be a little bit different. From DC to fzo1 V_{OUT}/V_{IN} will be flat. At fzo1, which is formed by R_{ISO} and CL V_{OUT}/V_{IN} will roll-off at -20dB/decade due to the single pole effect of R_{ISO} and CL. At fcl loop gain is gone and V_{OA} begins to roll-off at -20dB/decade due to the Modified Aol curve. But V_{OUT}/V_{IN} contains the additional pole due to R_{ISO} and CL. So, as shown in Fig. 6.20, V_{OUT}/V_{IN} will have a 2-pole roll-off or -40dB/decade slope after fcl.

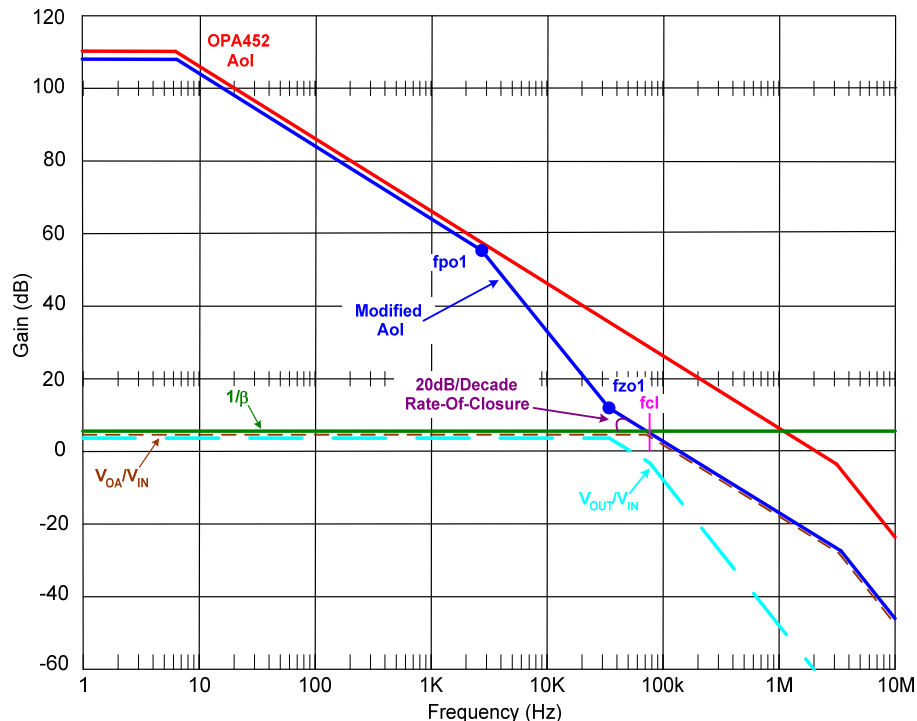


Fig. 6.20: First Order AC Analysis - R_{ISO} & CL V_{OUT}/V_{IN}

Our Tina SPICE simulations shown in Fig. 6.21 confirm our first order analysis of V_{OUT}/V_{IN} and V_{OA}/V_{IN} .

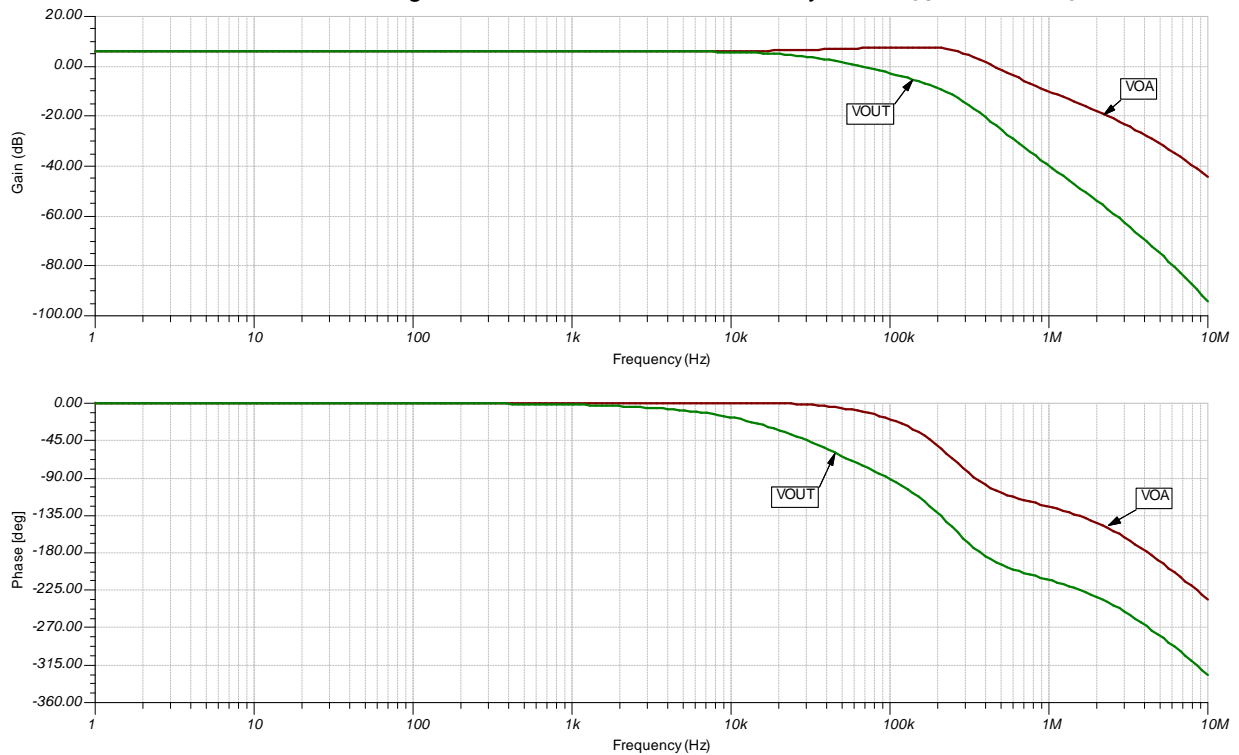


Fig. 6.21: Tina SPICE - R_{ISO} & CL V_{OUT}/V_{IN}

And for our final stability sanity check we run a transient analysis with the results as predicted in Fig. 6.22. From the V_{OA} curve, the point of feedback, the positive going output the transient analysis would predict about 60 degrees of loop gain phase margin while the negative going output would be greater than 45 degrees of phase margin (see Part 4 of this series). Since this SPICE model matches the real IC for characteristics we see that the negative output stage is a bit different than the positive output stage. However, overall stability looks solid.

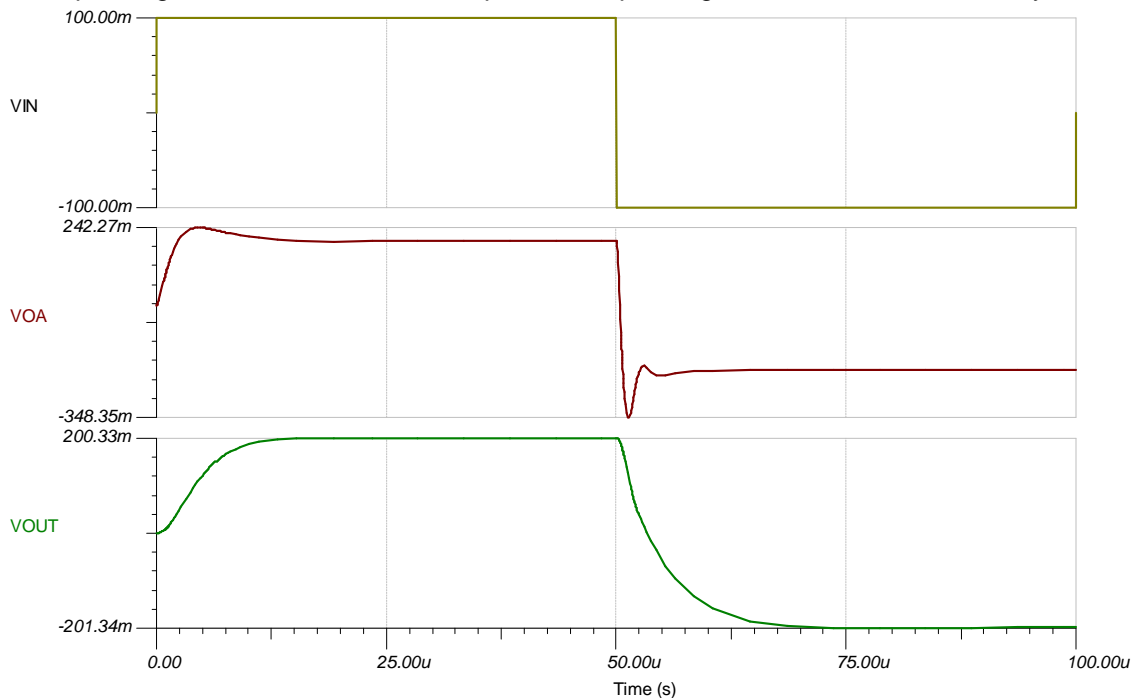


Fig. 6.22: Tina SPICE - R_{ISO} & CL V_{OUT}/V_{IN} Transient Analysis

High Gain & CF Compensation

Our second technique to stabilize an op amp driving a capacitive load is to use high gain and a feedback capacitor, CF. This topology is shown in Fig. 6.23. To see how this technique works we will plot a “Modified Aol” curve with a second pole formed by R_O and CL . In the $1/\beta$ plot we will add a pole at a frequency location which will cause an intersection of the $1/\beta$ curve with the Modified Aol curve at a rate-of-closure which is 20dB/decade.

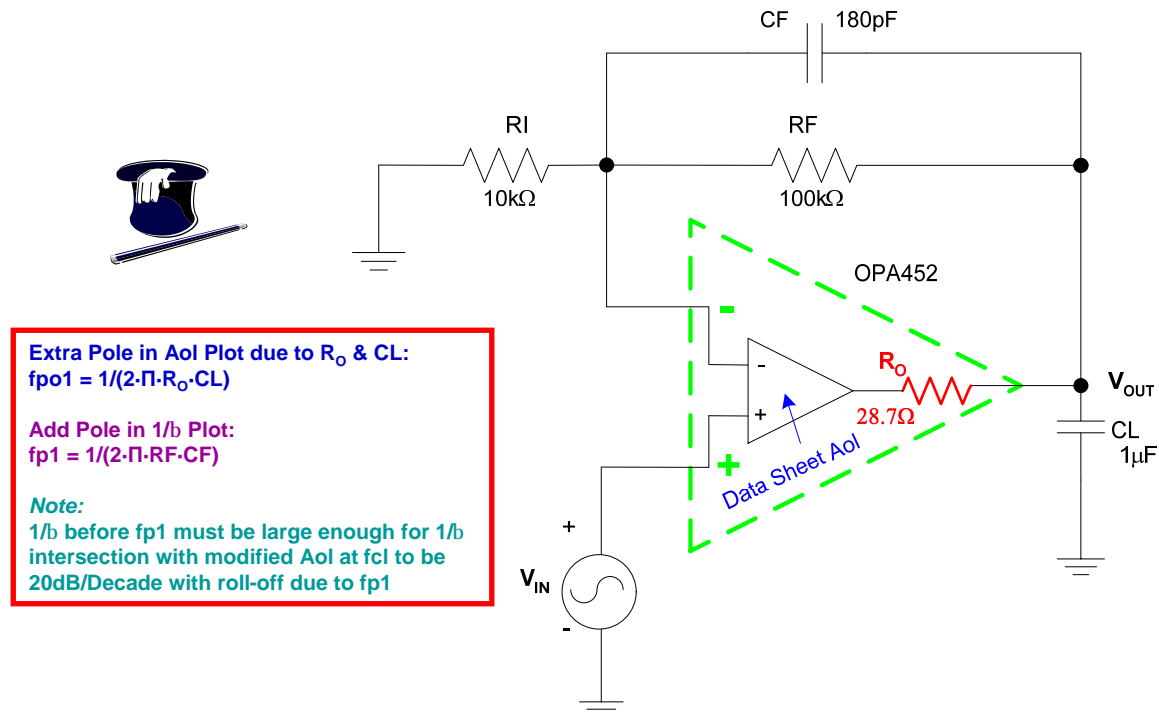


Fig. 6.23: High Gain & CF Compensation

Our first order analysis plots the second pole, fp_{01} , in the Modified Aol curve as shown in Fig. 6.24. We add a pole in the $1/\beta$ plot through the addition of C_F . Note how fp_1 was chosen to ensure the intersection of $1/\beta$ and the Modified Aol curve to be 20dB/decade rate-of-closure. With capacitor C_F in the op amp feedback the smallest value of $1/\beta$ will be 1 (0dB) by inspection, since at high frequencies C_F is a short and V_{OUT} is fed back directly to the minus input of the op amp. From this first order analysis we predict a stable circuit and since the point of feedback is directly at CL there will be no error in the V_{OUT}/V_{IN} transfer function. Our predicted V_{OUT}/V_{IN} AC transfer function will show a single pole roll-off at fp_1 , 8.84kHz, due to the interaction of C_F and R_F . This will continue down at -20dB/decade until f_{cl} , where loop gain goes to zero, and then V_{OUT}/V_{IN} will follow on down the Modified Aol curve.

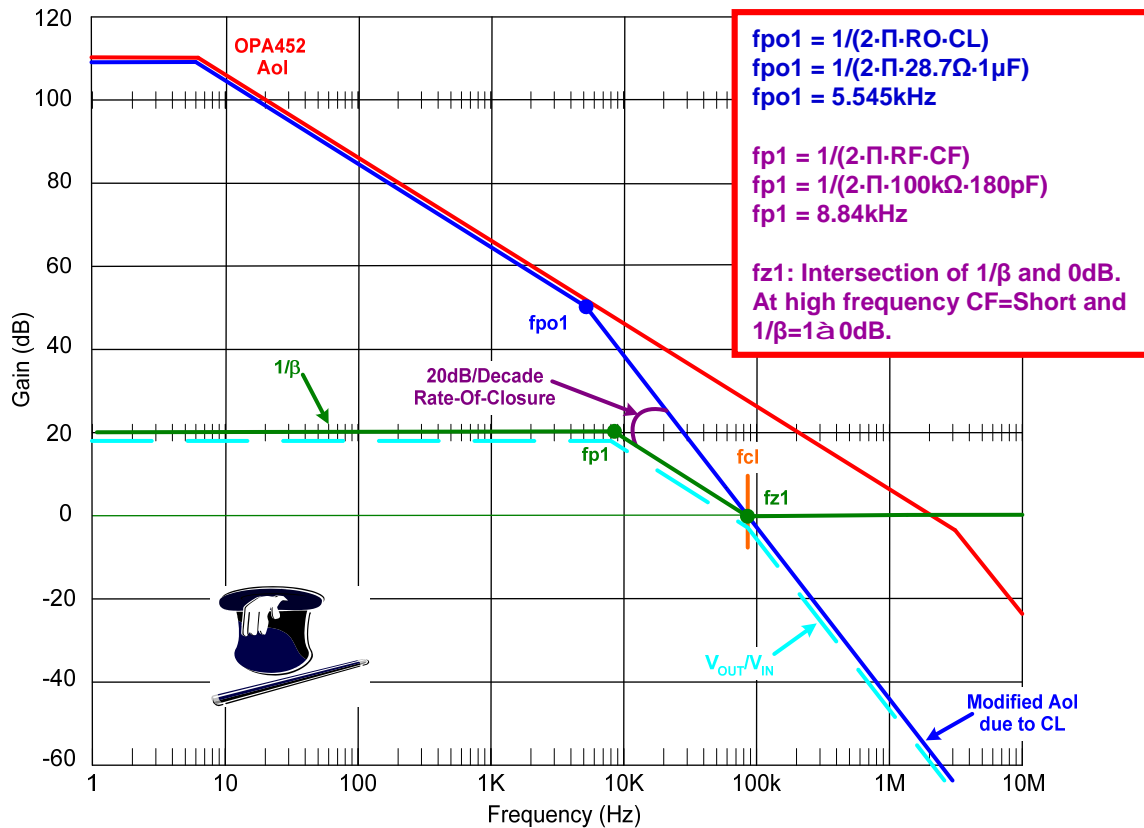


Fig. 6.24: First Order Analysis - High Gain & CF

Our Tina SPICE circuit for the High Gain & CF loop test is shown in Fig. 6.25. Again, breaking the loop at the minus input to the op amp allows us to accurately plot the Modified Aol curve.

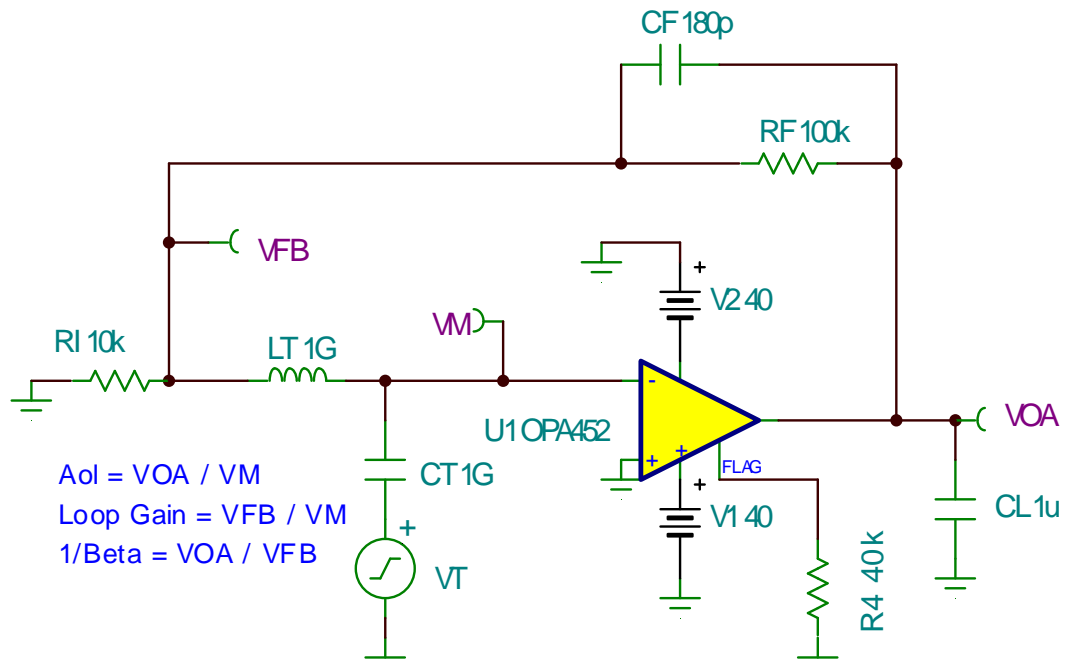


Fig. 6.25: Tina SPICE - High Gain & CF Loop Circuit

The $1/\beta$ plot and Modified Aol plot are seen in Fig. 6.26 to correlate directly with our first order predictions with a second Aol pole, f_p at about 5.45kHz and a $1/\beta$ plot with a pole, f_{p1} , at about 8.84kHz. Notice how $1/\beta$ continues down at a -20dB/decade slope from 8.84kHz until it intersects with 0db and then remains flat at 0dB.

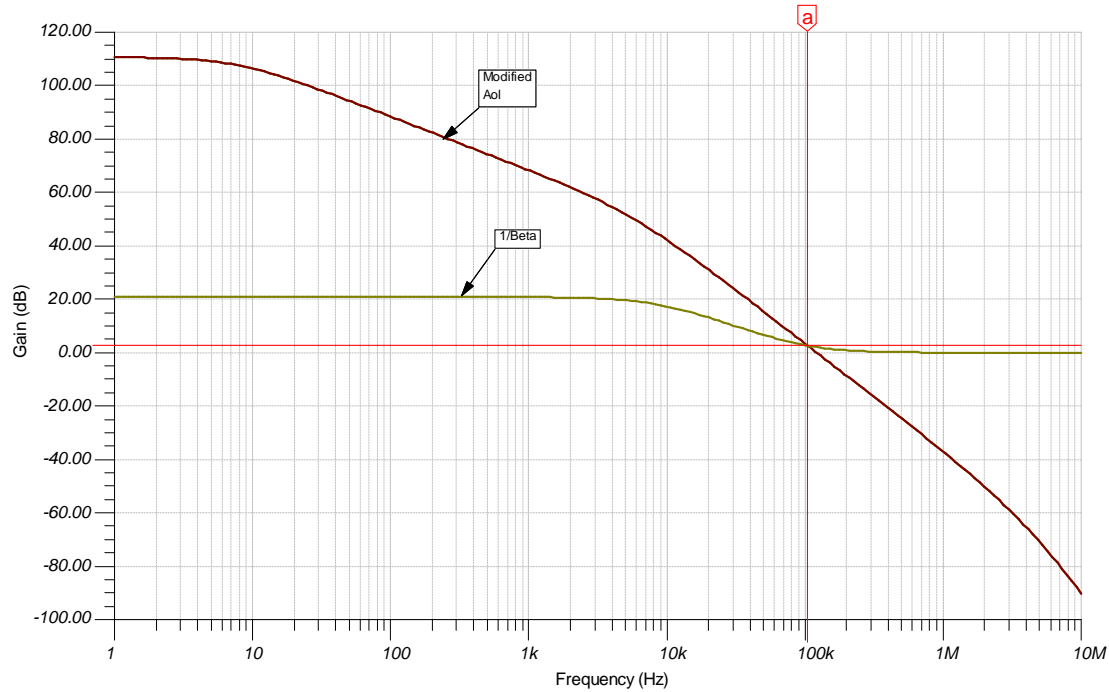


Fig. 6.26: Tina SPICE - High Gain & CF Modified Aol & $1/\beta$

Our Loop Gain plots for stability are shown in Fig 6.27 and phase margin wise, from DC to fcl our phase is >45 degrees as desired. At fcl we see a phase margin of 38.53 degrees. Let's see what the closed loop AC response and transient analysis look like to determine if this is an acceptable circuit for us.


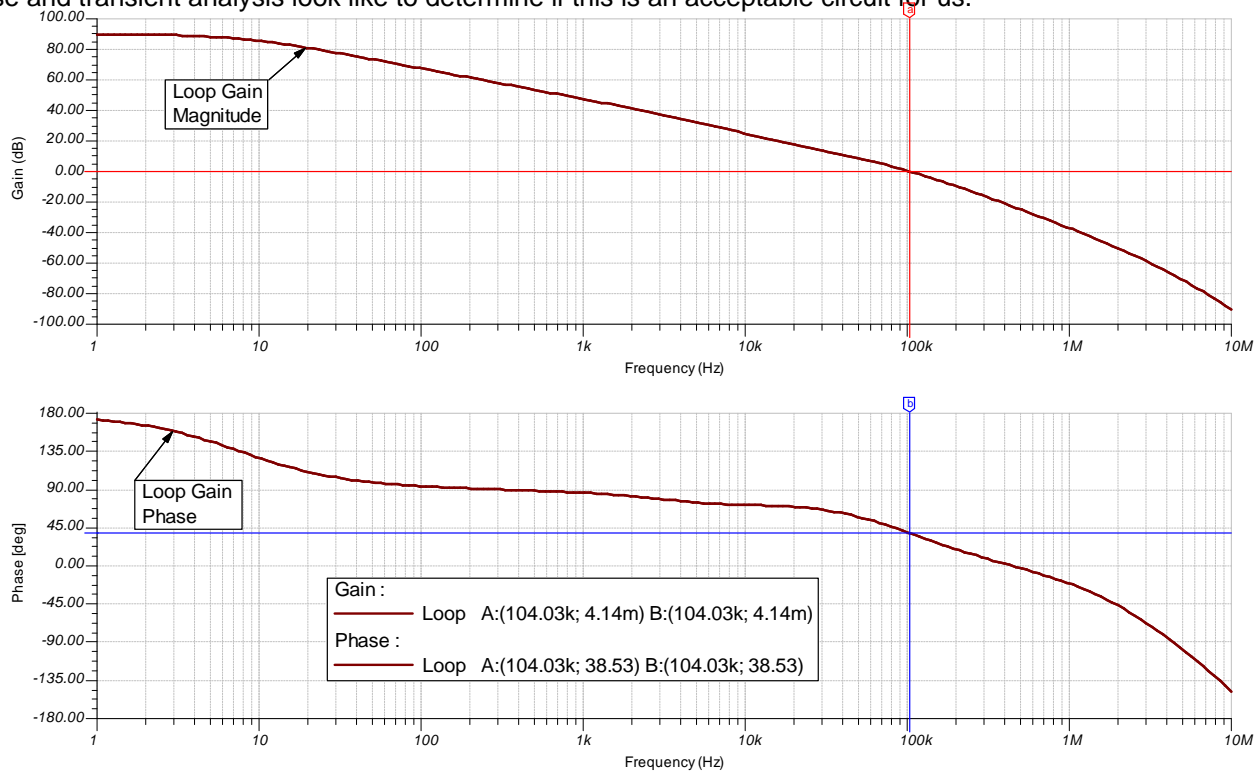


Fig. 6.27: Tina SPICE - High Gain & CF Loop Gain

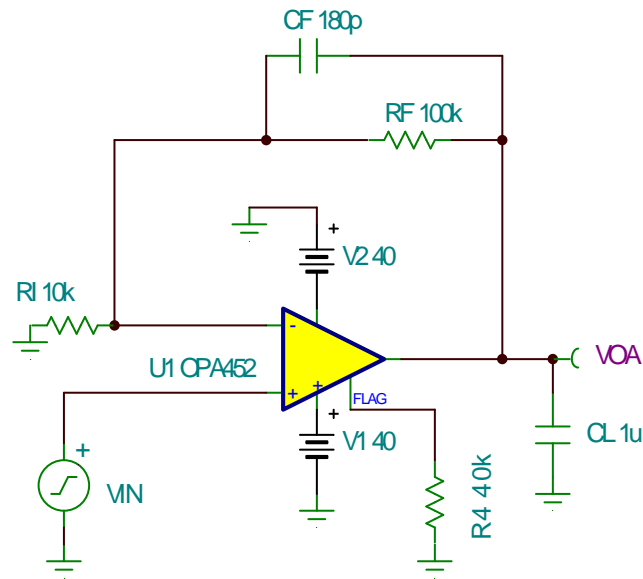The V_{OUT}/V_{IN} tests will be conducted using the Tina SPICE circuit in Fig 6.28.



AC Analysis: $V_{IN} = 1V_{pk}$

Transient Analysis $V_{IN} = 10mV_{pk}$, 1kHz, 10nS rise/f all time

Fig. 6.28: Tina SPICE - High Gain & CF V_{OUT}/V_{IN} Circuit

The V_{OUT}/V_{IN} AC transfer function is what we predicted by our first order analysis as shown in Fig. 6.29. A single pole roll-off around 10kHz with a -40dB/decade roll-off above 100Khz where loop gain is zero and V_{OUT}/V_{IN} follows the Modified Aol curve on down. Right around 100kHz there is a small flat spot that can be predicted from the actual 1/Beta plot on the modified Aol where this transition region occurs.

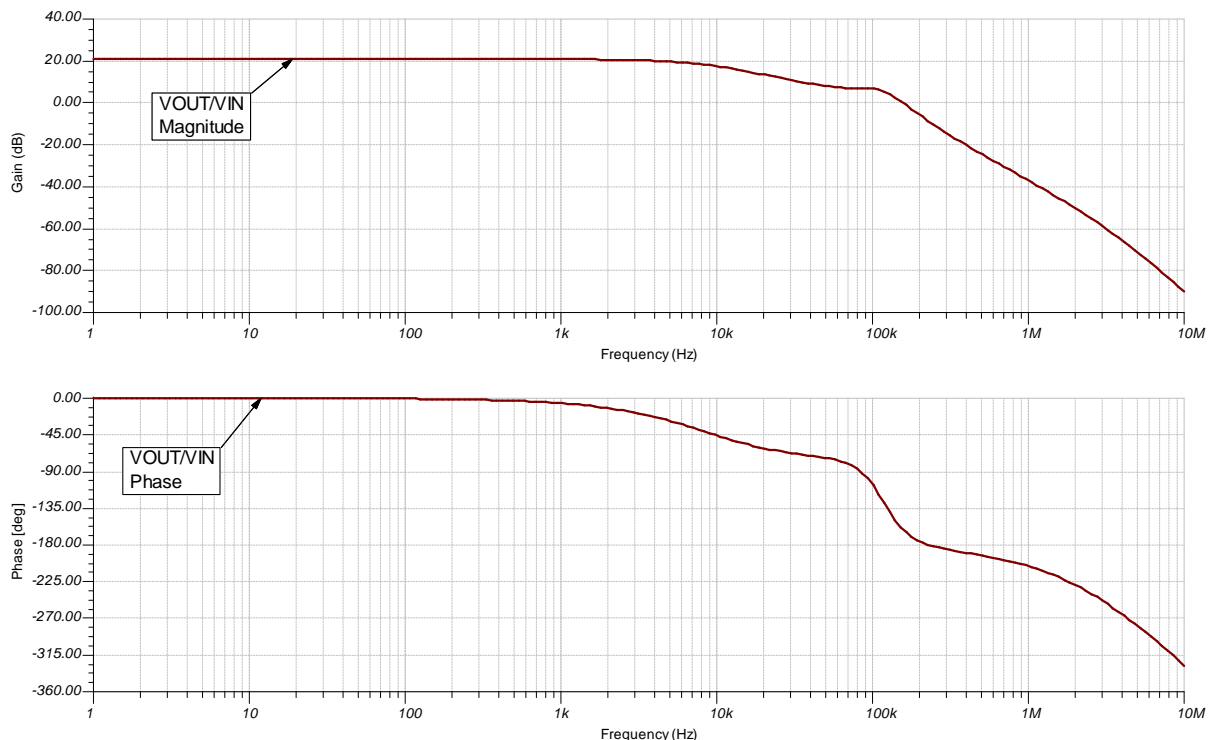


Fig. 6.29: Tina SPICE – High Gain & CF V_{OUT}/V_{IN}

A Tina SPICE transient V_{OUT}/V_{IN} analysis in Fig 6.30 shows a stable circuit without any overshoot or ringing.

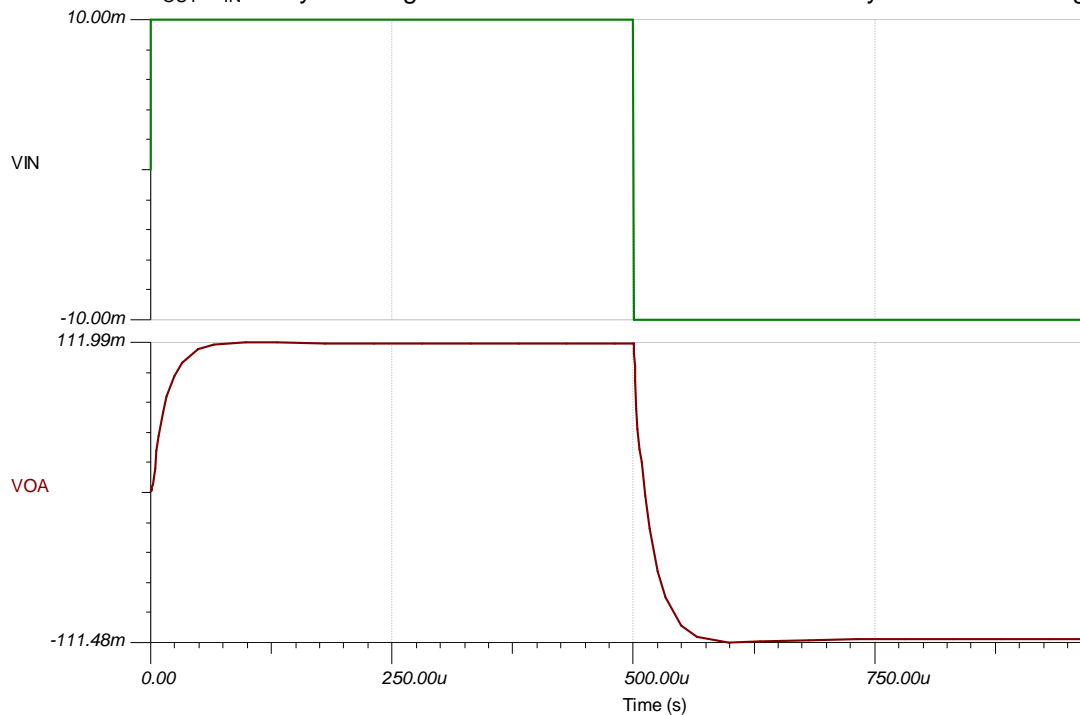


Fig. 6.30: Tina SPICE – High Gain & CF Transient Analysis


Noise Gain Compensation

Our third technique to stabilize an op amp driving a capacitive load is to Noise Gain. This topology is shown in Fig. 6.31. To see how this technique works we will plot a “Modified Aol” curve with a second pole formed by R_O and C_L . In the $1/\beta$ plot we will add a pole and zero such that we will raise the $1/\beta$ gain at high frequencies to be above the second pole in the Modified Aol curve. The added pole in the $1/\beta$ curve, f_{pn} , is set by R_n and C_n as shown. We do not need to compute the zero, f_{zn} , since we can plot it graphically starting from f_{pn} and going back down in frequency at a 20dB/decade slope to the DC $1/\beta$ value.

This technique is called Noise Gain because it does increase the overall noise gain of the op amp circuit. That is any noise internal to the op amp, usually referred to the input, is gained up to the output by the increase in gain over frequency of the $1/\beta$ curve.

For the Inverting Noise Gain configuration this topology can be thought of as a summing amplifier. In this regard it is easy for us to see that V_{OUT}/V_{IN} is simply $-R_F/R_I$. The additional summation of ground into the C_n - R_n network results in no output voltage contribution but does limit the bandwidth of the overall circuit since it modifies the $1/\beta$ curve. *This clearly emphasizes the fact that to make an op amp circuit stable we must give up bandwidth.*

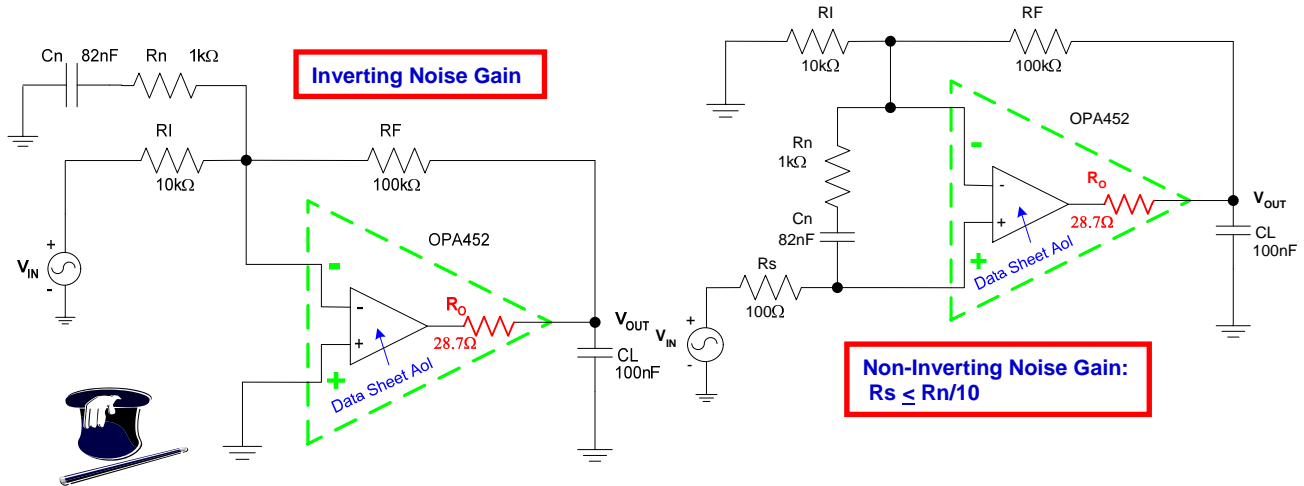For the Non-Inverting Noise Gain configuration we must ensure that R_s , the input signal source impedance is at least 10 times less than R_n to ensure that R_n will dominate in setting the high frequency $1/\beta$ gain. It is not as obvious that the Non-Inverting Noise Gain topology will yield $V_{OUT}/V_{IN} = 1 + R_F/R_I$. A derivation of this will be worthwhile.



Extra Pole in Aol Plot due to R_o & C_L :
 $f_{po1} = 1/(2 \cdot \pi \cdot R_o \cdot C_L)$

Add Noise Gain Zero & Pole in $1/b$ Plot:

$1/b \text{ DC} = R_F/R_I$

$1/b \text{ Hi-f} = R_F/R_n$ (Must intersect Modified Aol at 20dB/Decade)


$f_{pn} = 1/(2 \cdot \pi \cdot R_n \cdot C_n)$

$f_{zn} = \text{Intersect of } +20\text{dB/decade slope from } f_{pn} \text{ down to } 1/b \text{ DC value}$

$V_{OUT}/V_{IN} = R_F/R_I$
 V_{OUT}/V_{IN} High Frequency Noise Gain
 increases to R_F/R_n

Fig. 6.31: Noise Gain Compensation

In Fig 6.32 we derive the V_{OUT}/V_{IN} AC transfer function for the Non-Inverting Noise Gain topology. We assign the R_n - C_n network a single variable name Z_n to simplify our analysis. Using Superposition (see Part 4 of this series) and classical op amp gain theory we can solve for V_{OUT} by treating the op amp as a summer amplifier. The result is that V_{OUT}/V_{IN} is the simple $1+R_F/R_I$ gain ratio for any non-inverting op amp configuration. However, R_n - C_n will impact $1/\beta$ and reduce the bandwidth of V_{OUT}/V_{IN} and increase the overall noise gain of the circuit.

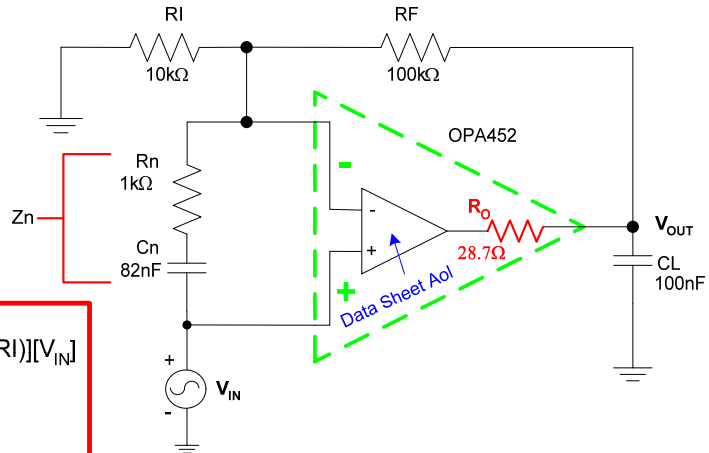

Use Superposition:

$$V_{OUT} = 0V(-R_F/R_I) + V_{IN}(-R_F/Z_n) + [1 + R_F/(Z_n/R_I)][V_{IN}]$$

$$= -V_{IN}(R_F/Z_n) + V_{IN} + [R_F/(Z_n/R_I)] V_{IN}$$

$$[R_F/(Z_n/R_I)] = R_F/[Z_n R_I/(Z_n + R_I)]$$

$$= (R_F Z_n + R_I R_F) / Z_n R_I$$

$$= R_F Z_n / Z_n R_I + R_I R_F / R_I Z_n$$

$$= R_F/R_I + R_F/Z_n$$

$$V_{OUT} = -V_{IN}(R_F/Z_n) + V_{IN} + [R_F/R_I + R_F/Z_n] V_{IN}$$

$$= -V_{IN}(R_F/Z_n) + V_{IN} + V_{IN}(R_F/R_I) + V_{IN}(R_F/Z_n)$$

$$= V_{IN} + V_{IN}(R_F/R_I)$$

$$V_{OUT} = V_{IN} [1 + (R_F/R_I)] \rightarrow V_{OUT}/V_{IN} = 1 + (R_F/R_I)$$

Fig. 6.32: Non-Inverting Noise Gain Compensation Derivation

Gain (dB)

Frequency (Hz)

OPA452 Aol

20dB/Decade Rate-Of-Closure

$1/\beta$

f_{zn}

f_{fn}

f_{cl}

f_{po1}

Modified Aol due to CL

V_{OUT}/V_{IN}

1/b DC = R_F/R_I
 1/b DC = $100k\Omega/10k\Omega = 10$ (20dB)
 1/b Hi-f = R_F/R_n
 1/b Hi-f = $100k\Omega/1k\Omega = 100$ (40dB)

$f_{po1} = 1/(2 \cdot \pi \cdot R_0 \cdot C_L)$
 $f_{po1} = 1/(2 \cdot \pi \cdot 28.7\Omega \cdot 100nF)$
 $f_{po1} = 55.45kHz$

$f_{fn} = 1/(2 \cdot \pi \cdot R_n \cdot C_n)$
 $f_{fn} = 1/(2 \cdot \pi \cdot 1k\Omega \cdot 82nF)$
 $f_{fn} = 1.94kHz$

f_{zn} : Plot graphically from f_{fn} to 1/b DC with +20dB/Decade slope

Fig. 6.33: First Order Analysis – Noise Gain Compensation

Fig. 6.34 is the Tina SPICE circuit to plot $1/\beta$, Modified Aol, and Loop Gain to check our first order analysis. Again, as before, the loop is broken at the minus input of the op amp for ease of Modified Aol plotting.

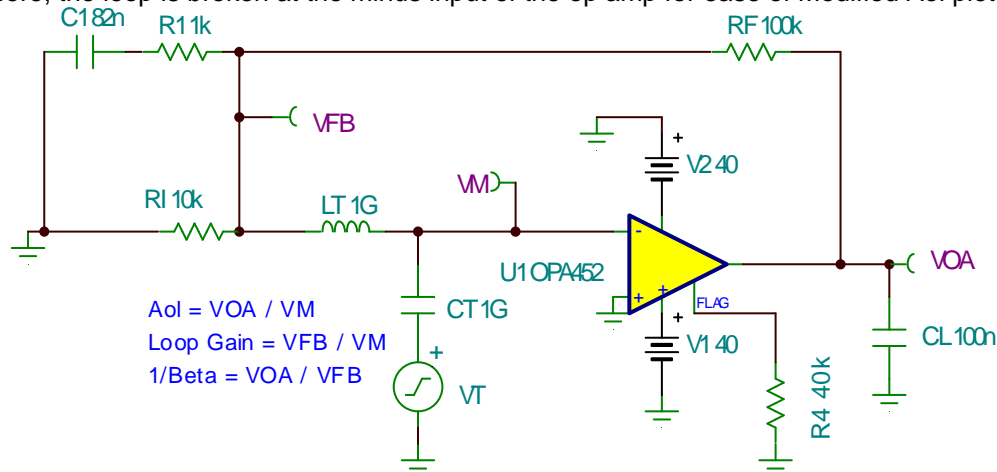


Fig. 6.34: Tina SPICE – Noise Gain Loop Circuit

Our Tina SPICE results once again match our first order predictions. The modified Aol in Fig 6.35 contains a second pole at about 55.45kHz. The $1/\beta$ plot is 20dB at low frequencies, 40dB at high frequencies, contains a pole at about 1.94kHz and a zero at about 194Hz. And at fcl, about 20kHz, a 20dB/decade rate-of-closure.

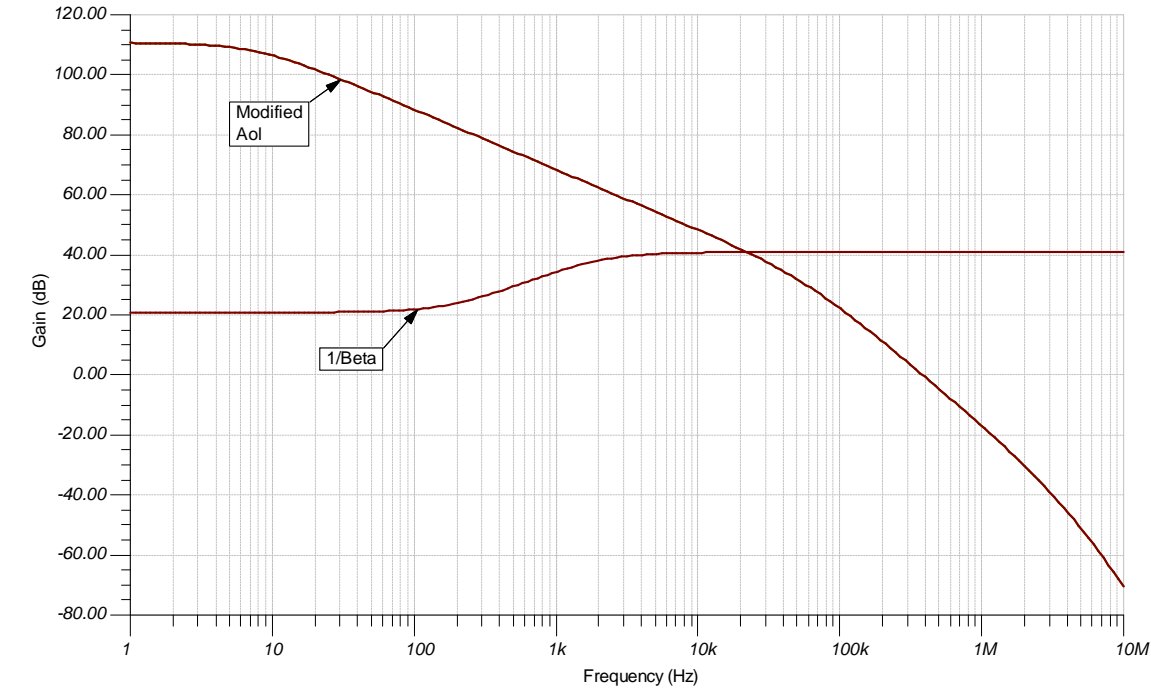


Fig. 6.35: Tina SPICE – Noise Gain Modified Aol & $1/\beta$

The Loop Gain plots in Fig 6.36 confirm a stable circuit with phase margin at fcl of 63.24 degrees. There is a slight dip of phase to under 45 degrees between 100Hz and 1kHz but not enough to cause concern.


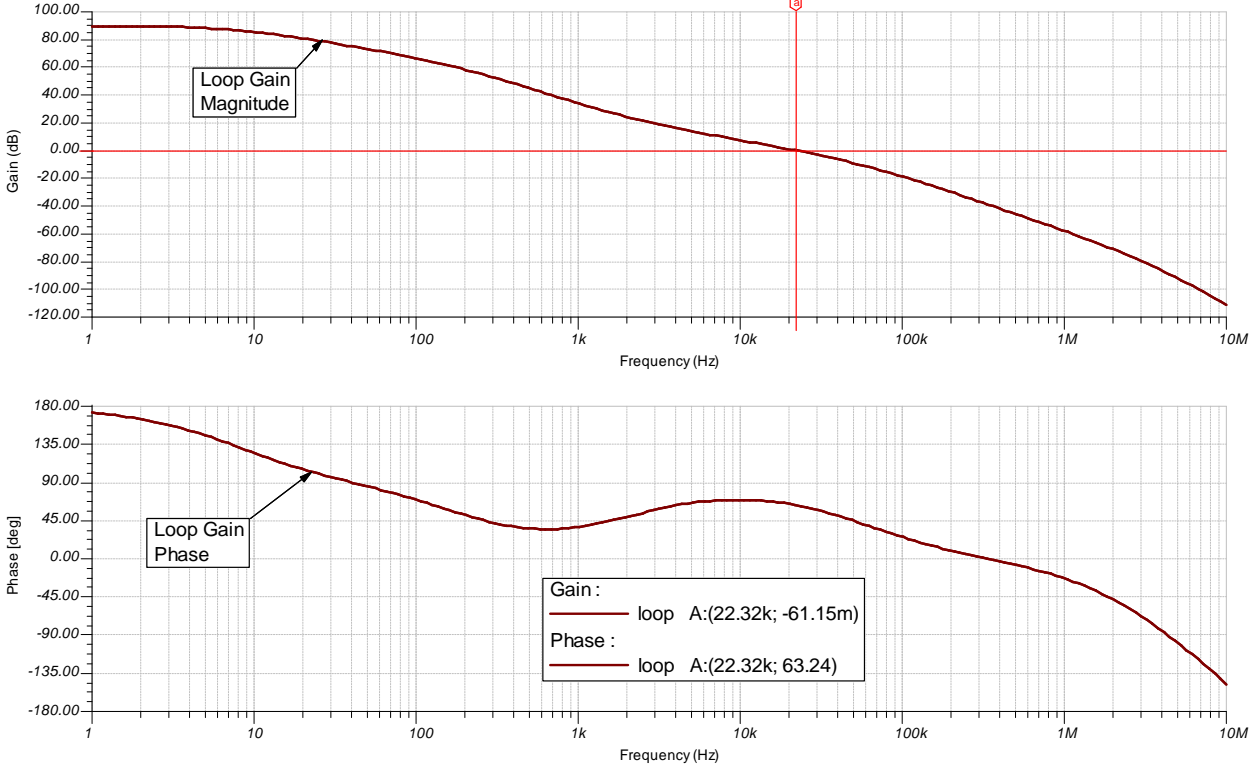


Fig. 6.36: Tina SPICE – Noise Gain Loop Gain

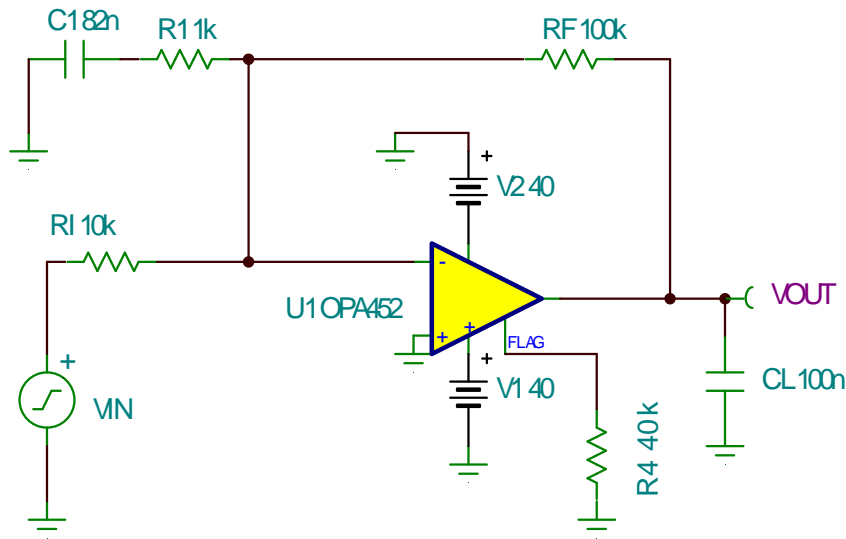For our V_{OUT}/V_{IN} AC transfer test and transient test we will use the circuit in Fig 6.37.



AC Analysis $V_{IN} = 1V_p$

Transient Analysis $V_{IN} = 10mV_{pk}$, 5kHz, 10ns rise/fall time

Fig. 6.37: Tina SPICE – Noise Gain V_{OUT}/V_{IN} Circuit

The V_{OUT}/V_{IN} AC transfer function in Fig 6.38 shows next to no peaking in its response and as we predicted a -20dB/decade slope from about 20kHz (where loop gain goes to zero) to about 50kHz where the Modified Aol breaks again to a -40dB/decade slope.

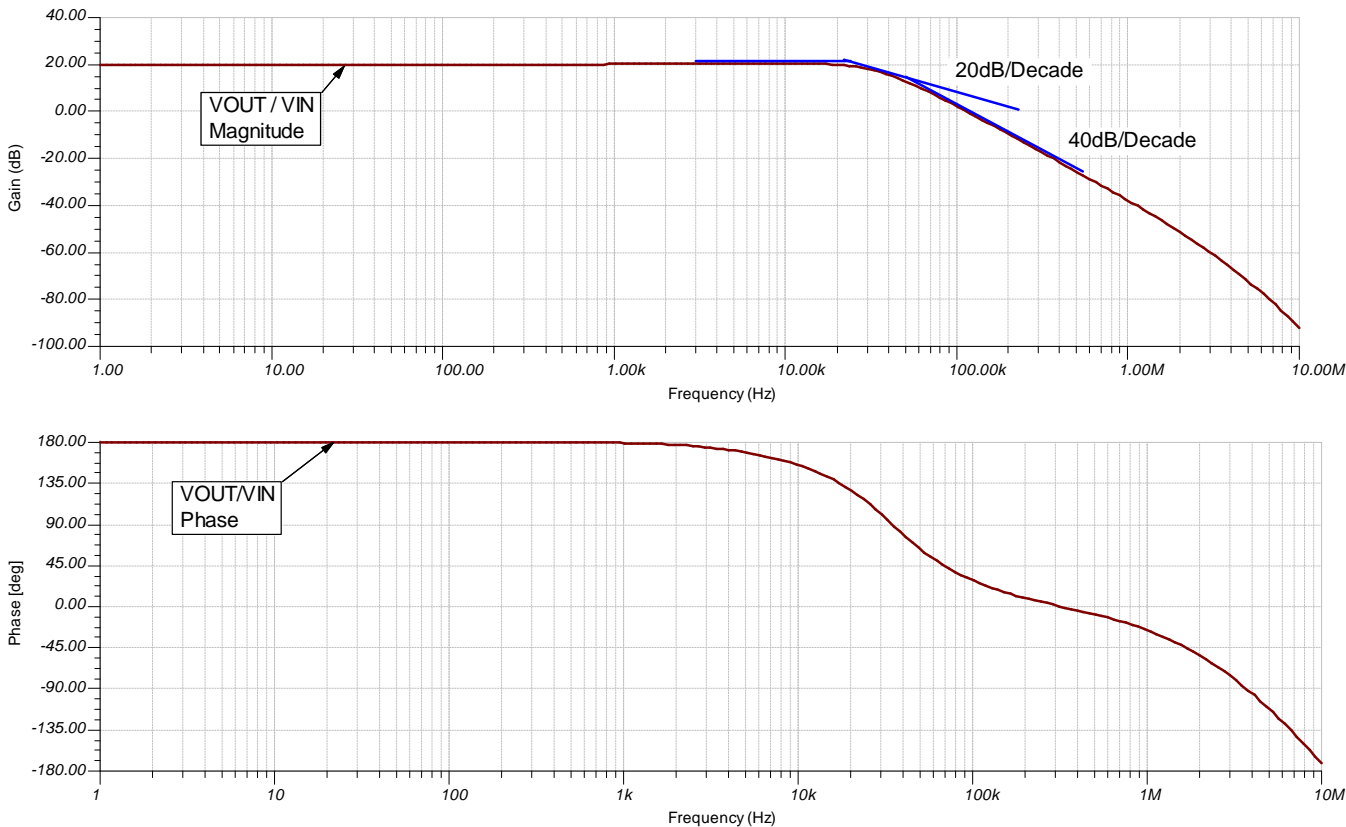


Fig. 6.38: Tina SPICE – Noise Gain V_{OUT}/V_{IN}

In Fig 6.39, based on the slight overshoot and no undershoot the transient V_{OUT}/V_{IN} test, phase margin correlates to about a 60 degree phase margin (see Transient Real World Stability Test and Second Order Transient Curves detailed in Part 4 of this series).

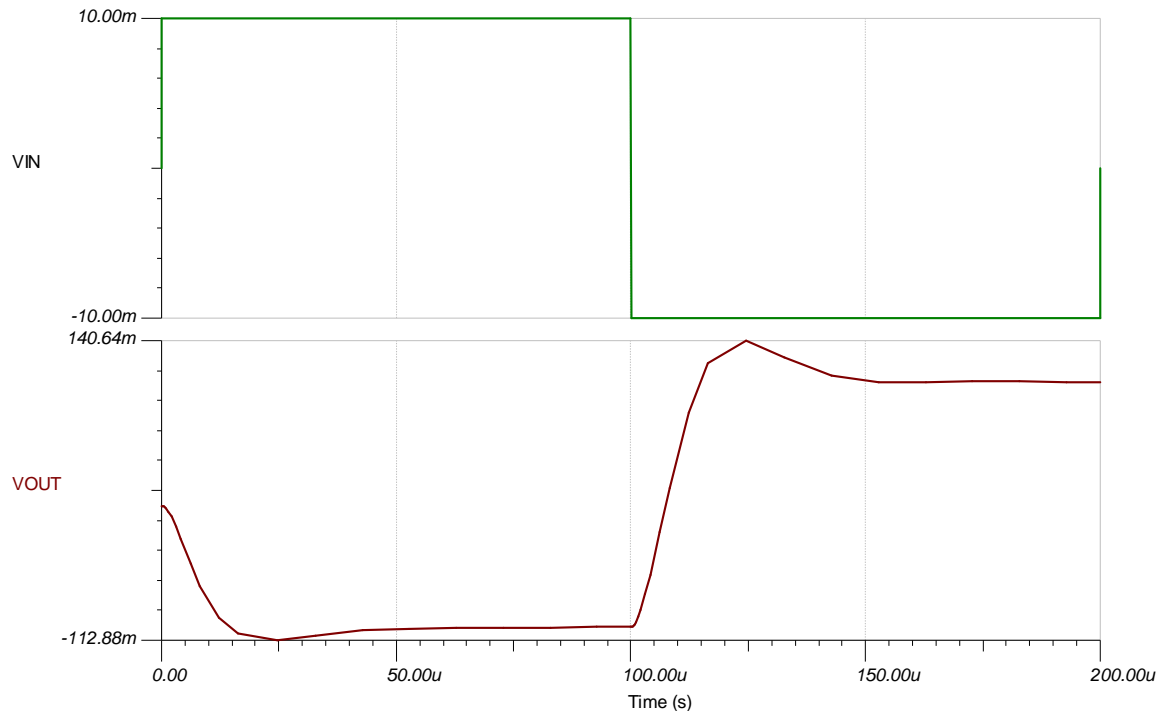


Fig. 6.39: Tina SPICE – Noise Gain V_{OUT}/V_{IN} Transient Analysis

Three (R_{ISO} , High Gain & CF, Noise Gain) of the “six ways to leave your capacitive load stable” have been covered in this part. For each technique we were able to analyze, synthesize, and simulate a stable circuit for an op amp driving a capacitive load. Part 7 will cover Noise Gain & CF and Output Pin Compensation techniques. And Part 8 will present the sixth technique, R_{ISO} w/Dual Feedback.

The Burr-Brown Products group of Texas Instruments has made available a free version of Tina SPICE. It contains almost all of Burr-Brown and Texas Instruments Op Amp Models and will run up to two op amp models in one circuit. Tina-TI SPICE is available at: www.ti.com/tina-ti

References:

Frederiksen, Thomas M. *Intuitive Operational Amplifiers*, From Basics to Useful Applications, Revised Edition. McGraw-Hill Book Company. New York, New York. 1988

Tobey – Graeme –Huelsman, Editors. *Burr-Brown Operational Amplifiers*, Design and Applications. McGraw-Hill Book Company. New York, New York. 1971