

## Operational Amplifier Stability

### Part 3 of 15: $R_O$ and $R_{OUT}$

By Tim Green

Strategic Development Engineer, Burr-Brown Products from Texas Instruments

Part 3 of this series will focus on clarifying some common misconceptions regarding op amp "Output Resistance". We will define two important *different* output resistances for an op amp,  $R_O$  and  $R_{OUT}$ .  $R_O$  will become extremely useful when we start to stabilize op amp circuits which are driving capacitive loads. We will present easy techniques to derive  $R_O$  from op amp manufacturers' data sheets and in addition a couple of real world measurement techniques for those op amps whose data sheets do not contain a specification for  $R_O$ . We will also show a trick for using SPICE op amp models and  $R_O$  which will allow you to use the SPICE Loop Gain Test while including the effects of  $R_O$  (extremely useful for capacitive load drive circuits).

#### Definition and Derivation of $R_O$ and $R_{OUT}$

$R_O$  is here, and throughout this series, defined as the Open Loop Output Resistance of an op amp.  $R_{OUT}$  is defined as the Closed Loop Output Resistance of an op amp. Fig. 3.0 emphasizes the important difference between these two different resistances.

$R_O$  = Op Amp **Open Loop** Output Resistance

$R_{OUT}$  = Op Amp **Closed Loop** Output Resistance

Fig. 3.0: Definition of  $R_O$  and  $R_{OUT}$

As hinted at in Fig. 3.0 slide  $R_O$  and  $R_{OUT}$  are related.  $R_{OUT}$  is  $R_O$  reduced by loop gain. Fig. 3.1 will define the op amp model used for the derivation of  $R_{OUT}$  from  $R_O$ . This simplified op amp model focuses solely on the basic DC characteristics of an op amp. A high input resistance (100m $\Omega$  to G $\Omega$ ) is between -IN and +IN.  $R_{DIFF}$  develops an error voltage across it,  $V_E$ , due to the voltage differences between -IN and +IN. The error voltage,  $V_E$ , is amplified by the open loop gain factor  $A_{ol}$  and becomes  $V_O$ . In series with  $V_O$  to the output,  $V_{OUT}$ , is  $R_O$ , the open loop output resistance.

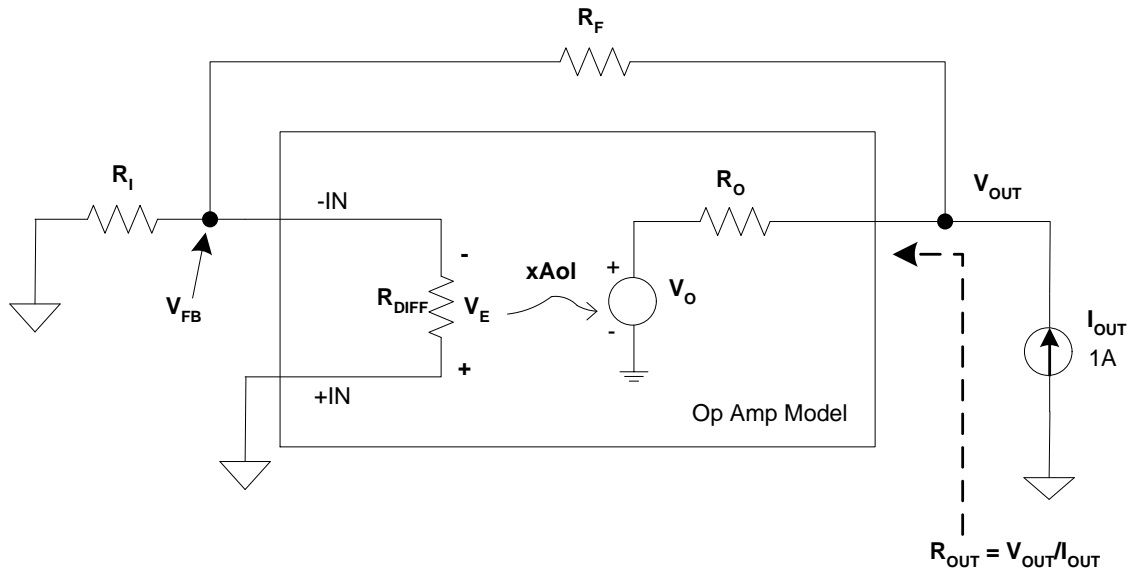


Fig. 3.1: Op Amp Model for Derivation of  $R_{OUT}$

Using the op amp model in the Fig. 3.1 we can solve for  $R_{OUT}$  as a function of  $R_O$  and  $Aol\beta$ . This derivation is detailed in Fig. 3.2. We see that  $Aol\beta$ , loop gain, reduces  $R_O$  so that the output resistance of the op amp with feedback,  $R_{OUT}$ , will be much lower than  $R_O$ , for large values of  $Aol\beta$ .

$$1) b = V_{FB} / V_{OUT} = [V_{OUT} (R_I / (R_F + R_I))] / V_{OUT} = R_I / (R_F + R_I)$$

$$2) R_{OUT} = V_{OUT} / I_{OUT}$$

$$3) V_O = -V_E Aol$$

$$4) V_E = V_{OUT} [R_I / (R_F + R_I)]$$

$$5) V_{OUT} = V_O + I_{OUT} R_O$$

$$6) V_{OUT} = -V_E Aol + I_{OUT} R_O \text{ Substitute 3) into 5) for } V_O$$

$$7) V_{OUT} = -V_{OUT} [R_I / (R_F + R_I)] Aol + I_{OUT} R_O \text{ Substitute 4) into 6) for } V_E$$

$$8) V_{OUT} + V_{OUT} [R_I / (R_F + R_I)] Aol = I_{OUT} R_O \text{ Rearrange 7) to get } V_{OUT} \text{ terms on left}$$

$$9) V_{OUT} = I_{OUT} R_O / \{1 + [R_I Aol / (R_F + R_I)]\} \text{ Divide in 8) to get } V_{OUT} \text{ on left}$$

$$10) R_{OUT} = V_{OUT} / I_{OUT} = [I_{OUT} R_O / \{1 + [R_I Aol / (R_F + R_I)]\}] / I_{OUT}$$

*Divide both sides of 9) by  $I_{OUT}$  to get  $R_{OUT}$  [from 2)] on left*

$$11) R_{OUT} = R_O / (1 + Aol\beta) \text{ Substitute 1) into 10)}$$

$$R_{OUT} = R_O / (1 + Aol\beta)$$


Fig. 3.2: Derivation of  $R_{OUT}$

### Computing $R_O$ from Data Sheet Curves

The OPA353 is a wideband (UGBW=44MHz, SR=22V/uS, Settle to 0.1%=0.1us) CMOS, single supply (2.7V to 5.5V), RRIO (Rail-To-Rail Input and Output) op amp. There is no  $R_O$  specification in the Specifications table of the manufacturer's data sheet. However, there are two helpful curves in the Typical Performance Curves to help us determine  $R_O$ . We will need to use the Open-Loop Gain/Phase vs Frequency curve (see Fig. 3.3) and the Closed-Loop Output Impedance vs Frequency curve (see Fig. 3.4) to easily calculate  $R_O$ . The Closed-Loop Output Impedance vs Frequency curve is actually a plot of  $R_{OUT}$  vs frequency. Within the unity gain bandwidth of voltage feedback op amps  $R_O$  and  $R_{OUT}$  are predominantly resistive. On the Closed-Loop Output Impedance vs Frequency curve, Fig. 3.4, we choose the G=10 curve and on its x-axis the point 1MHz (just choose an easy to read data point). At the intersection of 1MHz and G=10 Curve we see  $R_{OUT}=10\Omega$ . On the Open-Loop Gain/Phase vs Frequency curve, Fig. 3.3, we look at the 1MHz frequency point on the x-axis and read what the open loop gain as 29.54dB (We measured this one with a ruler and scaled it based on the linear dB y-axis. We did this on a cut and paste curve which was then enlarged as much as possible). The derivation of  $R_O$  from the information collected in Fig. 3.3 and Fig. 3.4 is detailed in Fig. 3.5. Now from our formula for  $R_O$  we rearrange the equation to give us  $R_O$  in terms of  $R_{OUT}$ ,  $Aol$ , and  $\beta$ . From this equation and our data sheet information we calculate the  $R_O$  for the OPA353 to be 40 $\Omega$ .

**OPA353 Specifications:**

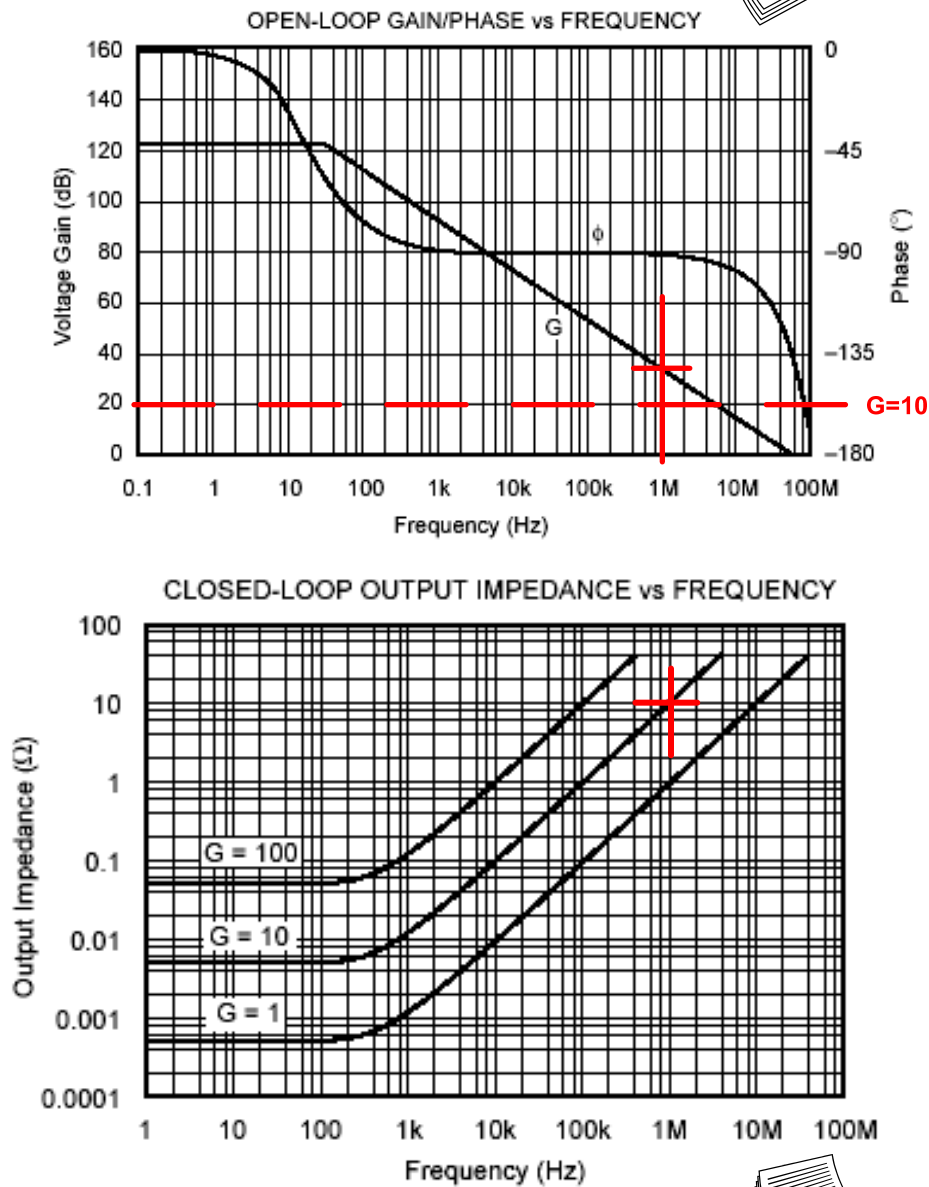**$A_{ol} @ 1\text{MHz} = 29.54\text{dB} = \times 30$**



**OPA353 Specifications:**

**$R_{OUT} (@1\text{MHz}, G=10) = 10\Omega$**



**Fig. 3.4: OPA353 Closed Loop Output Impedance Curve**

### OPA353 $R_O$ Calculation

$$R_{OUT} = R_O / (1 + Aol\beta)$$

$$R_O = R_{OUT} (1 + Aol\beta)$$

$$R_O = 10\Omega (1 + 30[1/10])$$

$$R_O = 40\Omega$$

Fig. 3.5: OPA353  $R_O$  Calculation

We can use the op amp model from Fig. 3.1, used for the derivation of  $R_{OUT}$  from  $R_O$ , and the information from the OPA353 data sheet to fill in actual values in the model. This is shown in Fig 3.6. So we see how our model correlates with real world op amps. Notice in this model we define  $V_O$  as the op amp's output before  $R_O$  and  $V_{OUT}$  as the actual op amp output. Of course in a real op amp we can only gain access to  $V_{OUT}$  but this model and the fact that we can get real world data to build this model will become very powerful in stability analysis.

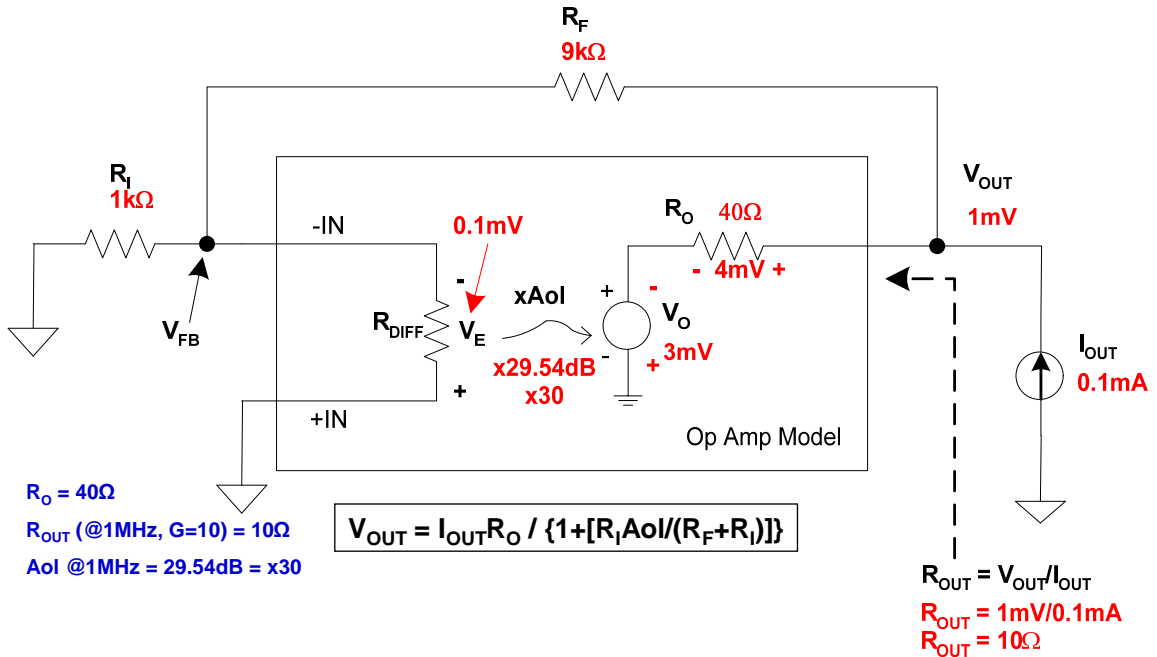


Fig. 3.6: OPA353  $R_O$  Calculation using Op Amp Model

### Summary of $R_O$ and $R_{OUT}$ Key Points

Fig 3.7 emphasizes the important differences between  $R_O$  and  $R_{OUT}$ . Fig 3.8 summarizes the key points of  $R_O$ .

Ø  $R_O$  does **NOT** change when Closed Loop feedback is used

Ø  $R_{OUT}$  is the effect of  $R_O$ ,  $Aol$ , and  $\beta$  controlling  $V_O$

ü Closed Loop feedback ( $\beta$ ) forces  $V_O$  to increase or decrease as needed to accommodate  $V_O$  loading

ü Closed Loop ( $\beta$ ) increase or decrease in  $V_O$  appears at  $V_{OUT}$  as a reduction in  $R_O$

ü  $R_{OUT}$  increases as Loop Gain ( $Aol\beta$ ) decreases

Fig. 3.7:  $R_O$  vs  $R_{OUT}$


- Ø  $R_O$  is constant over the Op Amp's bandwidth 
- Ø  $R_O$  is defined as the Op Amp's Open Loop Output Resistance
- Ø  $R_O$  is measured at  $I_{OUT} = 0$  Amps,  $f = 1\text{MHz}$   
(use the unloaded  $R_O$  for Loop Stability calculations since it will be the largest value à worst case for Loop Stability analysis)
- Ø  $R_O$  is included when calculating  $b$  for Loop Stability analysis

Fig. 3.8:  $R_O$  Key Points

### $R_O$ and SPICE Simulations

In Fig. 3.9 we show a Simple AC SPICE Model for the OPA353. Here we use the  $40\Omega$  we computed for  $R_O$ . Notice that we break the loop for AC Stability Analysis here using the SPICE Loop Gain Test. The loop break is made between  $R_O$  and  $V_O$  in order to analyze the effects of  $R_O$  on  $1/\beta$ . This will become extremely important in stabilizing capacitive loads driven by op amps (this topic will be covered in detail in Part 7 and Part 8 of this series).


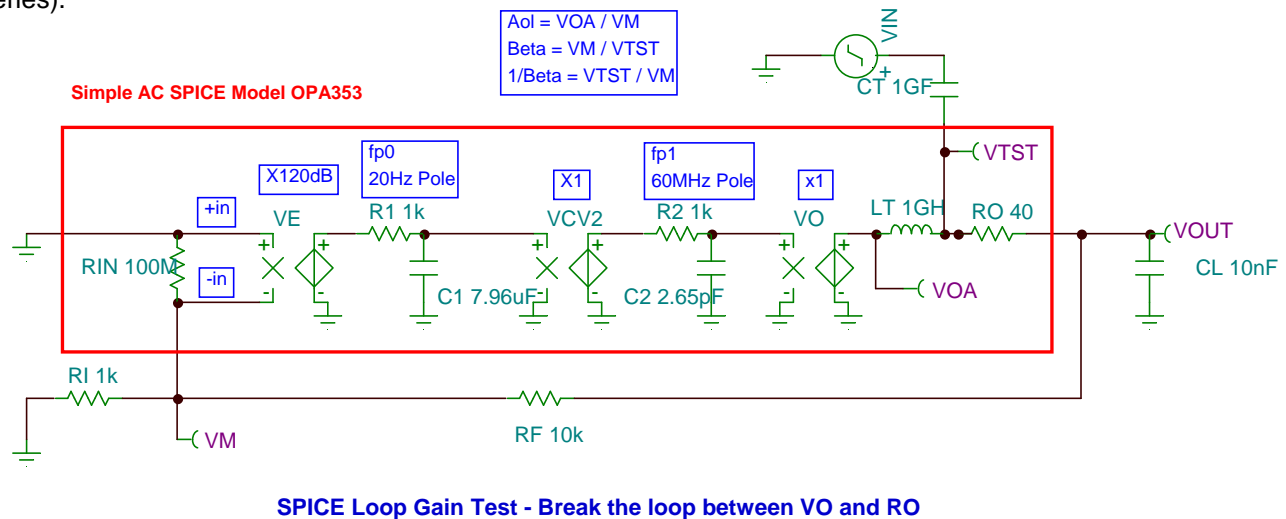


Fig. 3.9: Simple AC SPICE Model with  $R_O$

For a given existing manufacturer's op amp SPICE model we can easily add an external  $R_O$  so that when we use the SPICE Loop Gain Test to find  $1/\beta$  we can include the effects of  $R_O$ . In the Modified  $R_O$  SPICE MacroModel in Fig. 3.10 we add a Voltage Controlled Voltage Source (VCVS),  $V_O$ , with a gain equal to one. This isolates the op amp's output and any internal  $R_O$  it may have modeled internally from whatever connects to  $V_O$ . Now we can add our own  $R_O$  after the VCVS,  $V_O$ , and break the loop between  $V_O$  and  $R_O$  which is desired for including the effects of  $R_O$  when analyzing capacitive loads and their effects on  $1/\beta$ .

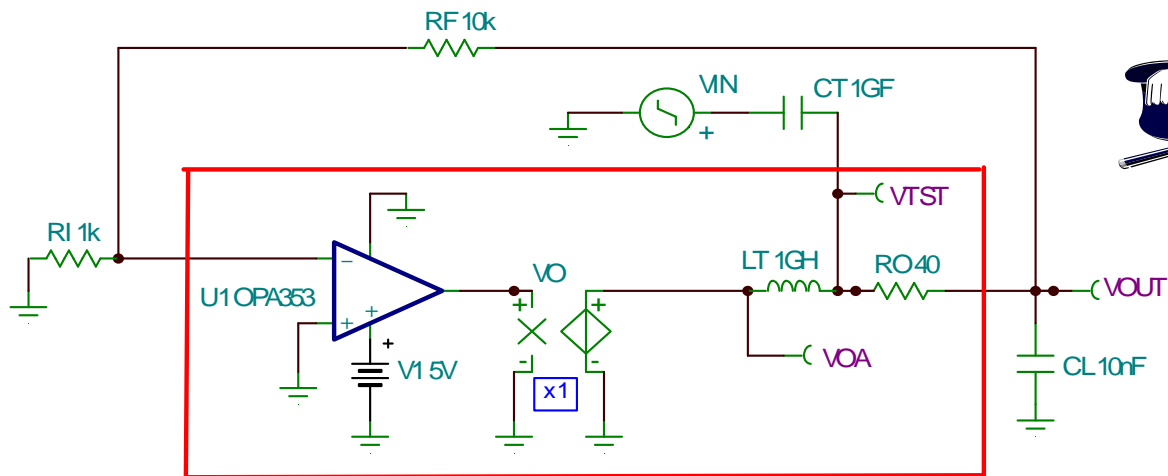

**Modified RO SPICE Model OPA353**

U1 is Mfr SPICE Model

Add VO (VCVS w/G=1) and new RO

Allows SPICE Loop Gain Test  $1/\beta$  curve to include effects of RO

**Fig. 3.10: Modified  $R_O$  SPICE MacroModel**

### Real World $R_O$ for Single Supply Op Amps

Fig.3.11 lists some actual real world measured  $R_O$  for many single supply op amps. Notice that the OPA353 we analyzed to be  $R_O=40\Omega$  has a measured value of  $44\Omega$ . This close correlation is because the data we used from the manufacturer's data sheet was also measured data on a typical part!

Part	$R_O$ (ohms)	Part	$R_O$ (ohms)	Part	$R_O$ (ohms)
OPA132	80	OPA348	600	OPA627	55
OPA227	40	OPA350	50	OPA684	50
OPA277	10	OPA353	44	THS4503	14
OPA300	20	OPA354	35	TLC080	100
OPA335	90	OPA355	40	TLC081	100
OPA336	250	OPA356	30	TLC2272	140
OPA340	80	OPA363	160	TLE2071	80
OPA343	80	OPA380	30	TLV2461	173

**Fig. 3.11: Real World  $R_O$  for Some Single Supply Op Amps**

## Real World Measurement Techniques for $R_O$

So what if we do not have any manufacturer's specifications for  $R_O$  and we want to know what it is? There are two real world techniques we can use to measure  $R_O$ . Each method starts by looking at the Open-Loop Gain/Phase vs Frequency curve. Such a curve is shown in Fig. 3.12 for the OPA364, a wideband (UGBW=7MHz, SR=5V/ $\mu$ S, Settle to 0.1%=1.5 $\mu$ s) CMOS, single supply (1.8V to 5.5V), RRIO (Rail-To-Rail Input and Output) op amp with "Linear Offset Over Common Mode Range". If we choose to test this op amp at a gain of 100 and at 1MHz there will be no loop gain,  $A_{ol}\beta$ , left. Therefore, if we measure  $R_{OUT}$  under these conditions we will really be getting a value for  $R_O$ !


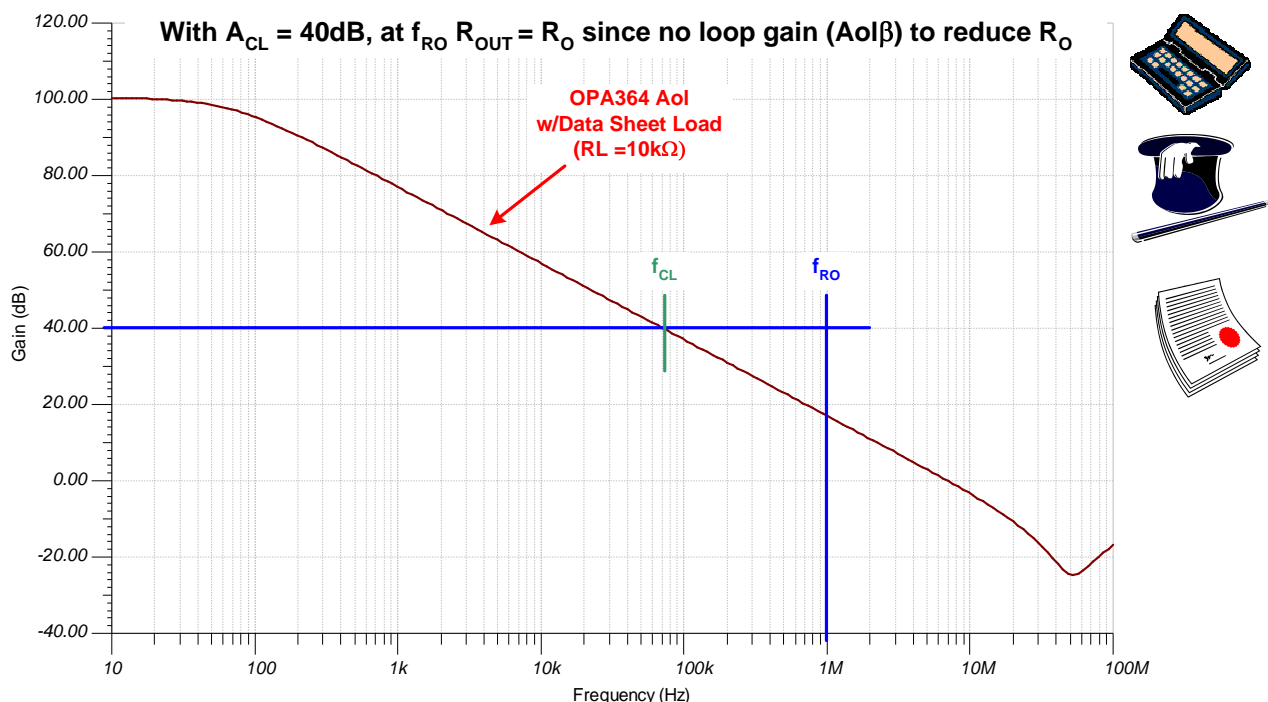


Fig. 3.12: Trick for Measuring  $R_O$

The test circuit in Fig. 3.13 shows one method for measuring  $R_O$  in the real world. This method we will call the  $R_O$  – Drive Method. Here the output of the OPA364 is driven through an AC coupling capacitor, C1. This is to ensure we do not load down the amplifier with any DC current. Most op amps'  $R_O$  gets smaller as large currents are driven through them. We want to measure  $R_O$  at its highest value (which will cause the most problem during AC stability analysis). In this technique the voltage at the output of the amplifier,  $V_O$ , is measured. Also measured is the voltage,  $V_{Test}$ , at the junction of the AC coupling capacitor, C1, and the current limiting resistor, R3. The current into the op amp's output is calculated and used to divide the voltage at the op amp to give us the measured  $R_O$  value! Note that although the OPA364 is a single supply op amp (1.8V to 5.5V) we can cleverly run it at +2.5V and -2.5V to avoid a more complicated level-shifting of our input or output signal.


**NOTE:** All measurements used in the "Drive Method" must be AC voltages without any DC component. If one uses the AC Analysis / Calculate Nodal Voltages in TINA SPICE he will get an rms voltage reading at the nodes which includes the DC voltages in the circuit (i.e. offset referred-to-output). If the Offset Voltage is significant in comparison to the AC Voltage components then an erroneous  $R_O$  will be calculated! In Fig. 3.13 the AC Analysis / Calculate Nodal Voltages was used but the DC Offset at VOA is about 87.63 $\mu$ V in comparison to 34.87mV and 353.55mV rms values which are dominated by AC voltage components.

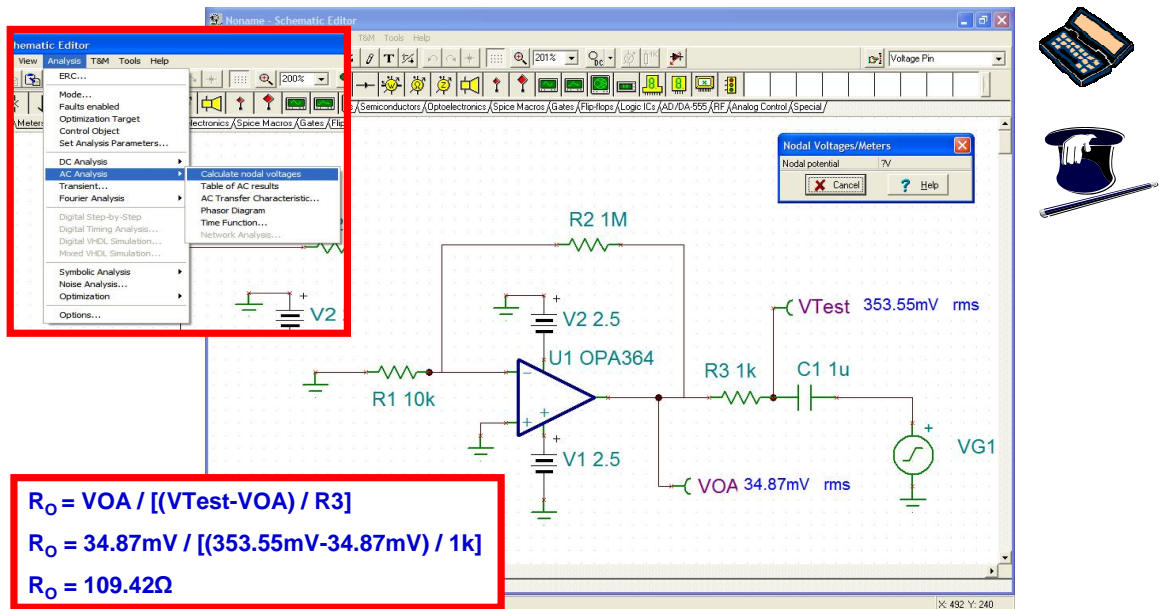

**Fig. 3.13: Measuring  $R_O$  – Drive Method**

The test circuits in Fig. 3.14 and Fig. 3.15 show another method for measuring  $R_O$  in the real world. This technique will take a voltage reading out of the op amp both loaded and unloaded and then compute the value for  $R_O$ . We will still need to use a high gain and high frequency combination to ensure there is no loop gain reducing  $R_{OUT}$  for our measurements. In this configuration a small AC signal is injected into the op amp's input. Inverting or non-inverting gain will work. In Fig. 3.14 we measure  $V_{OUT}$ , the unloaded voltage. Note that it is a small value of output so that when we do load it we will not pull much current since we are looking for the unloaded (and therefore highest value) of  $R_O$ .


**NOTE:** All measurements used in the “Load Method” must be AC voltages without any DC component. If one uses the AC Analysis / Calculate Nodal Voltages in TINA SPICE he will get an rms voltage reading at the nodes which includes the DC voltages in the circuit (i.e. offset referred-to-output). If the Offset Voltage is significant in comparison to the AC Voltage components then an erroneous  $R_O$  will be calculated!

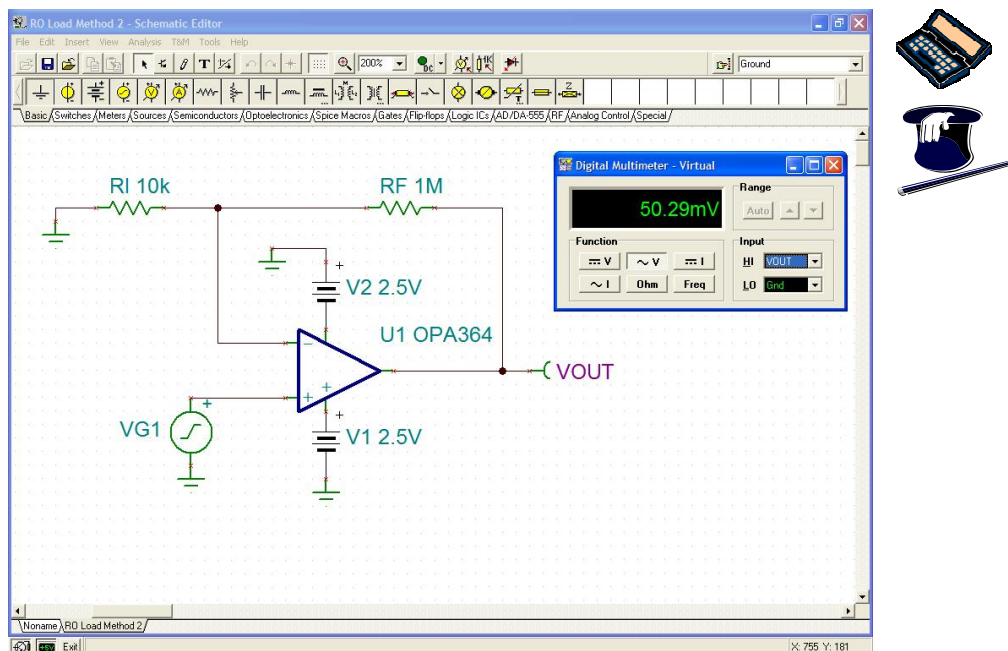

**Fig. 3.14: Measuring  $R_O$  – Load Method,  $V_{OUT}$  Unloaded**




In Fig. 3.15 we measure  $V_{OUTL}$ , the loaded value of  $V_{OUT}$  when  $R_L$  is attached to the output of the op amp. Note how the value of  $R_L$  does not cause large currents to flow into or out of the op amp's output.

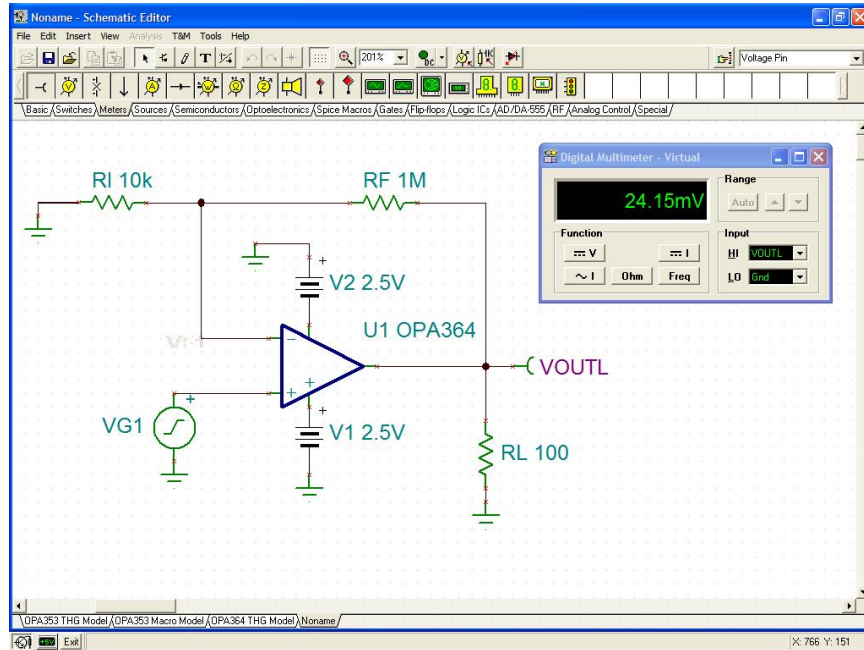

**Fig. 3.15: Measuring  $R_O$  – Load Method,  $V_{OUT}$  Loaded**

Now we have completed our measurements for the  $R_O$ -Load Method a simple calculation will result in the value for  $R_O$ . The unloaded value,  $V_{OUT}$ , is always there at  $VO$  whether or not a load,  $R_L$ , is present. From this we can create the final model shown in Fig. 3.16.  $I_{OUT}$  is, by inspection just  $V_{OUTL} / R_L$ . The drop across  $R_O$  is  $V_{OUT} - V_{OUTL}$ . The voltage drop across  $R_O$  divided by the current through it will give us the value for  $R_O$  as shown in this slide. Notice that this method yields  $R_O = 108.2\Omega$  and the  $R_O$ -Drive Method yielded  $R_O = 109.42\Omega$ . Either method is acceptable to measure real world  $R_O$ .

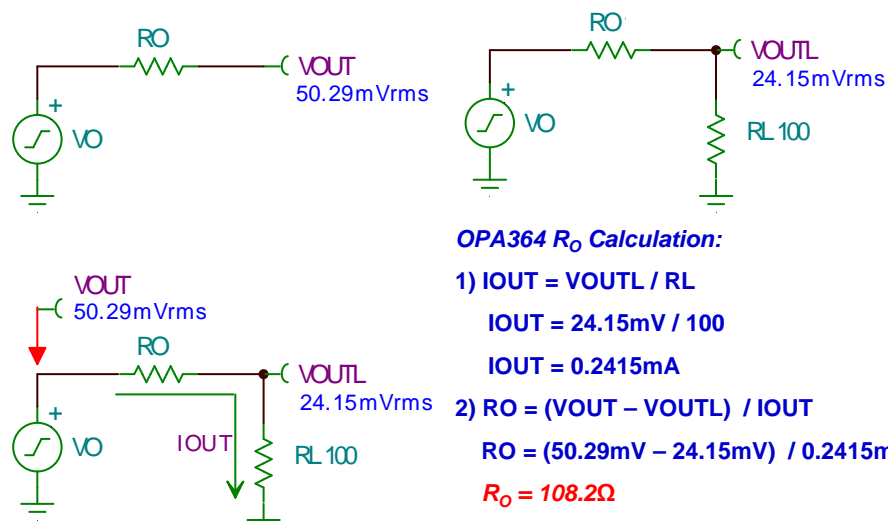

**OPA364  $R_O$  Calculation:**

$$1) I_{OUT} = V_{OUTL} / R_L$$

$$I_{OUT} = 24.15\text{mV} / 100$$

$$I_{OUT} = 0.2415\text{mA}$$

$$2) R_O = (V_{OUT} - V_{OUTL}) / I_{OUT}$$

$$R_O = (50.29\text{mV} - 24.15\text{mV}) / 0.2415\text{mA}$$

$$R_O = 108.2\Omega$$

$$3) R_O = [R_L (V_{OUT} - V_{OUTL})] / V_{OUTL}$$

{Substitute 1) into 2) and solve for  $R_O$ }

**Fig. 3.16: Measuring  $R_O$  – Load Method Calculation**

**References:**

Frederiksen, Thomas M. *Intuitive Operational Amplifiers, From Basics to Useful Applications*, Revised Edition. McGraw-Hill Book Company. New York, New York. 1988