## Comparing two-wire microphone circuits for automotive applications

By Peter Semig, Applications Manager Sanjeev Manandhar, Systems Engineer

Figure 3. Two-wire microphone circuit with op amps

