

Powering the AM335x With the TPS650250

This document details a power solution for the AM335x application processor with a TPS650250 Power Management Unit (PMU) or Power Management IC (PMIC).

Portable application solution size demands a high level of integration and the AM335x requires at least three different voltage rails with specific power-on and power-off sequencing requirements. The TPS650250 is a highly integrated power solution that provides the 1.8-, 3.3-, and 1.1-V rail signals required by the AM335x. The TPS650250 has three step-down converters, three low-dropout (LDO) regulators, and a voltage supervisor.

This document can be used as a reference for connectivity between the TPS650250 and the AM335x.

Contents

1	Power Requirements	2
	1.1 Power-On Sequence	3
	1.2 Power-Off Sequence	3
2	Schematic	4
3	Waveforms	5
4	Bill of Materials	8
5	Using the TPS650250 to Support DDR3	9
	5.1 Adjusting DCDC2 to 1.5 V	9
6	Use of a Clamping Circuit for Simultaneous Ramp Down	10
7	Conclusion	13
8	References	13

List of Figures

1	TPS650250 with Sequencing Circuit and AM335x Functional Block Diagram	2
2	TPS650250 Powering and Sequencing Circuit for the AM335x Powering Requirements	4
3	Power-on Sequence With PWRONRSTn	5
4	Power-on Sequence for the TPS650250 Converter Rails	6
5	Power-off Sequence With PWRONRSTn.....	6
6	Power-off Sequence for the TPS650250 Converter Rails	7
7	DCDC2 Resistor Change (R14) to Achieve 1.5 V	9
8	Clamping Circuit	10
9	TPS650250 Shutdown without Clamping Circuit	11
10	TPS650250 Shutdown with Clamping Circuit.....	12

List of Tables

1	AM335x Power Requirements.....	2
2	Bill of Materials	8
3	AM335x Power Requirements for Supporting DDR3.....	9
4	Clamp Circuit Testing	10

1 Power Requirements

Figure 1 shows a block diagram of the TPS650250-AM335x interface. A detailed circuit schematic detailing the power solution (TPS650250 and sequencing circuit) is found in Figure 2

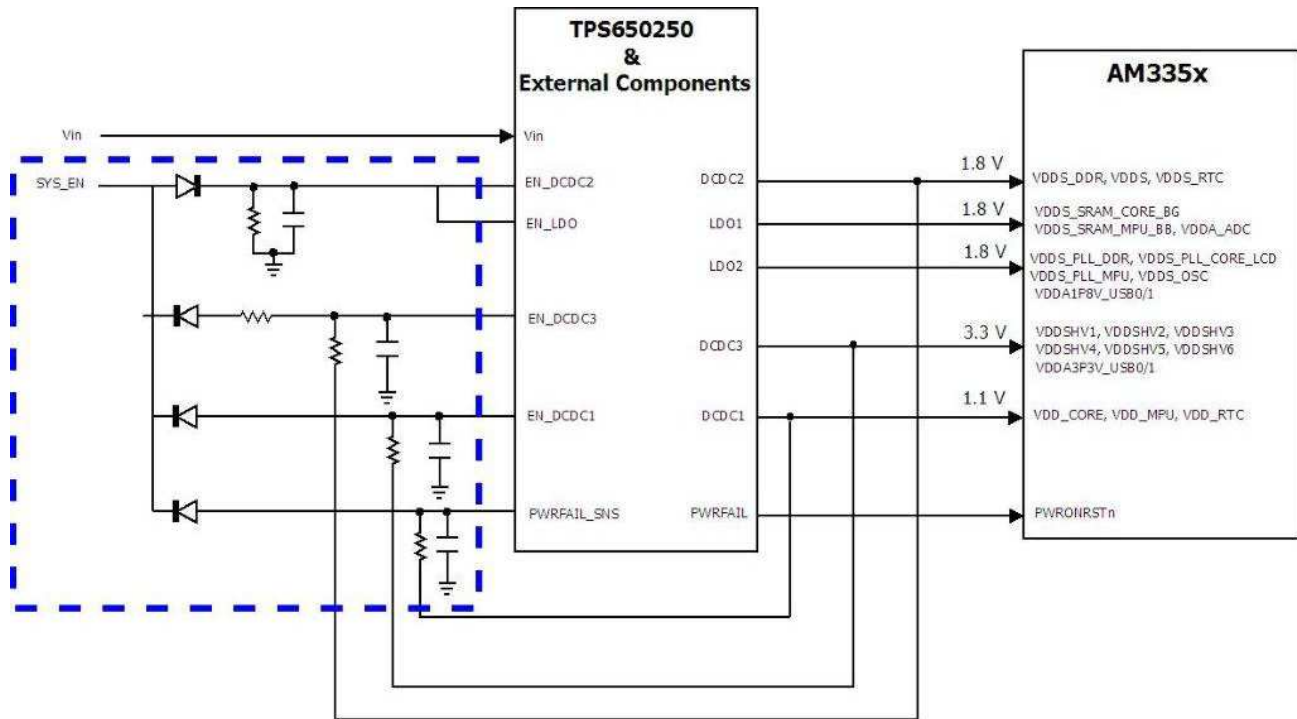


Figure 1. TPS650250 with Sequencing Circuit and AM335x Functional Block Diagram

The AM335x power requirements are listed on Table 1.

Table 1. AM335x Power Requirements

TPS650250						AM335x			
Power-Up Sequence	Power-Down Sequence	Power Supply	Vout [V]	Iout [mA]	Output Voltage [V]	Power Supply	Nominal Rating	Grouping	Max Current [mA]
3	1	DCDC1	2.8, 3.3, Adjustable	1600	1.1	VDD_CORE, VDD_MPU, VDD_RTC	1.1 V $\pm 4\%$	1.1-V Core	902
1	3	DCDC2	1.8, 2.5, Adjustable	800	1.8	VDDSD_DDR, VDDSD, VDDSD_RTC, VDDSHVx	1.8 V $\pm 5\%$	1.8-V IO	605
2	2	DCDC3	Adjustable	800	3.3	VDDA3P3V_USB0, VDDA3P3V_USB1, VDDSHVx	3.3 V $\pm 5\%$	3.3-V Analog and IO	370
1	3	VLDO1	1-3.3	200	1.8	VDDSD_SRAM_MPU_BB, VDDSD_SRAM_CORE_BG, VDDA_ADC	1.8 V $\pm 5\%$	1.8-V Analog	30
1	3	VLDO2	1-3.3	200	1.8	VDDSD_PLL_DDR, VDDSD_PLL_MPU, VDDSD_PLL_CORE_LCD, VDDSD_OSC, VDDA1P8V_USB0, VDDA1P8V_USB1	1.8 V $\pm 5\%$	1.8-V Analog	125
		VLDO3	1.0	30	1.0	n/a	n/a	n/a	n/a

The TPS650250 meets these power requirements with its three step-down converters and three LDO regulators. A simple sequencing circuit is needed to meet power-sequence requirements. This document details a power-sequencing solution for the RTC feature disable as described in the AM335x data sheet (SPRS717) and timing diagram Figure 4-5. *Power Supply Sequencing with RTC Feature Disabled.*

1.1 Power-On Sequence

According to the excerpt from the AM335x datasheet, the device must be powered on in the following order:

1. 1.8-V Analog and I/O
2. 3.3-V Analog and I/O
3. 1.1-V Core

An external system enable signal, SYS_EN, is enabled HIGH for power up. Diodes D2, D3, and D4 are reversed biased. Diode D1 is forward biased and EN1.8 is HIGH. This turns ON the 1.8-V rails DCDC2, LDO1, and LDO2. The output voltage of the DCDC2 converter, VO_1.8, is filtered into the enable of the DCDC3 converter EN3.3 and creates an RC (R7 and C12) delay before turning ON the 3.3-V rail. When EN3.3 reaches the turn-on threshold of the converter, VO_3.3 ramps up to nominal voltage. The output voltage of the DCDC3 converter, VO_3.3, is filtered into the enable of the DCDC1 converter EN1.1 and creates an RC (R16 and C15) delay before turning ON the 1.1 V rail. When EN1.1 reaches the turn-on threshold of the converter, VO_1.1 ramps up to nominal voltage. Lastly, the output voltage of the DCDC1 converter VO_1.1 is filtered into the power sense fail pin of the TPS650250 PWRRAIL_SNS and creates an RC (R17 and C16) delay between the last rail turning on and the Power On Reset signal, PWRONRSTn, pulling HIGH. The PWRFAIL_SNS signal is sensed through an internal comparator in the TPS650250 and triggers the PWRONRSTn signal HIGH when PWRRAIL_SNS reaches 1 V.

Power-on sequence is complete. The proper connections for this power-on sequencing are shown in [Figure 2](#).

1.2 Power-Off Sequence

As shown in the excerpt from the AM335x data sheet, the device must be powered off in reverse order as power-on.

1. 1.1-V Core
2. 3.3-V Analog and I/O
3. 1.8-V Analog and I/O

SYS_EN is LOW for power down. D2, D3, and D4 are forward biased. PWRFAIL_SNS becomes LOW to pull PWRONRSTn LOW. EN1.1 becomes LOW and VO_1.1 ramps down. EN3.3 signal is filtered to create an RC (R3 and C12) delay between VO_1.1 ramping down and VO_3.3 ramping down. Lastly, D1 is reversed biased and capacitor C11 discharges through resistor R2 with a delay longer than the ramping down of VO1.1 and VO3.3. After VO1.1 and VO3.3 are off, the 1.8-V rail ramps down.

Power-off sequence is complete.

The proper connections for this power-off sequencing are shown in [Figure 2](#).

2 Schematic

Figure 2 shows the circuit schematic detailing the external components required by the TPS650250 to achieve the 1.8-, 3.3-, and 1.1-V power rails required by the AM335x. In addition, Figure 2 shows the sequencing circuit that achieves the proper power-on, power-off, and PWRONRSTn sequencing required by the AM335x.



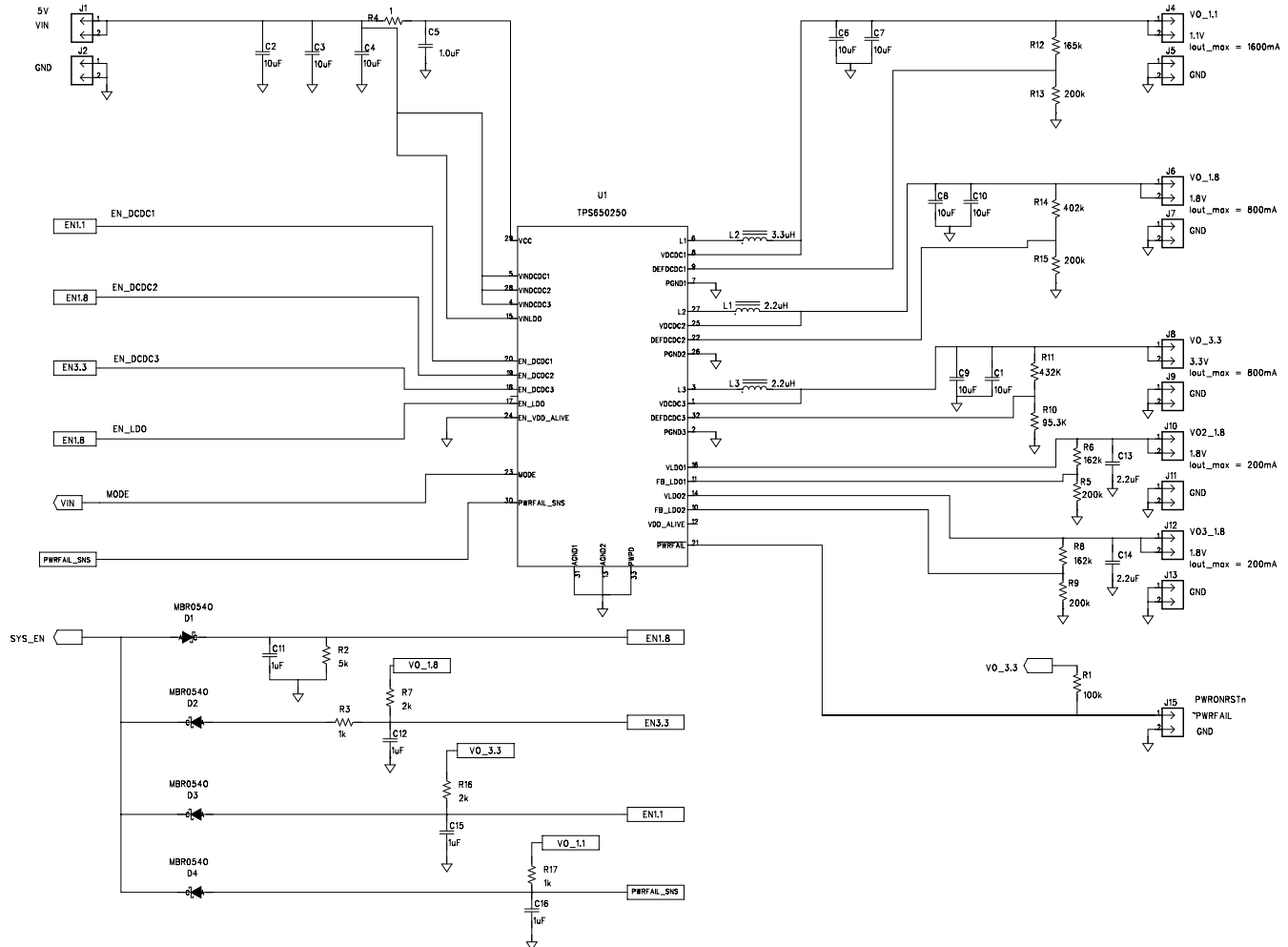


Figure 2. TPS650250 Powering and Sequencing Circuit for the AM335x Powering Requirements

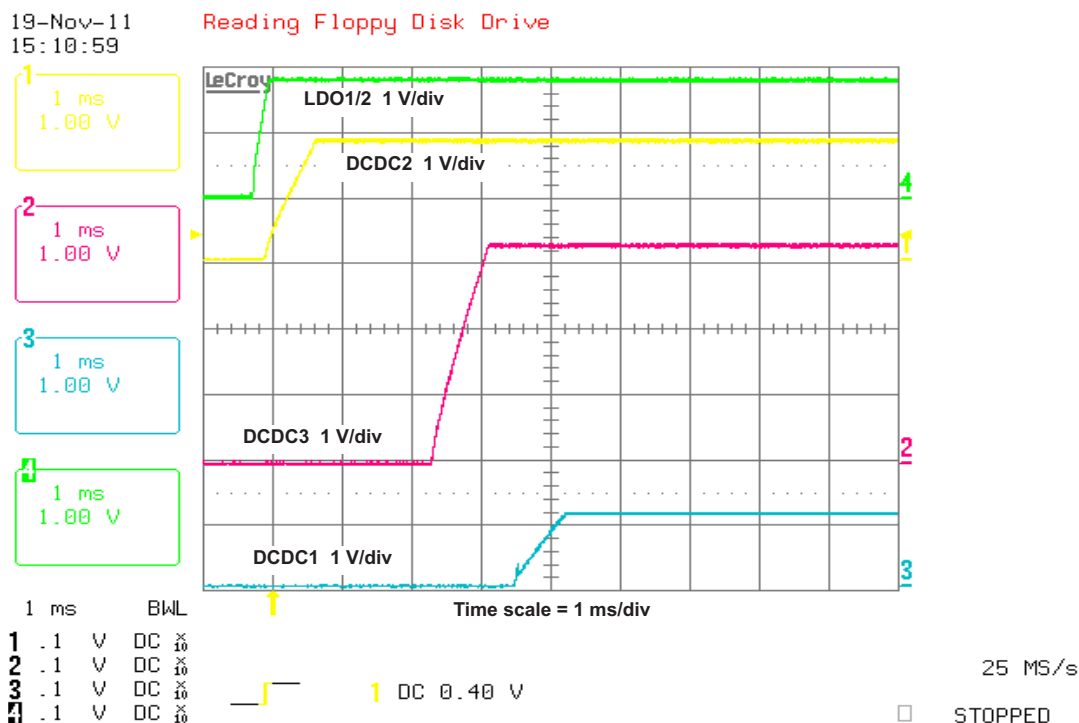

1.8-V (DCDC2,LDO1/2), 3.3-V (DCDC3), and 1.1-V (DCDC1) Rails


Figure 4. Power-on Sequence for the TPS650250 Converter Rails

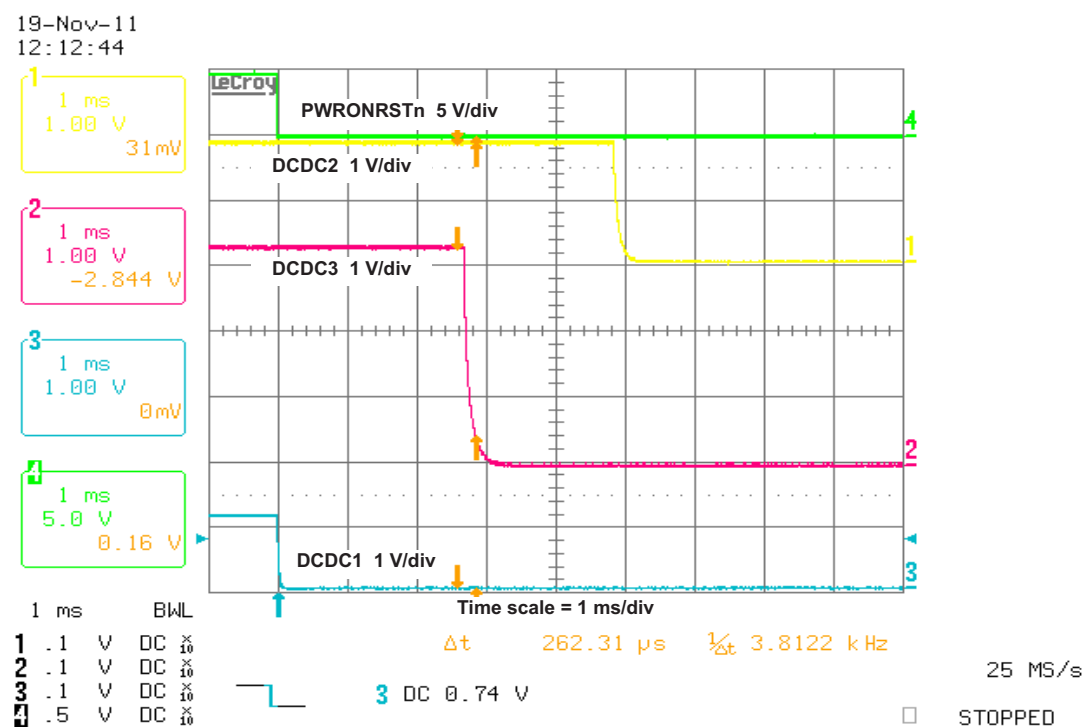

1.8-V (DCDC2), 3.3-V (DCDC3), and 1.1-V (DCDC1) Rails

Figure 5. Power-off Sequence With PWRONRSTn

19-Nov-11
15:11:30

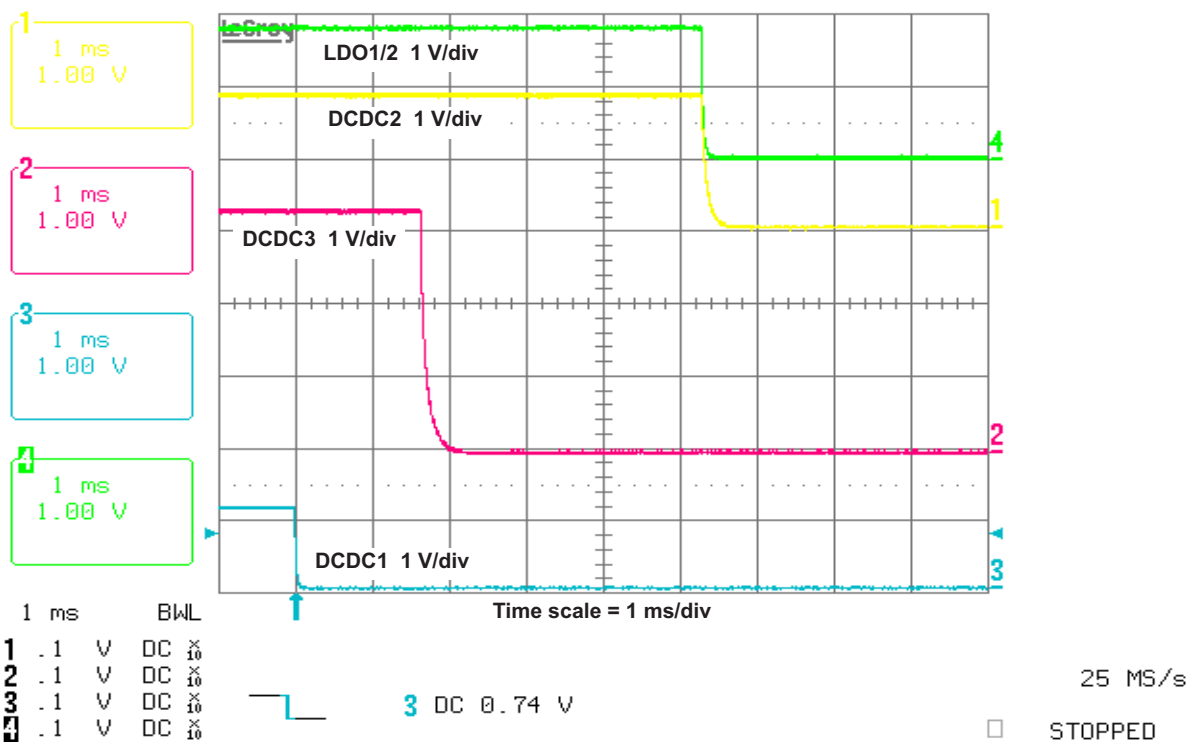

1.8-V (DCDC2,LDO1/2), 3.3-V (DCDC3), and 1.1-V (DCDC1) Rails

Figure 6. Power-off Sequence for the TPS650250 Converter Rails

4 Bill of Materials

The bill of materials is displayed in [Table 2](#).

Table 2. Bill of Materials

Count	RefDes	Value	Description	Size	Part Number	MFR
1	C1	10 μ F	Capacitor, ceramic, 6.3 V, X5R, 10%	0805	Std	Std
1	C2	10 μ F	Capacitor, ceramic, 6.3 V, X5R, 10%	0805	Std	Std
1	C3	10 μ F	Capacitor, ceramic, 6.3 V, X5R, 10%	0805	Std	Std
1	C4	10 μ F	Capacitor, ceramic, 6.3 V, X5R, 10%	0805	Std	Std
1	C5	1.0 μ F	Capacitor, ceramic, 6.3 V, X5R, 10%	0603	Std	Std
1	C6	10 μ F	Capacitor, ceramic, 6.3 V, X5R, 10%	0805	Std	Std
1	C7	10 μ F	Capacitor, ceramic, 6.3 V, X5R, 10%	0805	Std	Std
1	C8	10 μ F	Capacitor, ceramic, 6.3 V, X5R, 10%	0805	Std	Std
1	C9	10 μ F	Capacitor, ceramic, 6.3 V, X5R, 10%	0805	Std	Std
1	C10	10 μ F	Capacitor, ceramic, 6.3 V, X5R, 10%	0805	Std	Std
1	C11	1 μ F	Capacitor, ceramic, 6.3 V, X5R, 10%	0805	Std	Std
1	C12	1 μ F	Capacitor, ceramic, 6.3 V, X5R, 10%	0805	Std	Std
1	C13	2.2 μ F	Capacitor, ceramic, 6.3 V, X5R, 10%	0603	Std	Std
1	C14	2.2 μ F	Capacitor, ceramic, 6.3 V, X5R, 10%	0603	Std	Std
1	C15	1 μ F	Capacitor, ceramic, 6.3 V, X5R, 10%	0805	Std	Std
1	C16	1 μ F	Capacitor, ceramic, 6.3 V, X5R, 10%	0805	Std	Std
1	D1	MBR054O	Diode, Schottky, 0.5 A, x0V	SOD-123	MBR054O	MCC Semi
1	D2	MBR054O	Diode, Schottky, 0.5 A, x0V	SOD-123	MBR054O	MCC Semi
1	D3	MBR054O	Diode, Schottky, 0.5 A, x0V	SOD-123	MBR054O	MCC Semi
1	D4	MBR054O	Diode, Schottky, 0.5 A, x0V	SOD-123	MBR054O	MCC Semi
1	L1	2.2 μ H	Inductor, SMT, 1.72 A, 59 m Ω	0.157 \times 0.157 inch	VLCF4020T-2R2N1R7	TDK
1	L2	3.3 μ H	Inductor, SMT, 1.52 A, 78 m Ω	0.157 \times 0.157 inch	VLCF4020T-3R3N1R5	TDK
1	L3	2.2 μ H	Inductor, SMT, 1.72 A, 59 m Ω	0.157 \times 0.157 inch	VLCF4020T-2R2N1R7	TDK
1	R1	100 k Ω	Resistor, chip, 1/16W, 1%	0603	Std	Std
1	R2	5 k Ω	Resistor, chip, 1/16W, 5%	0603	Std	Std
1	R3	1 k Ω	Resistor, chip, 1/16W, 5%	0603	Std	Std
1	R4	1 Ω	Resistor, chip, 1/16W, 5%	0603	Std	Std
1	R5	200 k Ω	Resistor, chip, 1/16W, 1%	0603	Std	Std
1	R6	162 k Ω	Resistor, chip, 1/16W, 1%	0603	Std	Std
1	R7	2 k Ω	Resistor, chip, 1/16W, 5%	0603	Std	Std
1	R8	162 k Ω	Resistor, chip, 1/16W, 1%	0603	Std	Std
1	R9	200 k Ω	Resistor, chip, 1/16W, 1%	0603	Std	Std
1	R10	95.3 k Ω	Resistor, chip, 1/16W, 1%	0603	Std	Std
1	R11	432 k Ω	Resistor, chip, 1/16W, 1%	0603	Std	Std
1	R12	165 k Ω	Resistor, chip, 1/16W, 1%	0603	Std	Std
1	R13	200 k Ω	Resistor, chip, 1/16W, 1%	0603	Std	Std
1	R14	402 k Ω	Resistor, chip, 1/16W, 1%	0603	Std	Std
1	R15	200 k Ω	Resistor, chip, 1/16W, 1%	0603	Std	Std
1	R16	2 k Ω	Resistor, chip, 1/16W, 5%	0603	Std	Std
1	R17	1 k Ω	Resistor, chip, 1/16W, 5%	0603	Std	Std
1	U1	TPS650250	IC, Power Management ICs for Li-Ion Powered Systems	QFN-32	TI	

- Notes: 1. These assemblies are ESD sensitive, ESD precautions shall be observed.
2. These assemblies must be clean and free from flux and all contaminants. Use of no clean flux is not acceptable.
3. These assemblies must comply with workmanship standards IPC-A-610 Class 2.
4. Ref designators marked with an asterisk (***) cannot be substituted. All other components can be substituted with equivalent MFG components.

5 Using the TPS650250 to Support DDR3

The TPS650250 provides the power required by the AM335x and is capable of supporting external DDR3 memory applications. However, the 1.8-V I/O output current capabilities are reduced from what was presented in [Section 1](#). [Table 3](#) shows the power requirements for powering the AM335x with DDR3 support.

Table 3. AM335x Power Requirements for Supporting DDR3

TPS650250						AM335x			
Power-Up Sequence	Power-Down Sequence	Power Supply	Vout [V]	Iout [mA]	Output Voltage [V]	Power Supply	Nominal Rating	Grouping	Max Current [mA]
4	1	DCDC1	2.8, 3.3, Adjustable	1600	1.1	VDD_CORE, VDD_MPU, VDD_RTC	1.1 V \pm 4%	1.1-V Core	902
2	3	DCDC2	1.8, 2.5, Adjustable	800	1.5	VDDS_DDR	1.5 V \pm 5%	1.5-V DDR3	300
3	2	DCDC3	Adjustable	800	3.3	VDDA3P3V_USB0, VDDA3P3V_USB1, VDDSHVx	3.3 V \pm 5%	3.3-V Analog and IO	370
1	4	VLDO1	1–3.3	200	1.8	VDDS_SRAM_MPU_BB, VDDS_SRAM_CORE_BG, VDDA_ADC, VDDSHVx, VDDS_PLL_DDR, VDDS_PLL_MPU, VDDS_PLL_CORE_LCD, VDDS_OSC, VDDA1P8V_USB0, VDDA1P8V_USB1	1.8 V \pm 5%	1.8-V Analog	155
1	4	VLDO2	1–3.3	200	1.8	VDDS, VDDS_RTC, VDDSHVx	1.8 V \pm 5%	1.8-V IO	55
		VLDO3	1.0	30	1.0	n/a	n/a	n/a	n/a

On the TPS650250, DCDC2 is dedicated to 1.5 V to support external DDR3 applications. The AM335x DDR3 I/O domain (VDDS_DDR) must be 1.5 V, leaving 500 mA of available current for external DDR3 memory.

The 1.8-V I/O domains (VDDSHVx) are now powered through the 1.8-V rails, VLDO1 and VLDO2, of the TPS650250. The added loads cause current constraints on LDO1 and LDO2 so as not to go over the rated current of 200 mA. Therefore, the AM335x must be operated such that VDDSHVx does not cause each LDO current to exceed 200 mA on VLDO1 or VLDO2.

5.1 Adjusting DCDC2 to 1.5 V

A 1.5-V rail is required to power DDR3. If R15 is 200 k Ω , change R14 to 301 k Ω to adjust the output voltage of DCDC2 to 1.5 V. [Figure 7](#) shows this change of the resistor divider for DCDC2.

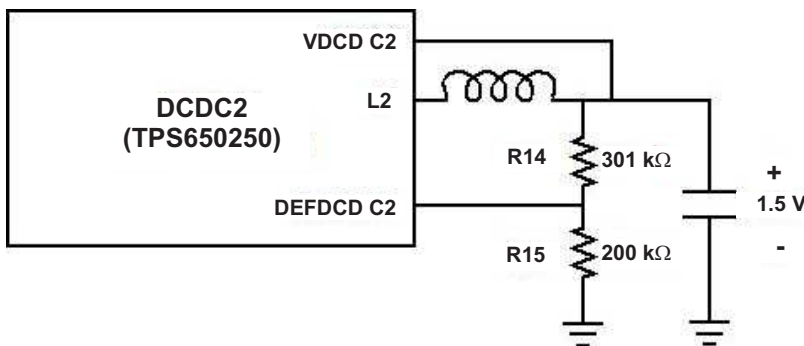


Figure 7. DCDC2 Resistor Change (R14) to Achieve 1.5 V

6 Use of a Clamping Circuit for Simultaneous Ramp Down

Reading the datasheet for the AM335x, ([SPRS717](#)), and the challenge when ramping down VDDS and VDDSHVx [1–6] simultaneously is obvious. “If it is desired to ramp down VDDS and VDDSHVx [1–6] simultaneously, it should always be ensured that the difference between VDDS and VDDSHVx [1–6] during the entire power-down sequence is < 2 V. If this is violated it can result in reliability risks for the device.” This only refers to 1.8-V VDDS and 3.3-V VDDSHVx rails. The worst-case scenario of this issue is the 3.3-V rail remains high possibly because of large output capacitance or no load being present on the output while, the 1.8-V rail ramps down quickly such as if it were fully loaded.

A solution to this issue is the use of a clamping circuit between the 1.8-V VDDS and 3.3-V VDDSHVx rails, ensuring proper shutdown when V_{IN} is removed. As illustrated in [Figure 8](#), the clamping circuit suggested is only five additional components, 3 of which are resistors. The TLVH431 is regulated at 1.5 V through resistor divider R1 and R2. Before the rails ramp down, Q1 is off. When the 1.8-V rail drops, Vbase drops and Q1 turns ON. The 3.3-V rail discharges through Q1 and the 1.8-V rail. This technique ensures that the difference between the 3.3-V VDDSHVx rails and the 1.8-V VDDS rail never exceeds 2 V.

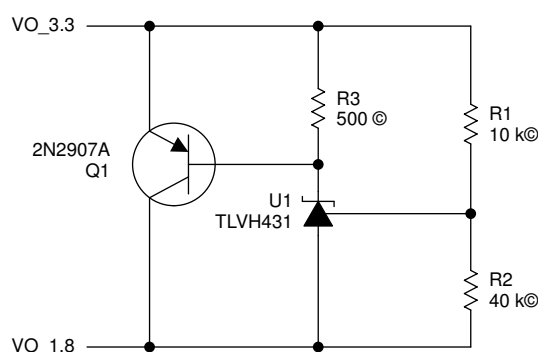


Figure 8. Clamping Circuit

[Figure 9](#) shows the power-down sequence for the DCDCs, LDOs and PWRONRSTn outputs and signals of the TPS650250 without the clamping circuit. This is the worst-case scenario since the VDDSHVx 3.3-V rail is not loaded at all while the VDDS 1.8-V rail is fully loaded. Notice that the difference between DCDC3 and DCDC2 (VDDSHVx and VDDS) exceeds 2 V. See [Table 4](#) for more testing details.

[Figure 10](#) shows the power-down sequence for the DCDCs, LDOs and PWRONRSTn output voltages of the TPS650250 with the clamping circuit. With the same load conditions, the clamp circuit test results show the difference between DCDC3 and DCDC2 is kept below 2 V. Notice how the 3.3-V rail tracks the 1.8-V rail. Refer to [Table 4](#) for more testing details.

Table 4. Clamp Circuit Testing

Rail	Current Load
DCDC1 1.1 V	1000 mA
DCDC2 1.8 V	600 mA
DCDC3 3.3 V	0.01 mA
LDOs 1.8 V	200 mA

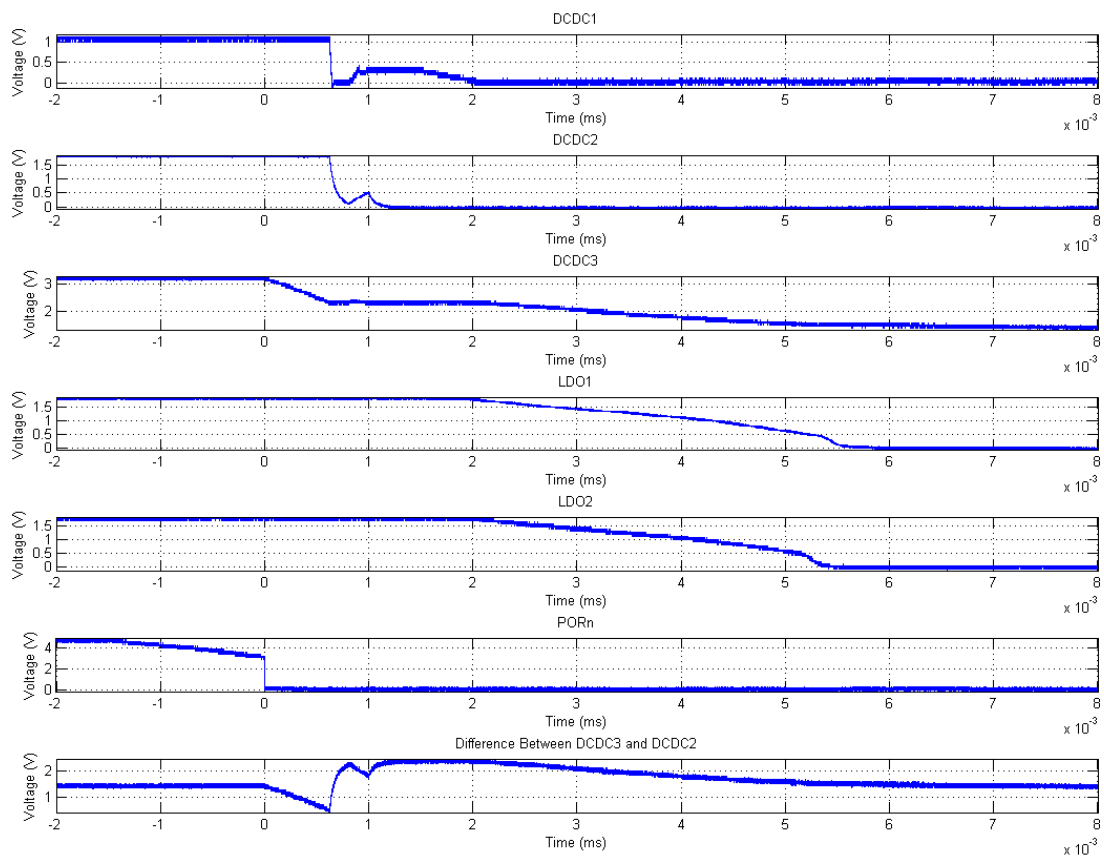


Figure 9. TPS650250 Shutdown without Clamping Circuit

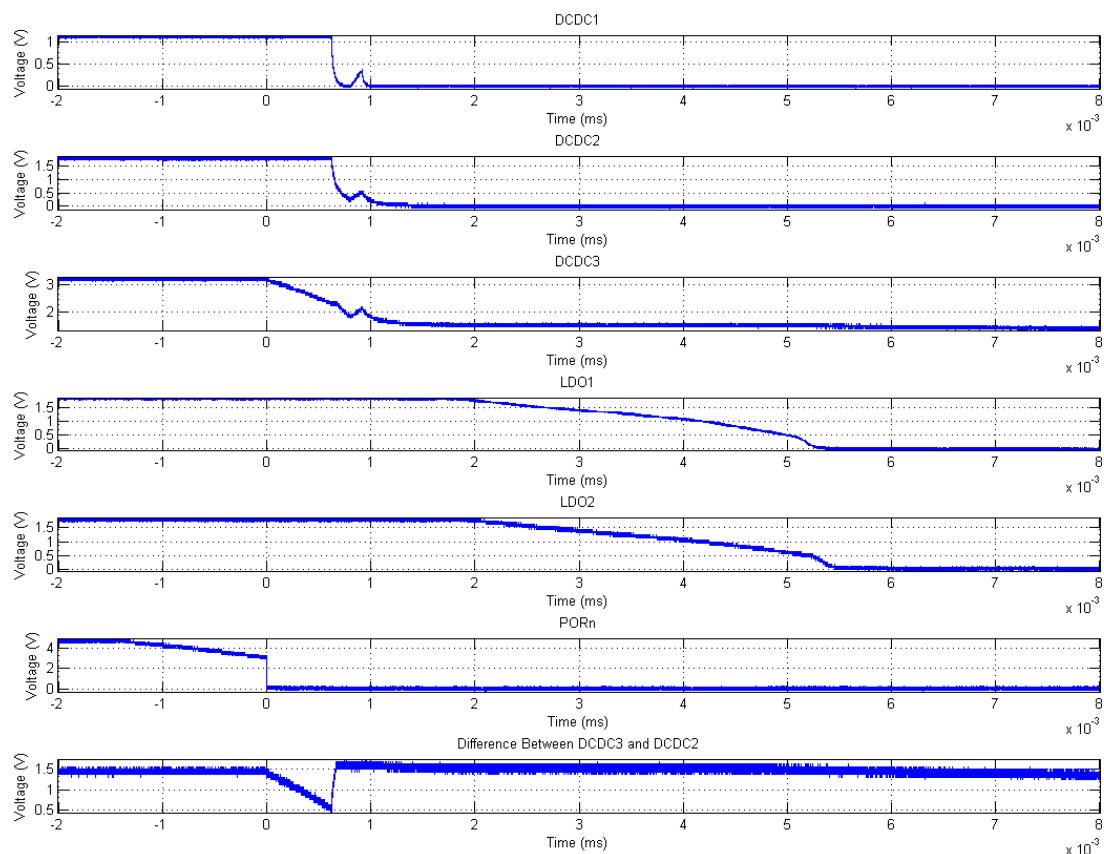


Figure 10. TPS650250 Shutdown with Clamping Circuit

7 Conclusion

The TPS650250 provides a low-cost, comprehensive power solution for the AM335x. This reference design demonstrates the external components of the TPS650250 to provide the required voltage rails and a simple sequencing circuit that meets power-on and power-off sequencing required by the AM335x. For external DDR3 applications, the output voltage of DCDC2 for the TPS650250 can be easily adjusted to accommodate a 1.5-V rail. However, this limits the output-current capabilities of the 1.8-V I/O Domains (VDDSHVx) in the AM335x. If simultaneous ramp down of the VDDSHVx and VDDS rail is desired a clamping circuit may be required.

8 References

1. *TPS650250, Power Management IC for Li-Ion Powered Systems* data sheet ([SLVS843](#))
2. *AM335x, AM335x ARM® Cortex™-A8 Microprocessors (MPUs)* data sheet ([SPRS717](#))

EVALUATION BOARD/KIT/MODULE (EVM) ADDITIONAL TERMS

Texas Instruments (TI) provides the enclosed Evaluation Board/Kit/Module (EVM) under the following conditions:

The user assumes all responsibility and liability for proper and safe handling of the goods. Further, the user indemnifies TI from all claims arising from the handling or use of the goods.

Should this evaluation board/kit not meet the specifications indicated in the User's Guide, the board/kit may be returned within 30 days from the date of delivery for a full refund. THE FOREGOING LIMITED WARRANTY IS THE EXCLUSIVE WARRANTY MADE BY SELLER TO BUYER AND IS IN LIEU OF ALL OTHER WARRANTIES, EXPRESSED, IMPLIED, OR STATUTORY, INCLUDING ANY WARRANTY OF MERCHANTABILITY OR FITNESS FOR ANY PARTICULAR PURPOSE. EXCEPT TO THE EXTENT OF THE INDEMNITY SET FORTH ABOVE, NEITHER PARTY SHALL BE LIABLE TO THE OTHER FOR ANY INDIRECT, SPECIAL, INCIDENTAL, OR CONSEQUENTIAL DAMAGES.

Please read the User's Guide and, specifically, the Warnings and Restrictions notice in the User's Guide prior to handling the product. This notice contains important safety information about temperatures and voltages. For additional information on TI's environmental and/or safety programs, please visit www.ti.com/esh or contact TI.

No license is granted under any patent right or other intellectual property right of TI covering or relating to any machine, process, or combination in which such TI products or services might be or are used. TI currently deals with a variety of customers for products, and therefore our arrangement with the user is not exclusive. TI assumes no liability for applications assistance, customer product design, software performance, or infringement of patents or services described herein.

REGULATORY COMPLIANCE INFORMATION

As noted in the EVM User's Guide and/or EVM itself, this EVM and/or accompanying hardware may or may not be subject to the Federal Communications Commission (FCC) and Industry Canada (IC) rules.

For EVMs **not** subject to the above rules, this evaluation board/kit/module is intended for use for ENGINEERING DEVELOPMENT, DEMONSTRATION OR EVALUATION PURPOSES ONLY and is not considered by TI to be a finished end product fit for general consumer use. It generates, uses, and can radiate radio frequency energy and has not been tested for compliance with the limits of computing devices pursuant to part 15 of FCC or ICES-003 rules, which are designed to provide reasonable protection against radio frequency interference. Operation of the equipment may cause interference with radio communications, in which case the user at his own expense will be required to take whatever measures may be required to correct this interference.

General Statement for EVMs including a radio

User Power/Frequency Use Obligations: This radio is intended for development/professional use only in legally allocated frequency and power limits. Any use of radio frequencies and/or power availability of this EVM and its development application(s) must comply with local laws governing radio spectrum allocation and power limits for this evaluation module. It is the user's sole responsibility to only operate this radio in legally acceptable frequency space and within legally mandated power limitations. Any exceptions to this are strictly prohibited and unauthorized by Texas Instruments unless user has obtained appropriate experimental/development licenses from local regulatory authorities, which is responsibility of user including its acceptable authorization.

For EVMs annotated as FCC – FEDERAL COMMUNICATIONS COMMISSION Part 15 Compliant

Caution

This device complies with part 15 of the FCC Rules. Operation is subject to the following two conditions: (1) This device may not cause harmful interference, and (2) this device must accept any interference received, including interference that may cause undesired operation.

Changes or modifications not expressly approved by the party responsible for compliance could void the user's authority to operate the equipment.

FCC Interference Statement for Class A EVM devices

This equipment has been tested and found to comply with the limits for a Class A digital device, pursuant to part 15 of the FCC Rules. These limits are designed to provide reasonable protection against harmful interference when the equipment is operated in a commercial environment. This equipment generates, uses, and can radiate radio frequency energy and, if not installed and used in accordance with the instruction manual, may cause harmful interference to radio communications. Operation of this equipment in a residential area is likely to cause harmful interference in which case the user will be required to correct the interference at his own expense.

FCC Interference Statement for Class B EVM devices

This equipment has been tested and found to comply with the limits for a Class B digital device, pursuant to part 15 of the FCC Rules. These limits are designed to provide reasonable protection against harmful interference in a residential installation. This equipment generates, uses and can radiate radio frequency energy and, if not installed and used in accordance with the instructions, may cause harmful interference to radio communications. However, there is no guarantee that interference will not occur in a particular installation. If this equipment does cause harmful interference to radio or television reception, which can be determined by turning the equipment off and on, the user is encouraged to try to correct the interference by one or more of the following measures:

- Reorient or relocate the receiving antenna.
- Increase the separation between the equipment and receiver.
- Connect the equipment into an outlet on a circuit different from that to which the receiver is connected.
- Consult the dealer or an experienced radio/TV technician for help.

For EVMs annotated as IC – INDUSTRY CANADA Compliant

This Class A or B digital apparatus complies with Canadian ICES-003.

Changes or modifications not expressly approved by the party responsible for compliance could void the user's authority to operate the equipment.

Concerning EVMs including radio transmitters

This device complies with Industry Canada licence-exempt RSS standard(s). Operation is subject to the following two conditions: (1) this device may not cause interference, and (2) this device must accept any interference, including interference that may cause undesired operation of the device.

Concerning EVMs including detachable antennas

Under Industry Canada regulations, this radio transmitter may only operate using an antenna of a type and maximum (or lesser) gain approved for the transmitter by Industry Canada. To reduce potential radio interference to other users, the antenna type and its gain should be so chosen that the equivalent isotropically radiated power (e.i.r.p.) is not more than that necessary for successful communication.

This radio transmitter has been approved by Industry Canada to operate with the antenna types listed in the user guide with the maximum permissible gain and required antenna impedance for each antenna type indicated. Antenna types not included in this list, having a gain greater than the maximum gain indicated for that type, are strictly prohibited for use with this device.

Cet appareil numérique de la classe A ou B est conforme à la norme NMB-003 du Canada.

Les changements ou les modifications pas expressément approuvés par la partie responsable de la conformité ont pu vider l'autorité de l'utilisateur pour actionner l'équipement.

Concernant les EVMs avec appareils radio

Le présent appareil est conforme aux CNR d'Industrie Canada applicables aux appareils radio exempts de licence. L'exploitation est autorisée aux deux conditions suivantes : (1) l'appareil ne doit pas produire de brouillage, et (2) l'utilisateur de l'appareil doit accepter tout brouillage radioélectrique subi, même si le brouillage est susceptible d'en compromettre le fonctionnement.

Concernant les EVMs avec antennes détachables

Conformément à la réglementation d'Industrie Canada, le présent émetteur radio peut fonctionner avec une antenne d'un type et d'un gain maximal (ou inférieur) approuvé pour l'émetteur par Industrie Canada. Dans le but de réduire les risques de brouillage radioélectrique à l'intention des autres utilisateurs, il faut choisir le type d'antenne et son gain de sorte que la puissance isotrope rayonnée équivalente (p.i.r.e.) ne dépasse pas l'intensité nécessaire à l'établissement d'une communication satisfaisante.

Le présent émetteur radio a été approuvé par Industrie Canada pour fonctionner avec les types d'antenne énumérés dans le manuel d'usage et ayant un gain admissible maximal et l'impédance requise pour chaque type d'antenne. Les types d'antenne non inclus dans cette liste, ou dont le gain est supérieur au gain maximal indiqué, sont strictement interdits pour l'exploitation de l'émetteur.

【Important Notice for Users of this Product in Japan】

This development kit is NOT certified as Confirming to Technical Regulations of Radio Law of Japan

If you use this product in Japan, you are required by Radio Law of Japan to follow the instructions below with respect to this product:

1. Use this product in a shielded room or any other test facility as defined in the notification #173 issued by Ministry of Internal Affairs and Communications on March 28, 2006, based on Sub-section 1.1 of Article 6 of the Ministry's Rule for Enforcement of Radio Law of Japan,
2. Use this product only after you obtained the license of Test Radio Station as provided in Radio Law of Japan with respect to this product, or
3. Use of this product only after you obtained the Technical Regulations Conformity Certification as provided in Radio Law of Japan with respect to this product. Also, please do not transfer this product, unless you give the same notice above to the transferee. Please note that if you could not follow the instructions above, you will be subject to penalties of Radio Law of Japan.

Texas Instruments Japan Limited
(address) 24-1, Nishi-Shinjuku 6 chome, Shinjuku-ku, Tokyo, Japan

<http://www.tij.co.jp>

【ご使用にあたっての注】

本開発キットは技術基準適合証明を受けておりません。

本製品のご使用に際しては、電波法遵守のため、以下のいずれかの措置を取っていただく必要がありますのでご注意ください。

1. 電波法施行規則第6条第1項第1号に基づく平成18年3月28日総務省告示第173号で定められた電波暗室等の試験設備でご使用いただく。
2. 実験局の免許を取得後ご使用いただく。
3. 技術基準適合証明を取得後ご使用いただく。

なお、本製品は、上記の「ご使用にあたっての注意」を譲渡先、移転先に通知しない限り、譲渡、移転できないものとします。

上記を遵守頂けない場合は、電波法の罰則が適用される可能性があることをご留意ください。

日本テキサス・インスツルメンツ株式会社
東京都新宿区西新宿 6 丁目 2 4 番 1 号
西新宿三井ビル

<http://www.tij.co.jp>

EVALUATION BOARD/KIT/MODULE (EVM) WARNINGS, RESTRICTIONS AND DISCLAIMERS

For Feasibility Evaluation Only, in Laboratory/Development Environments. Unless otherwise indicated, this EVM is not a finished electrical equipment and not intended for consumer use. It is intended solely for use for preliminary feasibility evaluation in laboratory/development environments by technically qualified electronics experts who are familiar with the dangers and application risks associated with handling electrical mechanical components, systems and subsystems. It should not be used as all or part of a finished end product.

Your Sole Responsibility and Risk. You acknowledge, represent and agree that:

1. You have unique knowledge concerning Federal, State and local regulatory requirements (including but not limited to Food and Drug Administration regulations, if applicable) which relate to your products and which relate to your use (and/or that of your employees, affiliates, contractors or designees) of the EVM for evaluation, testing and other purposes.
2. You have full and exclusive responsibility to assure the safety and compliance of your products with all such laws and other applicable regulatory requirements, and also to assure the safety of any activities to be conducted by you and/or your employees, affiliates, contractors or designees, using the EVM. Further, you are responsible to assure that any interfaces (electronic and/or mechanical) between the EVM and any human body are designed with suitable isolation and means to safely limit accessible leakage currents to minimize the risk of electrical shock hazard.
3. You will employ reasonable safeguards to ensure that your use of the EVM will not result in any property damage, injury or death, even if the EVM should fail to perform as described or expected.
4. You will take care of proper disposal and recycling of the EVM's electronic components and packing materials.

Certain Instructions. It is important to operate this EVM within TI's recommended specifications and environmental considerations per the user guidelines. Exceeding the specified EVM ratings (including but not limited to input and output voltage, current, power, and environmental ranges) may cause property damage, personal injury or death. If there are questions concerning these ratings please contact a TI field representative prior to connecting interface electronics including input power and intended loads. Any loads applied outside of the specified output range may result in unintended and/or inaccurate operation and/or possible permanent damage to the EVM and/or interface electronics. Please consult the EVM User's Guide prior to connecting any load to the EVM output. If there is uncertainty as to the load specification, please contact a TI field representative. During normal operation, some circuit components may have case temperatures greater than 60°C as long as the input and output are maintained at a normal ambient operating temperature. These components include but are not limited to linear regulators, switching transistors, pass transistors, and current sense resistors which can be identified using the EVM schematic located in the EVM User's Guide. When placing measurement probes near these devices during normal operation, please be aware that these devices may be very warm to the touch. As with all electronic evaluation tools, only qualified personnel knowledgeable in electronic measurement and diagnostics normally found in development environments should use these EVMs.

Agreement to Defend, Indemnify and Hold Harmless. You agree to defend, indemnify and hold TI, its licensors and their representatives harmless from and against any and all claims, damages, losses, expenses, costs and liabilities (collectively, "Claims") arising out of or in connection with any use of the EVM that is not in accordance with the terms of the agreement. This obligation shall apply whether Claims arise under law of tort or contract or any other legal theory, and even if the EVM fails to perform as described or expected.

Safety-Critical or Life-Critical Applications. If you intend to evaluate the components for possible use in safety critical applications (such as life support) where a failure of the TI product would reasonably be expected to cause severe personal injury or death, such as devices which are classified as FDA Class III or similar classification, then you must specifically notify TI of such intent and enter into a separate Assurance and Indemnity Agreement.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2012, Texas Instruments Incorporated

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products (also referred to herein as "components") are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of significant portions of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI components or services with statements different from or beyond the parameters stated by TI for that component or service voids all express and any implied warranties for the associated TI component or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards which anticipate dangerous consequences of failures, monitor failures and their consequences, lessen the likelihood of failures that might cause harm and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed a special agreement specifically governing such use.

Only those TI components which TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components which have **not** been so designated is solely at the Buyer's risk, and that Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.

Products

Audio	www.ti.com/audio
Amplifiers	amplifier.ti.com
Data Converters	dataconverter.ti.com
DLP® Products	www.dlp.com
DSP	dsp.ti.com
Clocks and Timers	www.ti.com/clocks
Interface	interface.ti.com
Logic	logic.ti.com
Power Mgmt	power.ti.com
Microcontrollers	microcontroller.ti.com
RFID	www.ti-rfid.com
OMAP Applications Processors	www.ti.com/omap
Wireless Connectivity	www.ti.com/wirelessconnectivity

Applications

Automotive and Transportation	www.ti.com/automotive
Communications and Telecom	www.ti.com/communications
Computers and Peripherals	www.ti.com/computers
Consumer Electronics	www.ti.com/consumer-apps
Energy and Lighting	www.ti.com/energy
Industrial	www.ti.com/industrial
Medical	www.ti.com/medical
Security	www.ti.com/security
Space, Avionics and Defense	www.ti.com/space-avionics-defense
Video and Imaging	www.ti.com/video

TI E2E Community

e2e.ti.com