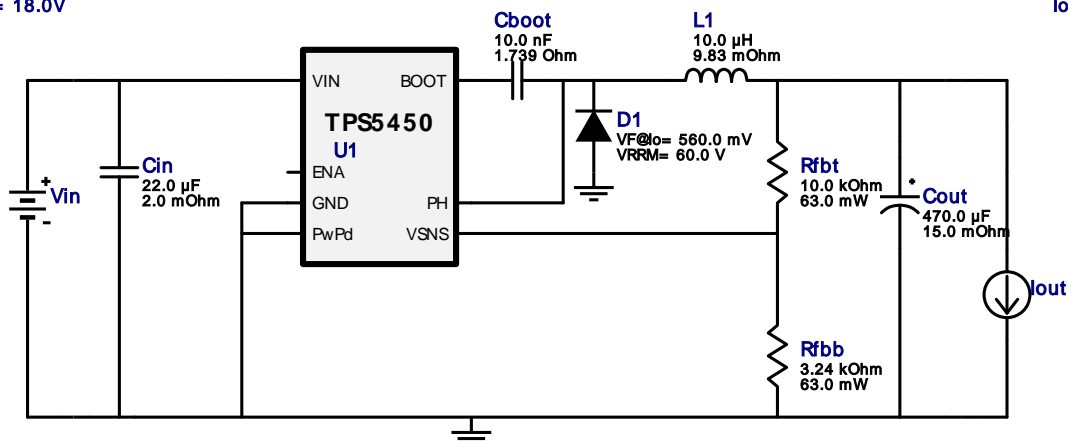


## WEBENCH<sup>®</sup> Design Report








Design : 3779120/653 TPS5450DDAR  
TPS5450DDAR 18.0V-18.0V to 5.0V @ 5.0A

VinMin = 18.0V  
VinMax = 18.0V


Vout = 5.0V  
Iout = 5.0A

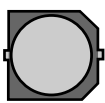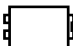


## Electrical BOM

#	Name	Manufacturer	Part Number	Properties	Qty	Price	Footprint
1.	Cboot	Kemet	C0805C103K5RACTU Series= X7R	Cap= 10.0 nF ESR= 1.739 Ohm VDC= 50.0 V IRMS= 411.0 mA	1	\$0.01	 0805 7mm2
2.	Cin	MuRata	GRM32ER61E226KE15L Series= X5R	Cap= 22.0 uF ESR= 2.0 mOhm VDC= 25.0 V IRMS= 3.67 A	1	\$0.28	 1210 15mm2
3.	Cout	Panasonic	6SVP470M Series= 261	Cap= 470.0 uF ESR= 15.0 mOhm VDC= 6.3 V IRMS= 4.21 A	1	\$0.56	 SM_RADIAL_8MM 113mm2
4.	D1	Diodes Inc.	PDS760-13	VF@Io= 560.0 mV VRRM= 60.0 V	1	\$0.60	 PowerDI5 50mm2
5.	L1	Coilcraft	SER1360-103KLB	L= 10.0 µH DCR= 9.83 mOhm	1	\$0.72	 SER1360 225mm2
6.	Rfbb	Vishay-Dale	CRCW04023K24FKED Series= CRCW..e3	Res= 3.24 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3mm2
7.	Rfht	Vishay-Dale	CRCW040210K0FKED Series= CRCW..e3	Res= 10.0 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3mm2



#	Name	Manufacturer	Part Number	Properties	Qty	Price	Footprint
8.	U1	Texas Instruments	TPS5450DDAR	Switcher	1	\$2.25	

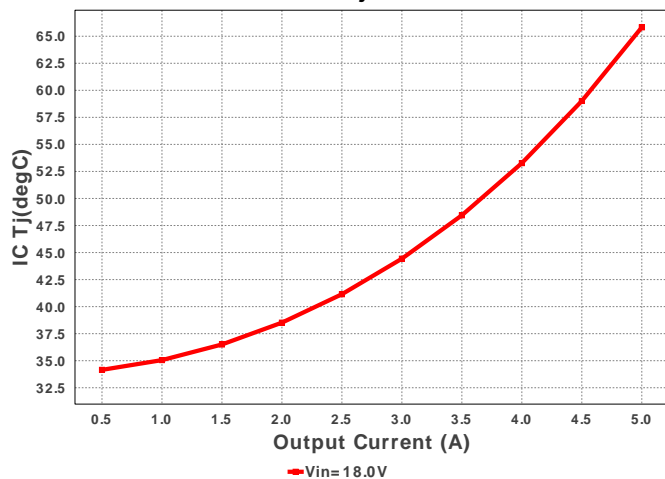R-PDSO-G8 57mm<sup>2</sup>IC T<sub>j</sub>



Duty Cycle





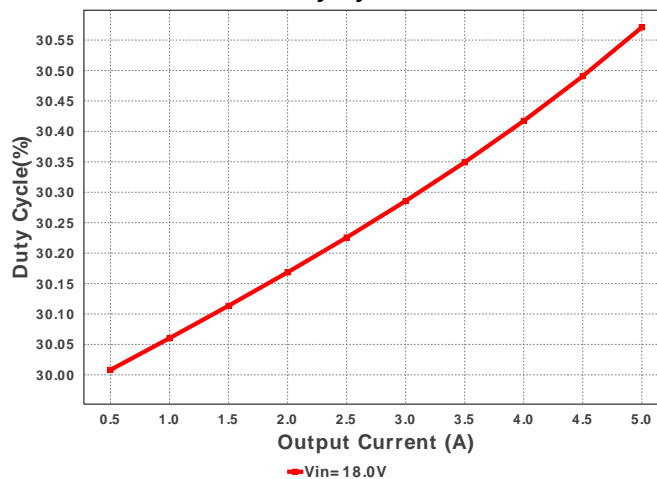








Cin IRMS

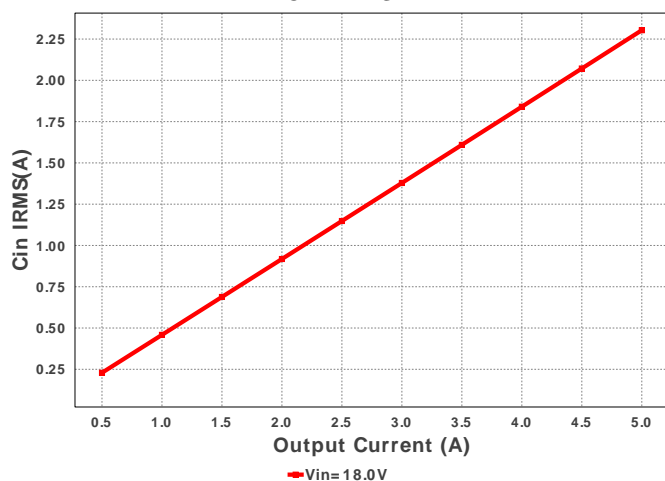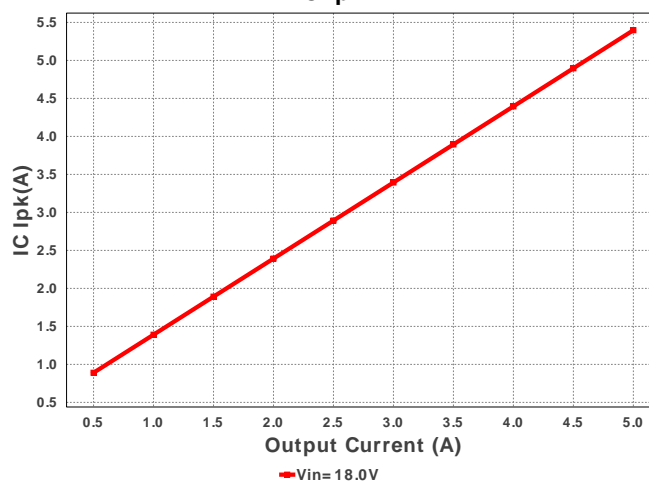
IC I<sub>pk</sub>

L Pd

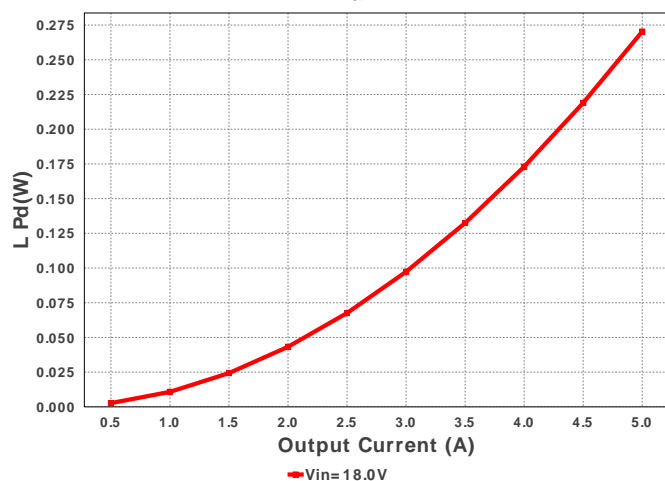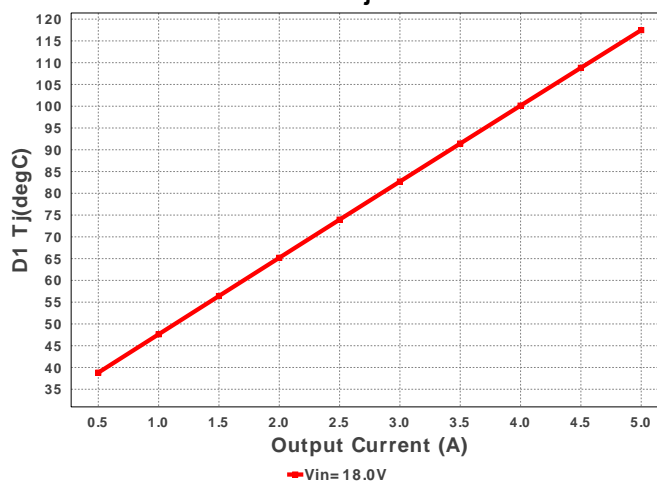D1 T<sub>j</sub>

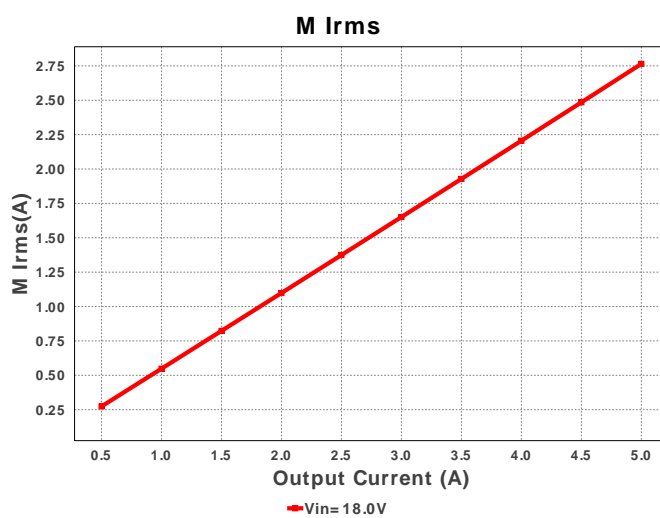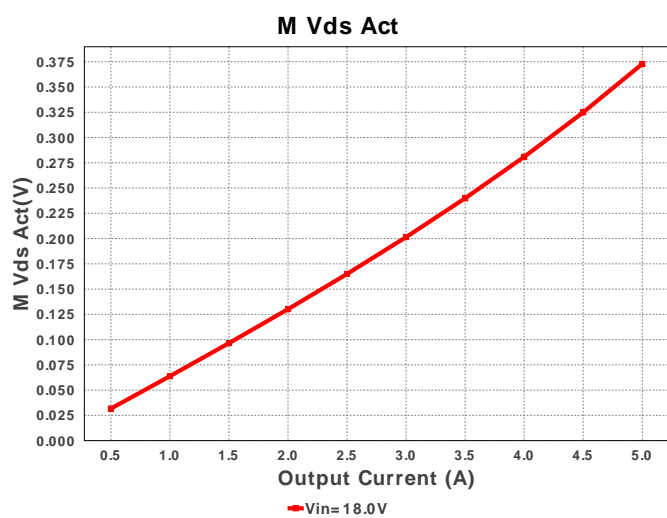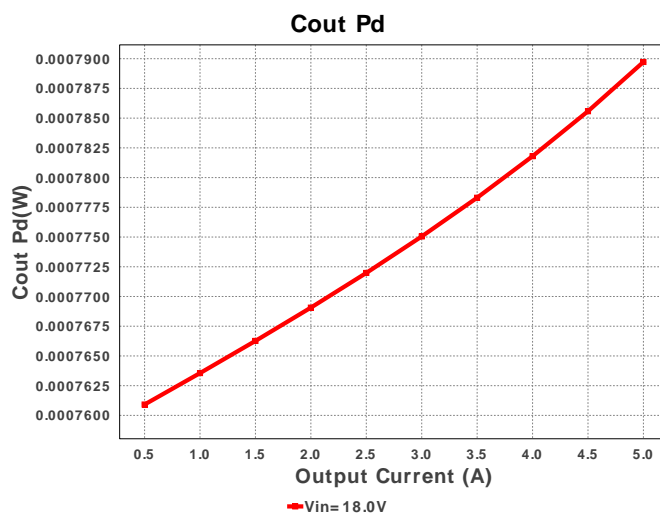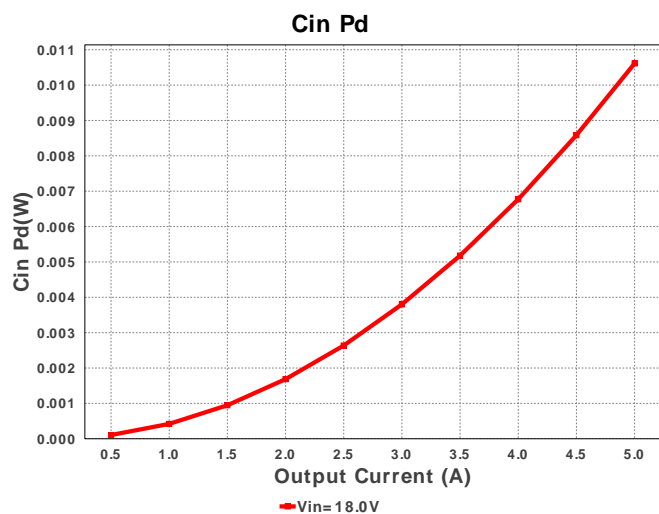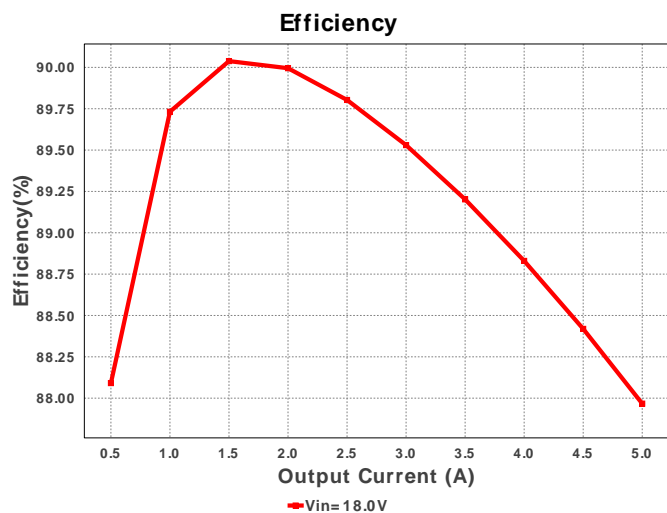

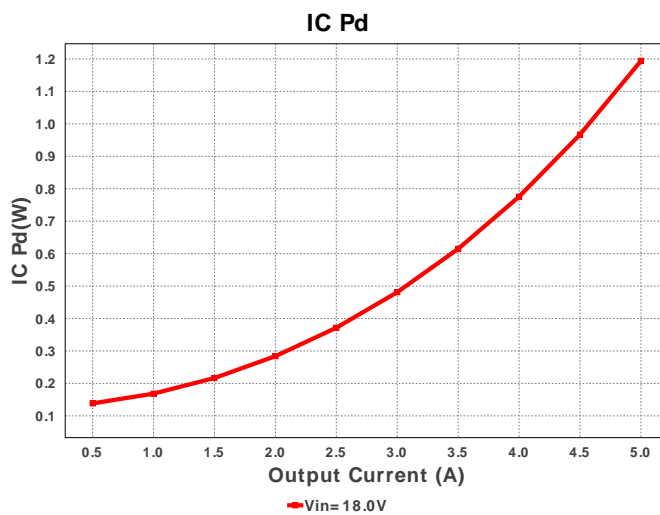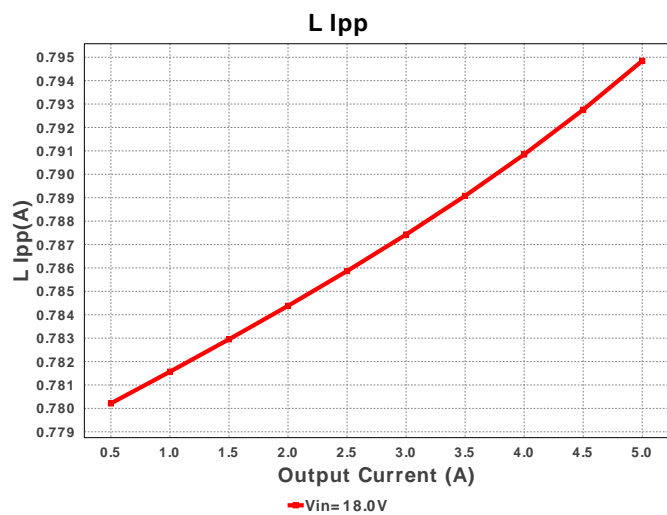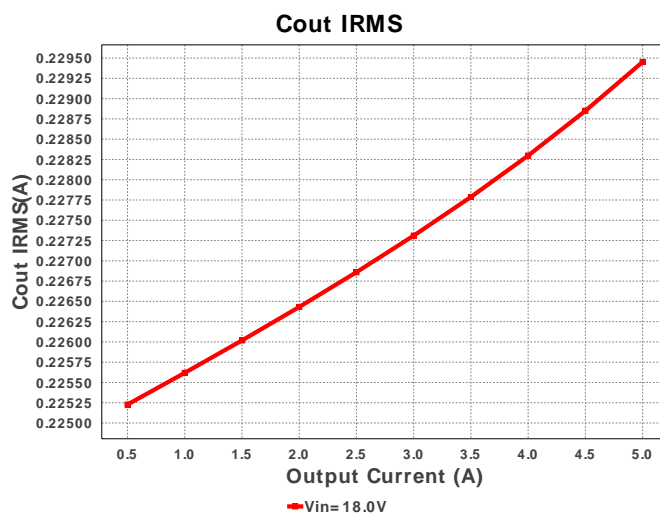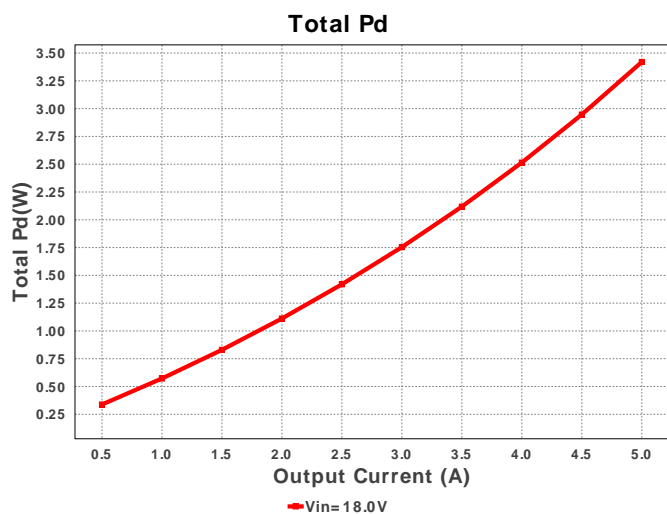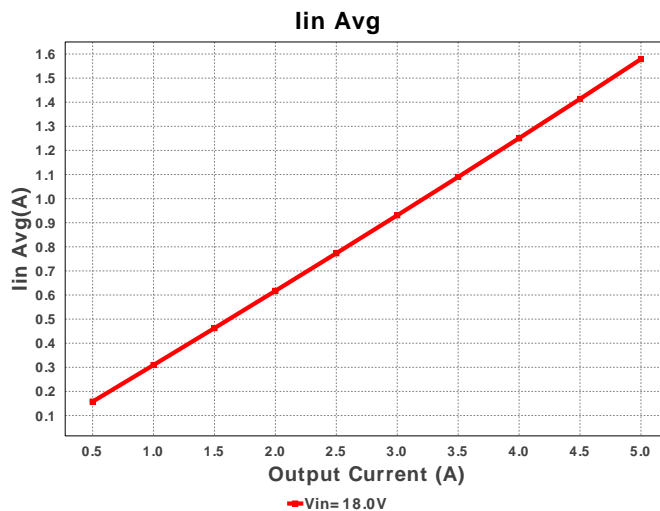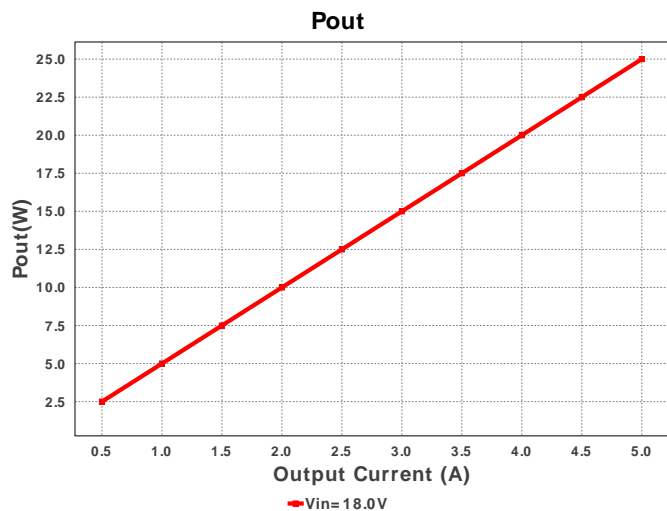

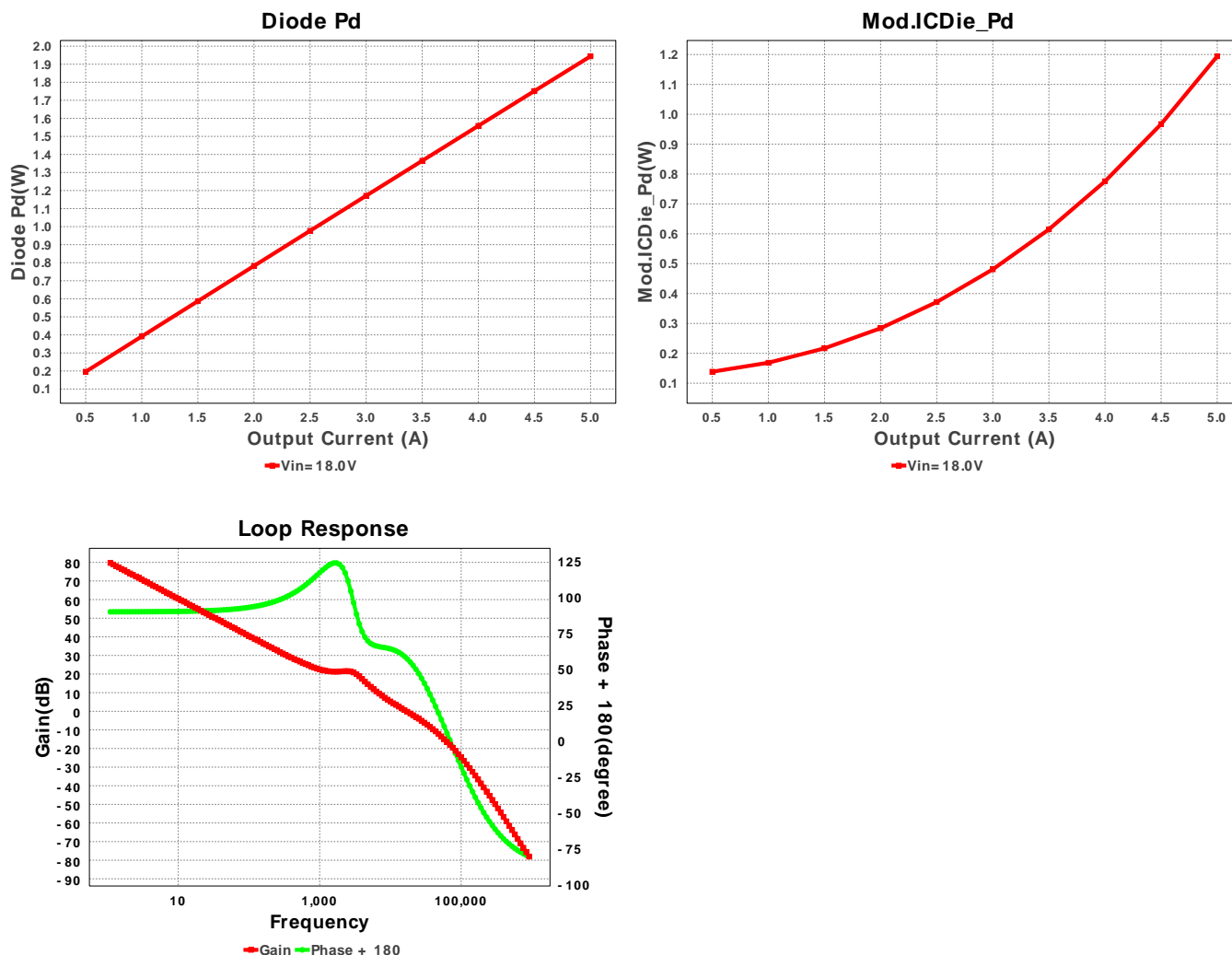

## Operating Values

#	Name	Value	Category	Description
1.	Cin IRMS	2.304 A	Current	Input capacitor RMS ripple current
2.	Cout IRMS	229.452 mA	Current	Output capacitor RMS ripple current
3.	IC Ipk	5.397 A	Current	Peak switch current in IC
4.	Iin Avg	1.579 A	Current	Average input current
5.	L Ipp	794.845 mA	Current	Peak-to-peak inductor ripple current
6.	M Irms	2.765 A	Current	MOSFET RMS current
7.	BOM Count	8	General	Total Design BOM count
8.	FootPrint	473.0 mm2	General	Total Foot Print Area of BOM components
9.	Frequency	500.0 kHz	General	Switching frequency
10.	IC Tolerance	18.315 mV	General	IC Feedback Tolerance
11.	M Vds Act	372.802 mV	General	Voltage drop across the MosFET
12.	Pout	25.0 W	General	Total output power
13.	Total BOM	\$4.44	General	Total BOM Cost
14.	D1 Tj	117.481 degC	Op_Point	D1 junction temperature
15.	Vout OP	5.0 V	Op_Point	Operational Output Voltage
16.	Cross Freq	16.977 kHz	Op_point	Bode plot crossover frequency
17.	Duty Cycle	30.571 %	Op_point	Duty cycle
18.	Efficiency	87.967 %	Op_point	Steady state efficiency
19.	IC Tj	65.824 degC	Op_point	IC junction temperature
20.	ICThetaJA	30.0 degC/W	Op_point	IC junction-to-ambient thermal resistance
21.	IOUT_OP	5.0 A	Op_point	Iout operating point
22.	Phase Marg	57.709 deg	Op_point	Bode Plot Phase Margin
23.	VIN_OP	18.0 V	Op_point	Vin operating point
24.	Vout p-p	11.93 mV	Op_point	Peak-to-peak output ripple voltage
25.	Cin Pd	10.613 mW	Power	Input capacitor power dissipation
26.	Cout Pd	789.723 μW	Power	Output capacitor power dissipation
27.	Diode Pd	1.944 W	Power	Diode power dissipation
28.	IC Pd	1.194 W	Power	IC power dissipation
29.	L Pd	270.325 mW	Power	Inductor power dissipation
30.	Total Pd	3.42 W	Power	Total Power Dissipation

## Design Inputs

#	Name	Value	Description
1.	Iout	5.0 A	Maximum Output Current
2.	Iout1	5.0 Amps	Output Current #1
3.	VinMax	18.0 V	Maximum input voltage
4.	VinMin	18.0 V	Minimum input voltage
5.	Vout	5.0 V	Output Voltage
6.	Vout1	5.0 Volt	Output Voltage #1
7.	base_pn	TPS5450	Texas Instruments Base Part Number
8.	source	DC	Input Source Type
9.	ta	30.0 degC	Ambient temperature

## Design Assistance

1. Feature Highlights: 5A, 500kHz Fixed Switching Frequency, Internal Compensation
2. TPS5450 Product Folder : <http://www.ti.com/product/tps5450> : contains the data sheet and other resources.

Texas Instruments' WEBENCH simulation tools attempt to recreate the performance of a substantially equivalent physical implementation of the design. Simulations are created using Texas Instruments' published specifications as well as the published specifications of other device manufacturers. While Texas Instruments does update this information periodically, this information may not be current at the time the simulation is built. Texas Instruments does not warrant the accuracy or completeness of the specifications or any information contained therein. Texas Instruments does not warrant that any designs or recommended parts will meet the specifications you entered, will be suitable for your application or fit for any particular purpose, or will operate as shown in the simulation in a physical implementation. Texas Instruments does not warrant that the designs are production worthy.

**You should completely validate and test your design implementation to confirm the system functionality for your application prior to production.**

Use of Texas Instruments' WEBENCH simulation tools is subject to [Texas Instruments' Site Terms and Conditions of Use](#). Prototype boards based on WEBENCH created designs are provided AS IS without warranty of any kind for evaluation and testing purposes and are subject to the terms of the [Evaluation License Agreement](#).