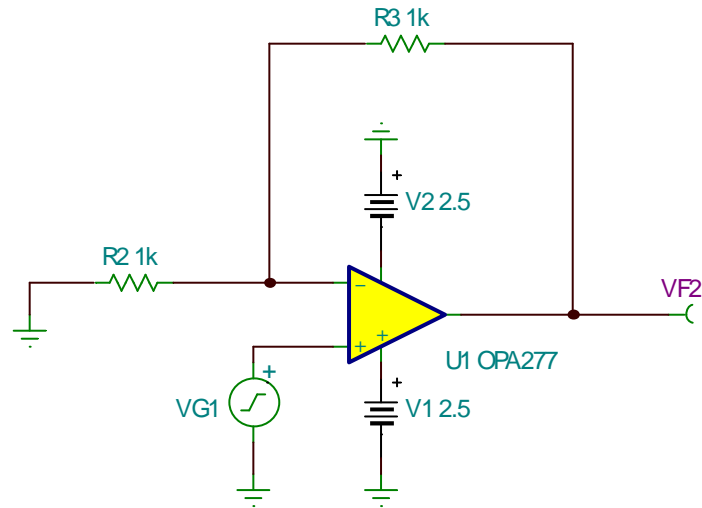




Hand Calculation Technique



Noise Analysis for Simple Op-Amp Circuit




Noise Sources

- Op-Amp Voltage Noise Source
- Op-Amp Current Noise Sources
- Resistor Noise Sources

Calculation Considerations


- Convert Noise Spectrum to Noise Voltage
 - External Filter Bandwidth Limit
 - Op-Amp Closed Loop Bandwidth

Noise Gain

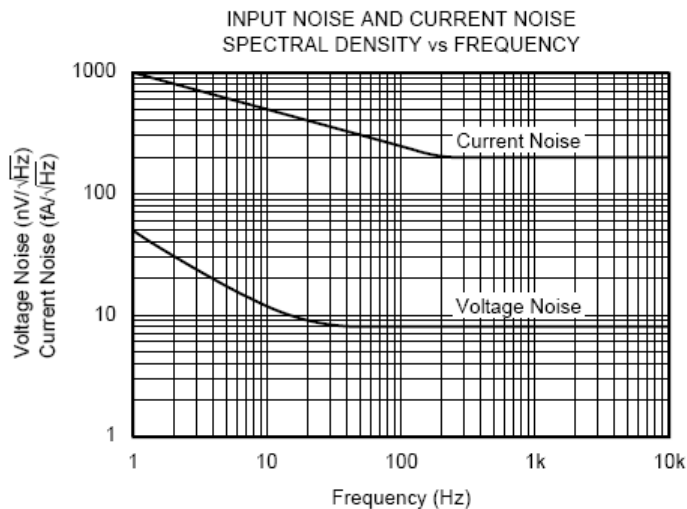



Calculus Reminder

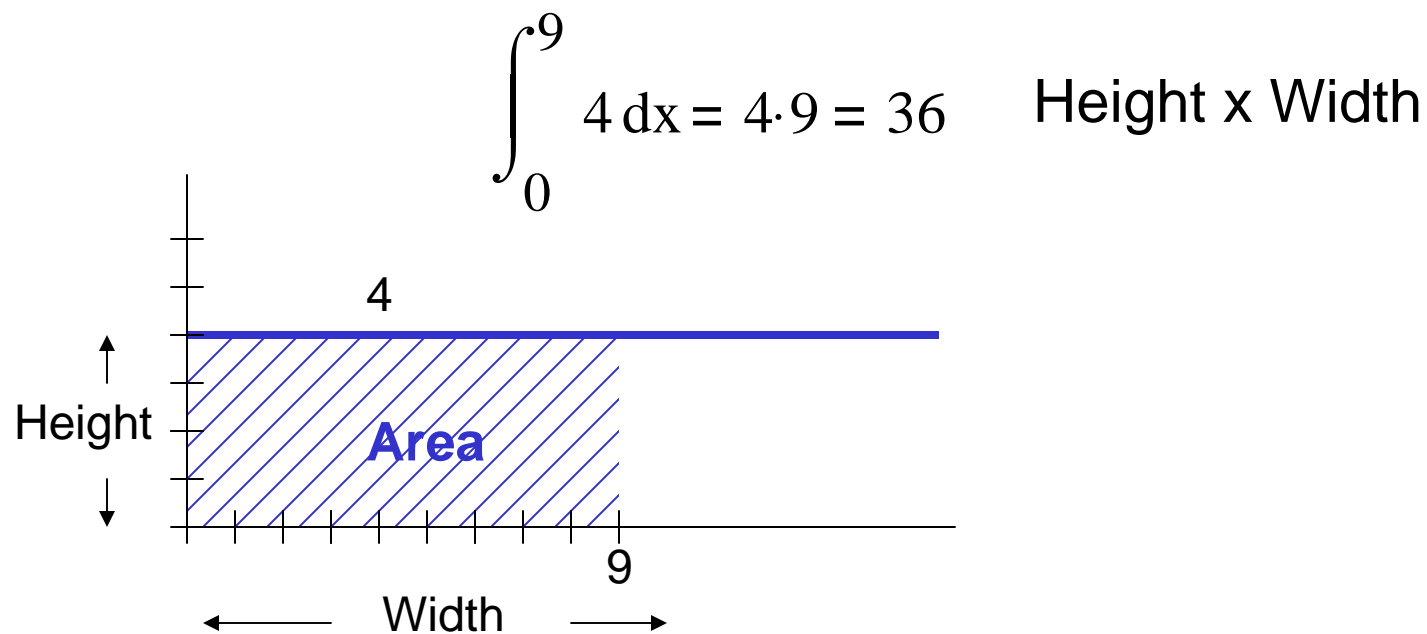


Integral = Area under the curve



Convert Noise Spectrum to Noise Voltage (Broadband Only – Simple Case)

Voltage
Spectral
Density
(V/rt-Hz)

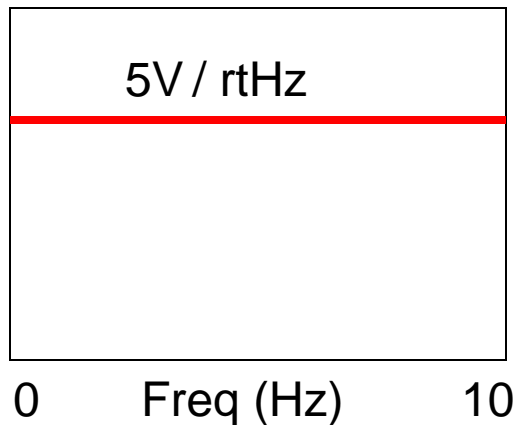


You can't integrate the **Voltage** spectral density curve to get noise

$$\int_0^{10} V_{\text{spec_dens}} df = 5 \cdot \frac{V}{\sqrt{\text{Hz}}} \cdot 10 \cdot \text{Hz} = 50 \cdot \frac{V \cdot \text{Hz}}{\sqrt{\text{Hz}}}$$

Wrong

Power
Spectral
Density
(V²/Hz)

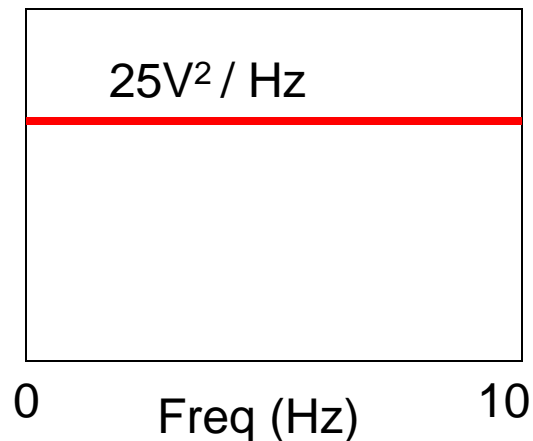

You integrate the **Power** spectral density curve to get noise

$$\text{NoisePower} = \int_0^{10} (V_{\text{spec_dens}})^2 df = 25 \cdot \frac{V^2}{\text{Hz}} \cdot 10 \cdot \text{Hz} = 250 \cdot V^2$$

$$\text{NoiseVoltage} = \sqrt{\text{NoisePower}} = \sqrt{250 \cdot V^2} = 15.811V \quad \text{RMS}$$

Correct



Convert Noise Spectrum to Noise Voltage (Broadband Only – Simple Case)

You integrate the **Power** spectral density curve to get noise

$$\text{NoisePower} = \int_0^{10} (\text{V_spec_dens})^2 df = 25 \cdot \frac{\text{V}^2}{\text{Hz}} \cdot 10 \cdot \text{Hz} = 250 \cdot \text{V}^2$$

$$\text{NoiseVoltage} = \sqrt{\text{NoisePower}} = \sqrt{250 \cdot \text{V}^2} = 15.811\text{V RMS}$$

Correct

$$\text{Noise Power} = \frac{\text{V}^2 * \text{BW (Hz)}}{\text{Hz}}$$

$$\text{Noise Voltage} = \frac{\text{V}}{\sqrt{\text{Hz}}} * \sqrt{\text{BW (Hz)}}$$



Noise Gain for Voltage Noise Source


Noise Gain – Gain seen by the noise source.

Example:

$$\text{Noise_Gain} = (R2/R1) + 1 = 2$$

$$\text{Signal_Gain} = -R2/R1 = -1$$
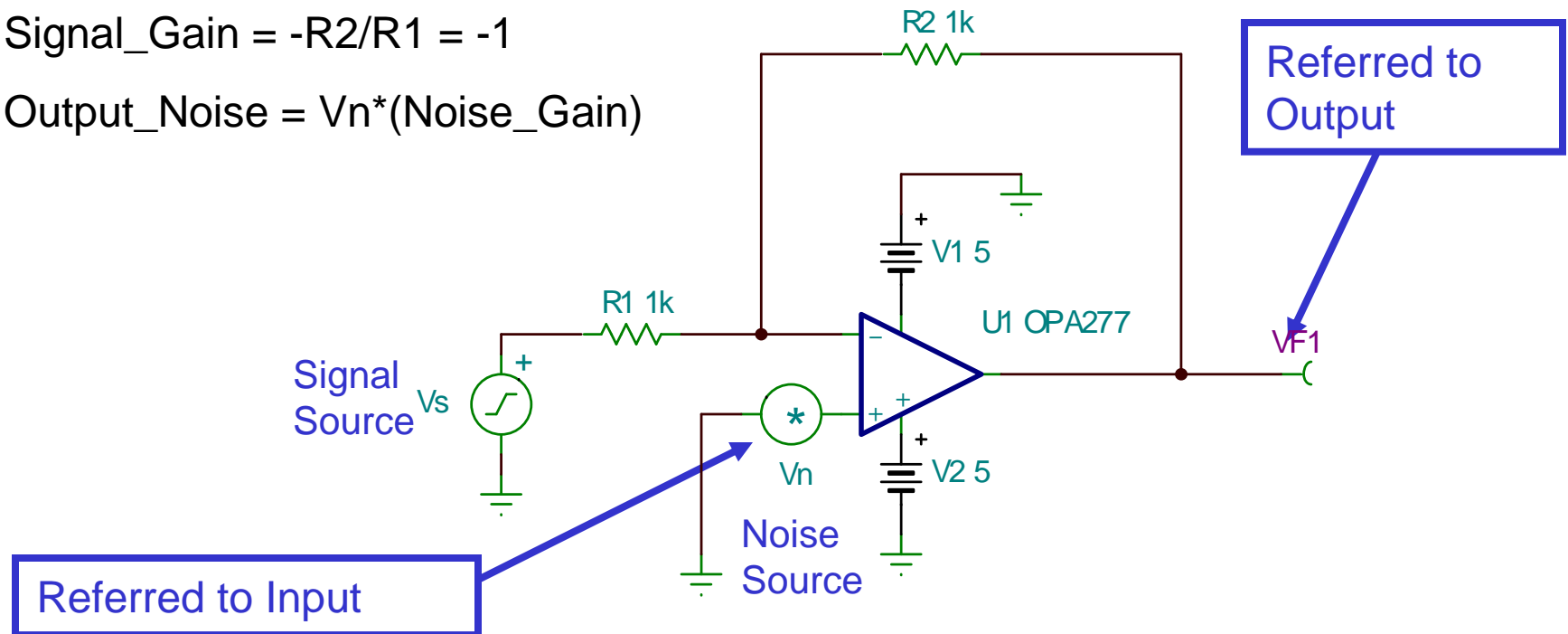
$$\text{Output_Noise} = Vn * (\text{Noise_Gain})$$





Understanding The Spectrum: Total Noise Equation (Current or Voltage)


$$e_{nT} = \sqrt{[(e_{n1/f})^2 + (e_{nBB})^2]}$$

where:

e_{nT} = Total rms Voltage Noise in volts rms

$e_{n1/f}$ = 1/f voltage noise in volts rms

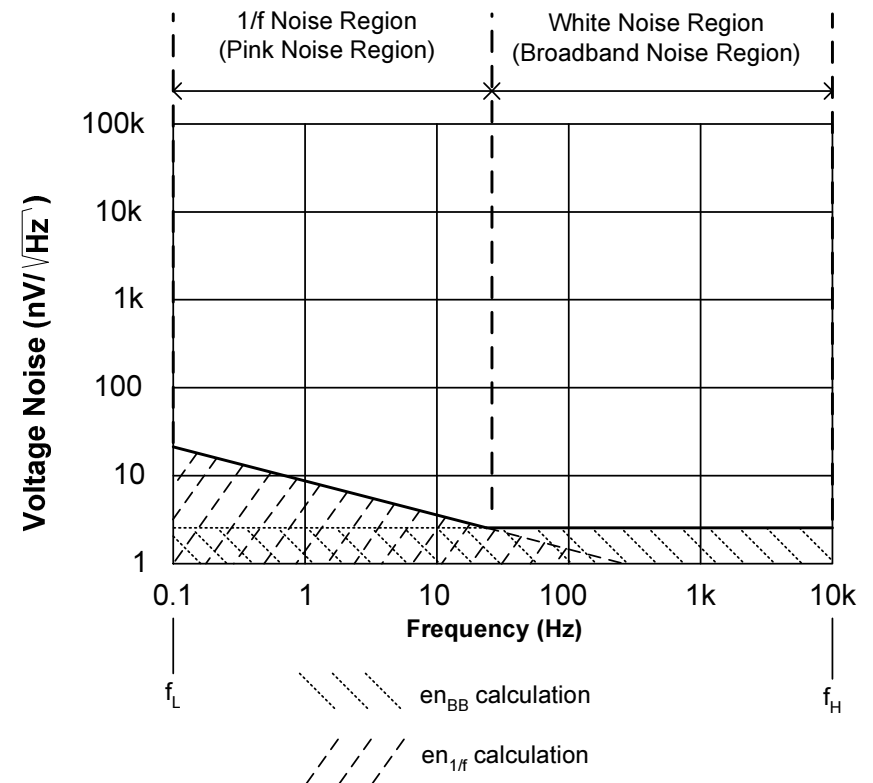
e_{nBB} = Broadband voltage noise in volts rms






Low Pass Filter Shapes the Spectrum

How do we convert this plot to noise?

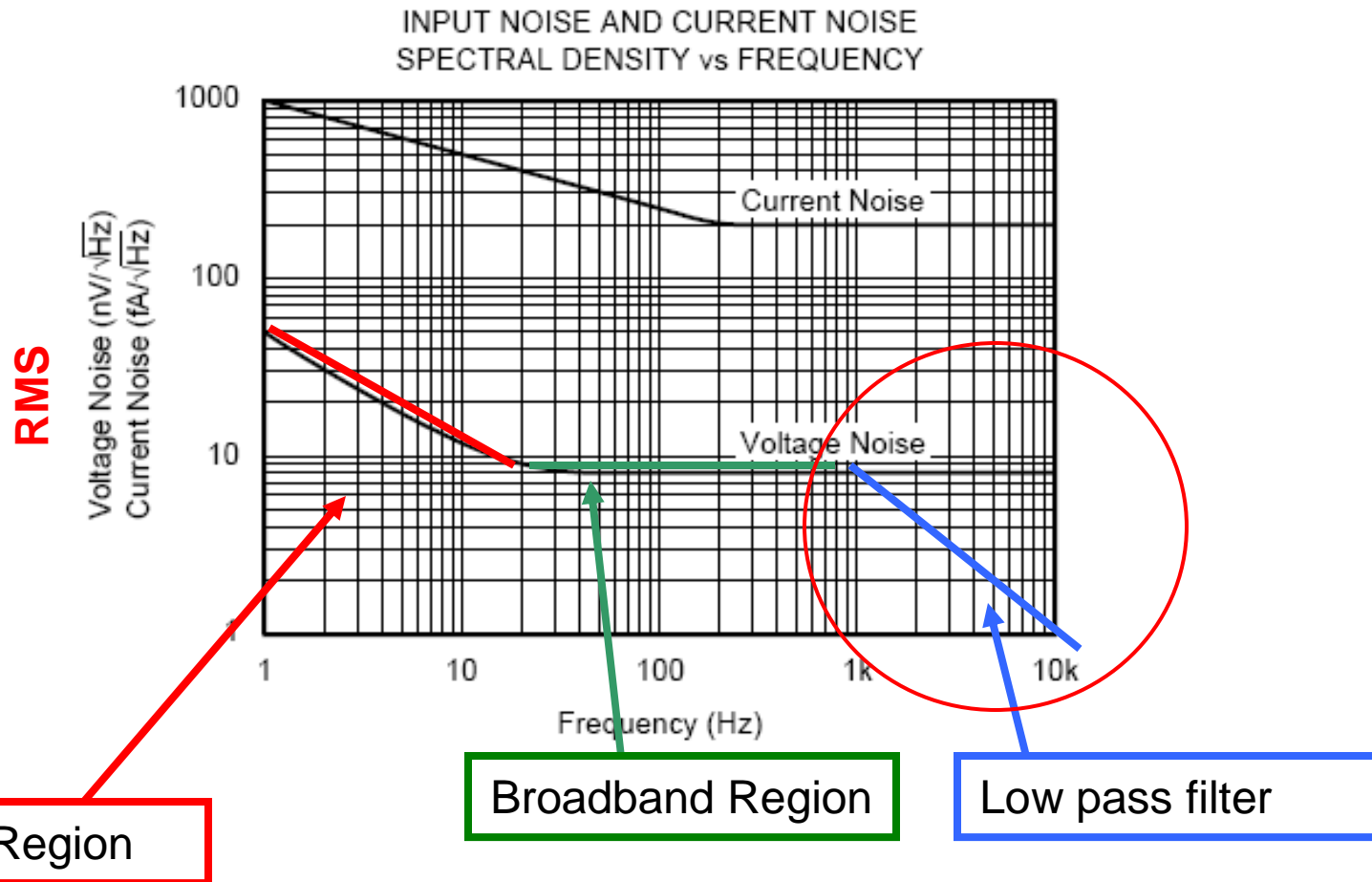



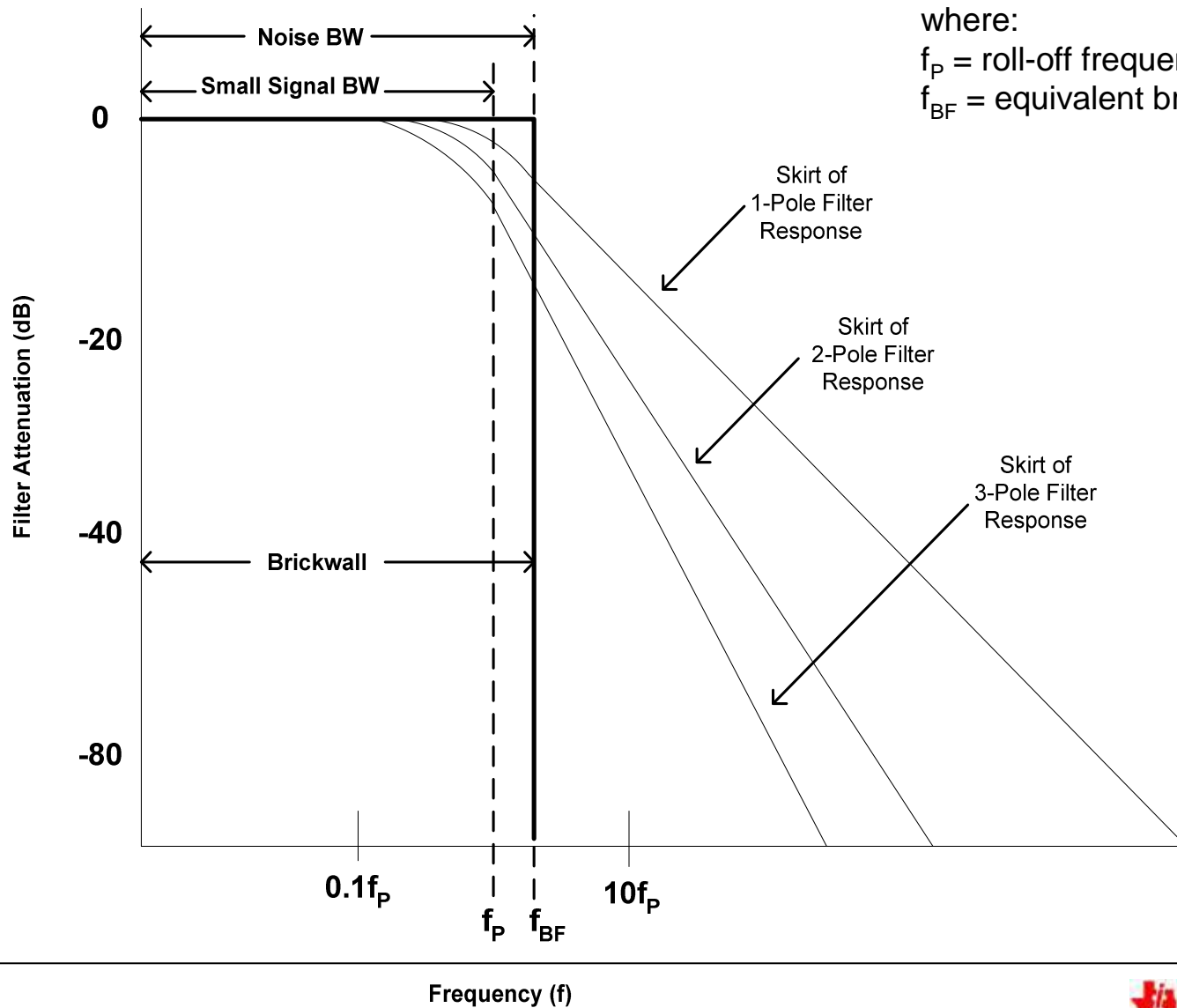Real Filter Correction vs Brickwall Filter



where:

f_p = roll-off frequency of pole or poles

f_{BF} = equivalent brickwall filter frequency



AC Noise Bandwidth Ratios for nth Order Low-Pass Filters


$$BW_n = (f_H)(K_n) \text{ Effective Noise Bandwidth}$$

Real Filter Correction vs Brickwall Filter

Number of Poles in Filter	K_n AC Noise Bandwidth Ratio
1	1.57
2	1.22
3	1.16
4	1.13
5	1.12



Broadband Noise Equation

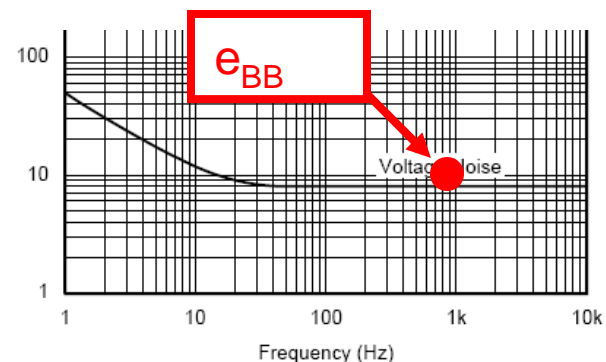

$$BW_n = (f_H)(K_n)$$

where:

BW_n = noise bandwidth for a given system

f_H = upper frequency of frequency range of operation

K_n = "Brickwall" filter multiplier to include the "skirt" effects of a low pass filter

$$en_{BB} = (e_{BB})(\sqrt{[BW_n]})$$

where:

en_{BB} = Broadband voltage noise in volts rms


e_{BB} = Broadband voltage noise density ; usually in nV/\sqrt{Hz}

BW_n = Noise bandwidth for a given system



1/f Noise Equation

(see appendix for derivation)

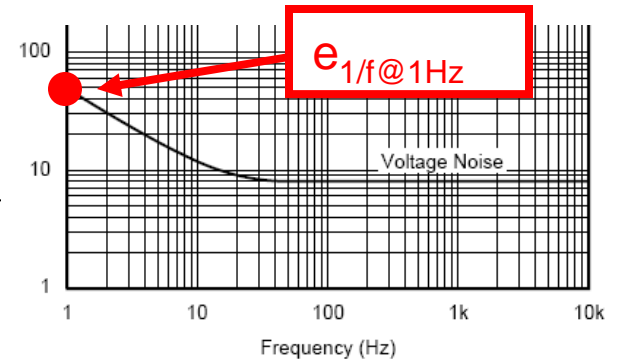

$$e_{1/f@1\text{Hz}} = (e_{1/f@f})(\sqrt{[f]})$$

where:

$e_{1/f@1\text{Hz}}$ = normalized noise at 1Hz (usually in nV)

$e_{1/f@f}$ = voltage noise density at f ; (usually in nV/ $\sqrt{\text{Hz}}$)

f = a frequency in the 1/f region where noise voltage density is known

$$en_{1/f} = (e_{1/f@1\text{Hz}})(\sqrt{[\ln(f_H/f_L)]})$$

where:

$en_{1/f}$ = 1/f voltage noise in volts rms over frequency range of operation

$e_{1/f@1\text{Hz}}$ = voltage noise density at 1Hz; (usually in nV)


f_H = upper frequency of frequency range of operation

(Use BW_n as an approximation for f_H)

f_L = lower frequency of frequency range of operation



Example Noise Calculation


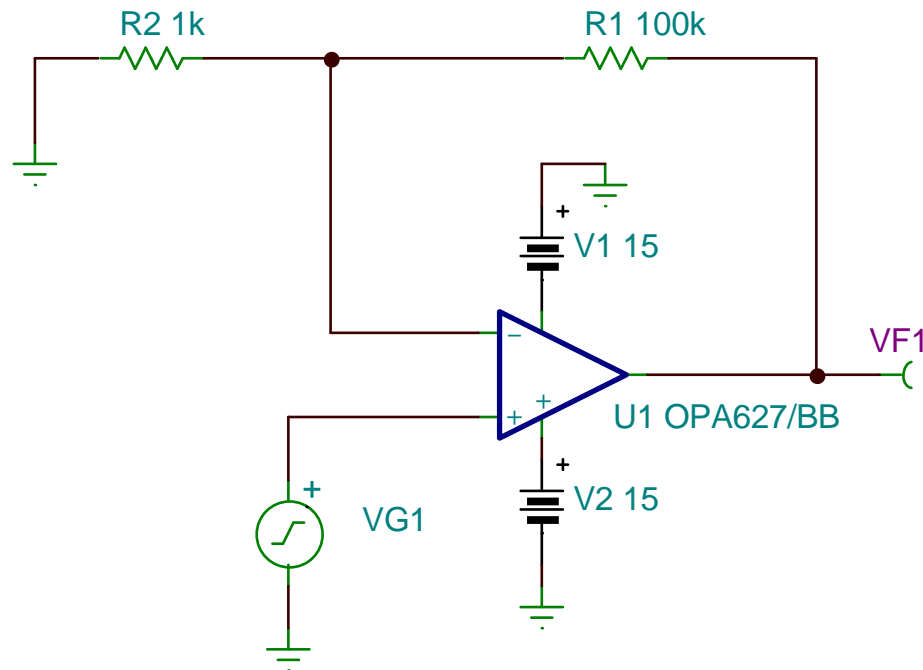


Given:
OPA627
Noise Gain of 101

Find (RTI, RTO):
Voltage Noise
Current Noise
Resistor Noise



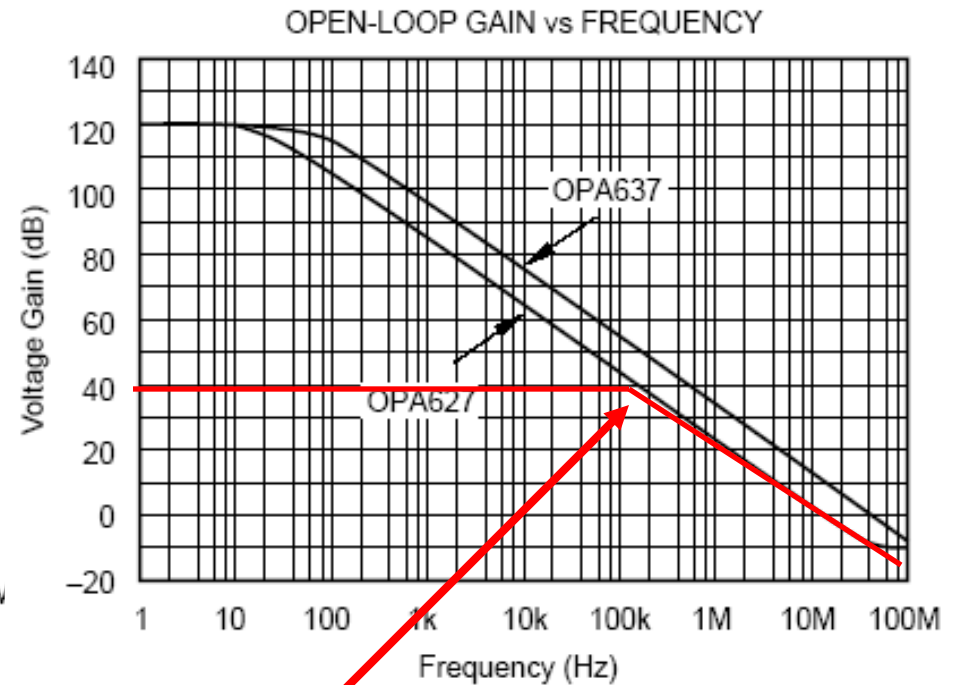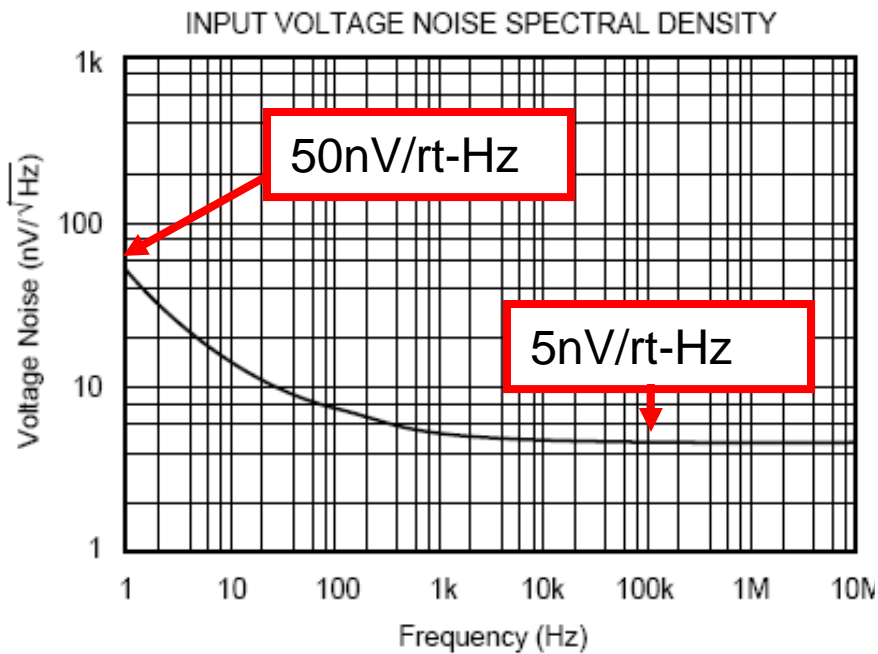Voltage Noise Spectrum and Noise Bandwidth



Unity Gain Bandwidth = 16MHz

Closed Loop Bandwidth = $16\text{MHz} / 101 = 158\text{kHz}$



Example Voltage Noise Calculation

Voltage Noise Calculation:

Broadband Voltage Noise Component:

$$BW_n \approx (f_H)(K_n) \quad (\text{note } K_n = 1.57 \text{ for single pole})$$

$$BW_n \approx (158\text{kHz})(1.57) = 248\text{kHz}$$

$$en_{BB} = (e_{BB})(\sqrt{BW_n})$$

$$en_{BB} = (5\text{nV}/\sqrt{\text{Hz}})(\sqrt{248\text{kHz}}) = 2490\text{nV rms}$$

1/f Voltage Noise Component:

$$e_{1/f@1\text{Hz}} = (e_{1/f@f})(\sqrt{f})$$

$$e_{1/f@1\text{Hz}} = (50\text{nV}/\sqrt{\text{Hz}})(\sqrt{1\text{Hz}}) = 50\text{nV}$$

$$en_{1/f} = (e_{1/f@1\text{Hz}})(\sqrt{[\ln(f_H/f_L)]}) \quad \text{Use } f_H = BW_n$$

$$en_{1/f} = (50\text{nV})(\sqrt{[\ln(248\text{kHz}/1\text{Hz})]}) = 176\text{nV rms}$$

Total Voltage Noise (referred to the input of the amplifier):

$$en_T = \sqrt{[(en_{1/f})^2 + (en_{BB})^2]}$$

$$en_T = \sqrt{[(176\text{nV rms})^2 + (2490\text{nV rms})^2]} = 2496\text{nV rms}$$


30



Example Current Noise Calculation

PARAMETER	OPA627BM, BP, SM OPA637BM, BP, SM			UNITS
	MIN	TYP	MAX	
NOISE				
Input Voltage Noise				
Noise Density: f = 10Hz		15	40	nV/√Hz
f = 100Hz		8	20	nV/√Hz
f = 1kHz		5.2	8	nV/√Hz
f = 10kHz		4.5	6	nV/√Hz
Voltage Noise, BW = 0.1Hz to 10Hz		0.6	1.6	μVp-p
Input Bias Current Noise				
Noise Density, f = 100Hz		1.6	2.5	fA/√Hz
Current Noise, BW = 0.1Hz to 10Hz		30	60	fAp-p

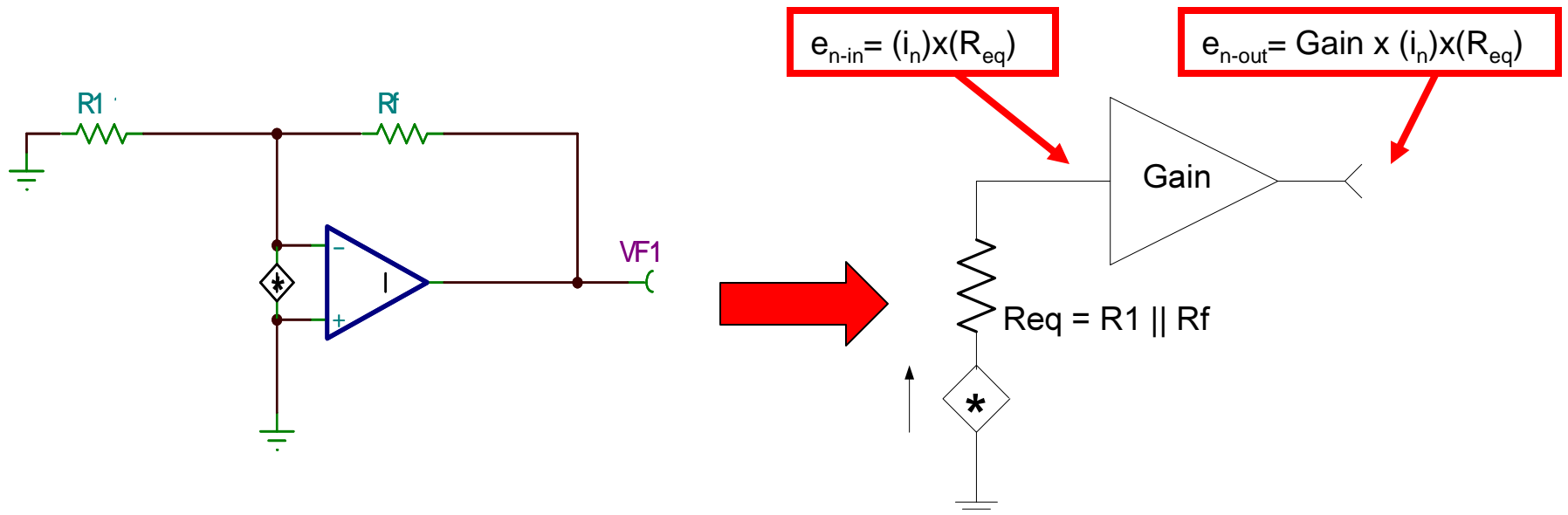Note: This example amp doesn't have 1/f component for current noise.





Example Current Noise Calculation

Broadband Current Noise Component:

$$BW_n \approx (f_H)(K_n)$$

$$BW_n \approx (158\text{kHz})(1.57) = 248\text{kHz}$$

$$i_{nBB} = (i_{BB})(\sqrt{BW_n})$$

$$i_{nBB} = (2.5\text{fA}/\sqrt{\text{Hz}})(\sqrt{248\text{kHz}}) = 1.244\text{pA rms}$$

$$R_{eq} = R_f \parallel R_1 = 100\text{k} \parallel 1\text{k} = 0.99\text{k}$$

$$e_{ni} = (i_n)(R_{eq}) = (1.244\text{pA})(0.99\text{k}) = 1.23\text{nV rms} \quad \text{neglect}$$

Since the Total Voltage noise is $e_{nvt} = 2496\text{nV rms}$
the current noise can be neglected.

PARAMETER	OPA627BM, BP, SM OPA637BM, BP, SM			UNITS
	MIN	TYP	MAX	
NOISE				
Input Voltage Noise				
Noise Density: f = 10Hz		15	40	nV/√Hz
f = 100Hz		8	20	nV/√Hz
f = 1kHz		5.2	8	nV/√Hz
f = 10kHz		4.5	6	nV/√Hz
Voltage Noise, BW = 0.1Hz to 10Hz		0.6	1.6	μVp-p
Input Bias Current Noise				
Noise Density, f = 100Hz		1.6	2.5	fA/√Hz
Current Noise, BW = 0.1Hz to 10Hz		30	60	fAp-p



Example Resistor Noise Calculation


$$e_{nr} = \sqrt{4kT_K R \Delta f}$$

where:

$$R = R_{eq} = R1 || Rf$$

$$\Delta f = BW_n$$
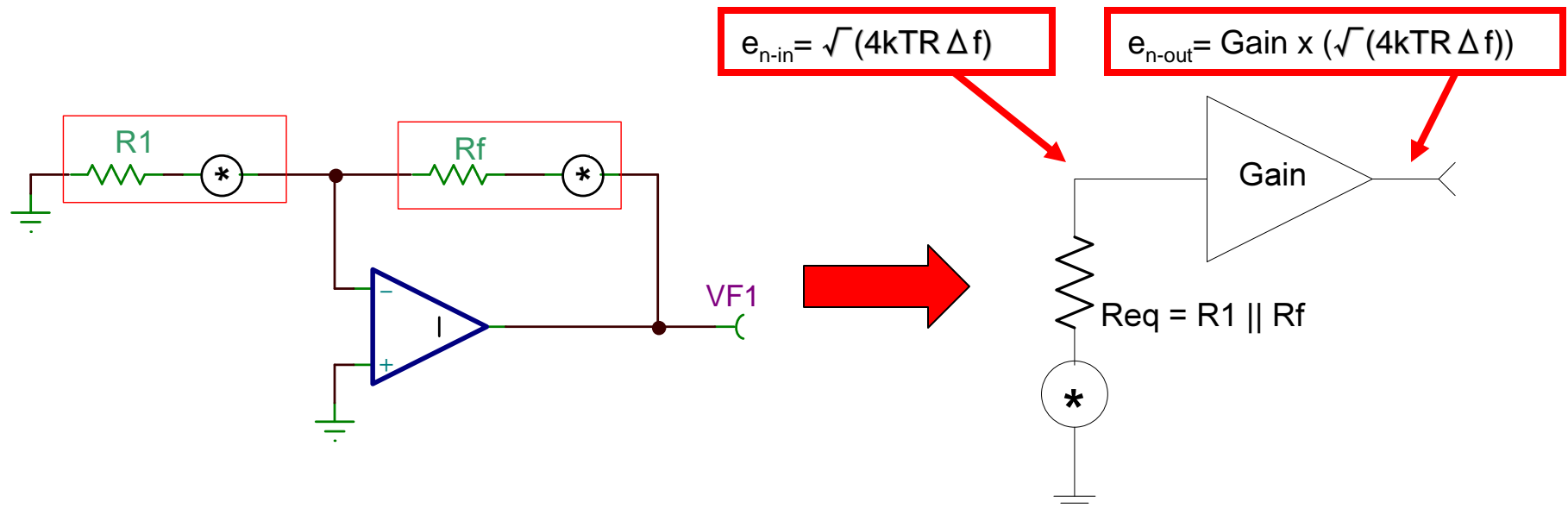
$$e_{nr} = \sqrt{4 (1.38E-23) (273 + 25) (0.99k)(248kHz)} = 2010nV \text{ rms}$$





Total Noise Calculation

Voltage Noise From Op-Amp RTI:

$$e_{nv} = 2510\text{nV rms}$$

Current Noise From Op-Amp RTI (as a voltage):

$$e_{ni} = 1.24\text{nV rms}$$

Resistor Noise RTI:

$$e_{nr} = 2020\text{nV rms}$$

Total Noise RTI:

$$e_{n\text{ in}} = \sqrt{((2510\text{nV})^2 + ((1.2\text{nV})^2 + ((2010\text{nV})^2)) = 3216\text{nV rms}$$

Total Noise RTO:

$$e_{n\text{ out}} = e_{n\text{ in}} \times \text{gain} = (3216\text{nV})(101) = 325\text{uV rms}$$



Calculating Noise V_{pp} from Noise V_{rms}


Relation of Peak-to-Peak Value of AC Noise Voltage to rms Value

Peak-to-Peak Amplitude	Probability of Having a Larger Amplitude
2 X rms	32%
3 X rms	13%
4 X rms	4.6%
5 X rms	1.2%
6 X rms *	0.3%
6.6 X rms	0.1%

***Common Practice is to use:
Peak-to-Peak Amplitude = 6 X rms**



Peak to Peak Output For our Example

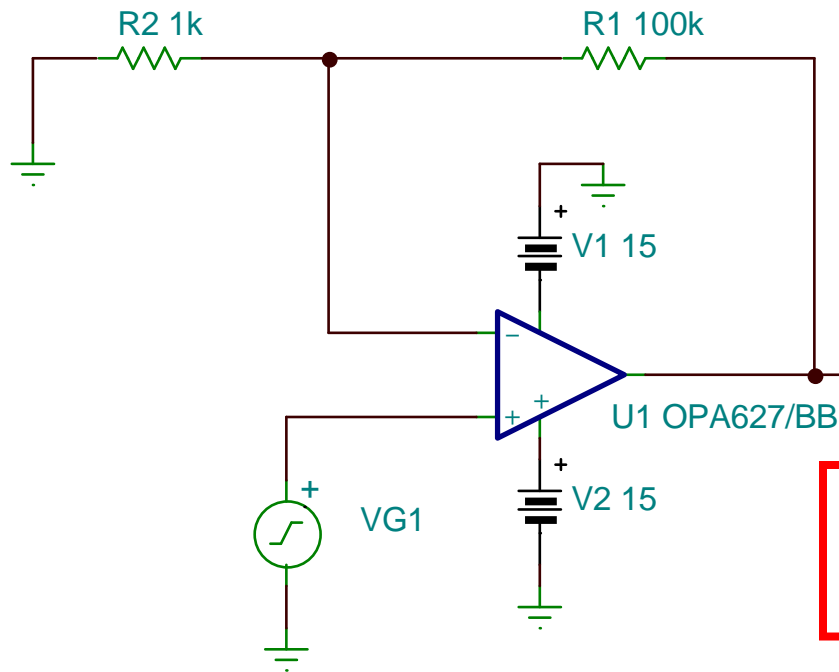

$e_{n\ out} = 325\mu\text{V rms}$
 $e_{n\ out\ p-p} = (325\mu\text{V rms}) \times 6 = 1.95\text{mVp-p}$