



Four Voltage References, an ADC and MSP430

Tadija Janjic

HPL – Tucson

Michael Ashton

DAP



Motivation

- u *Total Solution Concept*
- u *Application section of datasheets*
- u *New REF products from TI*
- u *Greed*
 - n *Product Recognition*
 - n *Increased Revenue*




Experiment

- u *Verify setup/measurements*
- u *Evaluate TI REFs with ADS1256*
- u *Compare different TI REF results*
- u *Suggest the optimal circuitry*




Basic Setup

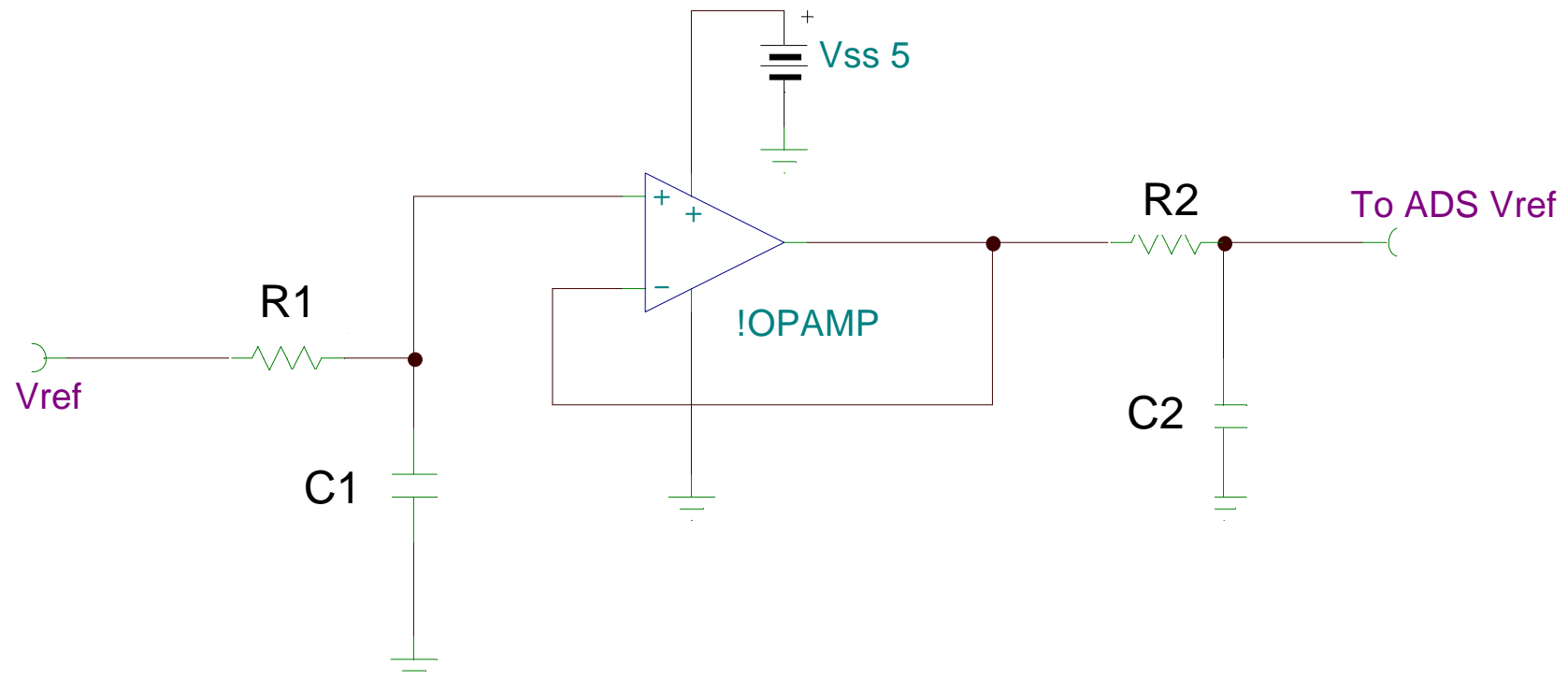


ADS1256, PGA=1, Vref=2.5V

Board

 



Board (side view)

 



Considerations

- u *Low Noise*
- u *Long term stability*
 - n *Time*
 - n *Temperature*



Experiment Design

<i>R1</i>	<i>C1</i>	<i>OPA</i>	<i>R2</i>	<i>C2</i>	<i>RMS noise free bits</i>
.....	335	100	10u	
		227	100	10u	

Additional considerations:

Vin amplitude, f_s (data output rate)



Confirm the Setup

**Table 2. Effective Number of Bits (ENOB, rms)
with Buffer On**

DATA RATE (SPS)	PGA						
	1	2	4	8	16	32	64
50	23.9	23.6	23.0	22.5	21.8	21.1	20.3
60	23.8	23.4	22.9	22.4	21.7	21.0	20.2

<i>REF</i>	<i>R1</i>	<i>C1</i>	<i>OPA</i>	<i>R2</i>	<i>C2</i>	<i>RMSnfb</i>
1004	10k	47u	227	100	10u	23.8

$V_{In}=0V$, shorted inputs,



Results

<i>REF</i>	<i>R1</i>	<i>C1</i>	<i>OPA</i>	<i>R2</i>	<i>C2</i>	<i>RMSnfb</i>
1004	-----	-----	OPA335	100	10u	20.7
1004	10k	220u	same	same	same	22.3
1004	10k	47u	same	same	same	22.4
3025	same	same	same	same	same	20.8
3125	same	same	same	same	same	20
1112*	same	same	same	same	same	22.1
1004	same	same	OPA227	same	same	22.4

* OPA in a gain of 2

Vin=2.5V, data output rate = 60Hz,



Conclusions

- ⌋ *On ADS1256 one needs external buffer*
 - ⌋ *Input impedance 18k*
- ⌋ *Noise-wise OPA227 and OPA335 equal*
 - ⌋ *However, we tried at $T=25^{\circ}\text{C}$*
- ⌋ *REF1004 and REF1112 similar results*
- ⌋ *REF3xxx family good for lower precision*
- ⌋ *RC (settling time vs. noise) trade off*



MSP430

- ⌋ *Has 12 bit ADC (ADC12)*
- ⌋ *Has Vref (2.5V or 1.5V)*
 - n *800uA max*
 - n *100ppm/ ° C max*
 - n *4% initial accuracy*

•TI REFs:

- 8uA -110 uA max current

- 15 -100ppm/ ° C

- 2.048/2.5/3.0V/3.3V 0.2%



Results

<i>REF</i>	<i>R1</i>	<i>C1</i>	<i>Noise RMS bits</i>
<i>Internal (2.5V)</i>	-----	-----	~3.1
<i>1004 – 2.5V</i>	<i>100</i>	<i>47u</i>	~3.0
<i>3025</i>	<i>10k</i>	<i>47u</i>	~2.7
<i>3125</i>	<i>same</i>	<i>same</i>	~2.7
<i>1004</i>	<i>same</i>	<i>same</i>	~2.7
<i>3125</i>	<i>100</i>	<i>same</i>	~3.0
<i>3025</i>	<i>same</i>	<i>same</i>	~3.0
<i>1112</i>	<i>same</i>	<i>same</i>	5.5



Conclusions – Part II

- ⌋ *External REFs improve performance*
 - n *Lower noise*
 - n *Lower supply current*
- ⌋ *REF1112 can not be used with MSP430*
 - n *VeRef is 1.4V min!!!!*



Summary

- ⌋ *Built tools for evaluations*
- ⌋ *Got preliminary results*
- ⌋ *Will work on other ADCs and MSP430*
 - ⌋ *SARs, Delta-Sigma*
- ⌋ *Will improve datasheets*
- ⌋ **Support customers** *with optimal solution*

Thank You



Amplifier to A/D Interface Study

*Or...that short task
that will not go away*



Bill Klein

Senior Applications
Engineer




Miro Oljaca

Strategic Marketing:
Motor Control

*With major contributions from: Tom Hendrick, Tim Green,
Rick Downs, Rod Burt, Bob Benjamin, Bernd Rundel,
Bruce Trump, Dennis Goeke, Pat Highton*

16

The Interface Circuit

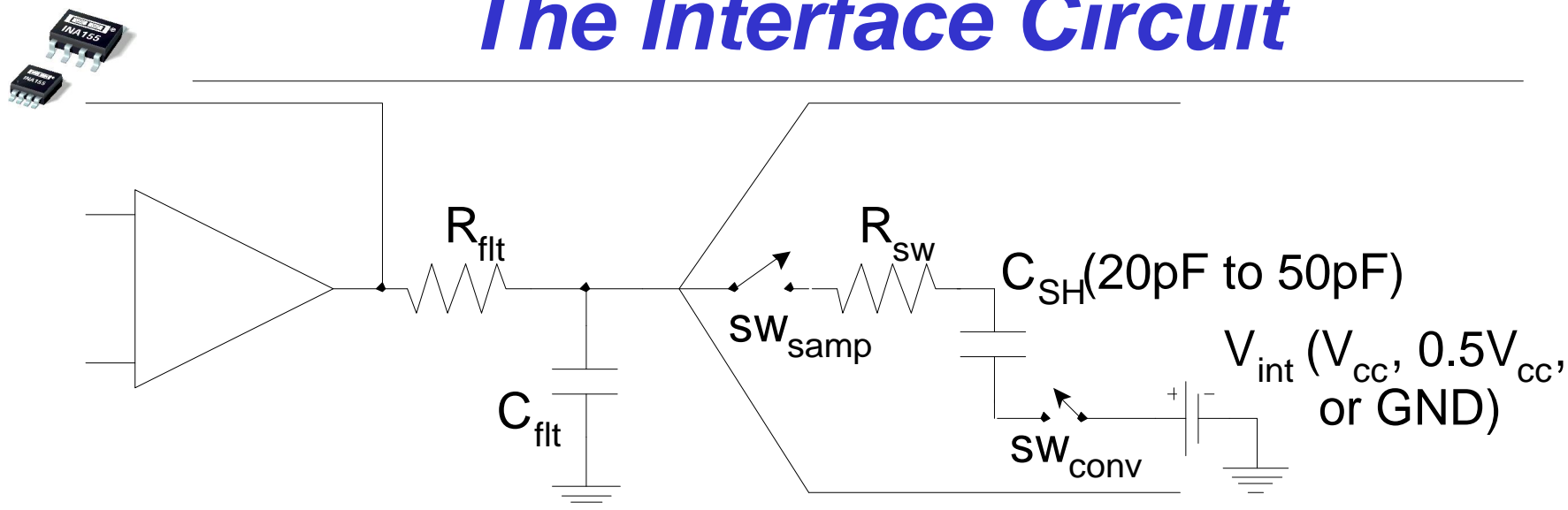

Op Amp

CMV Range, V_{OS} vs CMV

RR Out-Swing to the rail

Slew Rate, Signal BW,

Load Transient, Settling Time,

Output Impedance,

Filter

Charge Bucket

Filtering,

C_{load} Isolation,

A/D

Acquisition Time

Input Circuit Parameters

Initial Voltage on C_{SH}



LSB Size

u Signal range:

n $\pm 10V$ is a 20V range

w 12 bits: $20V/4,096 = 4.88mV$ per LSB

w 16 bits: $20V/65,536 = 305\mu V$ per LSB

n $\pm 5V$ range

w 12 bits: $5V/4,096 = 1.22mV$ per LSB

w 16 bits: $5V/65,536 = 76.2\mu V$ per LSB

w 24 bits: $5V/16,777,216 = 298nV$ per LSB

n $\pm 3.3V$ range

w 12 bits: $3.3V/4,096 = 806\mu V$ per LSB


w 16 bits: $3.3V/65,536 = 50.4\mu V$ per LSB

w 24 bits: $3.3V/16,777,216 = 196nV$ per LSB



Op Amp Input Concerns

See Appendix

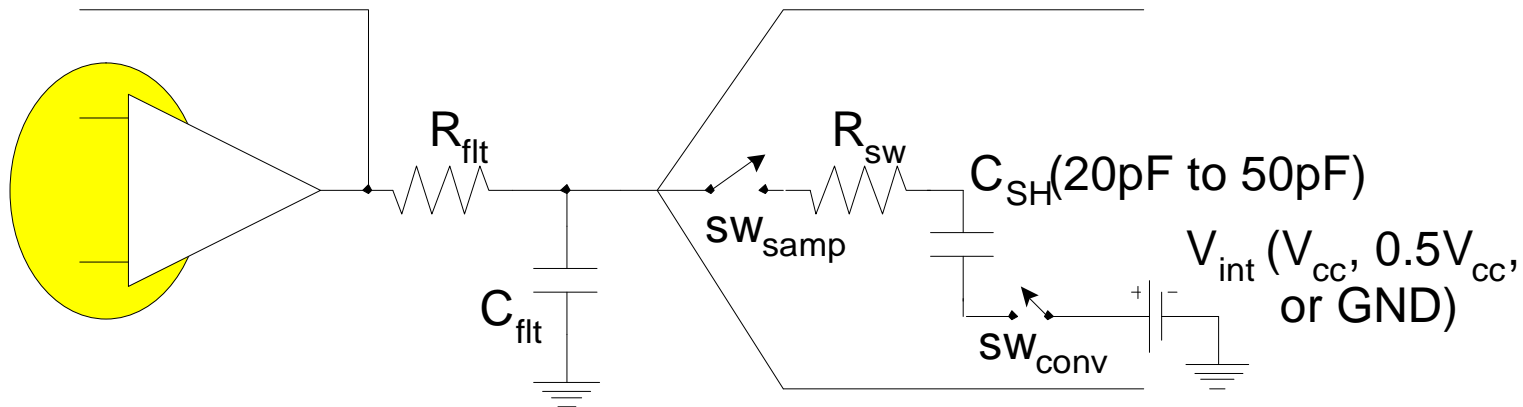


Rail-to-Rail Input



Output Stage Concerns


See Appendix

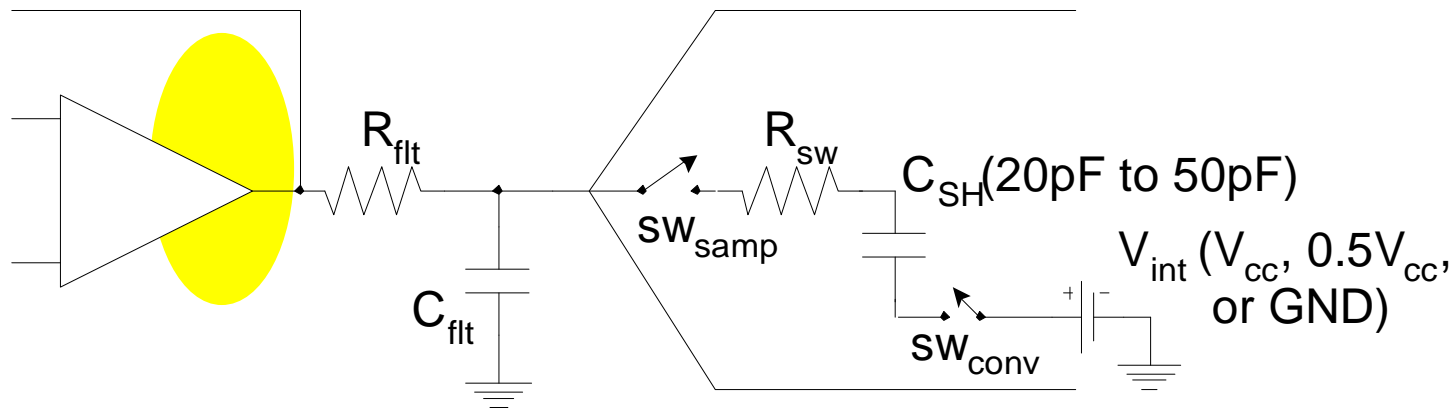

Rail-to-Rail Output



How Fast does that Op Amp Settle

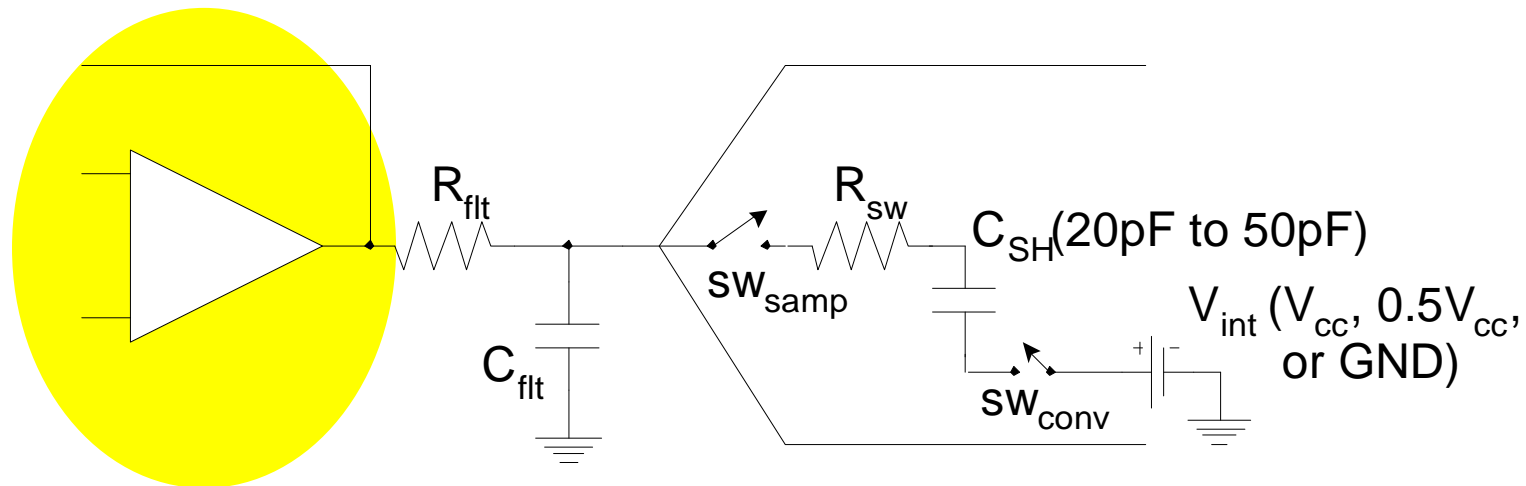



What Settling Time?

u *Think of a linear voltage regulator, there are **TWO** Settling Times.*



n *Line Transient*

n *Load Transient*

u **Same** *applies here.*


u *Data sheets report settling time to 0.01% at best.*

The Test Circuit

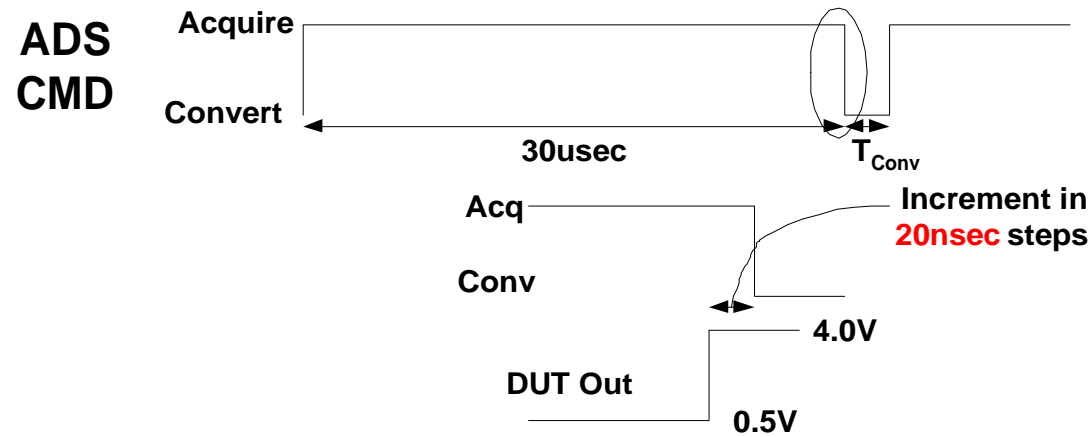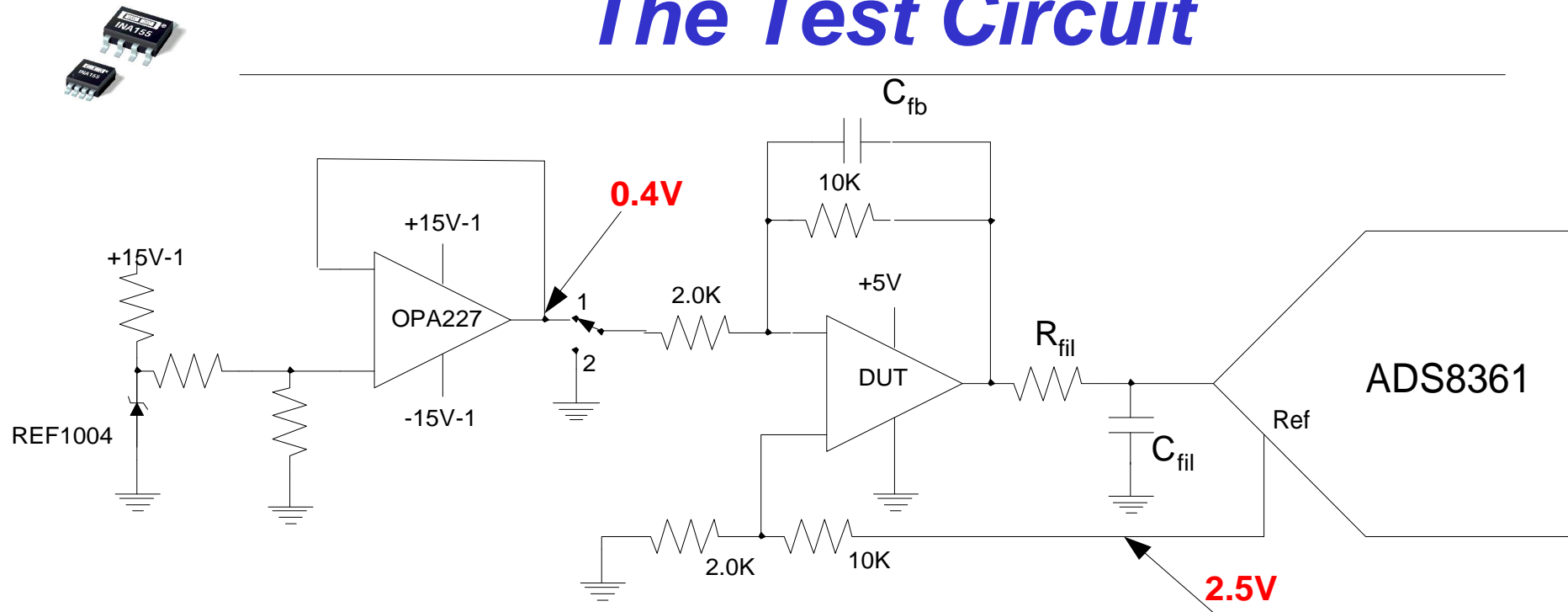




OPA300

 




OPA340

 

25

OPA350

 



Line Transient Becomes

- u Response to change in input signal*
- u Includes Slew Rate.*
- u Op Amp data sheets MAY address Settling Time to 0.01%*
- u But we need 0.0007629% for a 16 bit system*



Required Settling Time

Number of bits	0.5LSB
10	0.0488281%
12	0.0122070%
14	0.0030518%
16	0.0007629%
18	0.0001907%
20	0.0000477%
22	0.0000119%
24	0.0000030%

See appendix for calculations



Load Transient is UNKNOWN

- ⌋ *We know the load is the input capacitance of the A/D*
- ⌋ *We do NOT know the starting voltage.*
 - ⌋ *Possible voltages: GND, Mid-Rail, Random*
 - ⌋ *Not given in data sheet*
- ⌋ *The Op Amp data sheet does NOT even mention this settling time.*



$SAR\ A/D \leq 500kHz$

u 70% Applications


- n *Slow Moving “Real World Process” Signals*
- n *Fast Acquisition & Conversion Allows More System Time For Processing, Computation, Decision Making*
- n *Multiplexed, Scanning Systems for Slow Moving Signals*

u 30% Applications

- n *AC Fast Moving Dynamic Signals*
- n *“Real Time” Processing of Input Signals*




Look at the Charge Transients

 




Capacitor Type is Critical

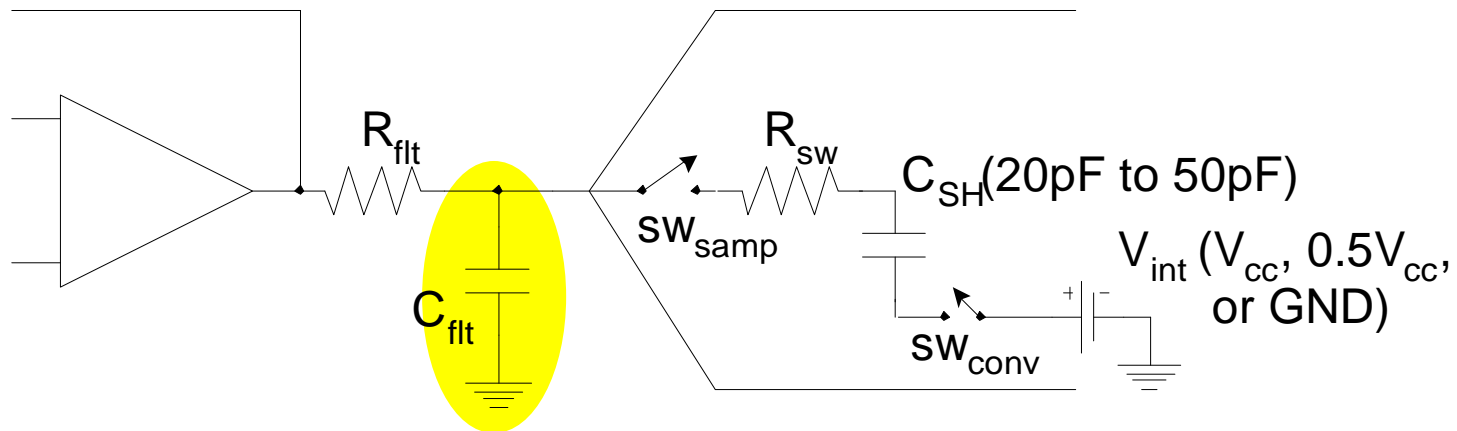



 THD+N vs. Frequency for Various Capacitor types




Sweep	Trace	Color	Line Style	Thick	Data	Axis	Comment
1	1	Yellow	Solid	1	Anlr.THd+N Ratio	Left	C = 0
2	1	Red	Solid	1	Anlr.THd+N Ratio	Left	C1
3	1	Blue	Solid	1	Anlr.THd+N Ratio	Left	C2
4	1	Cyan	Solid	1	Anlr.THd+N Ratio	Left	C3
5	1	Green	Solid	1	Anlr.THd+N Ratio	Left	C4

R = 100 ohm, C = 3.3 nF, Vp-p = 5V f(-3dB) = 482 kHz

3



 THD+N vs. Voltage for Various Capacitor Types



Sweep	Trace	Color	Line Style	Thick	Data	Axis	Comment
1	1	Yellow	Solid	1	Anlr.THd+N Ratio	Left	C = 0
2	1	Red	Solid	1	Anlr.THd+N Ratio	Left	C1
3	1	Blue	Solid	1	Anlr.THd+N Ratio	Left	C2
4	1	Cyan	Solid	1	Anlr.THd+N Ratio	Left	C3
5	1	Green	Solid	1	Anlr.THd+N Ratio	Left	C4

R = 100 ohm, C = 3.3 nF, f = 10 kHz, f(-3dB) = 482 kHz

4




Conclusions on “C” Type

- u *Best performance: Sliver Mica or COG(NPO)*
- u *Avoid all other*
- u *Others may cost less and be smaller but can distort signal*



Selecting the Fly-wheel Values

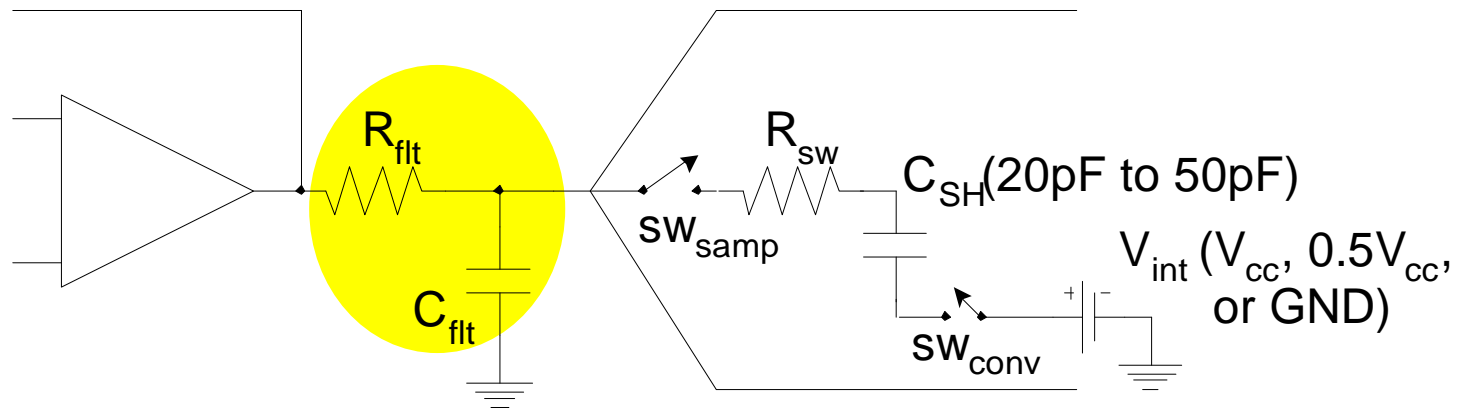



Fly Wheel Component Selection

u Pick $C_{flt} = 20 * C_{SH}$ (See Appendix for proof)

u R_{flt} Calculation

$$n \quad t_{flt_settle} = t_{SAMPL} = 12 \tau_{FLT}$$

Theoretical Minimum



n *Practical results*

w Use $t = 18 \tau_{FLT}$ Margin for:



- o Op Amp Output Load Transient
- o Op Amp Output Small Signal Settling Time

$$n \quad R_{flt} = t_{SAMPL} / 18 C_{flt}$$



ADC Sampling Considerations

  Voltage on the sampling capacitor during sampling period



$$V_C(t) = V_0 + (E - V_0) \times (1 - e^{-\frac{t}{\tau}})$$

$$E - V_C(t_{AQ}) \leq \frac{1}{2} LSB$$


$$V_C(t_{AQ}) \geq E \times (1 - \frac{1}{2^{17}})$$

$$\tau \leq \frac{t_{AQ}}{\ln(\frac{E - V_0}{E} \times 2^{17})}$$



ADC Sampling Considerations

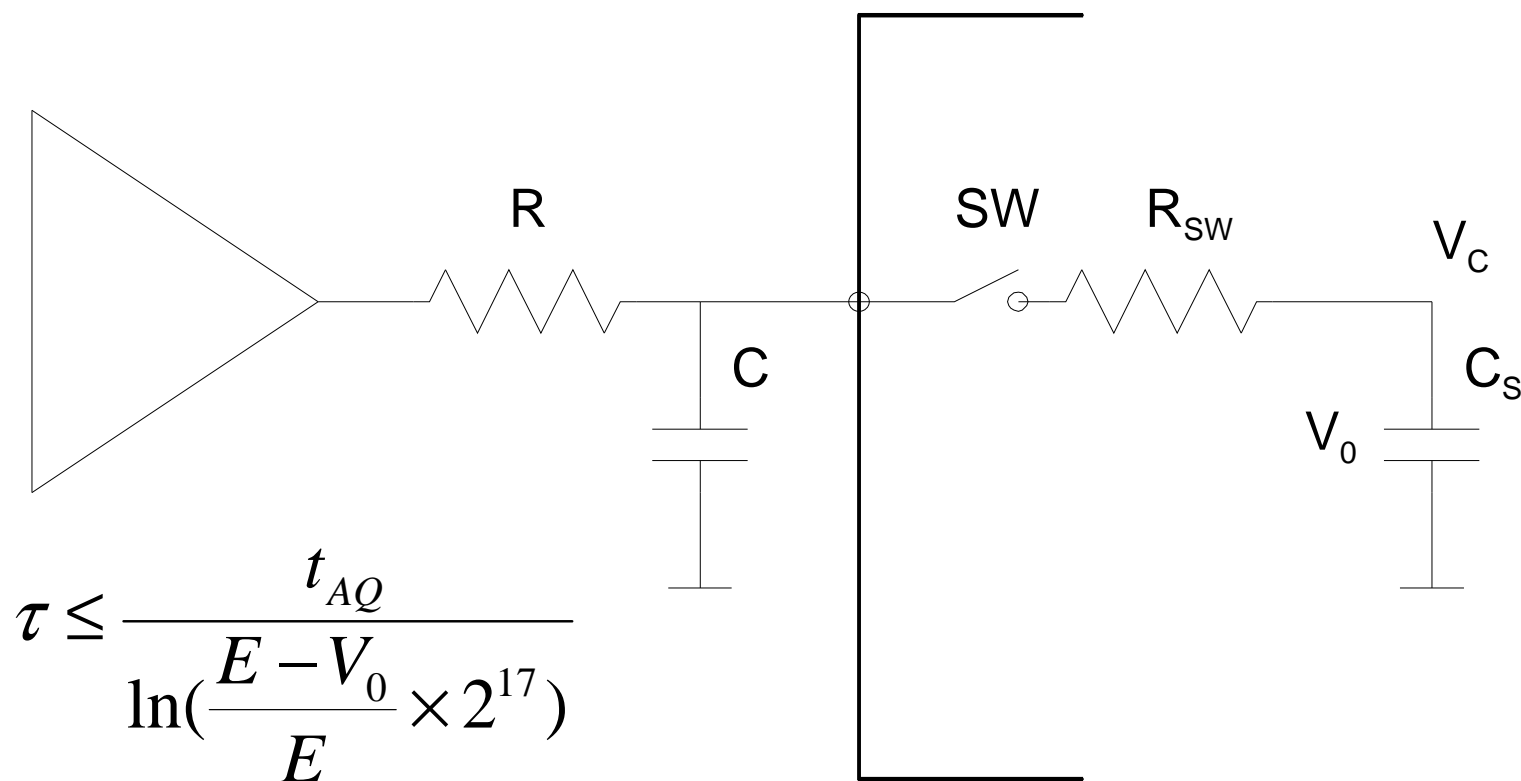Suggested input sampling switch transient-immunity RC filter





Required Settling Time

Number of bits	0.5LSB	Time Constants
10	0.0488281%	8
12	0.0122070%	9
14	0.0030518%	11
16	0.0007629%	12
18	0.0001907%	13
20	0.0000477%	15
22	0.0000119%	17
24	0.0000030%	18

See appendix for calculations



Establish Op Amp Specs

Determine Op Amp specs needed based on system values set in design.

Op Amp specs to be determined:

u UGBW

u Slew Rate

u I_{out}



Impact on UGBW

⌋ *Modified A_{ol} due to R_{FLT} & C_{FLT}*

⌋ $f_{PX} = 1/[2 \Pi (R_O + R_{FLT}) C_{FLT}]$

⌋ $f_{ZX} = 1/[2 \Pi R_{FLT} C_{FLT}]$

⌋ *Stability Check*


⌋ At f_{cl} “Rate-of-closure” is
20dB/decade $\Rightarrow f_{ZX}$ cancels f_{PX}
before f_{cl}

⌋ f_{PX} and f_{ZX} are \leq decade apart
w Phase of pole will be cancelled by
phase of zero

⌋ This implies: $R_{FLT} < 9 R_O$


⌋ *Impact on UGBW*

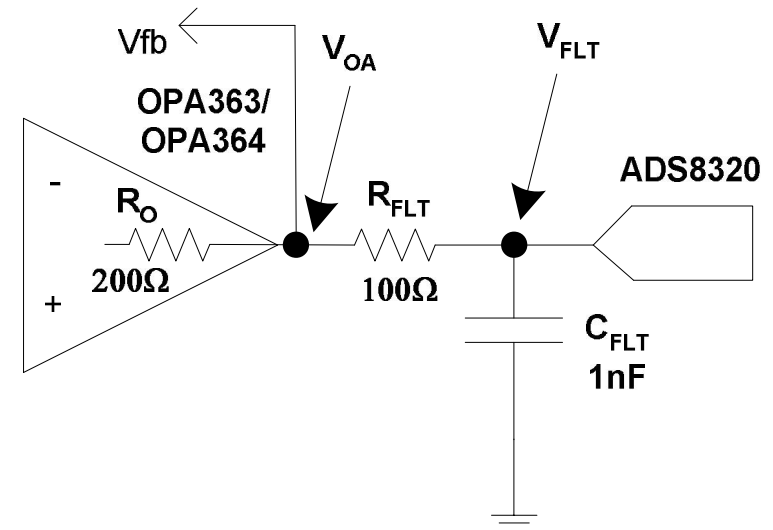⌋ $UGBW_{mod} = UGBW_{orig} - (f_{ZX} - f_{PX})$





Impact on U_{GBW} -cont

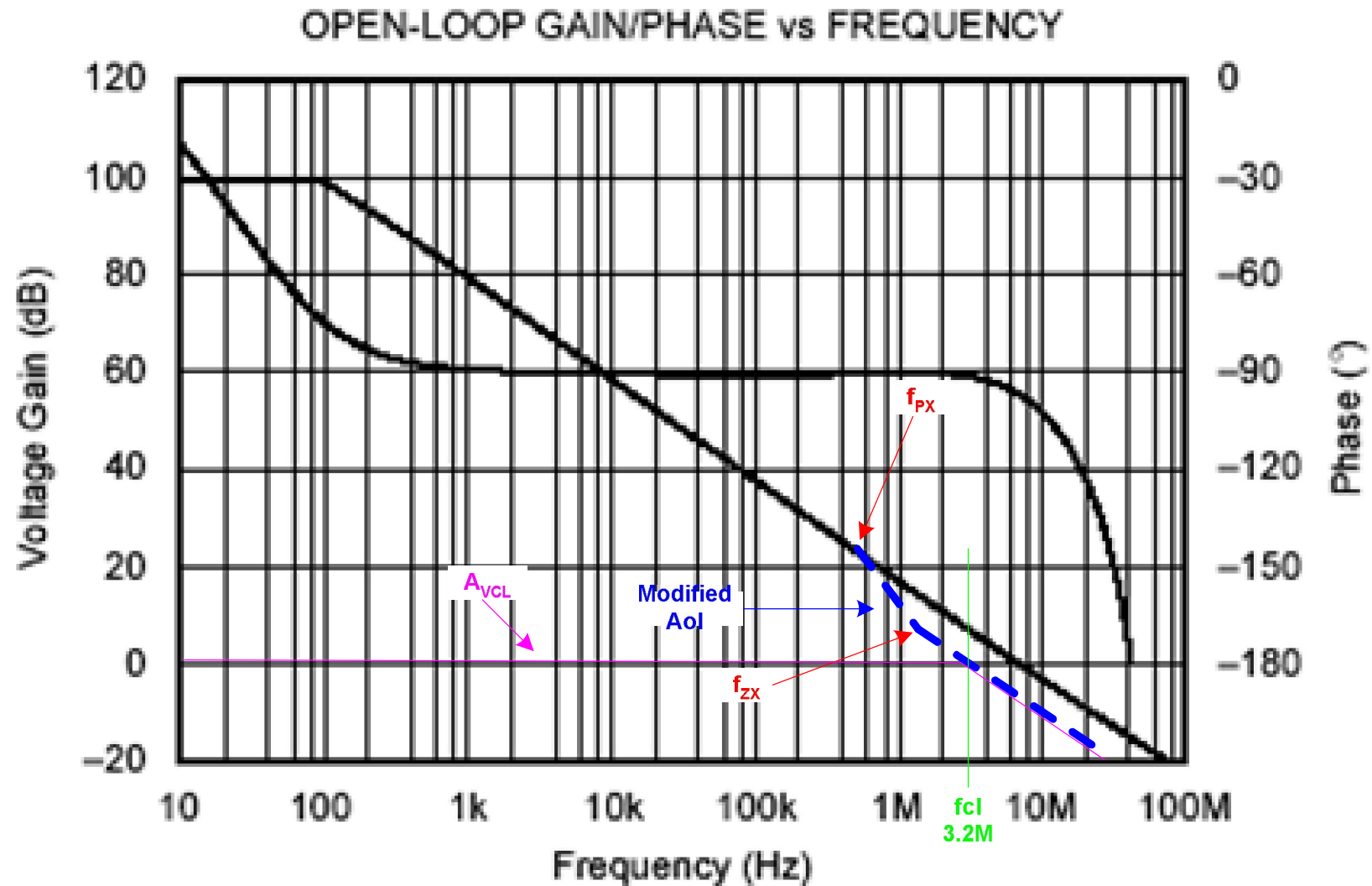



Op Amp Specs to Check

u $U_{GBW_{mod}} > 2 * 1/[2 \Pi R_{FLT} C_{FLT}]$

u Op Amp Transient Output Drive
to R_{FLT} & C_{FLT}

$$n I_{Opk max} = (5\% V_{REF})/(R_{FLT})$$



Interface Design Check List

- u Op Amp Common Mode Voltage*
- u Op Amp Output Swing to Rail*
- u Op Amp Settling Time*
- u Filter Capacitor Type*
- u Filter Component Values*
- u Op Amp Specifications*



Appendix – Calculation Details

1. C_{flt} as a Function of C_{sh}

2. Open Loop Output Resistance

VS.


Closed Loop Output Resistance

3. Modified A_{ol} Calculations

4. Time to Charge Capacitor




Op Amp Input Concerns

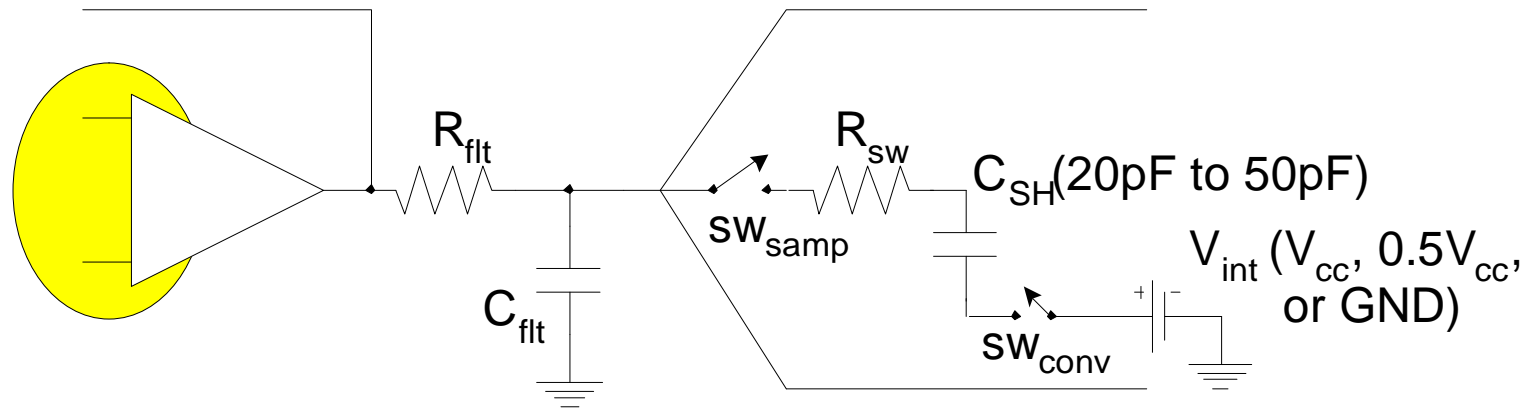

Rail-to-Rail Input




Input Stage-Parallel P-ch & N-ch

 



Looking at Input Stage Performance

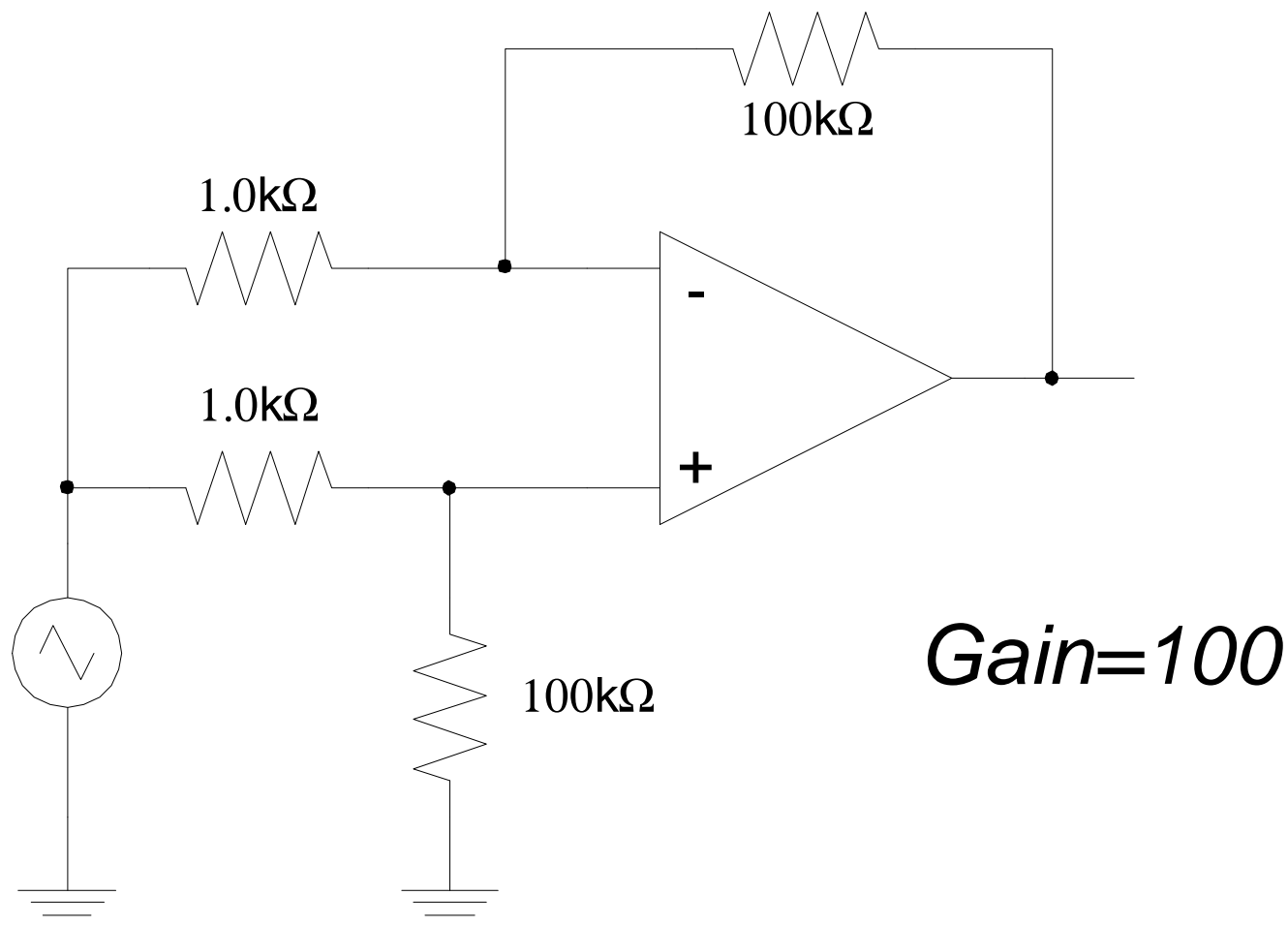




Single Supply RRI Plot- V_{OS} vs CMV

(Most RRI Op Amps Except OPA363/OPA364)

 OPA2340 (Dual: V_{OUT1} & V_{OUT2} from different halves)




50



Performance Requirements

 
The simple buffer stage.
Most accurate unity gain.



Bits	(mV)	(dB)
10	2.44	66.2
12	0.61	78.3
16	0.0382	102.3




OPA350 Data Sheet THD+N

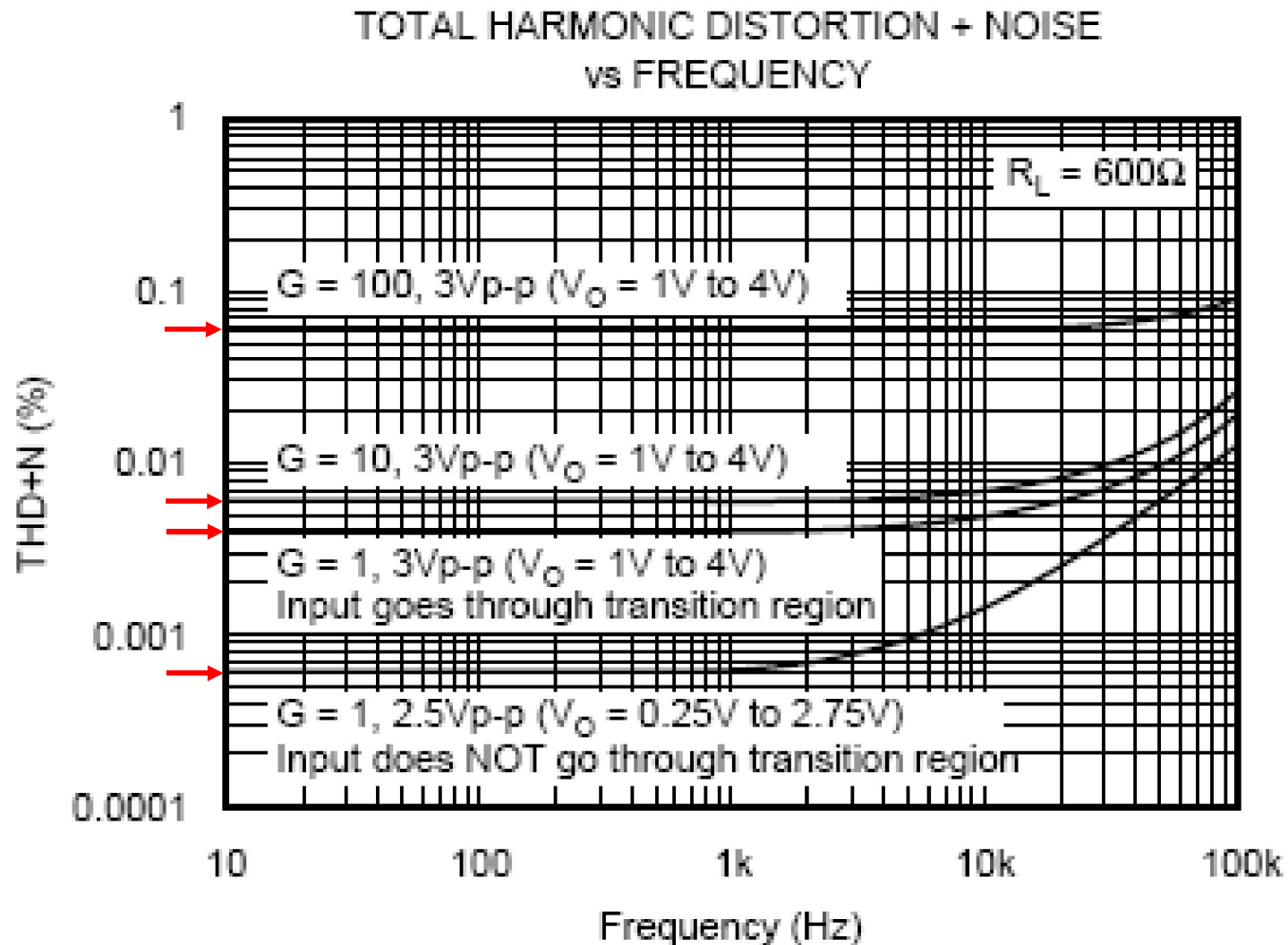




Possible Input Schemes

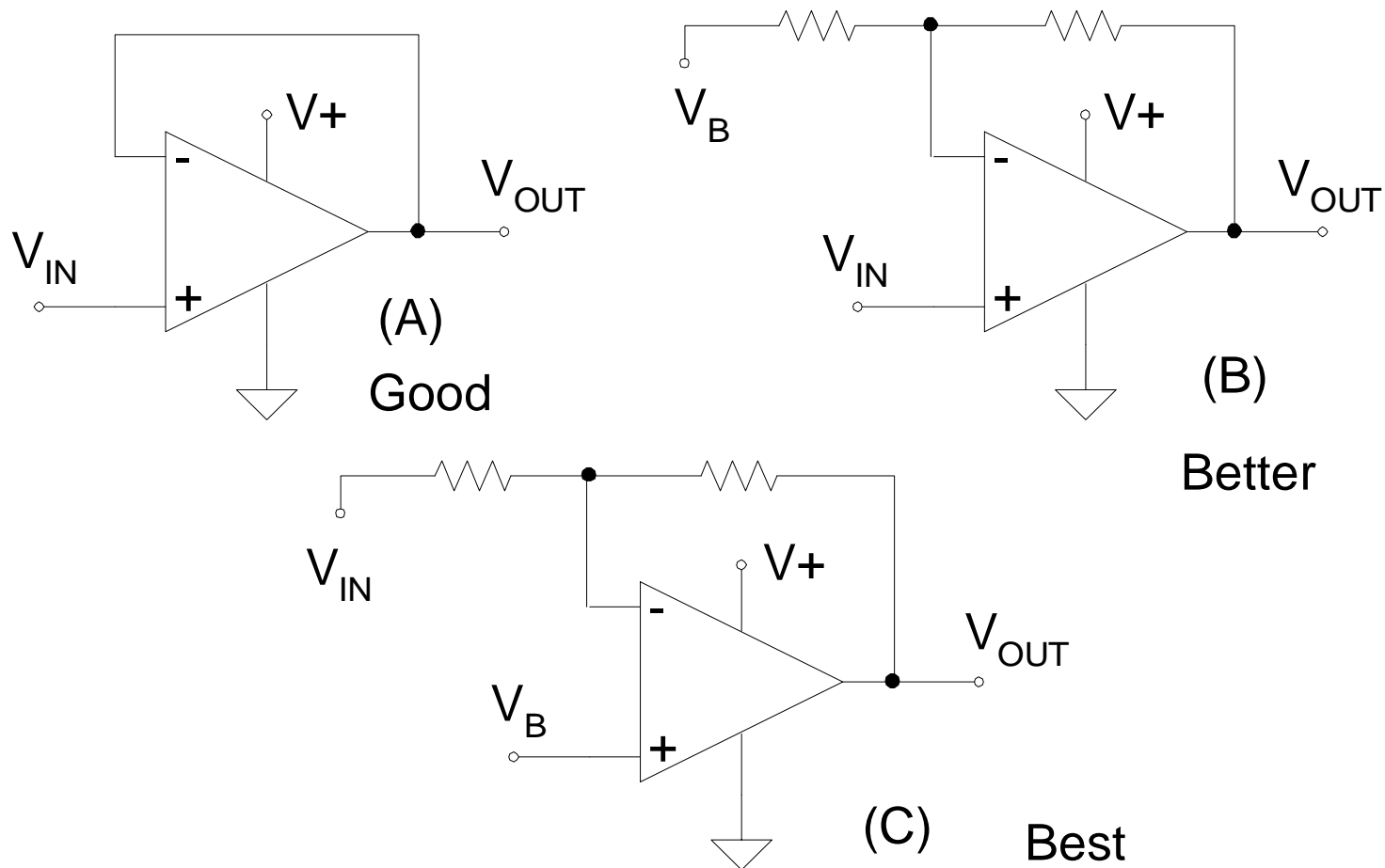



OPA350 THD+N vs Frequency

 


Sweep	Trace	Color	Line Style	Thick	Data	Axis	Comment
1	1	Yellow	Solid	1	Anlr.THd+N Ratio	Left	OPA350 High CMRR G=-1
2	1	Red	Solid	1	Anlr.THd+N Ratio	Left	OPA350 High CMRR G=+1
3	1	Blue	Solid	1	Anlr.THd+N Ratio	Left	OPA350 Low CMRR G=+1
4	1	Cyan	Solid	1	Anlr.THd+N Ratio	Left	OPA350 Low CMRR G=-1

OPA 350, R = 0 ohm, C = 0 nF, Vp-p = 4 V, G = +1or -1



OPA350 with RC, THD+N vs Frequency

 


Sweep	Trace	Color	Line Style	Thick	Data	Axis	Comment
1	1	Yellow	Solid	1	Anl. THD+N Ratio	Left	OPA350 Low CMRR G=+1 C1
2	1	Red	Solid	1	Anl. THD+N Ratio	Left	OPA350 Low CMRR G=-1 C4

OPA 350, R = 100 ohm, C = 3.3 nF, Vp-p = 4 V, f(-3dB) = 482 kHz, G = +1or -1



OPA350 THD+N vs Input Voltage

 


Sweep	Trace	Color	Line Style	Thick	Data	Axis	Comment
1	1	Yellow	Solid	1	Anlr.THd+N Ratio	Left	OPA350 Low CMRR 1kHz
2	1	Red	Solid	1	Anlr.THd+N Ratio	Left	OPA350 Low CMRR 10kHz
3	1	Cyan	Solid	1	Anlr.THd+N Ratio	Left	OPA350 Low CMRR 50kHz
4	1	Green	Solid	1	Anlr.THd+N Ratio	Left	OPA350 Low CMRR 100kHz

OPA 350, R = 0 ohm, C = 0 nF, G = -1




Output Stage Concerns

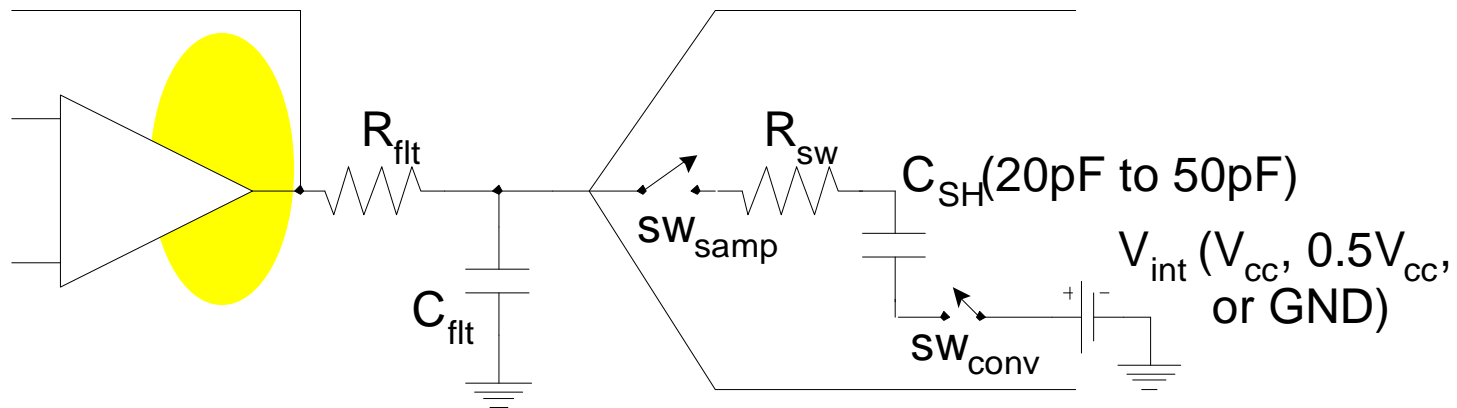

Rail-to-Rail Output




OPA300

 




OPA350

 

Solution Circuit

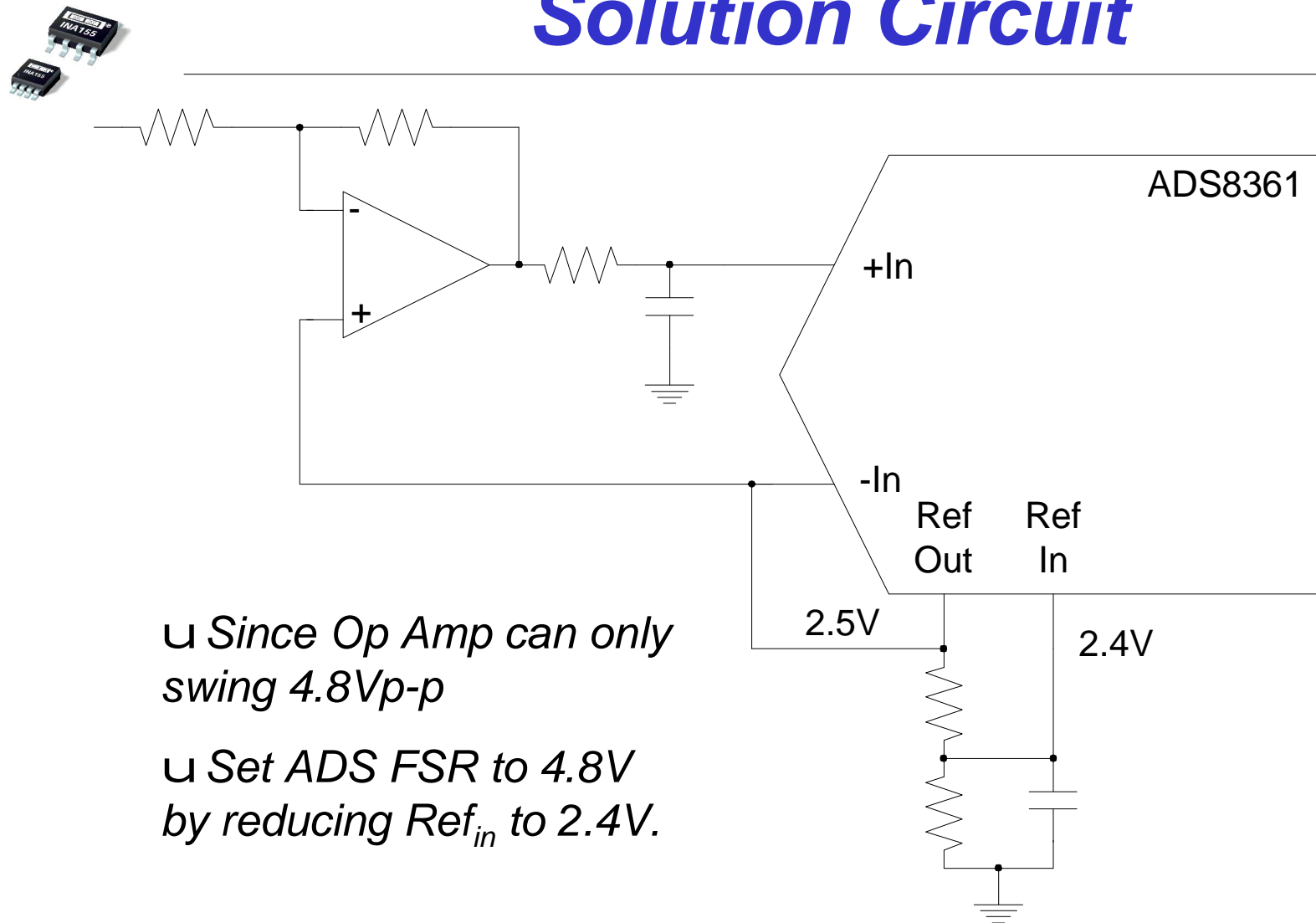


⌋ Since Op Amp can only swing 4.8Vp-p

⌋ Set ADS FSR to 4.8V by reducing Ref_{in} to 2.4V.



Filter Design Example

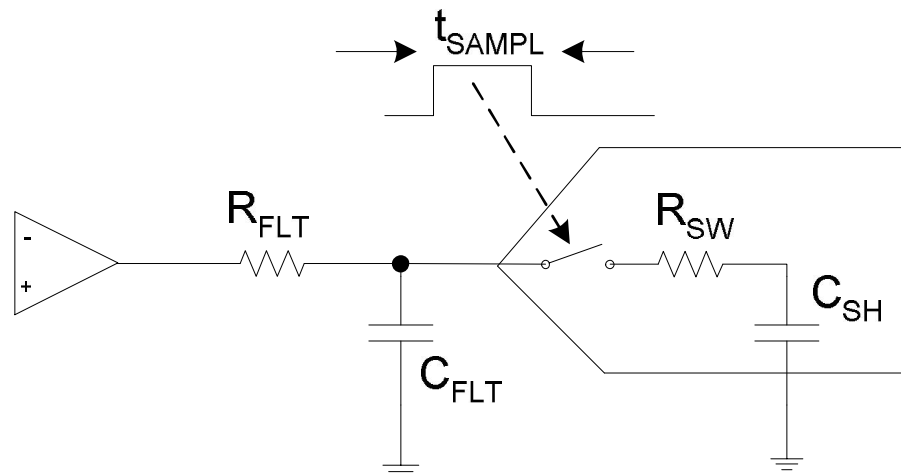

u $R_{SW} = 100$ (Not needed for Buffer & Filter Calculations)



u $C_{SH} = 50pF$ [for ADS8361]



u Worst case V across C_{SH} is V_{REF}
n $V_{REF} = +5V$



u $t_{SAMPL} = 1.88\mu s$ [for ADS8361]



Filter Design Example(cont)

⌋ Charge Transfer Equation: $Q = CV$

⌋ Charge required to charge C_{SH} to V_{REF}



n $Q_{SH} = C_{SH} V_{REF}$

n $Q_{SH} = 50\text{pF} \cdot 5\text{V} = 250\text{pC}$

⌋ IDEAL C_{FLT}

n “Charge Bucket” to fill C_{SH} with only a $76\mu\text{V}$ (1/2LSB) droop on C_{FLT}

n $Q_{FLT} = Q_{SH}$

n $Q_{FLT} = C_{FLT} (38\mu\text{V})$

n $250\text{pC} = C_{FLT} (38\mu\text{V}) \quad C_{FLT} = 6.6\mu\text{F}$

⌋ IDEAL $C_{FLT} = 6.6\mu\text{F}$

n Not a good, small, cheap high frequency ceramic capacitor

n Not practical for Op Amp to drive directly (stability, transient current)

n Isolation resistor likely not large enough to help isolate Cload and still meet necessary filter time constant



Filter Design Example(cont)

⌋ Partition the “Charge Bucket”

- n 95% from C_{FLT}
- n 5% from Op Amp



⌋ C_{FLT} value required to provide Q_{SH} with <5% droop on C_{FLT}

- n $Q_{FLT} = Q_{SH}$
- n $Q_{FLT} = C_{FLT} (0.05V_{REF})$
- n $250pC = C_{FLT} (0.05 \cdot 5V) \quad C_{FLT} = 1nF$




⌋ During t_{SAMPL} the Op Amp must provide 5% V_{REF} to C_{FLT}

- n Ensure C_{FLT} is at least $10X > C_{SH}$
 - w This implies dominant load for Op Amp Buffer is C_{FLT}
 - w $1nF = 20 \times 50pF \Rightarrow C_{FLT} = 20X C_{SH}$





Op Amp Model for Derivation of R_{OUT}

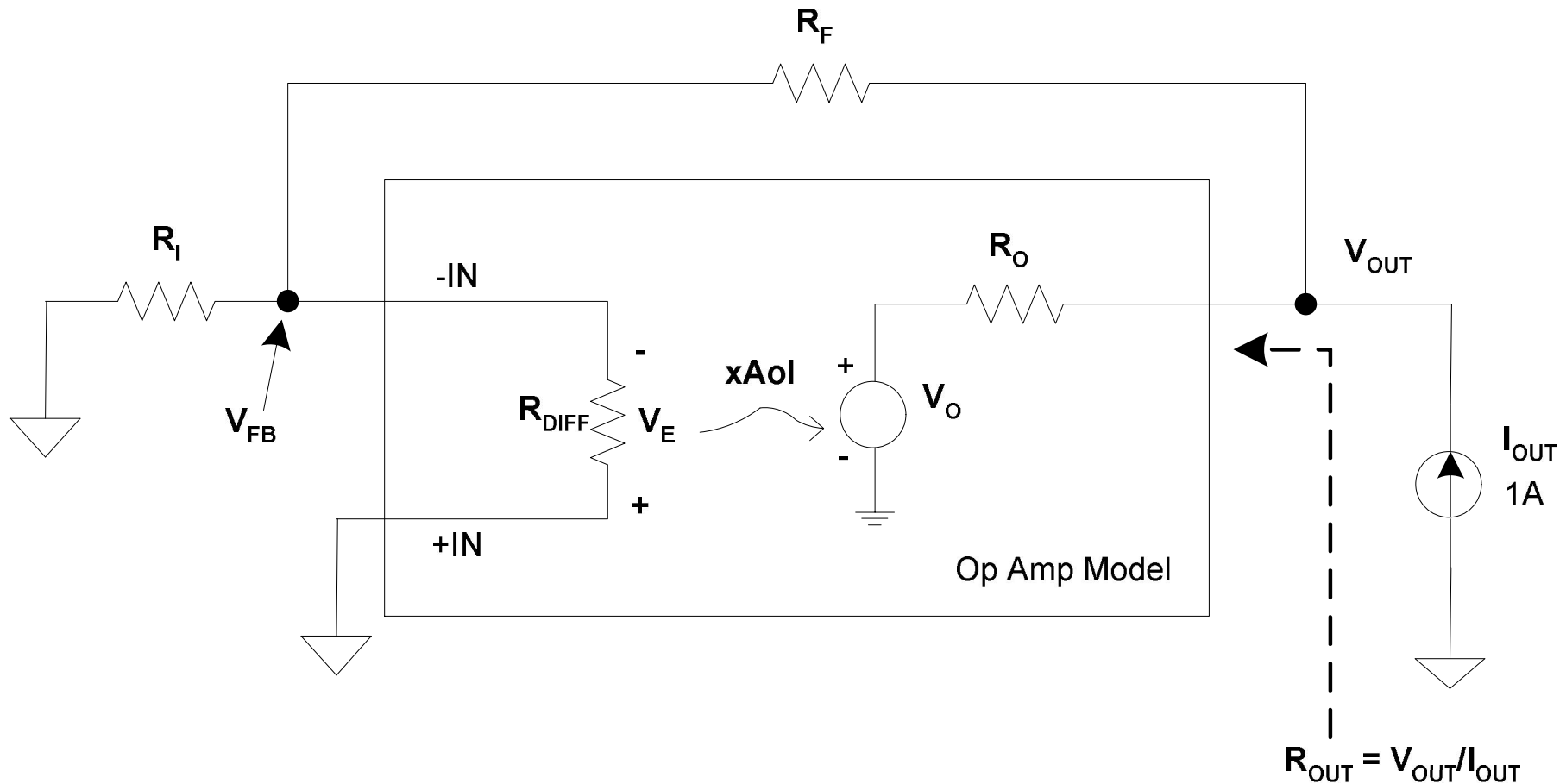



Derivation of R_{OUT} (Closed Loop Output Resistance)

$$\beta = V_{FB}/V_{OUT} = [V_{OUT} (R_I / \{R_F + R_I\})]/V_{OUT} = R_I / (R_F + R_I)$$

$$R_{OUT} = V_{OUT}/I_{OUT}$$

$$V_O = -V_E A_{ol}$$

$$V_E = V_{OUT} [R_I/(R_F + R_I)]$$

$$V_{OUT} = V_O + I_{OUT} R_O$$

$$V_{OUT} = -V_E A_{ol} + I_{OUT} R_O$$

$$V_{OUT} = -V_{OUT} [R_I/(R_F + R_I)] A_{ol} + I_{OUT} R_O$$

$$V_{OUT} + V_{OUT} [R_I/(R_F + R_I)] A_{ol} = I_{OUT} R_O$$

$$V_{OUT} = I_{OUT} R_O / \{1 + [R_I A_{ol}/(R_F + R_I)]\}$$

$$R_{OUT} = V_{OUT}/I_{OUT} = I_{OUT} R_O / \{1 + [R_I A_{ol}/(R_F + R_I)]\}$$

$$R_{OUT} = R_O / (1 + A_{ol}\beta)$$





OPA353 Specifications

$$R_O = 40$$


$$R_{OUT} (@1\text{MHz}, G=10) = 10$$
  
$$A_{ol} @1\text{MHz} = 29.54\text{dB} = \times 30$$





OPA353 R_{OUT} Calculation

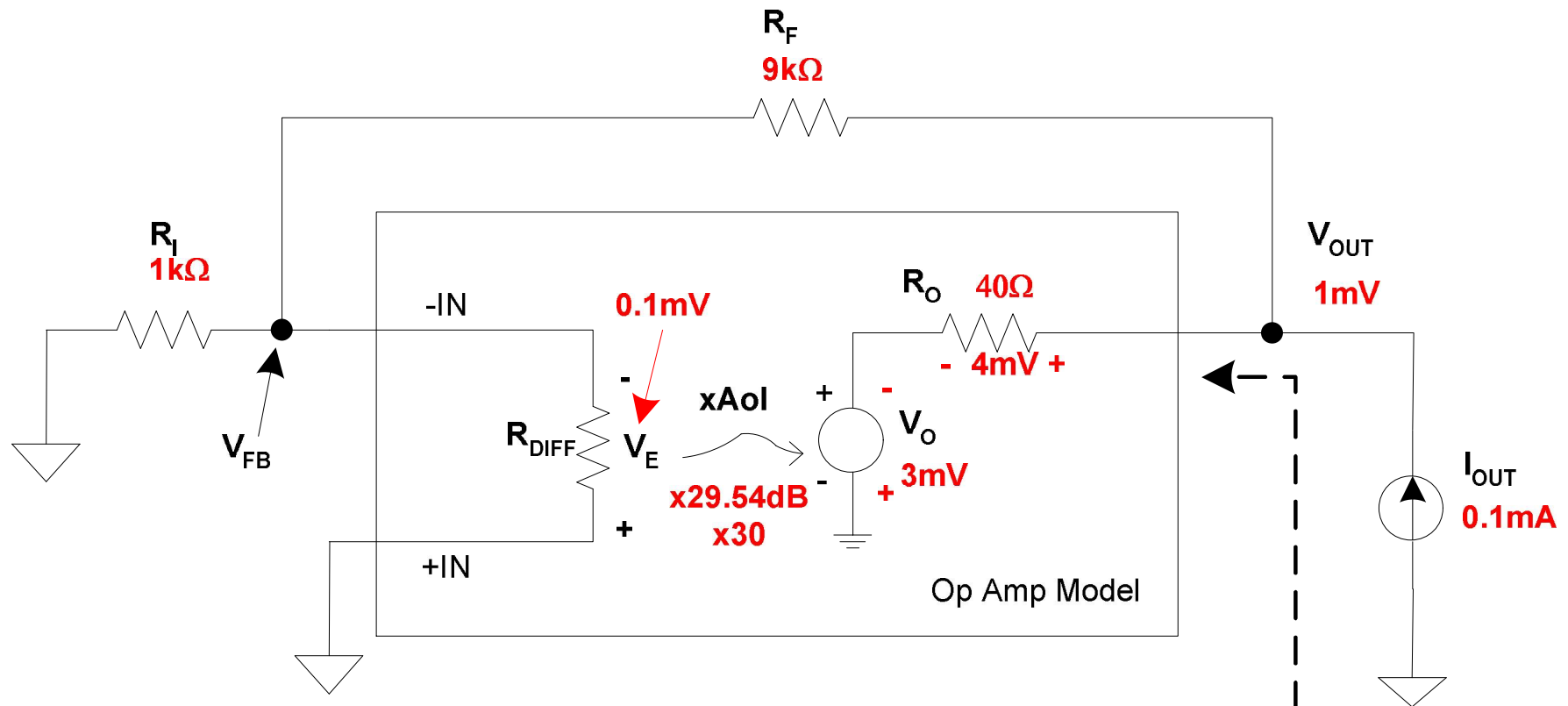

$$R_O = 40$$

$$R_{OUT} (@1\text{MHz}, G=10) = 10$$

$$A_{ol} @10\text{mHz} = 29.54\text{dB} = x30$$

$$R_{OUT} = V_{OUT} / I_{OUT}$$

$$R_{OUT} = 1\text{mV} / 0.1\text{mA}$$

$$R_{OUT} = 10\Omega$$




R_{OUT} vs R_O

- ⌋ R_O does not change when feedback is used to close the loop
- ⌋ Closed loop feedback forces V_O to increase/decrease
- ⌋ The increase/decrease in V_O appears at V_{OUT} as a reduction in R_O
- ⌋ R_{OUT} is the net effect of R_O and closed loop feedback controlling V_O




Op Amp Model for AC Stability Analysis

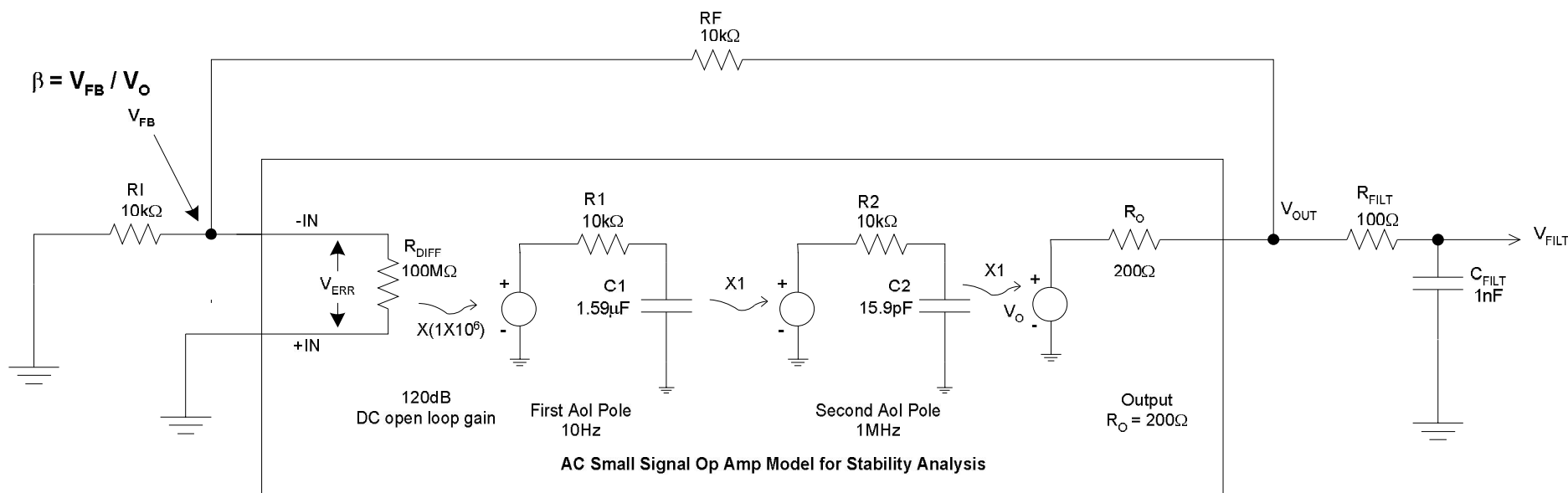- Ø R_O is constant over the Op Amp's bandwidth
- Ø R_O is defined as the Op Amp's Open Loop Output Resistance
- Ø R_O is measured at $I_{OUT} = 0$ Amps, $f = 1\text{MHz}$
- Ø R_O is included in β calculation





Aol Modified by Filter

 



Modified Aol-The Math

$$V_{OUT} = \frac{V_O \left(R_{flt} + \frac{1}{sC_{flt}} \right)}{R_O + R_{flt} + \frac{1}{sC_{flt}}}$$

$$\frac{V_{OUT}}{V_O} = K = \frac{\left(R_{flt} + \frac{1}{sC_{flt}} \right)}{R_O + R_{flt} + \frac{1}{sC_{flt}}}$$

$$\frac{V_{OUT}}{V_O} = K = \frac{sC_{flt}R_{flt} + 1}{sC_{flt}(R_O + R_{flt}) + 1}$$

$$\frac{V_{OUT}}{V_O} = K = \frac{s + \frac{1}{C_{flt}R_{flt}}}{\frac{C_{flt}(R_O + R_{flt})}{C_{flt}R_{flt}} s + \frac{1}{C_{flt}R_{flt}}}$$



Modified Aol-The Math – cont.

$$\frac{V_{OUT}}{V_O} = K = \frac{\left(s + \frac{1}{C_{flt} R_{flt}} \right) \left(\frac{C_{flt} R_{flt}}{C_{flt} (R_O + R_{flt})} \right)}{s + \left(\frac{1}{C_{flt} R_{flt}} \right) \left(\frac{C_f R_f}{C_{flt} (R_O + R_{flt})} \right)}$$



$$\frac{V_{OUT}}{V_O} = K = \frac{\left(s + \frac{1}{C_{flt} R_{flt}} \right) \left(\frac{R_{flt}}{(R_O + R_{flt})} \right)}{s + \left(\frac{1}{C_{flt} R_{flt}} \right) \left(\frac{R_{flt}}{(R_O + R_{flt})} \right)}$$

$$\frac{V_{OUT}}{V_O} = K = \left(\frac{R_{flt}}{(R_O + R_{flt})} \right) \frac{\left(s + \frac{1}{C_{flt} R_{flt}} \right)}{\left(s + \frac{1}{C_{flt} (R_O + R_{flt})} \right)}$$

$$f_p = \frac{1}{2\pi C_{flt} (R_O + R_{flt})}; \quad f_z = \frac{1}{2\pi C_{flt} R_{flt}}$$



  Voltage on the sampling capacitor during sampling period



$$V_C(t) = V_0 + (E - V_0) \times (1 - e^{-\frac{t}{\tau}})$$

$$E - V_C(t_{AQ}) \leq \frac{1}{2} LSB$$

$$V_C(t_{AQ}) \geq E \times (1 - \frac{1}{2^{17}})$$

$$\tau \leq \frac{t_{AQ}}{\ln(\frac{E - V_0}{E} \times 2^{17})}$$