

Precision DAC Essentials

Precision DAC Applications


What is this presentation?

- A guide to understanding fundamental DAC specifications
- An explanation of DAC architectures to leverage when making device selection
- How TI measures each specification to provide an 'apples to apples' comparison to competitors devices

Presentation Agenda

- TI DAC Landscape & Precision DACs
- The Ideal DAC
- DAC Architectures
 - String
 - R2R MDAC
 - R2R BDAC
- Static DAC Specifications
 - TUE & Calibration
- Dynamic Specifications
- Closing the Loop

DAC Architectures & Applications

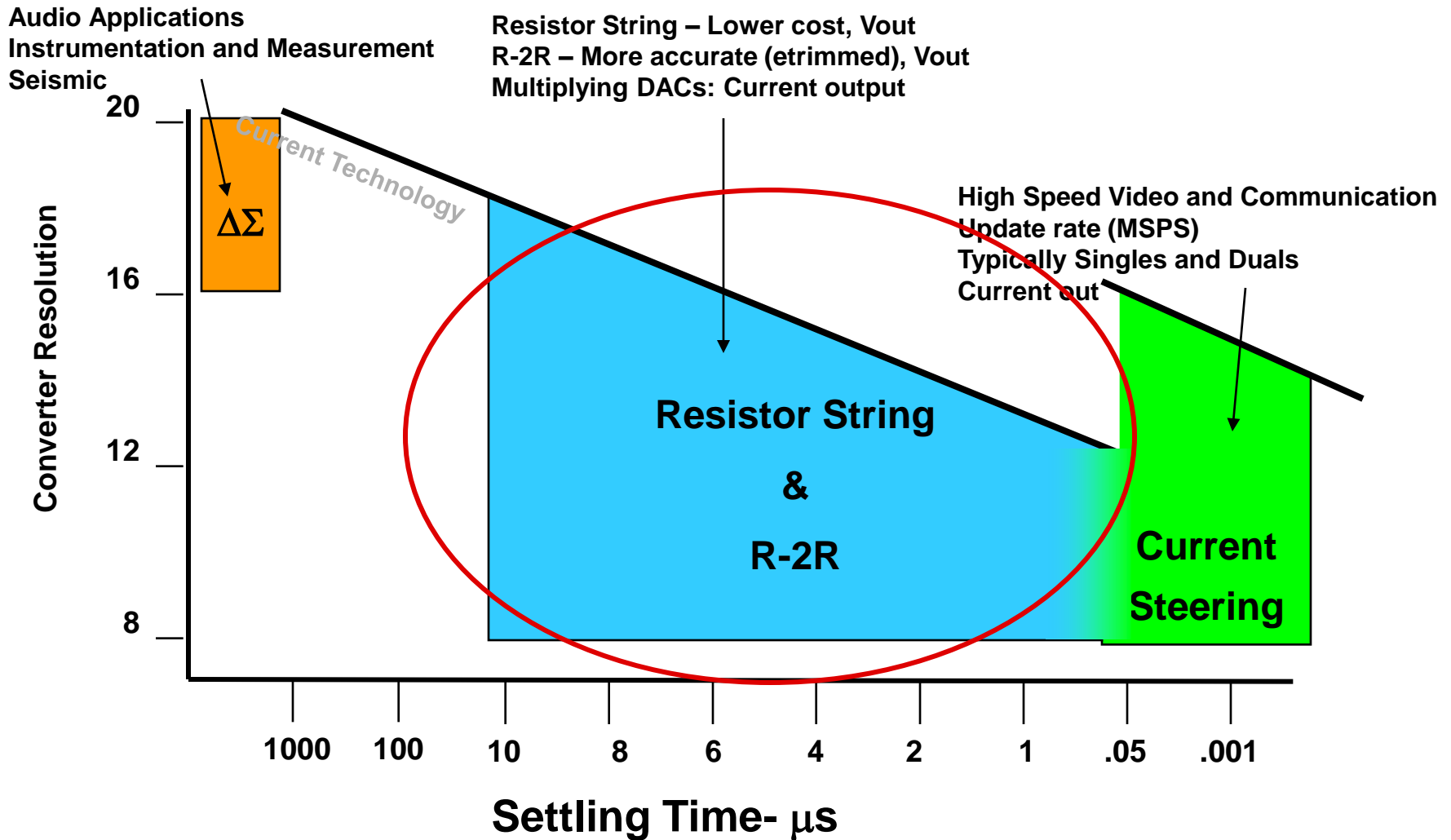

Precision DAC Strategy and Growth Areas



Industrial



Applications:
Industrial Automation - Sensors/PLC -
Motor Control -
Test & Measurement Equipment



Products:
DAC8750/60 with 4-20mA and $\pm 10V$
DAC8770 with Power Management
DAC874x loop powered w. HART



Communications



Applications:
Basestation Analog Monitor and
Control (AMC) -
WI - Backhaul - Optical Networking



Products:
AMC7832 12 bit integrated ADC & DAC
AMC7834: 12 bit integrated ADC & DAC
AMC7812 12 bit integrated ADC & DAC



Catalog & Automotive



Applications:
Medical -Automotive - Consumer -
Computer



Products:
DAC8562 smallest 2-channel DAC
DAC7311 1-channel DAC in SC70
DAC8568 8-channel 16-Bit DAC

*Devices in **RED** are not yet released

> 600 orderables

> 1500 customers

 TEXAS INSTRUMENTS


Where are Precision DACs used?

- DC Bias and offset control
- Closed loop control systems
- Driving a voltage controlled oscillator
- Automated test equipment
- Industrial Communication

Presentation Agenda

- TI DAC Landscape & Precision DACs
- **The Ideal DAC**
- DAC Architectures
 - String
 - R2R MDAC
 - R2R BDAC
- Static DAC Specifications
 - TUE & Calibration
- Dynamic Specifications
- Closing the Loop

Ideal Transfer Function

 

Resolution = n – The number of bits used to quantify the output

Codes = 2^n – The number of input code combinations

Full Scale code = $2^n - 1$ – The largest code that can be written


Reference Voltage = V_{ref} – Sets the LSB voltage or current size and converter range

LSB = $V_{ref} / 2^n$ – The output voltage or current step size of each code

Full Scale Voltage = $V_{ref} - 1\text{LSB}$
– Full scale output voltage of the DAC

Transfer Function =
 $V_{ref} \times (\text{code} / 2^n)$ – Relationship between input data word and output voltage or current


Example DAC Transfer Function

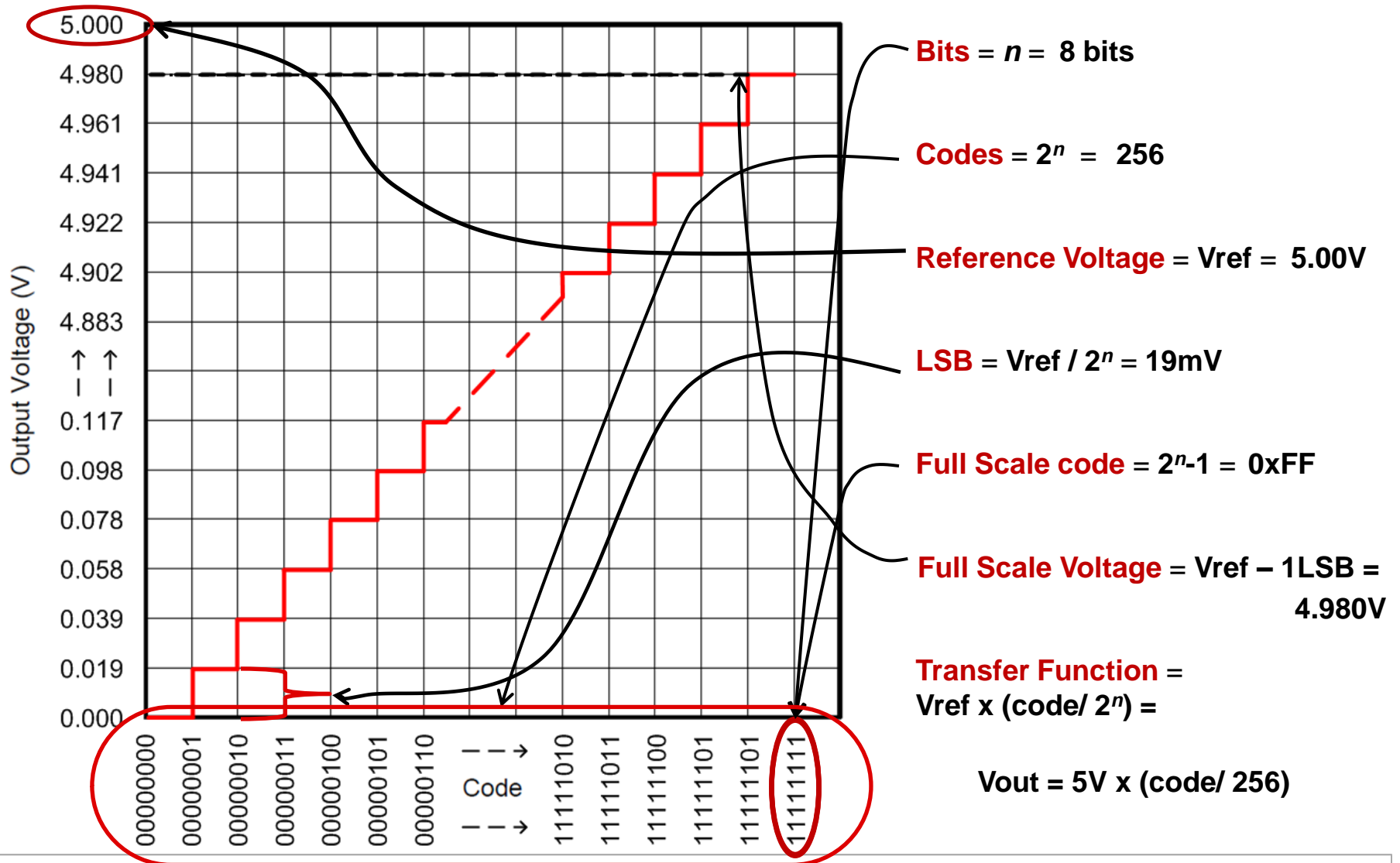

Ideal DAC Properties

- Near rail-to-rail output set by the reference input
 - Remember the full scale output voltage is $V_{ref} - 1 \text{ LSB}$
- Any two sequential codes are exactly 1 LSB apart
- No missing codes
- Instantaneous transition from code-to-code
- Fully monotonic

But what's Monotonicity?

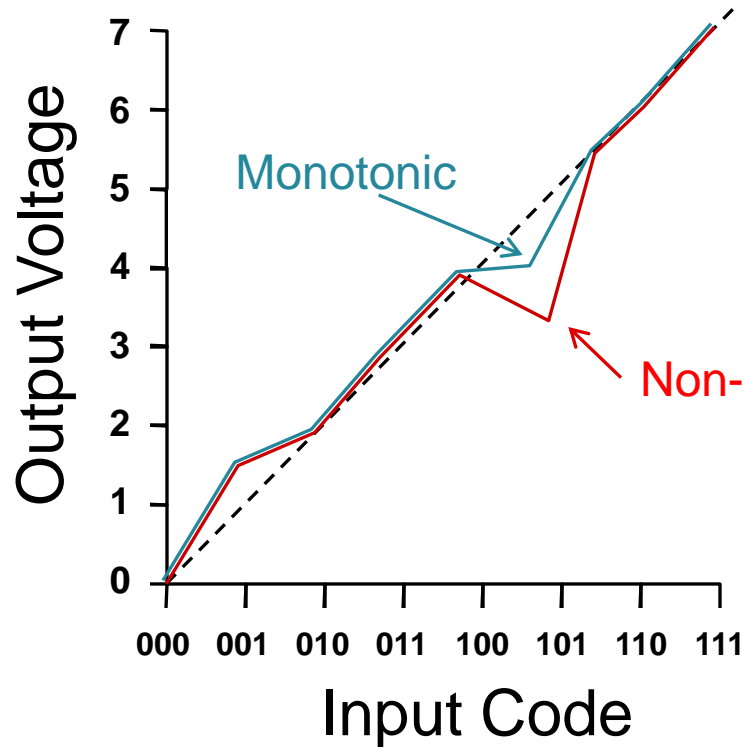

In a monotonic DAC


- Analog output always increases or remains constant as the digital input increases.

Presentation Agenda

- TI DAC Landscape & Precision DACs
- The Ideal DAC
- DAC Architectures
 - String
 - R2R MDAC
 - R2R BDAC
- Static DAC Specifications
 - TUE & Calibration
- Dynamic Specifications
- Closing the Loop

String DAC / Kelvin Divider DAC

The String DAC Architecture

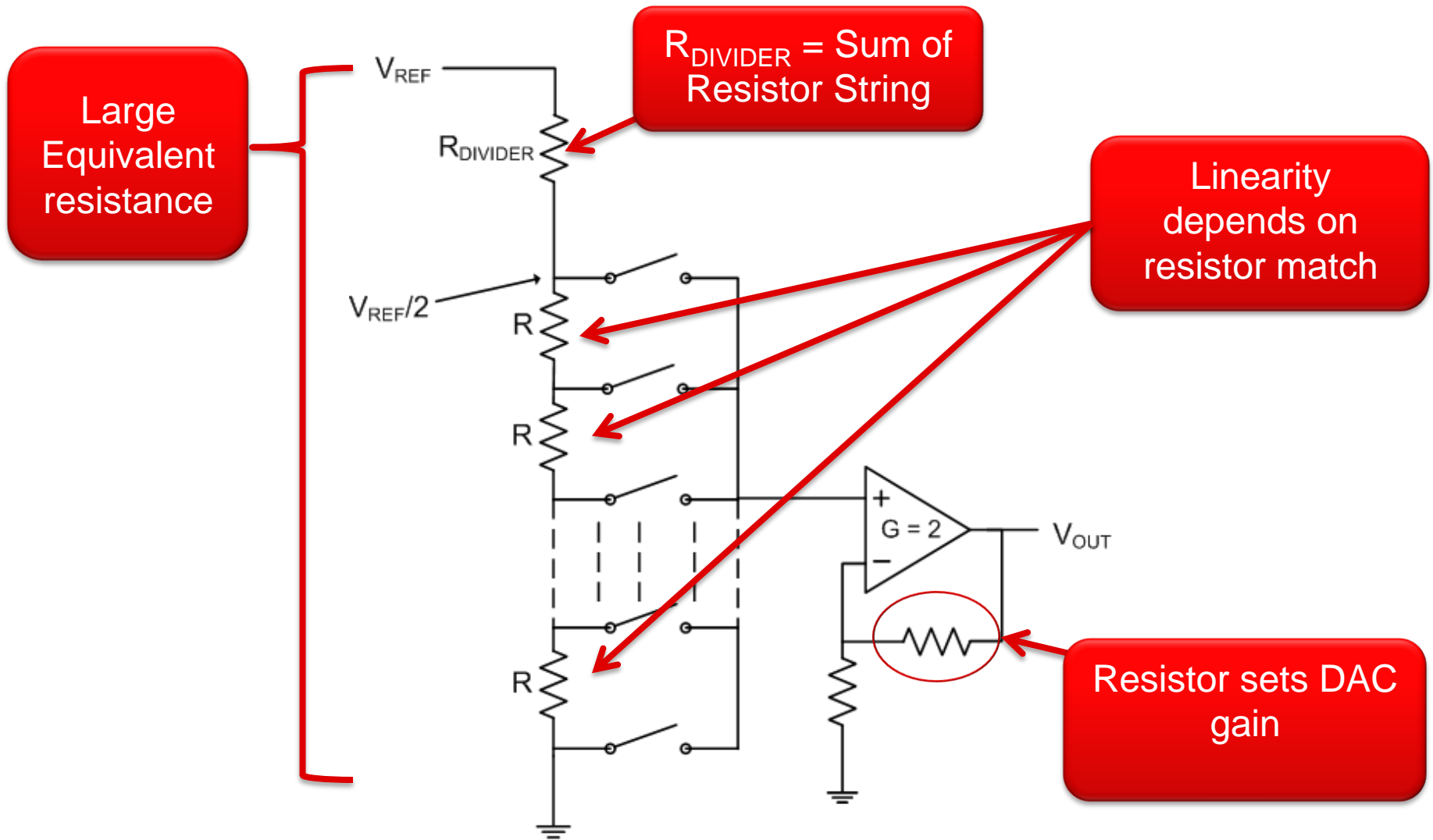

String DAC

Advantages

- Inexpensive
- Low glitch energy
- Inherently monotonic
- Low power
- Small package

Disadvantages

- Limited resolution
- Linearity
- Buffer required to isolate from point of load

Applications

Portable equipment

Closed Loop Systems


Adjustable Reference

DC Biasing

•Example parts: DAC8562, DAC8560, DAC8568, DAC7678, DAC8411, DAC8718, DAC8728

R-2R DAC / Back DAC

R-2R Back DAC

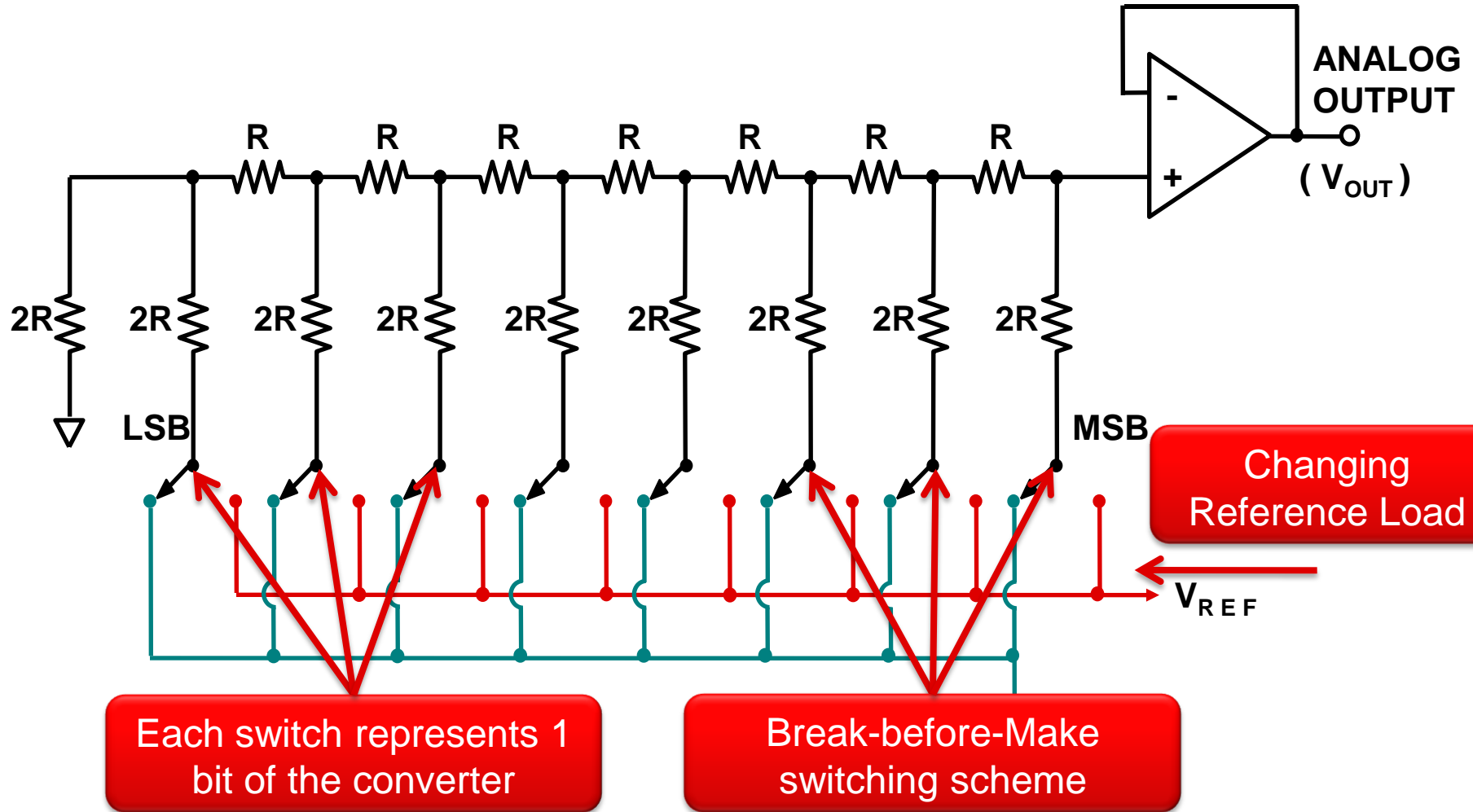

R-2R DAC

Advantages

- Strong linearity
- Low noise

Disadvantages

- Code dependent reference loading
- High glitch impulse
- Longer settling
- Output buffer requirements

Applications

Precision Instrumentation

Industrial Control & Automation


Test Equipment

•Example parts: DAC7644, DAC7654, DAC8881, DAC9881

MDAC / R-2R Multiplying DAC

R-2R Multiplying DAC Architecture

 Reference voltage polarity inverted at output



MDAC

Advantages

- Strong linearity
- Low noise
- Fastest switching
- Lower glitch vs R-2R
- Constant reference loading

Disadvantages

- Transimpedance output stage
- Output is inverted referred to the reference

Applications

Industrial Control PLCs

Waveform Generation


AC Applications

•Example parts: DAC8801, DAC8811, DAC8814, DAC8822, DAC8734

Presentation Agenda

- TI DAC Landscape & Precision DACs
- The Ideal DAC
- DAC Architectures
 - String
 - R2R MDAC
 - R2R BDAC
- Static DAC Specifications
 - TUE & Calibration
- Dynamic Specifications
- Closing the Loop

Offset & Zero Code Error

 

Offset Error(mV):


- Difference between **measured** and **ideal** output voltage in the **linear** region of the transfer function
- Indicates how much the entire transfer function is **shifted** from the ideal transfer function

Zero Code Error (mV):

- Output when loading all zeros into the DAC register
- Error is created from the internal op amp headroom from the negative rail.

Offset error	Extrapolated from two-point line ⁽¹⁾ , unloaded	±1	±4	mV
Zero-code error	DAC register loaded with all '0's	1	4	mV

Gain Error

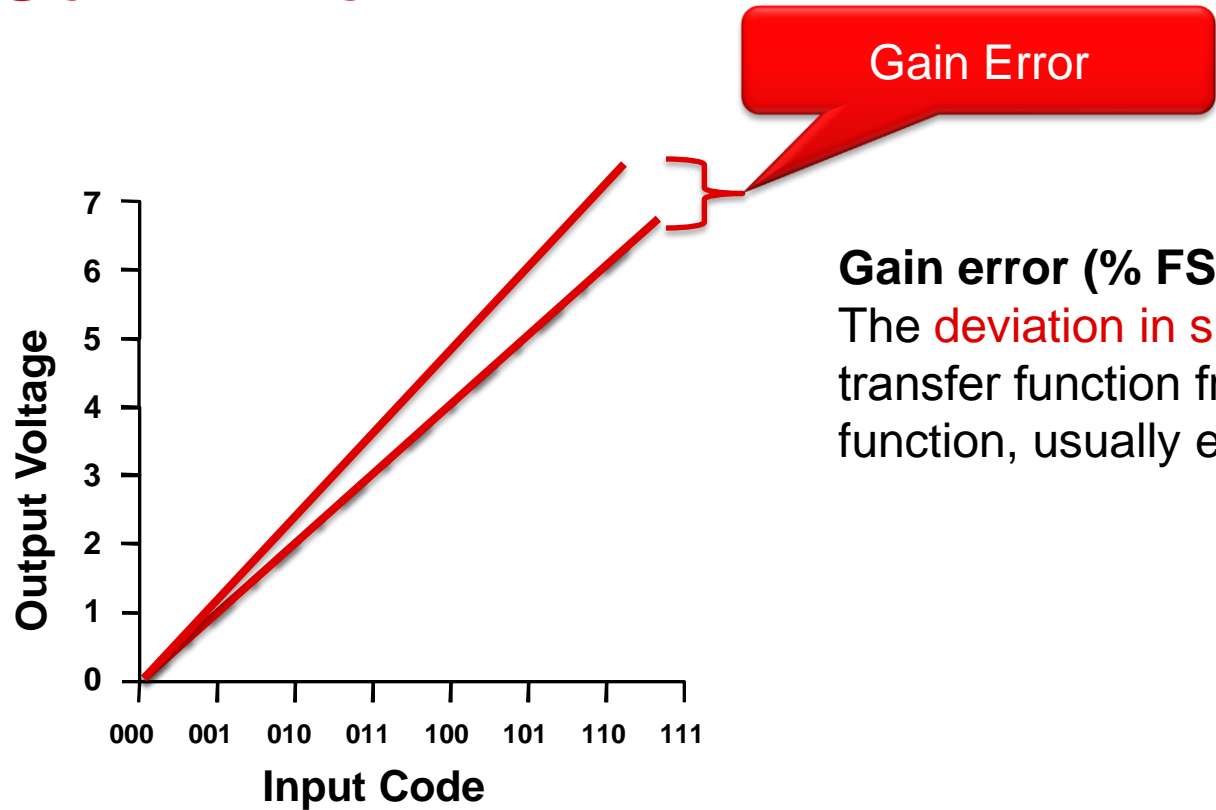


Gain error (% FSR):

The **deviation in slope** of the DAC's **measured** transfer function from its **ideal** transfer function, usually expressed in %FSR

Gain error	Extrapolated from two-point line ⁽¹⁾ , unloaded	±0.01	±0.15	% of FSR
------------	--	-------	-------	----------

Differential Non Linearity (DNL)

 

- Ideally LSB width stays constant for every sequential code transition - **DNL = 0**


- Actual DAC sequential code transitions are not all equal to 1 LSB - **DNL = +/- 1, 2, etc**

- DNL expresses the difference between measured LSB size and ideal LSB size for sequential DAC codes

$$DNL = \frac{V_{n+1} - V_n}{V_{lsb}} - 1$$

Resolution		16		Bits
Relative accuracy	Measured by the line passing through codes 485 and 64714	±4	±12	LSB
Differential nonlinearity	16-bit monotonic	±0.2	±1	LSB

Integral Non Linearity (INL)

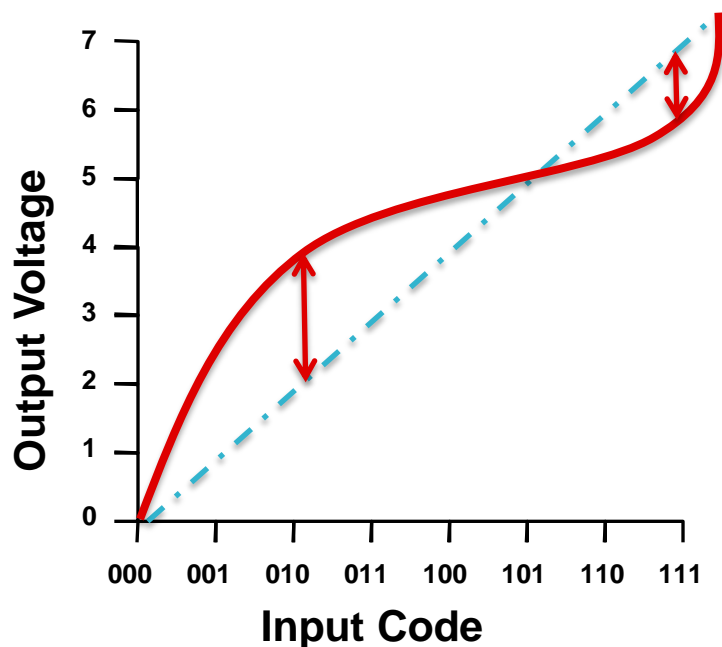

INL is the **maximum** deviation between the ideal output of a DAC and the actual output level (corrected for offset and gain)

INL is often referred to as “**Relative Accuracy**”


Low max INL (≤ 1 LSB) is important in high accuracy applications

$$INL \cong \frac{V_n - V_{zero-scale}}{V_{lsb}} - n$$

Resolution		16		Bits
Relative accuracy	Measured by the line passing through codes 485 and 64714	± 4	± 12	LSB
Differential nonlinearity	16-bit monotonic	± 0.2	± 1	LSB

INL & DNL Graphs

 DAC7311 12-BIT LINEARITY ERROR AND DIFFERENTIAL LINEARITY ERROR vs CODE (-40°C)



Comparing Specifications

	LSB	Volts	% FSR	PPM
LSB	***	$\frac{LSB}{2^N} \times V_{REF}$	$\frac{LSB}{2^N} \times 100$	$\frac{LSB}{2^N} \times 10^6$
Volts	$\frac{V \times 2^N}{V_{REF}}$	***	$\frac{V}{V_{REF}} \times 100$	$\frac{V}{V_{REF}} \times 10^6$
% FSR	$\frac{\%}{100} \times 2^N$	$\% \times V_{REF}$	***	$\% \times 10^4$
PPM	$\frac{PPM}{10^6} \times 2^N$	$\frac{PPM}{10^6} \times V_{REF}$	$\frac{PPM}{10^4}$	***

Total Unadjusted Error

- Static specifications likely carry the largest impact on total unadjusted error in any system
 - INL/DNL
 - Offset Error
 - Gain Error
- Reference accuracy in any data conversion is key
- A root-sum-squared approach is appropriate to summarize the TUE

$$TUE = \sqrt{inlError^2 + gainError^2 + offsetError^2}$$

Total Unadjusted Error

$$TUE = \sqrt{inlError^2 + gainError^2 + offsetError^2}$$

- DAC8562 – 16 bit, 0-5V output
 - INL Error: +/- 12 LSB 12 LSBs
 - Offset Error: +/- 4mV 52 LSBs
 - Gain Error: +/- 0.15% FSR 98 LSBs
- Probable Maximum TUE = +/-111 LSBs, +/-8.5mV, or 0.17% FSR
- Typical TUE = +/- 23 LSBs, 1.78 mV, or 0.0356% FSR
- Absolute Maximum TUE = 150 LSBs

Calibration & Total Unadjusted Error

$$TUE = \sqrt{inlError^2 + gainError^2 + offsetError^2}$$

- INL errors are unavoidable
- Digital calibration can remove offset & gain error
- First, calibrate offset error by taking a two point measurement to determine system offset error

$$AdjustedCode = Code + OffsetCalCode$$

- Next, determine the required scalar to set the offset corrected DAC output full scale output to the ideal full scale output voltage


$$AdjustedCode = GainCalRatio * Code + OffsetCalCode$$

- TUE is greatly improved by removal of offset & gain error
 - Max calibrated TUE: 12 LSBs, 0.91mV, or 0.01% FSR
 - Typ calibrated TUE: 4 LSBs, 0.305mV, or 0.006% FSR


Presentation Agenda

- TI DAC Landscape & Precision DACs
- The Ideal DAC
- DAC Architectures
 - String
 - R2R MDAC
 - R2R BDAC
- Static DAC Specifications
 - TUE & Calibration
- **Dynamic Specifications**
- Closing the Loop

Settling Time

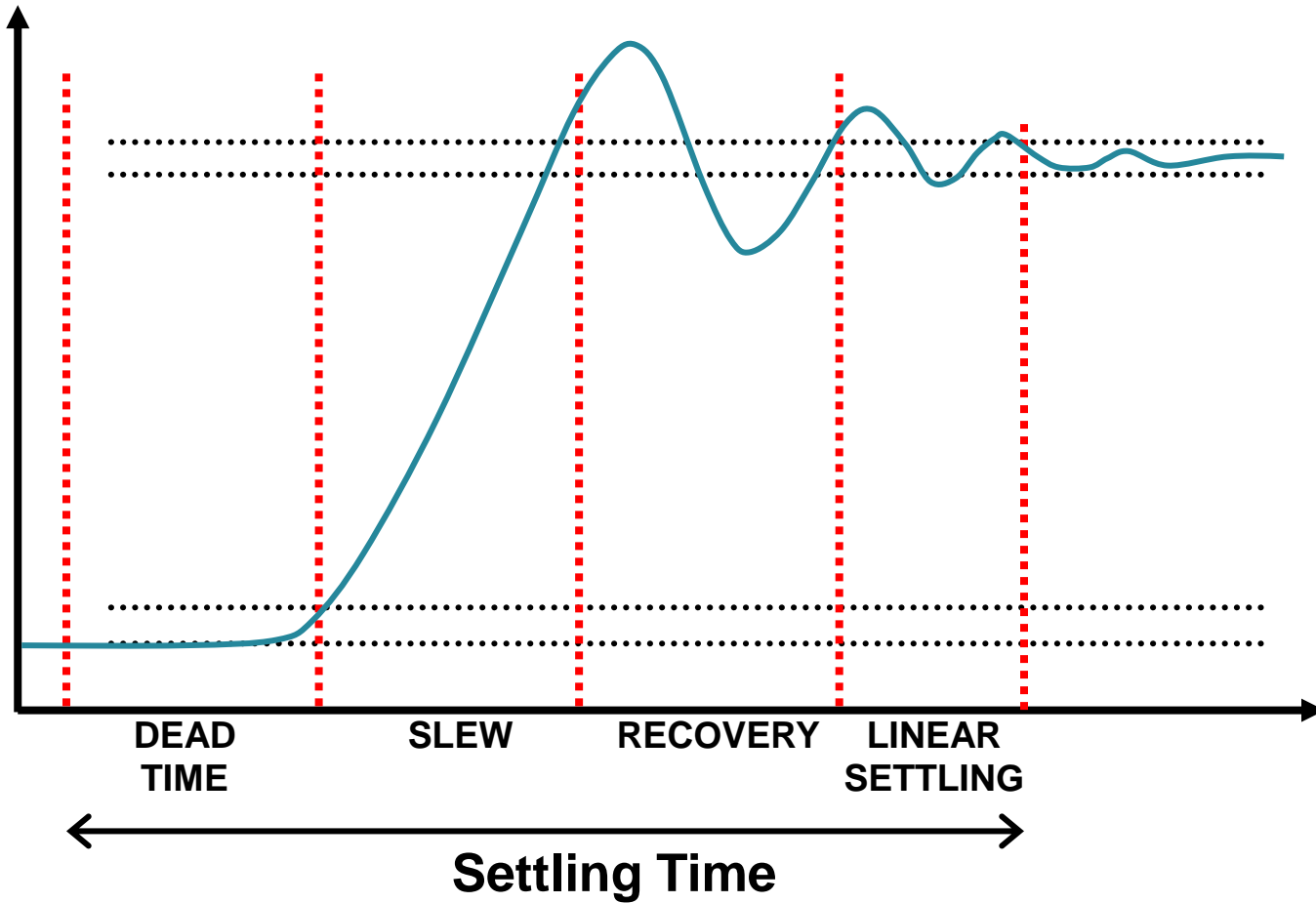

Settling Time in Real Devices

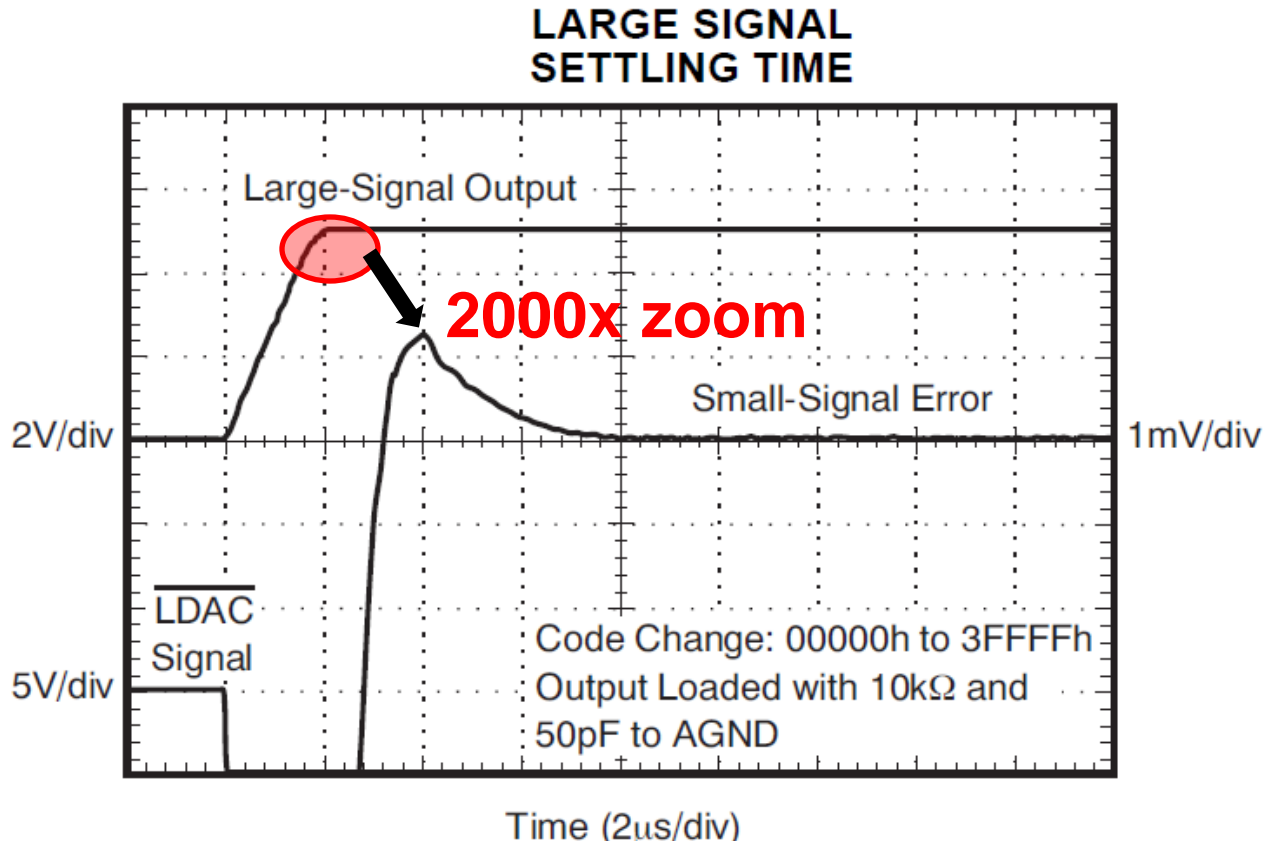

DYNAMIC PERFORMANCE⁽²⁾


Settling time	To $\pm 0.003\%$ FS, $R_L = 10k\Omega$, $C_L = 50pF$, code 04000h to 3C000h	5	μ s
---------------	---	---	---------

DAC9881

Settling Time in Real Devices


150mV Output Voltage Step

Code 0x02000 to 0x04000

 


Less than 1mV
amplitude

Glitch

 

$$\text{Glitch-impulse} = G_2 - G_1$$

a.) Two Lobe Glitch

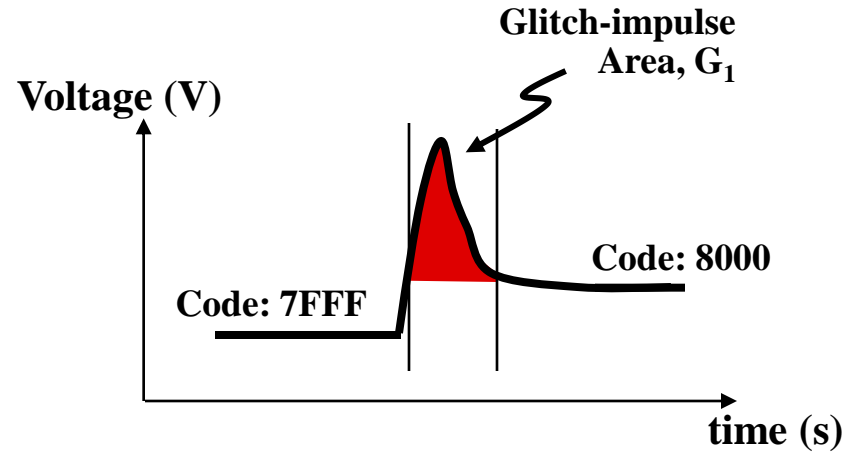


$$\text{Glitch-impulse} = G_1$$

b.) Single Lobe Glitch


Glitch Sources

- Two main sources
 - Switches switching!
 - When the switches transition the current has to take a new path
 - Switch synchronization
 - The switches will not be perfectly synchronized
- Major Carry Transition
 - Code changes that cause a majority of switches to transition in an R-2R or MDAC
 - This is the worst case possible
 - 0111 → 1000
 - 0100 → 1011


Major Carry Transition

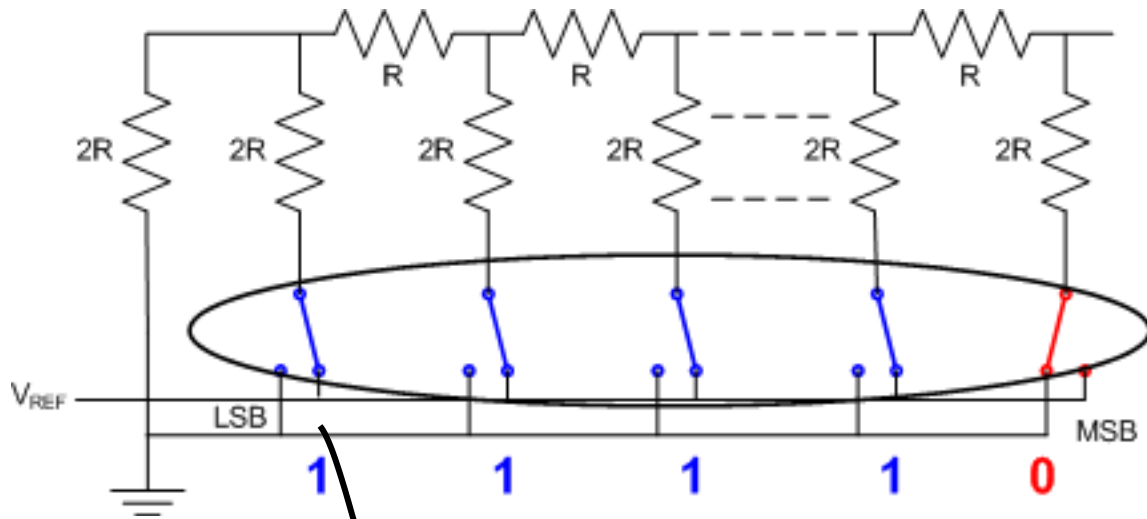


**Code 0b01111
to
Code 0b10000**

 

Major Carry Transition

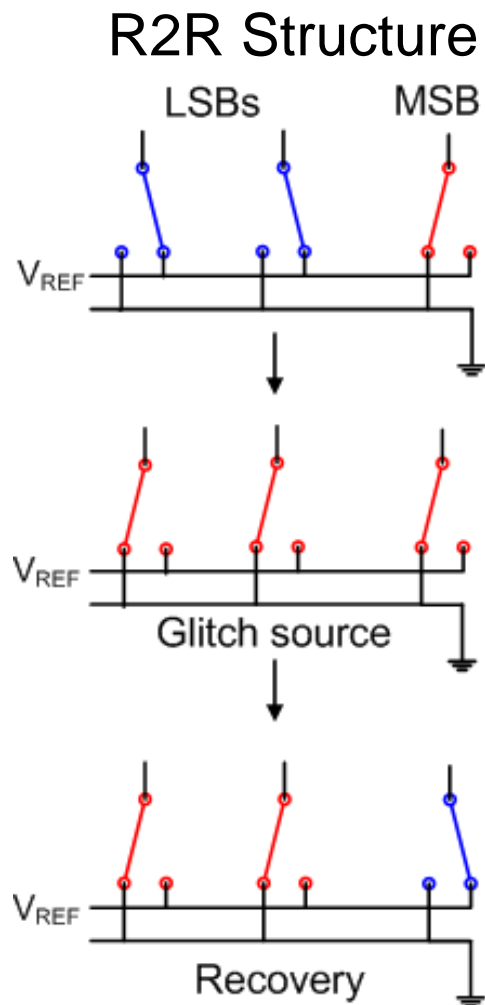


Output Voltage Glitch

 


DAC Major Carry Transition

Code to Code Glitch

 0x1FFFF to 0x20000
(major carry transition)



0x20000 to 0x20001


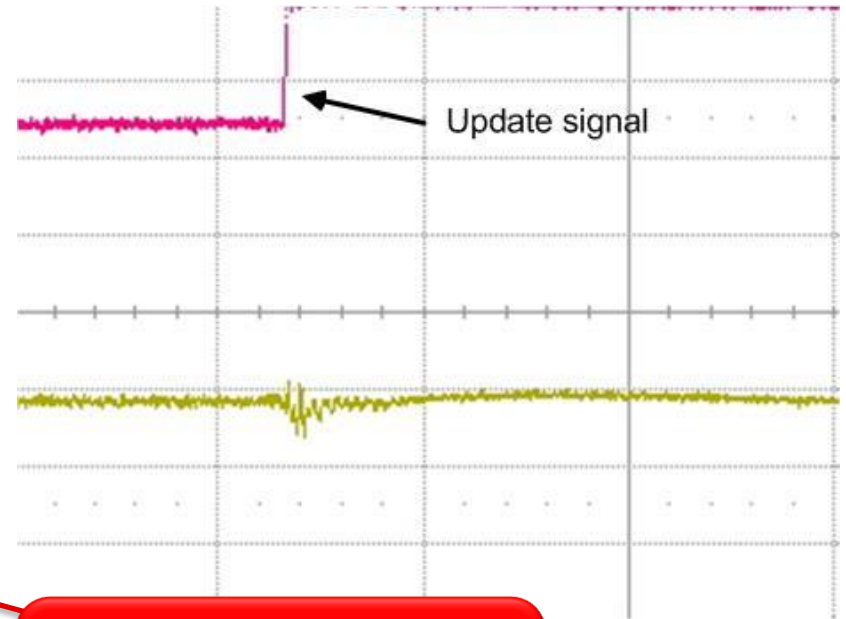


150mV amplitude
glitch

Glitch vs. DAC structure

- R2R DAC – DAC9881
 - Simultaneous switching
 - Synchronization
 - Large glitch amplitude
 - Settling of Internal Amplifier
- String DAC – DAC8562
 - Simple switch network
 - Tap into resistor string
 - Single Lobe glitch
 - Small glitch amplitude

Graphs: 500ns/div 50mV/div

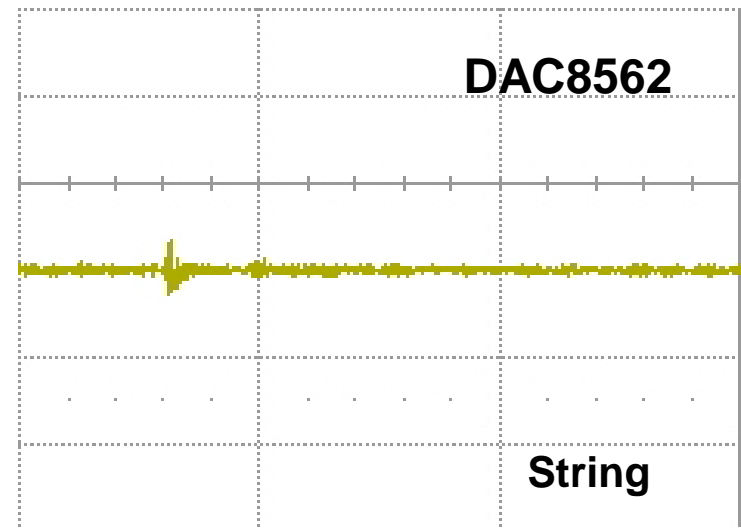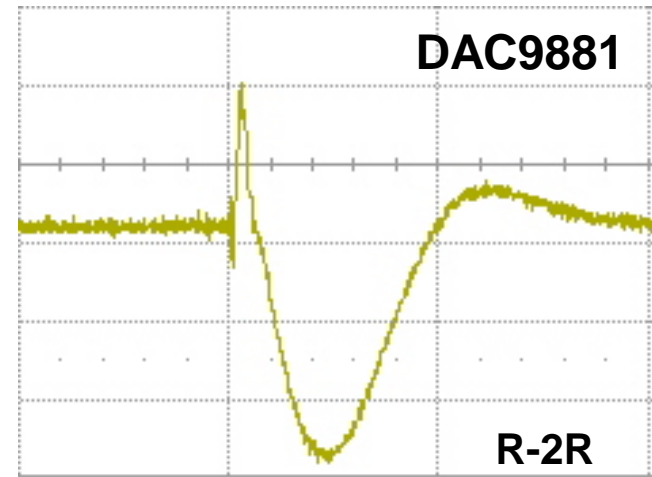


Code 0x7FFF to 0x8000


Glitch Reduction - RC Filter

- Attenuate glitch at cost of increased settling time
- Easy to implement
 - Cost effective
 - Uses minimal board space
- Voltage loss across resistor in network
 - Voltage dependent on output load
- RC value determined by period of the glitch
 - Period = $2\pi RC$
 - Select 3dB point a decade prior to glitch

$$F_c = \frac{1}{2\pi RC}$$

 

Glitch Reduction - RC Filter cont.

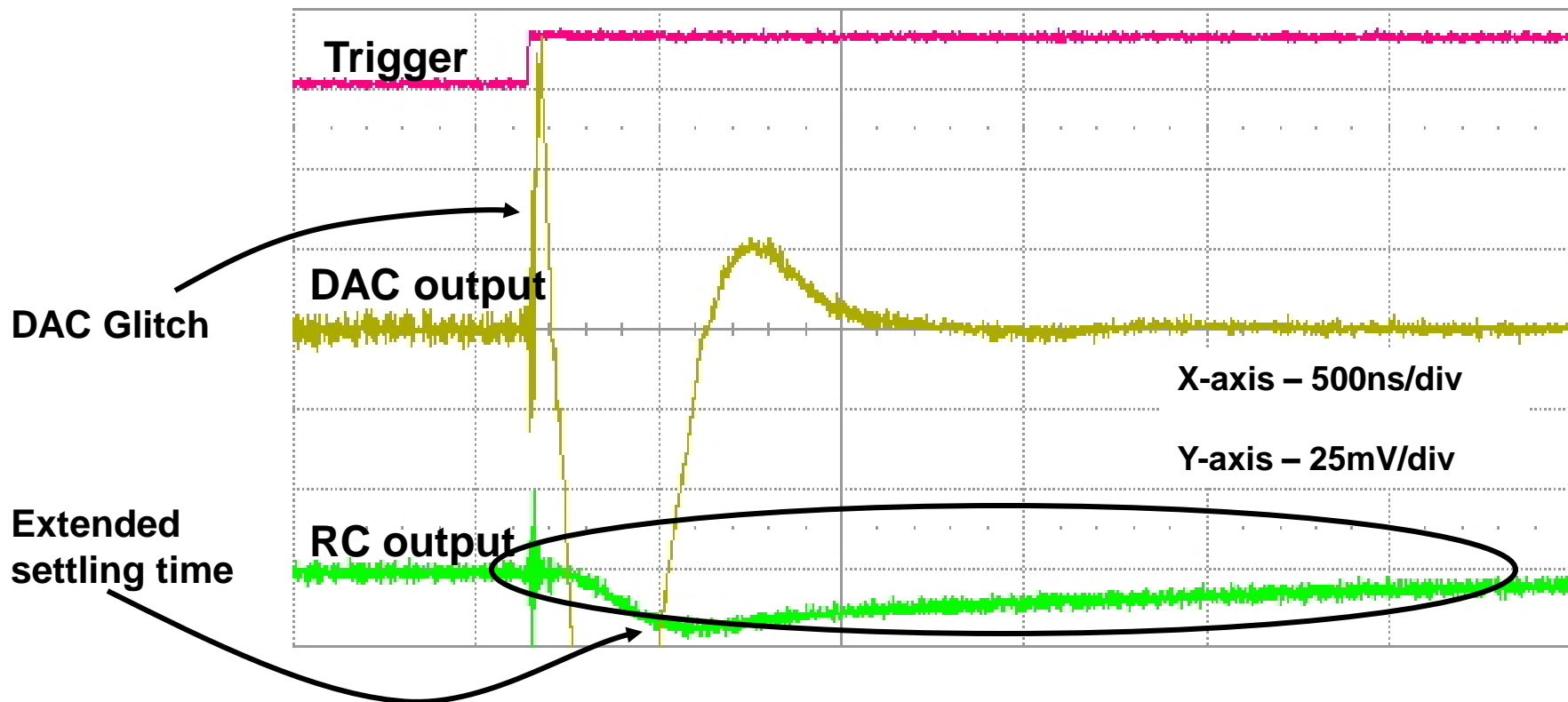


Texas Instruments DAC8881

Conditions: Vref = 5V, AVDD = 5V, Code transition 0x7FFF to 0x8000


R = 20 ohm, C = 100nF

Glitch Reduction – Sample and Hold

 - Eliminate Glitch from R2R ladder
 - No increase to settling time
 - Small transient from S/H switch
- Complex implementation - Strict timing
- Cost, board space, etc.




Glitch Reduction – S/H cap cont.

 

DAC7644 – without S/H amp

Glitch Reduction – S/H cap cont.

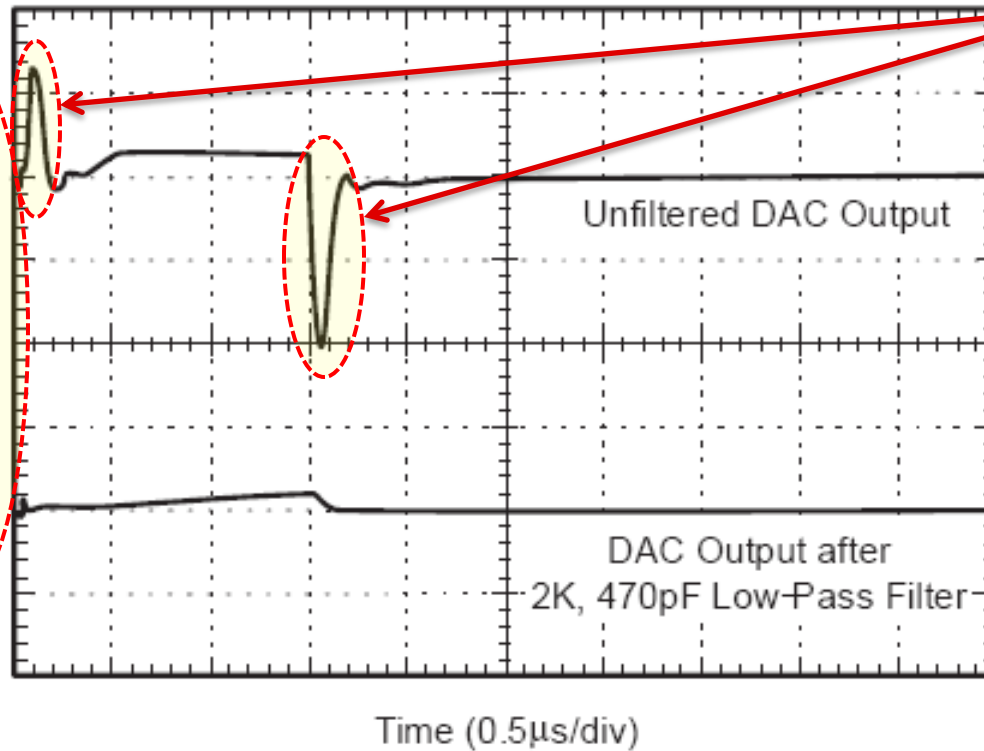MIDSCALE GLITCH PERFORMANCE
CODE 7FFFh to 8000h





Amplitude
5X smaller

Small glitch
due to
external
switch charge
injection

DAC7654 – Includes S/H amp

Glitch Reduction Techniques

  
- RC filter
 - Easy to implement
 - Not a complete removal of the glitch
 - Decrease glitch amplitude
 - Increased settling time
- Switch cap solution
 - Completely remove glitch
 - Strict timing
 - Difficult to implement
 - Slower update rates



DAC Output Noise sources

- Internal resistor string
- Output amplifier
- Reference voltage

Internal Resistor String Noise

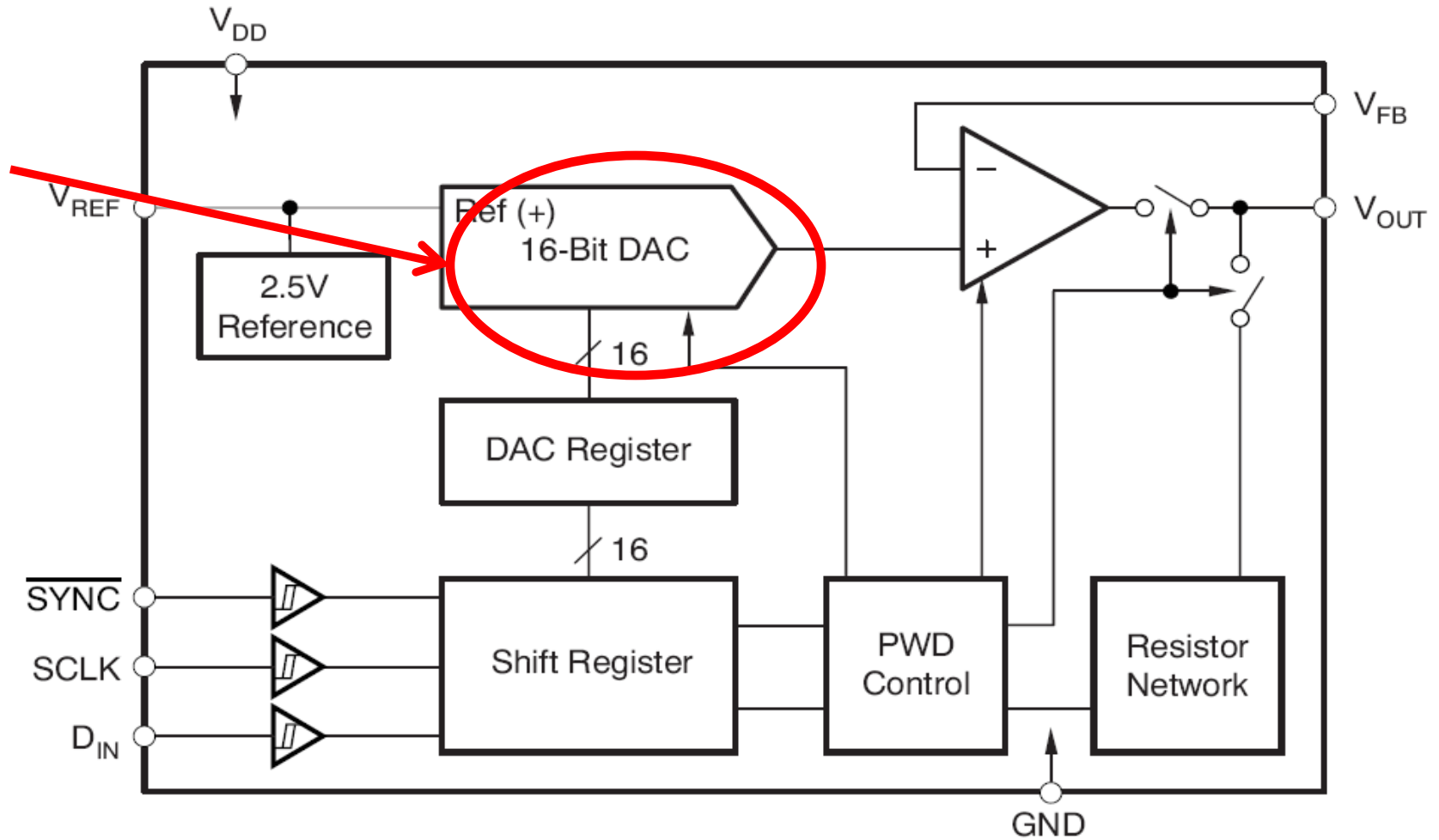


Internal Resistor String Noise

- Thermal Resistor noise

- K = Boltzman constant = $1.3806503 \times 10^{-23}$
- T = Temperature = 300 deg K for room temperature
- R = Equivalent Resistance of Resistor String
- B = Normalized Bandwidth = 1 Hz
 
$$e_n = \sqrt{4 \times K \times T \times R \times B}$$



Resistor Noise

Verification using DAC8801 current output DAC

- Simple R2R resistor string
- No Internal Op amp
- Full scale equivalent resistance = 5K

$$e_n = \sqrt{4 \bullet 1.38e-23 \bullet 300 \bullet 5000 \bullet 1} = 9.1 \frac{nV}{\sqrt{Hz}}$$


Does not include feedback resistor

$$\sqrt{2 \bullet e_n^2} = \sqrt{9.1^2 + 9.1^2} = 12.87 \frac{nV}{\sqrt{Hz}}$$


Use Sum squared to account for feedback resistor

PARAMETER	CONDITIONS	DAC8801			UNITS
		MIN	TYP	MAX	
Total harmonic distortion	$V_{REF} = 5 V_{PP}$, Data = 3FFFh, $f = 1$ kHz		-105		dB
Output spot noise voltage	$f = 1$ kHz, BW = 1 Hz		12		nV/ \sqrt{Hz}

DAC Amplifier Output Noise

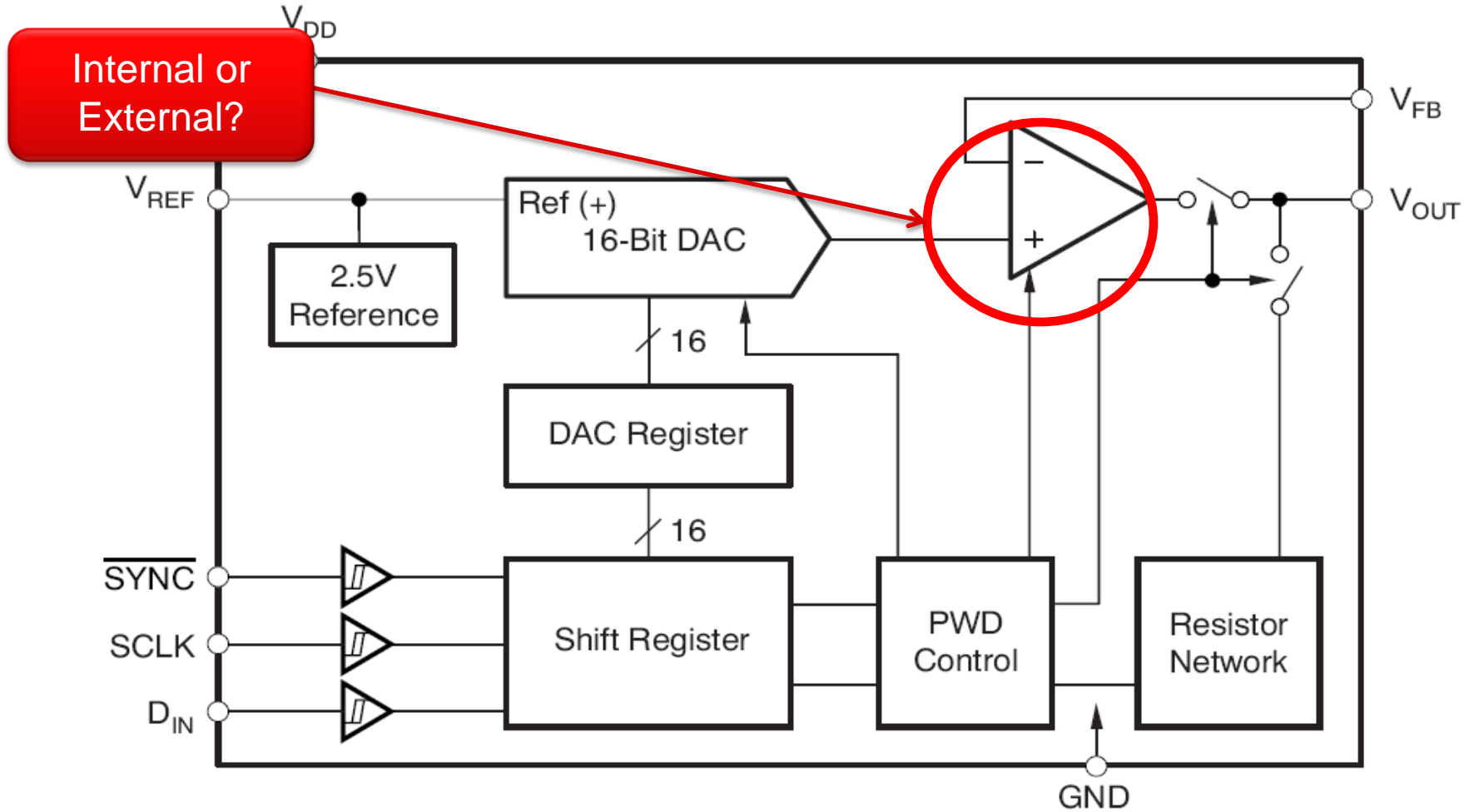

DAC Amplifier Output Noise

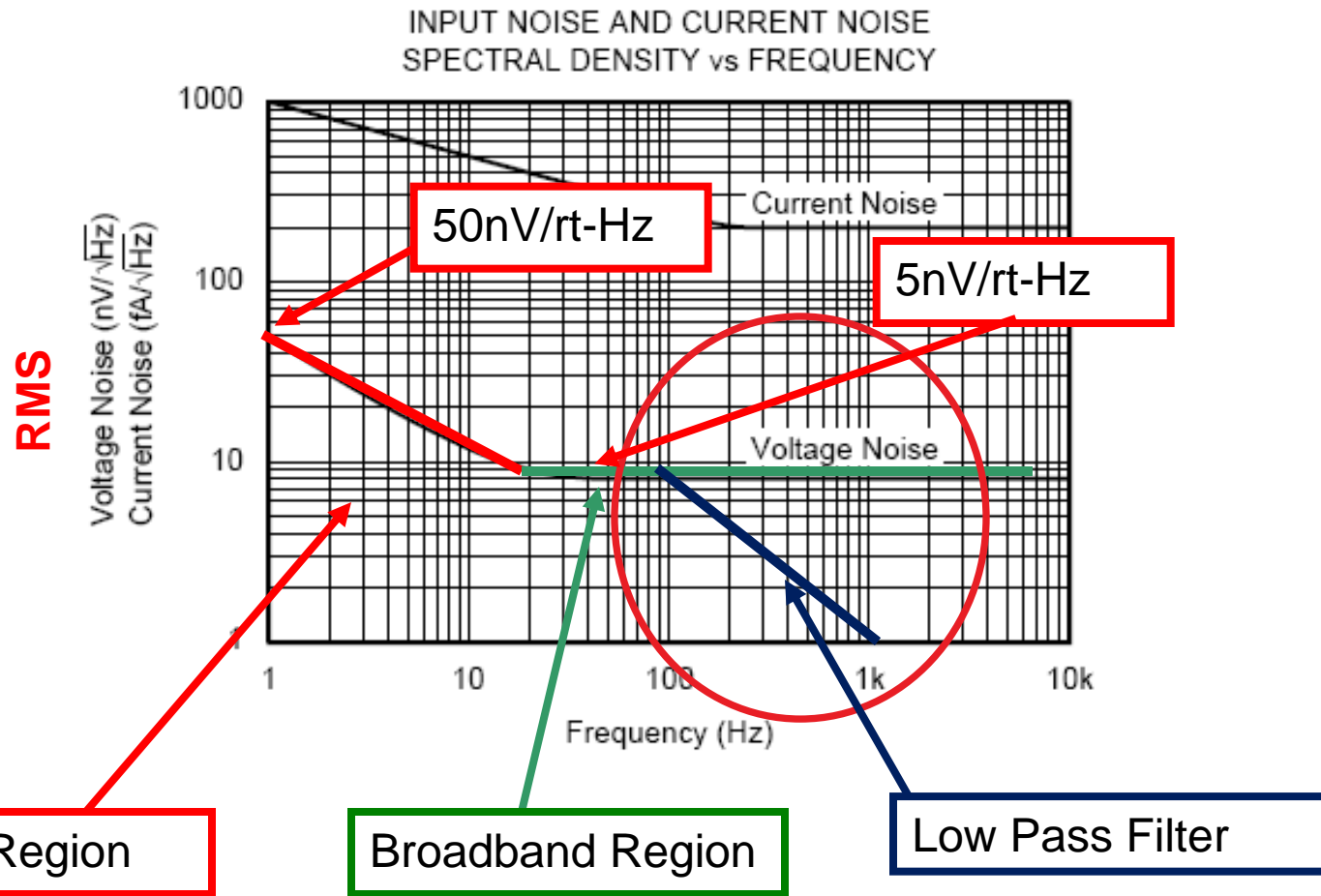


Source: Art Kay, Op Amp Noise 2006

Output Amplifier Noise


- For external output amplifiers, follow Art Kay's noise presentation for complete noise analysis
 - In general, search for amplifiers with low 1/f noise
- For the internal case, a typical DAC datasheet does a lot of this work for you
 - Usually a number provided in the electrical characteristics table
 - Sometimes a figure to illustrate the noise spectrum

AC PERFORMANCE ⁽²⁾			
DAC output noise density	$T_A = 25^\circ\text{C}$, at mid-scale input, $f_{\text{OUT}} = 1 \text{ kHz}$	90	$\text{nV}/\sqrt{\text{Hz}}$
DAC output noise	$T_A = 25^\circ\text{C}$, at mid-scale input, 0.1 Hz to 10 Hz	2.6	μV_{PP}

Voltage Reference Selection

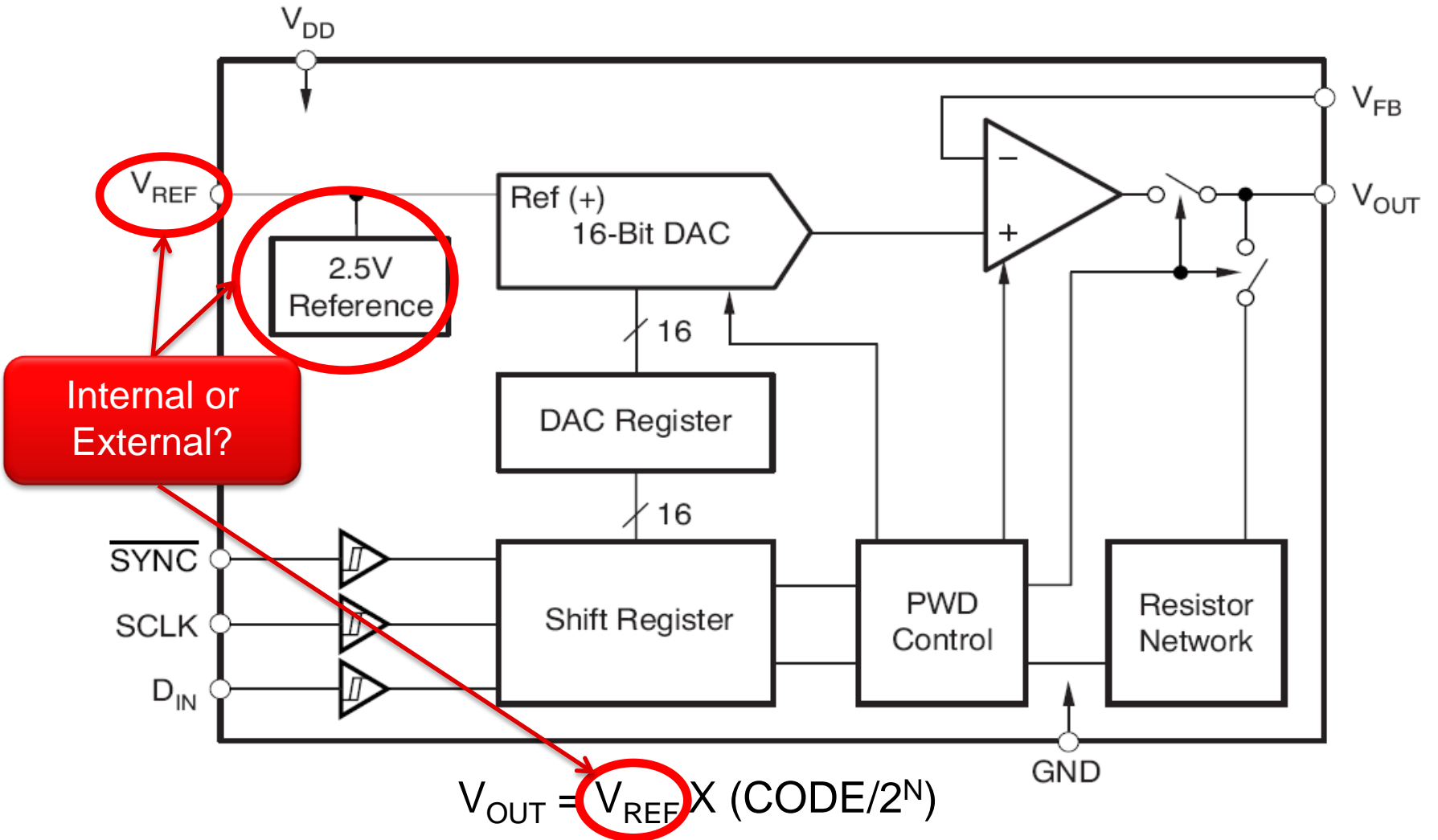

Noise Contribution

 

Source: Miro Oljaca; ESC224 2008


$$V_{OUT} = V_{REF} \times (CODE/2^N)$$

Internal vs. External Voltage References

<u>Device</u>	<u>Initial Accuracy (%)</u>		<u>Tmp. Coef. (ppm/C)</u>		<u>Total Accuracy (%)</u>	
	Max	Typ	Max	Typ	Max	Typ
MSP430F167	+/-4	---	+/-100	---	+/-4.60	
TLV5638	+/-4	---	---	---	---	---
DAC7678	+/-0.2	+/-5	+/-25	+/-0.23	+/-0.35	
DAC8562	+/-0.2	+/-4	+/-10	+/-0.22	+/-0.26	
DAC8564/8	+/-0.1	+/-2	+/-5	+/-0.11	+/-0.13	
REF30xx	+/-0.2	+/-20	+/-50	+/-0.32	+/-0.50	
REF31xx	+/-0.2	+/-10	+/-20	+/-0.26	+/-0.32	
REF32xx	+/-0.2	+/-4.0	+/-7.0	+/-0.22	+/-0.24	
REF33xx	+/-0.15	+/-30	+/-30	+/-0.33	+/-0.33	
REF50xx	+/-0.05	+/-2.5	+/-3.0	+/-0.07	+/-0.09	

Voltage Reference Selection

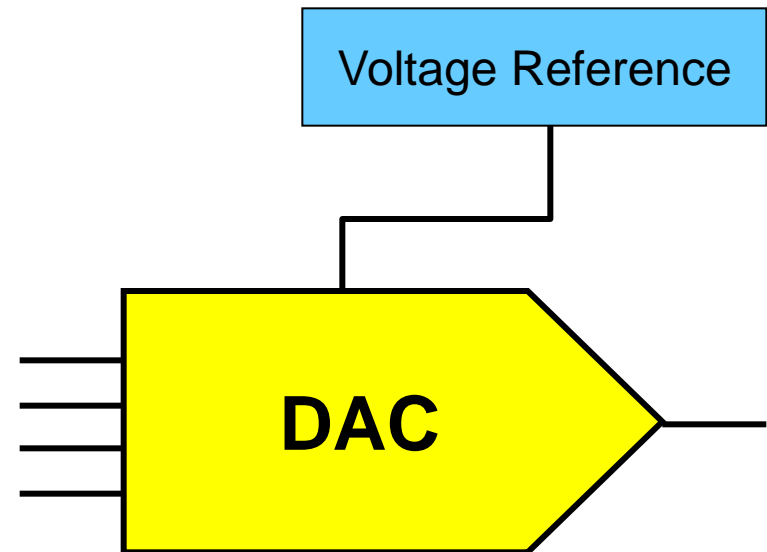- Design issues to consider
 - Noise
 - Initial Accuracy
 - Power Consumption
 - Source and Sink Current Capability
 - Temperature Drift
 - Long Term Stability



Basic Selection Criteria

- Primary Criteria¹
 - Resolution
 - Channels
 - Interface
 - Current/Voltage Output
 - Settling Time
 - DNL, INL, Offset, Gain Errors
 - Output Voltage Range
 - Power
 - Package
- Secondary Criteria²
 - Reset to mid-scale/zero scale
 - Supply Range
 - Operating Temp Range
 - Integrated Reference
(reference drift, accuracy, drive capability)
 - Glitch Energy
 - Integrated Amplifiers/Multiplying DACs


Conclusion

- What does your Application look like?
- Leverage architectural tendencies to narrow the DACs under consideration
- Understand how specifications are measured, what they mean, and how to apply them into application specific circumstances



Precision DAC Applications

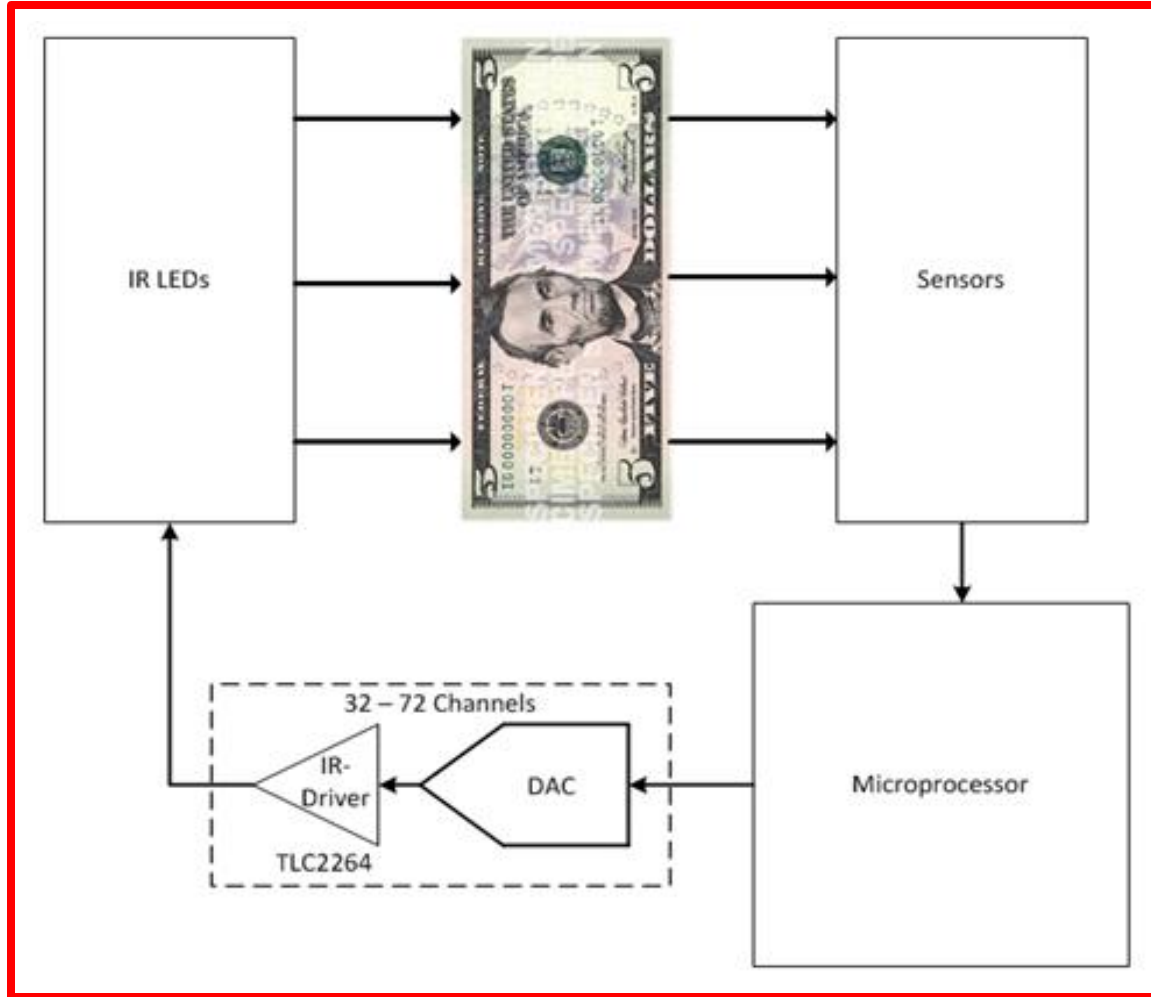Application#1 – ATM, Currency Counters Automated fair collectors




IR LED Driver

- ✓ DAC Key Care about
 - ✓ 8-12-bit
 - ✓ Multichannel
 - ✓ Low cost, I2C

Architecture → String

Application#2 – Digital Walkie-Talkie

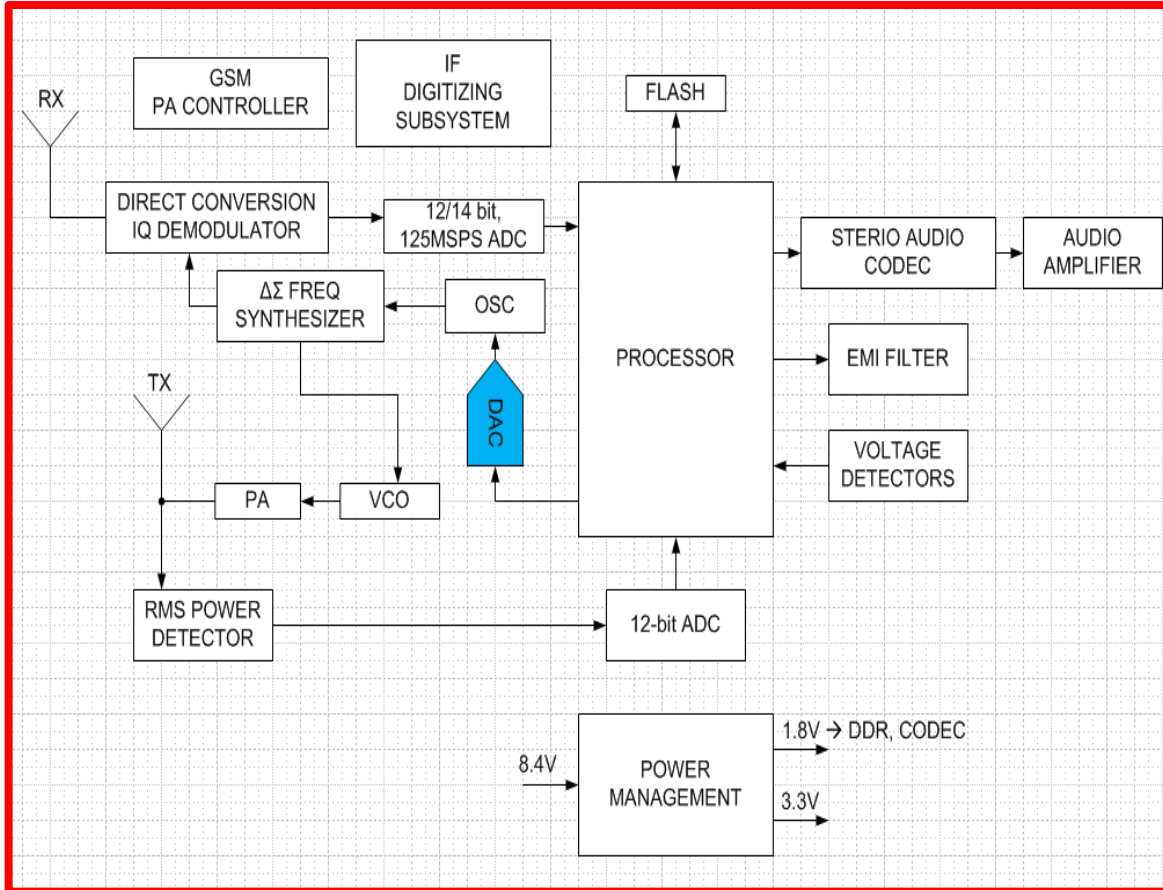

Automatic Power Control

PA Bias Control

TCXO Bias (PLL Ref Clock)

✓ DAC Key Care about


✓ 12-bit accuracy

✓ Multichannel

✓ Low power, area

Architecture → String

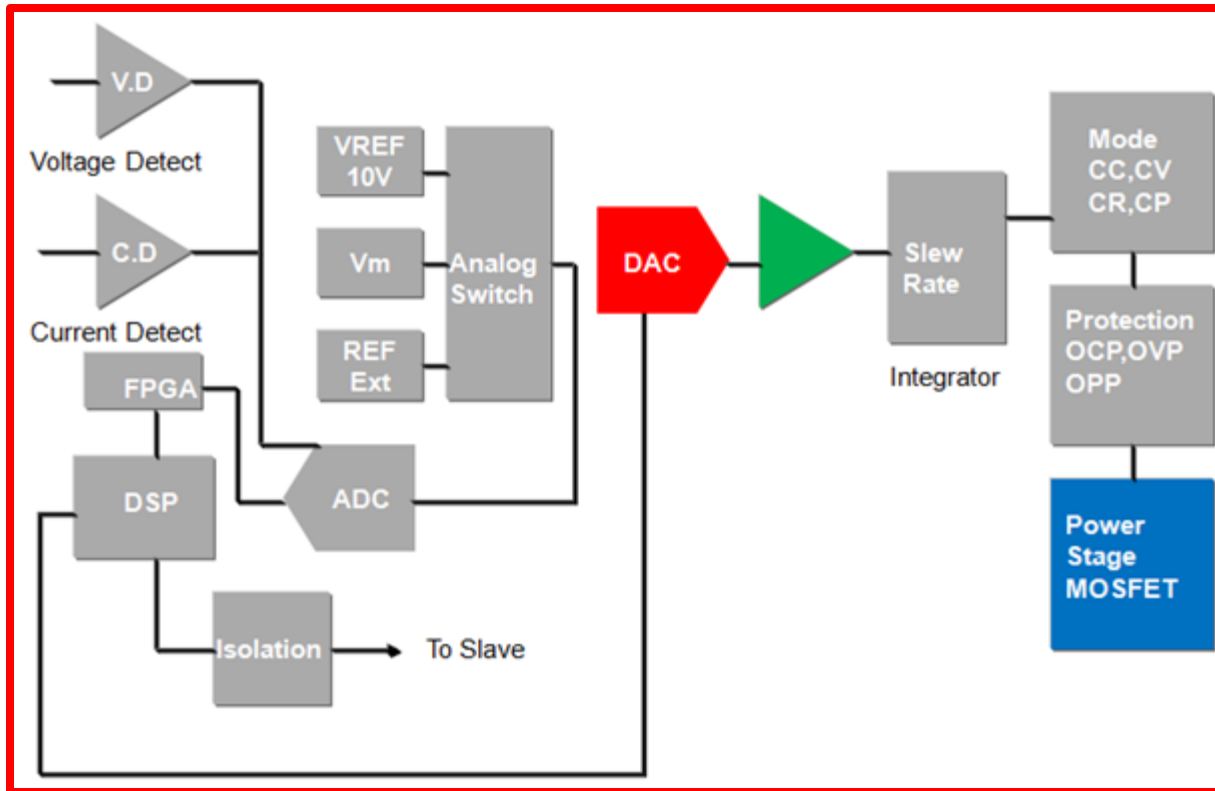Application#3 – Power Supply Testing DC Load




Power MOS gate control

- ✓ DAC Key Care about
 - ✓ 16-bit
 - ✓ Fast settling <1usec
 - ✓ INL<2LSB

Architecture → MDAC

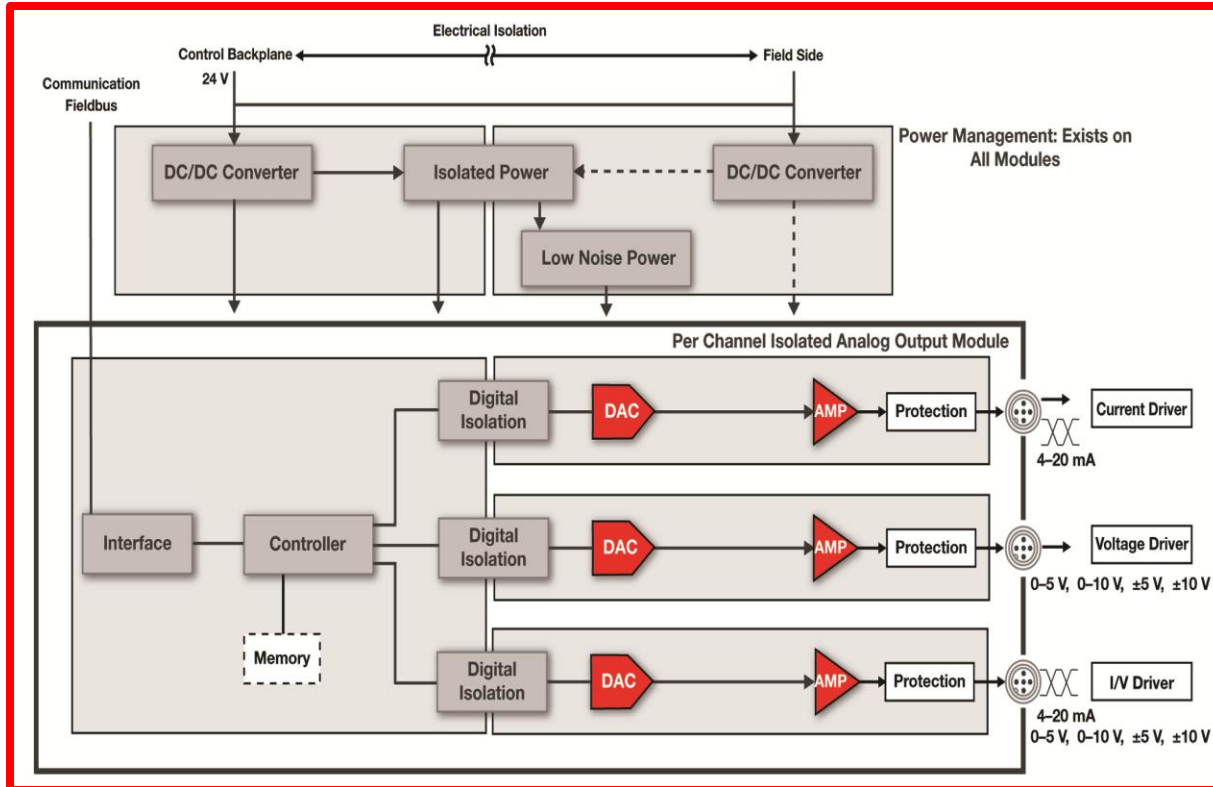Application#4 – High End Analog Output Modules




Create V/I Outputs

- ✓ DAC Key Care about
 - ✓ 16-bit
 - ✓ Single/Dual/Quads
 - ✓ <0.05% Total Error

Architecture → R2R,
High performance string

Application#5 – Pressure Sensors

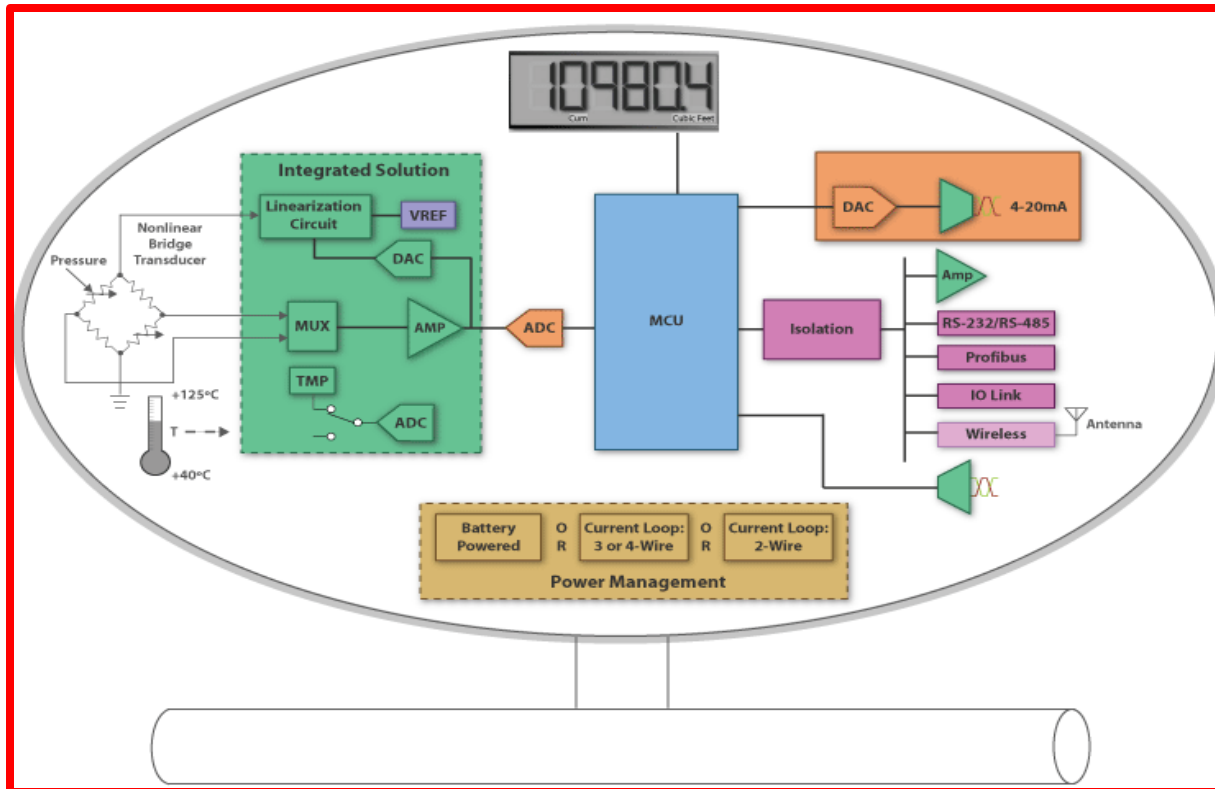


Create 4-20mA current

- ✓ DAC Key Care about
 - ✓ 16-bit
 - ✓ <0.05% Total error
 - ✓ Low Power

Architecture → High performance string


Application#6 – MRI Machines

 

Control Coil gradient

- ✓ DAC Key Care about
 - ✓ ≥ 16 -bit
 - ✓ High Accuracy, speed
 - ✓ ≤ 1 LSB-INL

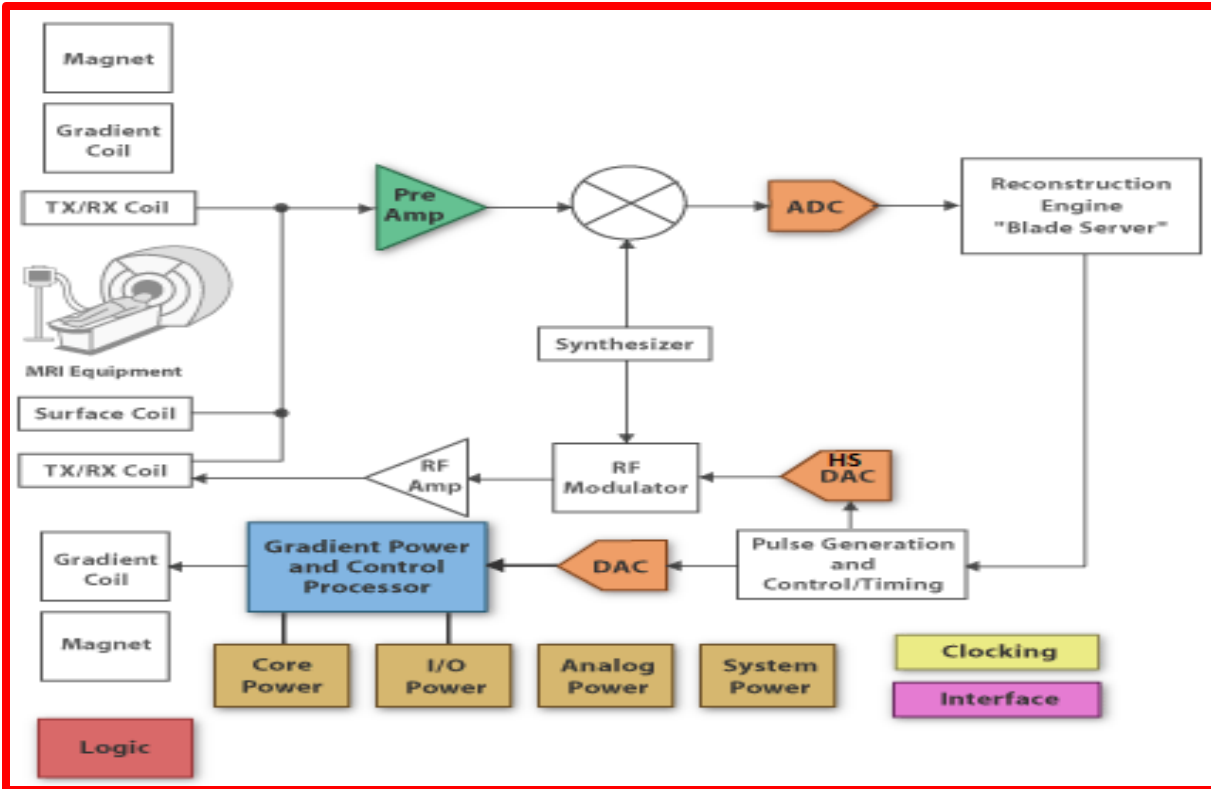Architecture \rightarrow MDACs, Unbuffered R2R




Application#7 – Tunable State Variable Filter



- ω (Frequency) Control
- Q (Quality Factor) Control
- A_v (Gain) Control

- ✓ DAC Key Care about
 - ✓ 8-bit, Multichannel
 - ✓ Tunable resistor
 - ✓ Matching

Architecture → MDACs, Unbuffered R2R

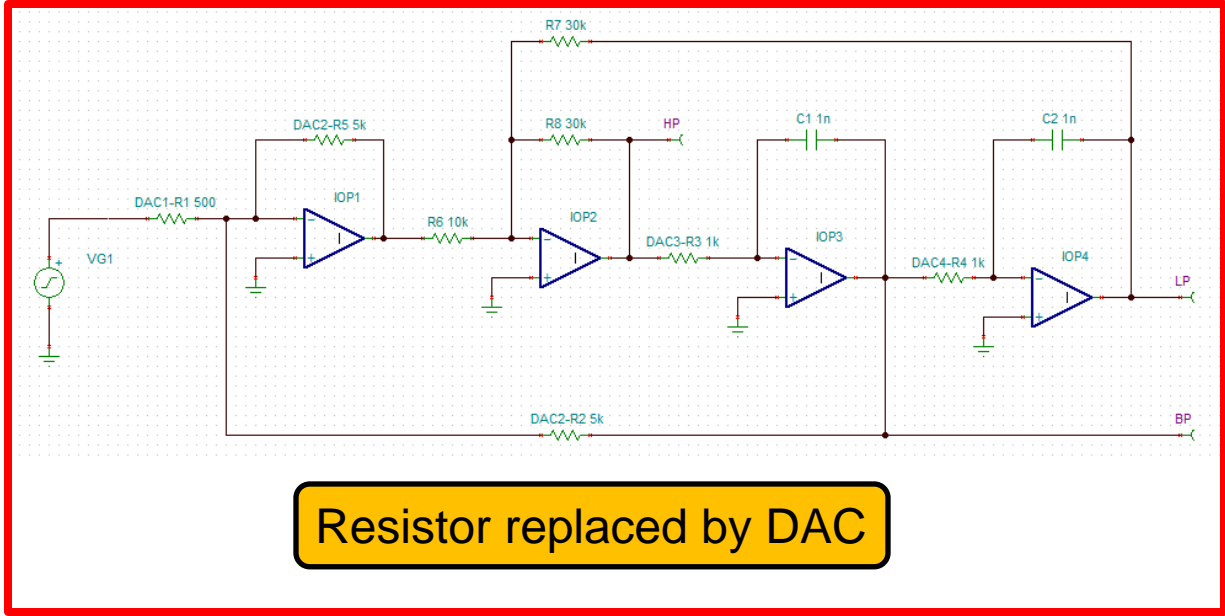

Resistor replaced by DAC

Application#7 – Tunable State Variable Filter

