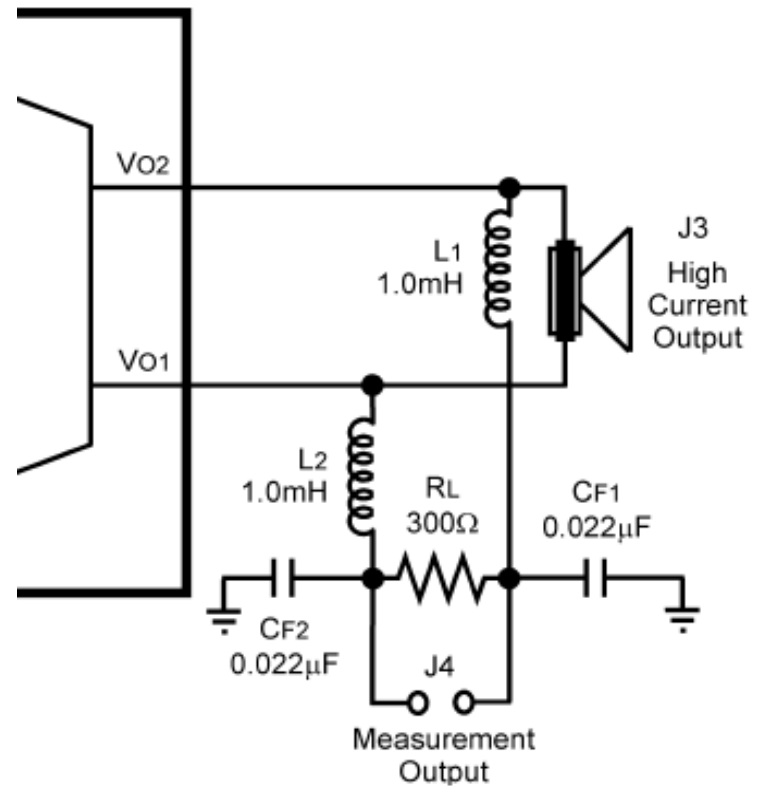


Class D test

# Filterless Class D Measurement Filter

- **A measurement filter is used to extract useful audio data from the switching waveform**



# Filterless Class D Output Power Calculation

- **Goal:**

**To find the easiest way to get the correct output power into the unfiltered load. This involves entering a load value on the AP so that the output power displayed takes into account all other factors.**

# Filterless Class D Output Power Calculation Assumptions

- **LC filter loss is 0.35dB – 0.40dB (as measured and verified)**
- **Resistive component of load has zero inductance**
- **Inductive component of load has zero resistance**

# Filterless Class D Output Power Calculation (Step 1)

- **Actual load impedance at 1kHz**

$$R_L = 15\mu F + 8\Omega + 15\mu H$$

- **Impedance at 1kHz**

$$= (2\pi * 1\text{kHz} * 30\mu H) + 8\Omega$$

$$= 0.1885 + 8\Omega$$

$$= 8.1885\Omega$$

# Filterless Class D Output Power Calculation (Step 2)

- **LC Filter loss in Voltage**  
 **$20 \log X = 0.35\text{dB} - 0.40\text{dB}$**   
 **$= 0.0411 - 0.0471$**   
 **$= 4.11\% - 4.71\%$  loss**
- **Voltage at filter output is 95.29% - 95.89% of actual voltage at unfiltered load**

# Filterless Class D Output Power Calculation (Step 3)

- **Given 1W with AP set to  $8\Omega$  measured at LC filter output's,  $P_{OUT} = (V^2/R_L)$**
- **Voltage at filter output =  $8^{1/2} = 2.828V$**
- **Actual voltage at unfiltered load  
=  $V_{UFL} * (95.29\% - 95.89\%) = 2.828V$   
 $V_{UFL} = 2.97V - 2.95V$**
- **Power in actual load impedance at 1kHz  
=  $(2.95V^2)/8.1885\Omega - (2.97V^2)/8.1885\Omega$   
=  $1.063W - 1.076W$**

# Filterless Class D Output Power Calculation (Step 4)

- **Resistor setting on AP to obtain same output power taking into account LC filter loss and actual load impedance**

$$P_{OUT} = (V^2/R_L)$$

$$R_L = (V^2/P_{OUT})$$

$$\begin{aligned} R_L &= (2.83V^2)/1.063W - (2.83V^2)/1.076W \\ &= 7.538\Omega_{(0.35dB)} - 7.444\Omega_{(0.40dB)} \end{aligned}$$



# Filterless Class D Output Power Calculation (Step 5)

- $R_L = 7.538\Omega_{(0.35\text{dB})} - 7.444\Omega_{(0.40\text{dB})}$
- Set  $R_L = 7.49\Omega_{(\text{AVERAGE})}$

$$P_{\text{OUT}} = V_{\text{OUT}}^2 / R_L$$