
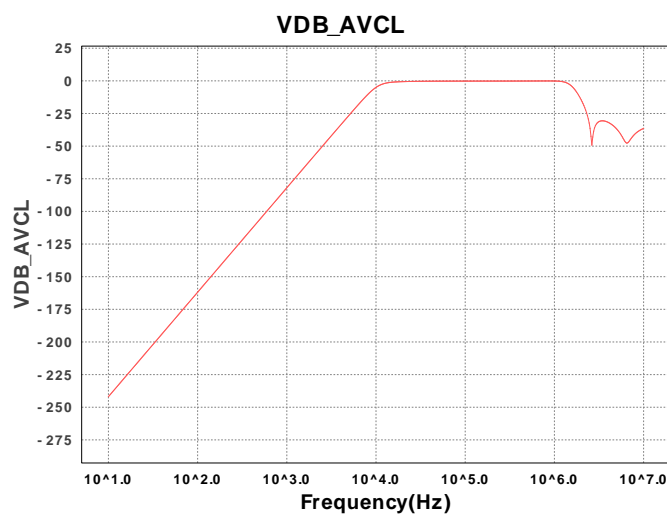


## Electrical BOM

#	Name	Manufacturer	Part Number	Properties	Qty	Price	Footprint
1.	A1_S1	Texas Instruments	LMC6032IM	GbwTyp= 1.4 MHz VccMin= 4.75 V VccMax= 15.5 V	1	\$0.32	SOIC 0 mm <sup>2</sup>
2.	A1_S2	Texas Instruments	LMC6032IM	GbwTyp= 1.4 MHz VccMin= 4.75 V VccMax= 15.5 V	1	\$0.32	SOIC 0 mm <sup>2</sup>
3.	C1_S1	MuRata	GRM155R70J222KA01D Series= X7R	Cap= 2.2 nF VDC= 6.3 V IRMS= 0.0 A	1	\$0.01	0402 3 mm <sup>2</sup>
4.	C1_S2	MuRata	GRM188R71E682KA01D Series= X7R	Cap= 6.8 nF ESR= 400.0 mOhm VDC= 25.0 V IRMS= 0.0 A	1	\$0.01	0603 5 mm <sup>2</sup>
5.	C2_S1	Samsung Electro-Mechanics	CL10C681JA8NNNC Series= C0G/NP0	Cap= 680.0 pF VDC= 25.0 V IRMS= 0.0 A	1	\$0.01	0603 5 mm <sup>2</sup>
6.	C2_S2	MuRata	GRM188R71E152KA01D Series= X7R	Cap= 1.5 nF ESR= 1.8 Ohm VDC= 25.0 V IRMS= 0.0 A	1	\$0.01	0603 5 mm <sup>2</sup>
7.	R1_S1	Vishay-Dale	CRCW040215K0JNED Series= CRCW..e3	Res= 15.0 kOhm Power= 63.0 mW Tolerance= 5.0%	1	\$0.01	0402 3 mm <sup>2</sup>
8.	R1_S2	Vishay-Dale	CRCW040215K0JNED Series= CRCW..e3	Res= 15.0 kOhm Power= 63.0 mW Tolerance= 5.0%	1	\$0.01	0402 3 mm <sup>2</sup>
9.	R2_S1	Vishay-Dale	CRCW040210K0JNED Series= CRCW..e3	Res= 10.0 kOhm Power= 63.0 mW Tolerance= 5.0%	1	\$0.01	0402 3 mm <sup>2</sup>
10.	R2_S2	Vishay-Dale	CRCW04021K50JNED Series= CRCW..e3	Res= 1.5 kOhm Power= 63.0 mW Tolerance= 5.0%	1	\$0.01	0402 3 mm <sup>2</sup>

## Simulation Parameters

#	Name	Parameter Name	Description	Values
1.	Vsignal	AC DC	AC Voltage Source Amplitude AC Voltage Source DC Offset	1 V 0.0 V
2.	Vcc	V	Vcc Supply Rail Value	5.0 V
3.	Vee	V	Vee Supply Rail Value	-5.0 V

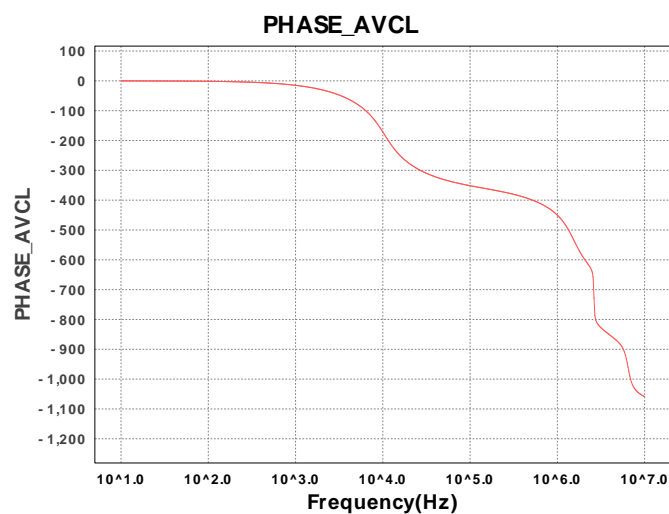

## Design Inputs


#	Name	Value	Description
1.	FilterType	Highpass	
2.	FilterResponse	Butterworth	
3.	FilterOrder	4.0	
4.	FilterTopology	Sallen_Key	
5.	NumberOfStages	2.0	
6.	PassbandFrequency	10.0 kHz	
7.	StopbandAttenuation	-45.0 dB	
8.	StopbandFrequency	2.0 kHz	
9.	Gain	1.0 V/V	
10.	DualSupply	+/-5.0 V	Power supply(s) to active chips
11.	ResistorTolerance	E6	Resistor series - 20% Passive resistor tolerance
12.	CapacitorTolerance	E6	Capacitor series - 20% Passive capacitance tolerance
13.	SeedCapacitance	1.0 nF	Seed Capacitance to start design of filter

## Design Assistance

1. **LMC6032IM** Product Folder : <http://www.ti.com/product/LMC6032> : contains the data sheet and other resources.
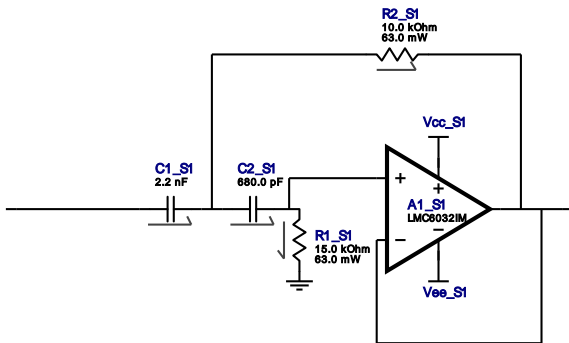
## Filter Stage :1

Cutoff Frequency 10.0 kHz  
 Min GBW Req'd 540.0 kHz  
 Stage Gain 1.0 V/V  
 Stage Q 540.0 m  
 Stage Topology Sallen\_Key




## Electrical BOM

#	Name	Manufacturer	Part Number	Properties	Qty	Price	Footprint
1.	A1_S1	Texas Instruments	LMC6032IM	GbwTyp= 1.4 MHz VccMin= 4.75 V VccMax= 15.5 V	1	\$0.32	SOIC 0 mm <sup>2</sup>
2.	C1_S1	MuRata	GRM155R70J222KA01D Series= X7R	Cap= 2.2 nF VDC= 6.3 V IRMS= 0.0 A	1	\$0.01	0402 3 mm <sup>2</sup>
3.	C2_S1	Samsung Electro-Mechanics	CL10C681JA8NNNC Series= C0G/NP0	Cap= 680.0 pF VDC= 25.0 V IRMS= 0.0 A	1	\$0.01	0603 5 mm <sup>2</sup>
4.	R1_S1	Vishay-Dale	CRCW040215K0JNED Series= CRCW..e3	Res= 15.0 kOhm Power= 63.0 mW Tolerance= 5.0%	1	\$0.01	0402 3 mm <sup>2</sup>
5.	R2_S1	Vishay-Dale	CRCW040210K0JNED Series= CRCW..e3	Res= 10.0 kOhm Power= 63.0 mW Tolerance= 5.0%	1	\$0.01	0402 3 mm <sup>2</sup>

## Filter Stage :2

Cutoff Frequency	10.0 kHz
Min GBW Req'd	1.31 MHz
Stage Gain	1.0 V/V
Stage Q	1.31
Stage Topology	Sallen_Key

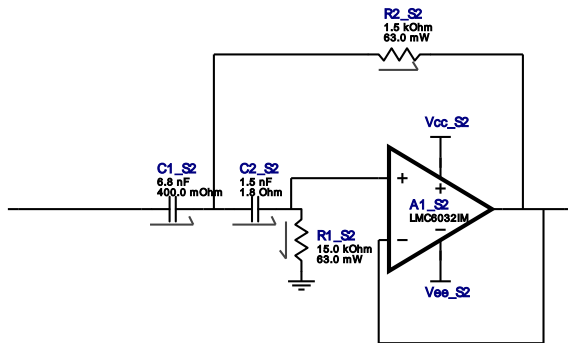

## Electrical BOM

#	Name	Manufacturer	Part Number	Properties	Qty	Price	Footprint
1.	A1_S2	Texas Instruments	LMC6032IM	GbwTyp= 1.4 MHz VccMin= 4.75 V VccMax= 15.5 V	1	\$0.32	SOIC 0 mm <sup>2</sup>
2.	C1_S2	MuRata	GRM188R71E682KA01D Series= X7R	Cap= 6.8 nF ESR= 400.0 mOhm VDC= 25.0 V IRMS= 0.0 A	1	\$0.01	0603 5 mm <sup>2</sup>
3.	C2_S2	MuRata	GRM188R71E152KA01D Series= X7R	Cap= 1.5 nF ESR= 1.8 Ohm VDC= 25.0 V IRMS= 0.0 A	1	\$0.01	0603 5 mm <sup>2</sup>
4.	R1_S2	Vishay-Dale	CRCW040215K0JNED Series= CRCW..e3	Res= 15.0 kOhm Power= 63.0 mW Tolerance= 5.0%	1	\$0.01	0402 3 mm <sup>2</sup>
5.	R2_S2	Vishay-Dale	CRCW04021K50JNED Series= CRCW..e3	Res= 1.5 kOhm Power= 63.0 mW Tolerance= 5.0%	1	\$0.01	0402 3 mm <sup>2</sup>

Texas Instruments' WEBENCH simulation tools attempt to recreate the performance of a substantially equivalent physical implementation of the design. Simulations are created using Texas Instruments' published specifications as well as the published specifications of other device manufacturers. While Texas Instruments does update this information periodically, this information may not be current at the time the simulation is built. Texas Instruments does not warrant the accuracy or completeness of the specifications or any information contained therein. Texas Instruments does not warrant that any designs or recommended parts will meet the specifications you entered, will be suitable for your application or fit for any particular purpose, or will operate as shown in the simulation in a physical implementation. Texas Instruments does not warrant that the designs are production worthy.

**You should completely validate and test your design implementation to confirm the system functionality for your application prior to production.**

Use of Texas Instruments' WEBENCH simulation tools is subject to [Texas Instruments' Site Terms and Conditions of Use](#). Prototype boards based on WEBENCH created designs are provided AS IS without warranty of any kind for evaluation and testing purposes and are subject to the terms of the [Evaluation License Agreement](#).