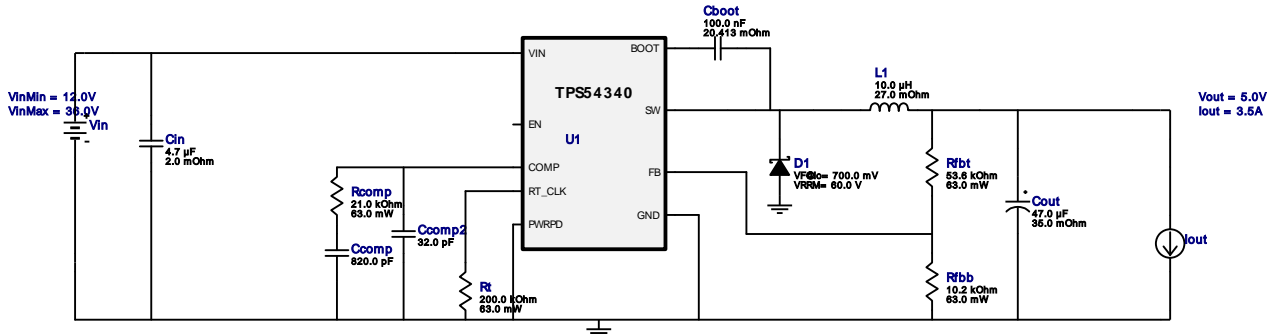


WEBENCH[®] Design Report







 Design : 1931319/2 TPS54340DDAR
 TPS54340DDAR 12.0V-36.0V to 5.00V @ 3.5A

Electrical BOM







#	Name	Manufacturer	Part Number	Properties	Qty	Price	Footprint
1.	Cboot	TDK	C1005X5R1A104K Series= X5R	Cap= 100.0 nF ESR= 20.413 mOhm VDC= 10.0 V IRMS= 0.0 A	1	\$0.01	 0402 3 mm ²
2.	Ccomp	Yageo America	CC0805KRX7R9BB821 Series= X7R	Cap= 820.0 pF VDC= 50.0 V IRMS= 0.0 A	1	\$0.01	 0805 7 mm ²
3.	Ccomp2	AVX	06033A320FAT2A Series= C0G/NP0	Cap= 32.0 pF VDC= 25.0 V IRMS= 0.0 A	1	\$0.10	 0603 5 mm ²
4.	Cin	MuRata	GRM32ER71H475KA88L Series= X7R	Cap= 4.7 uF ESR= 2.0 mOhm VDC= 50.0 V IRMS= 5.35 A	1	\$0.29	 1210 15 mm ²
5.	Cout	Panasonic	10TPE47MAZB Series= 1281	Cap= 47.0 uF ESR= 35.0 mOhm VDC= 10.0 V IRMS= 1.4 A	1	\$0.39	 3528-21 17 mm ²
6.	D1	Diodes Inc.	B560C-13-F	VF@Io= 700.0 mV VRRM= 60.0 V	1	\$0.19	 SMC 83 mm ²
7.	L1	Coilcraft	XAL6060-103MEB	L= 10.0 uH DCR= 27.0 mOhm	1	\$0.82	 XAL6060 72 mm ²
8.	Rcomp	Vishay-Dale	CRCW040221K0FKED Series= CRCW..e3	Res= 21.0 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm ²
9.	Rfbb	Vishay-Dale	CRCW040210K2FKED Series= CRCW..e3	Res= 10.2 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm ²
10.	Rfbt	Vishay-Dale	CRCW040253K6FKED Series= CRCW..e3	Res= 53.6 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm ²
11.	Rt	Vishay-Dale	CRCW0402200KFKED Series= CRCW..e3	Res= 200.0 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm ²







#	Name	Manufacturer	Part Number	Properties	Qty	Price	Footprint
12.	U1	Texas Instruments	TPS54340DDAR	Switcher	1	\$1.68	

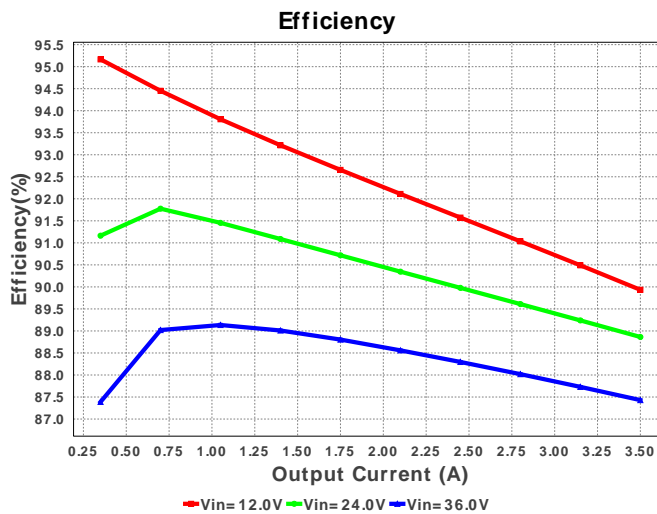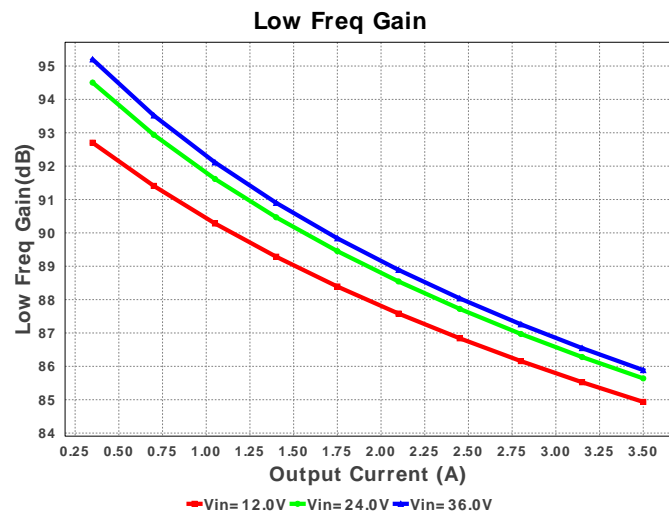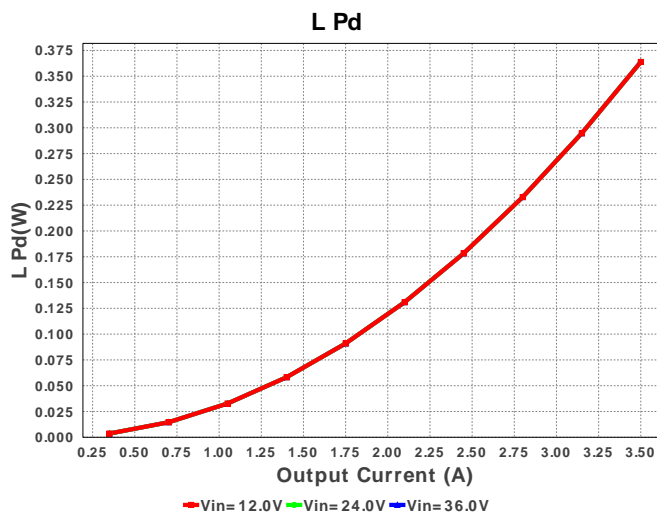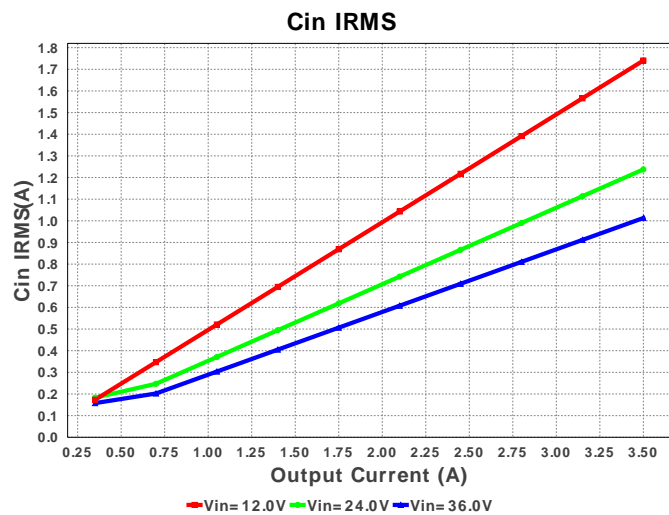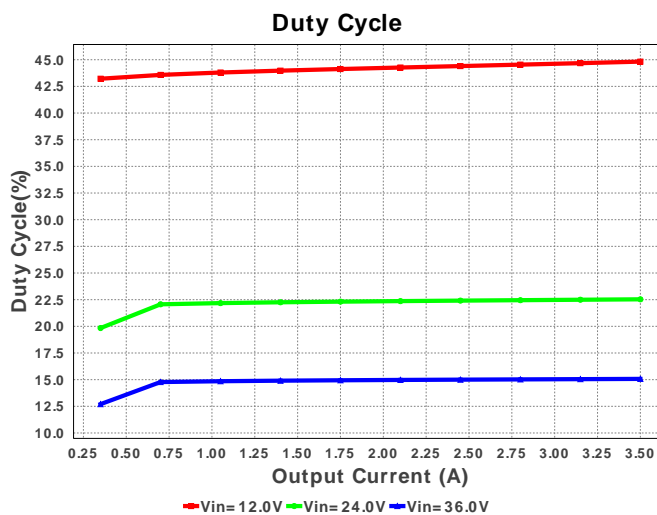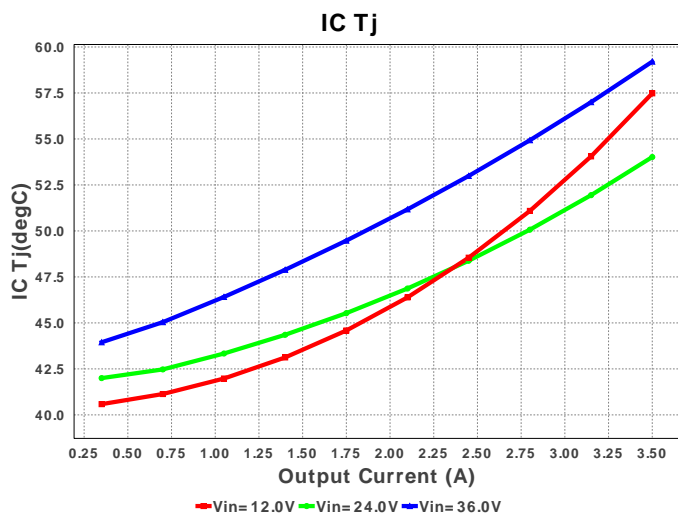


R-PDSO-G8 57 mm²



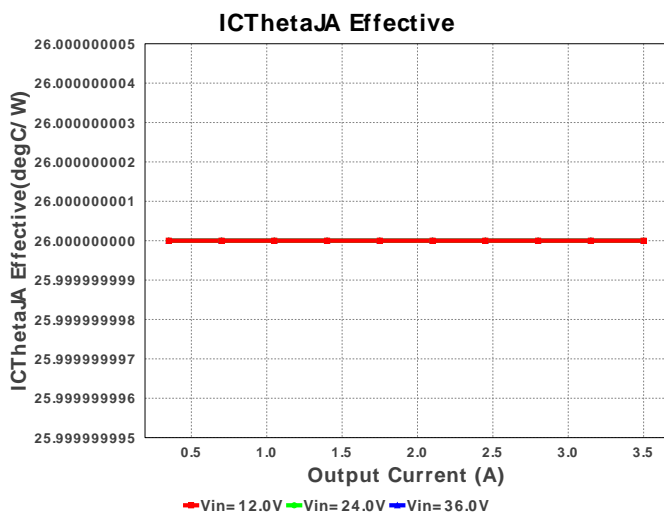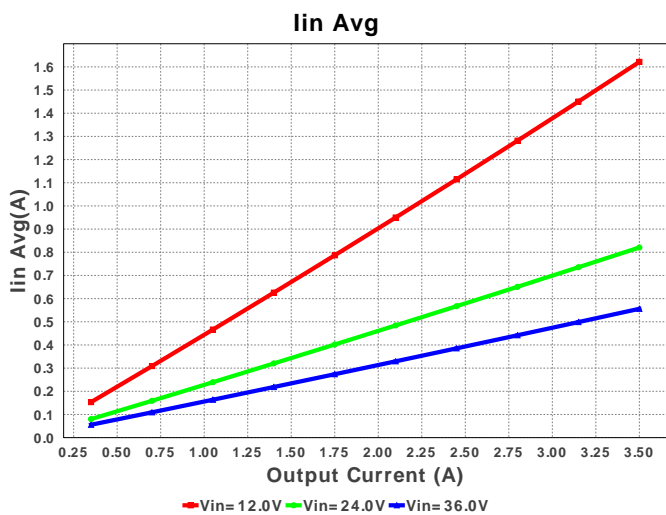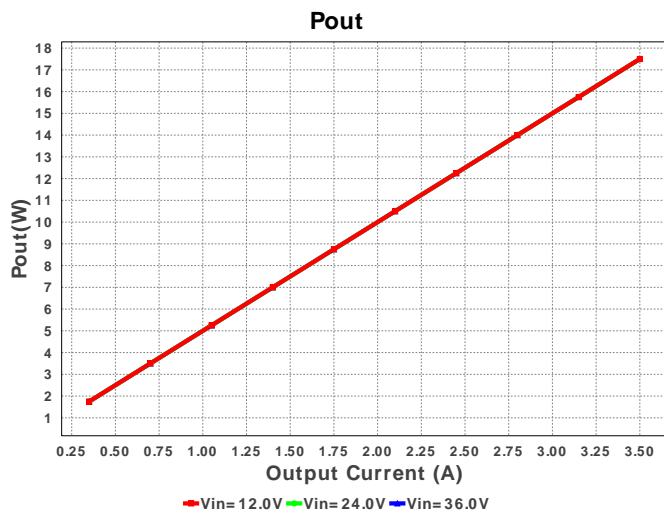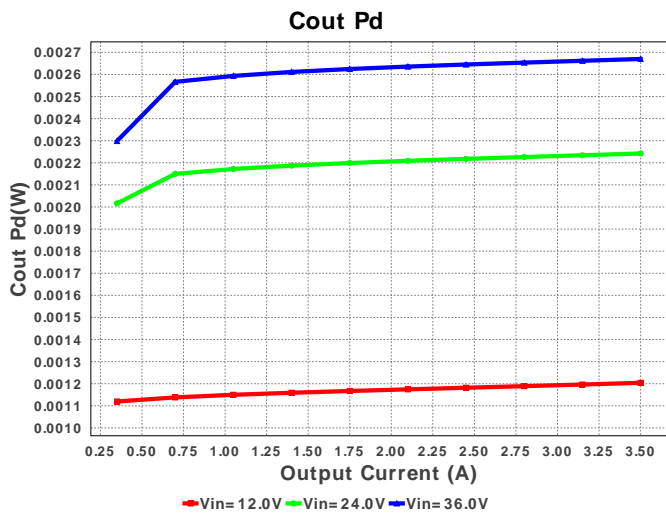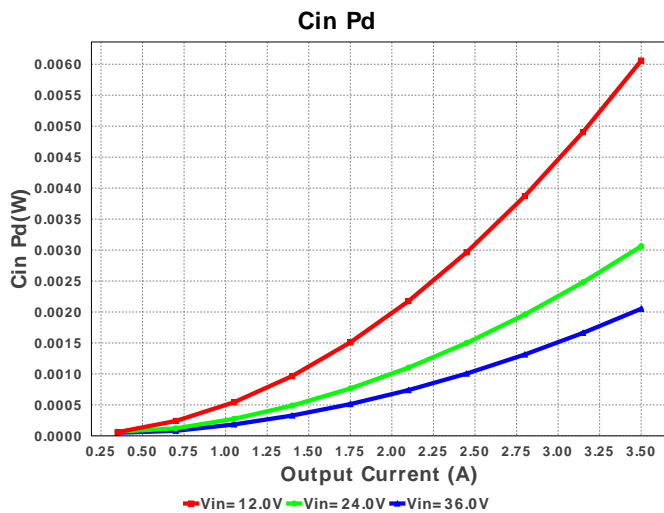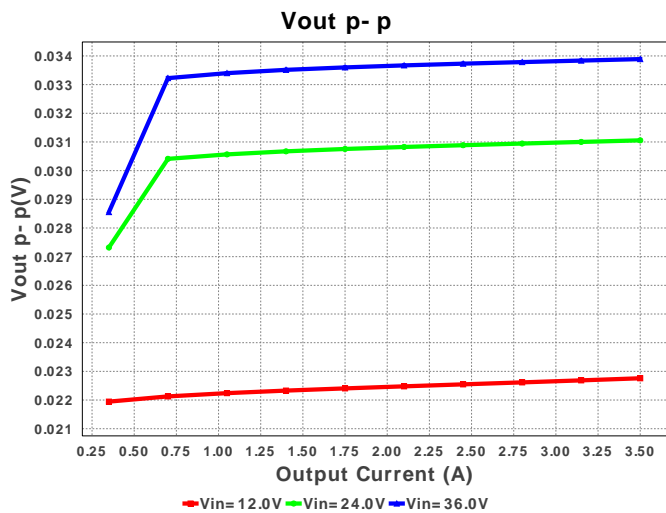

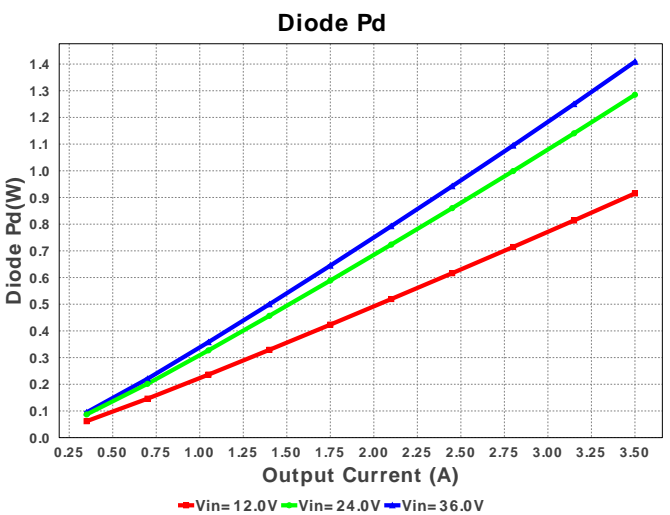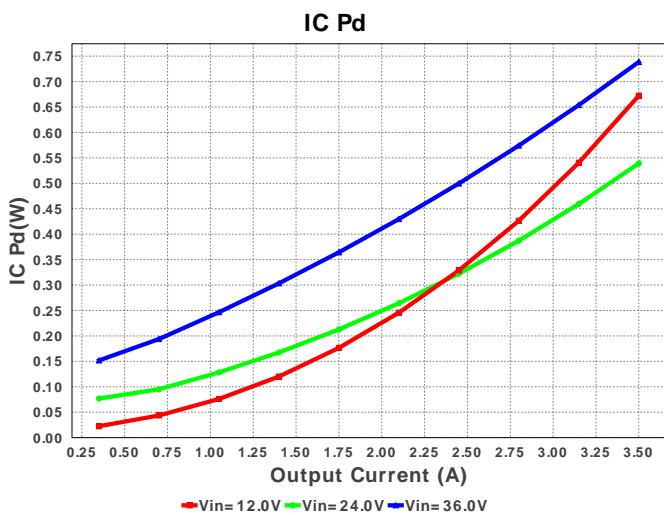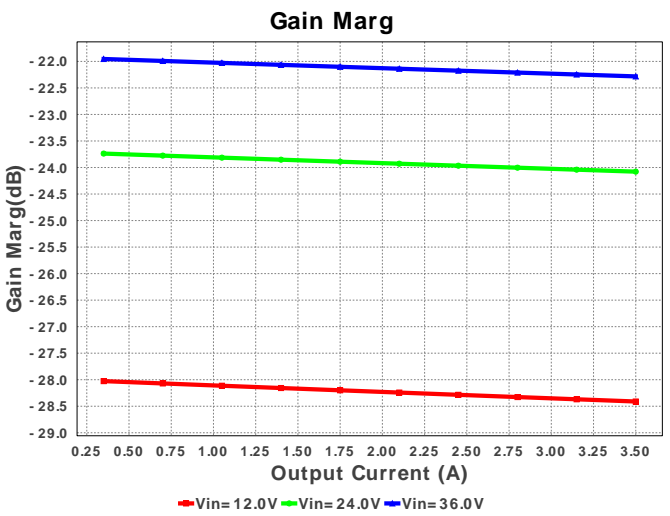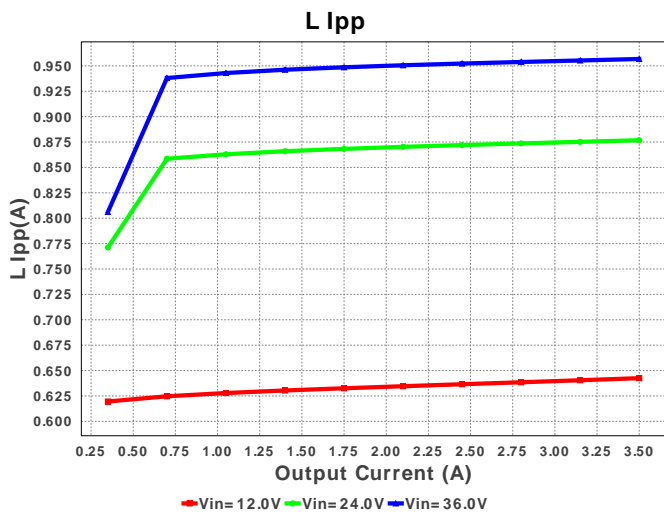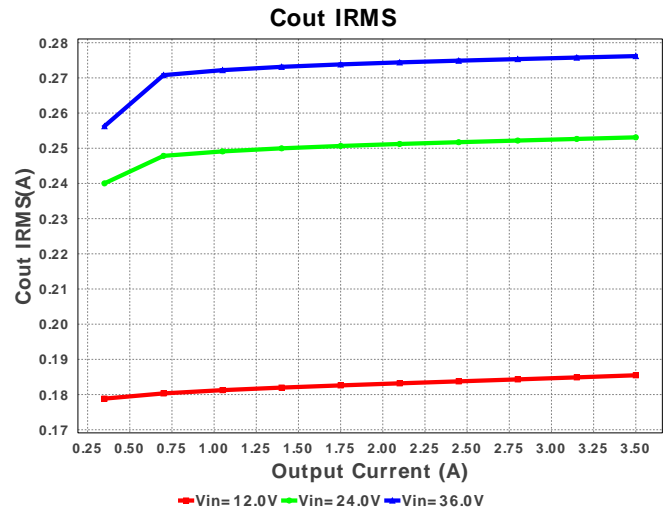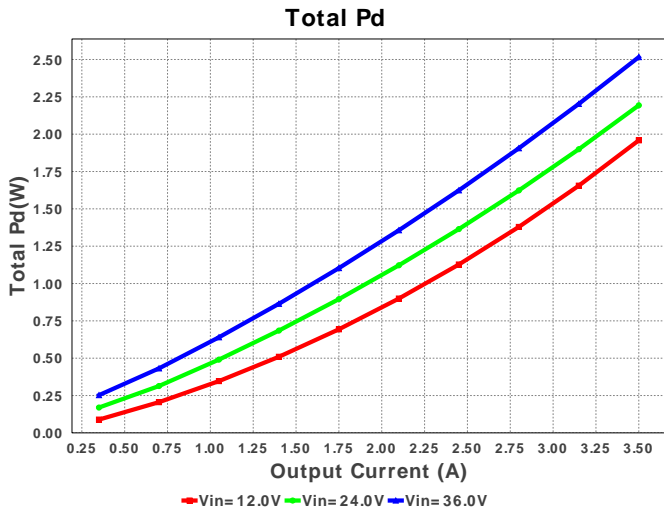

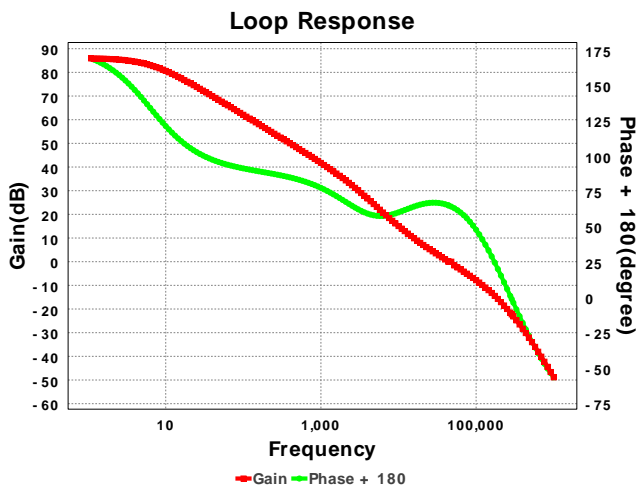

Operating Values

#	Name	Value	Category	Description
1.	Cin IRMS	1.013 A	Current	Input capacitor RMS ripple current
2.	Cout IRMS	276.192 mA	Current	Output capacitor RMS ripple current
3.	Iin Avg	556.0 mA	Current	Average input current
4.	L Ipp	956.76 mA	Current	Peak-to-peak inductor ripple current
5.	BOM Count	12	General	Total Design BOM count
6.	FootPrint	270.0 mm ²	General	Total Foot Print Area of BOM components
7.	Frequency	488.316 kHz	General	Switching frequency
8.	Pout	17.5 W	General	Total output power
9.	Total BOM	\$3.53	General	Total BOM Cost
10.	ICThetaJA Effective	26.0 degC/W	Op_Point	Effective IC Junction-to-Ambient Thermal Resistance
11.	Vout OP	5.0 V	Op_Point	Operational Output Voltage
12.	Cross Freq	44.172 kHz	Op_point	Bode plot crossover frequency
13.	Duty Cycle	15.071 %	Op_point	Duty cycle
14.	Efficiency	87.43 %	Op_point	Steady state efficiency
15.	Gain Marg	-22.283 dB	Op_point	Bode Plot Gain Margin
16.	IC Tj	59.204 degC	Op_point	IC junction temperature
17.	IOUT_OP	3.5 A	Op_point	Iout operating point
18.	Phase Marg	66.217 deg	Op_point	Bode Plot Phase Margin
19.	VIN_OP	36.0 V	Op_point	Vin operating point
20.	Vout p-p	5.211 mV	Op_point	Peak-to-peak output ripple voltage
21.	Cin Pd	2.052 mW	Power	Input capacitor power dissipation
22.	Cout Pd	2.67 mW	Power	Output capacitor power dissipation
23.	Diode Pd	1.409 W	Power	Diode power dissipation
24.	IC Pd	738.617 mW	Power	IC power dissipation
25.	L Pd	363.825 mW	Power	Inductor power dissipation
26.	Total Pd	2.516 W	Power	Total Power Dissipation
27.	Low Freq Gain	85.887 dB	Unknown	Gain at 10Hz

Design Inputs

#	Name	Value	Description
1.	Iout	3.5	Maximum Output Current
2.	Iout1	3.5	Output Current #1
3.	VinMax	36.0	Maximum input voltage
4.	VinMin	12.0	Minimum input voltage
5.	Vout	5.0	Output Voltage
6.	Vout1	5.0	Output Voltage #1
7.	base_pn	TPS54340	Texas Instruments Base Part Number
8.	source	DC	Input Source Type
9.	ta	40.0	Ambient temperature

Design Assistance

1. TPS54340 Product Folder : <http://www.ti.com/product/TPS54340> : contains the data sheet and other resources.

Texas Instruments' WEBENCH simulation tools attempt to recreate the performance of a substantially equivalent physical implementation of the design. Simulations are created using Texas Instruments' published specifications as well as the published specifications of other device manufacturers. While Texas Instruments does update this information periodically, this information may not be current at the time the simulation is built. Texas Instruments does not warrant the accuracy or completeness of the specifications or any information contained therein. Texas Instruments does not warrant that any designs or recommended parts will meet the specifications you entered, will be suitable for your application or fit for any particular purpose, or will operate as shown in the simulation in a physical implementation. Texas Instruments does not warrant that the designs are production worthy.

You should completely validate and test your design implementation to confirm the system functionality for your application prior to production.

Use of Texas Instruments' WEBENCH simulation tools is subject to [Texas Instruments' Site Terms and Conditions of Use](#). Prototype boards based on WEBENCH created designs are provided AS IS without warranty of any kind for evaluation and testing purposes and are subject to the terms of the [Evaluation License Agreement](#).