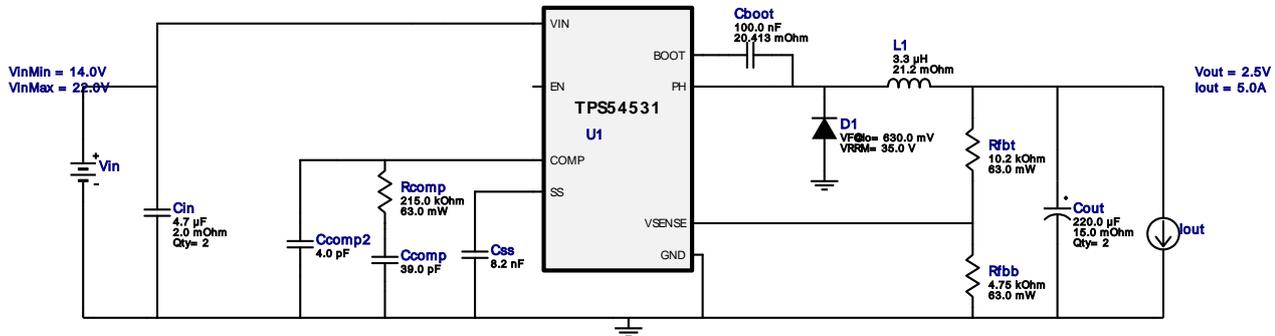
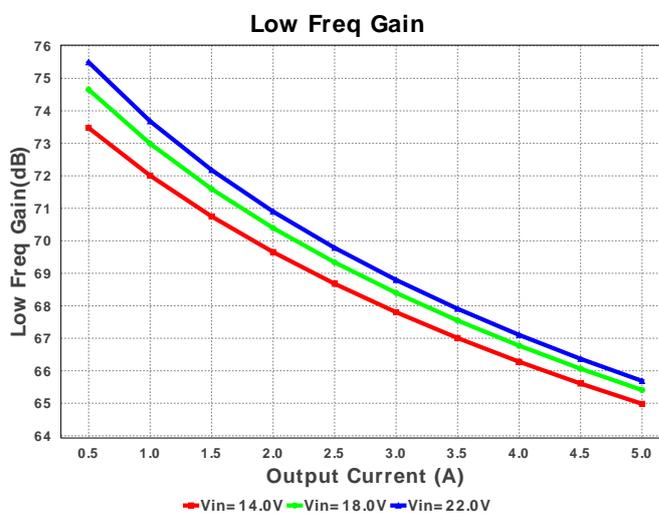
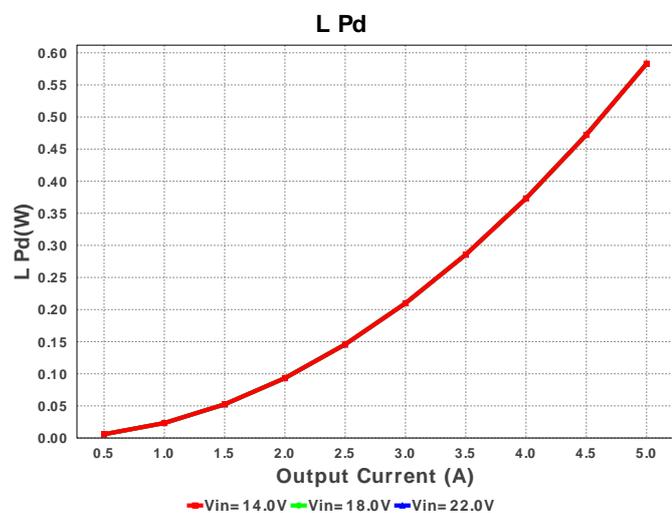
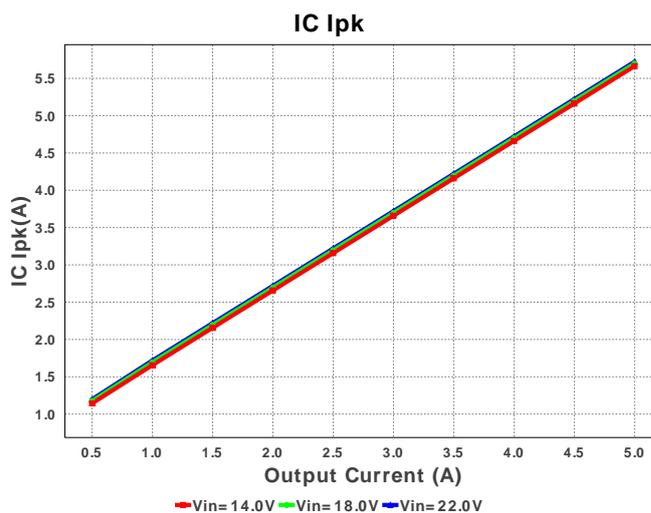
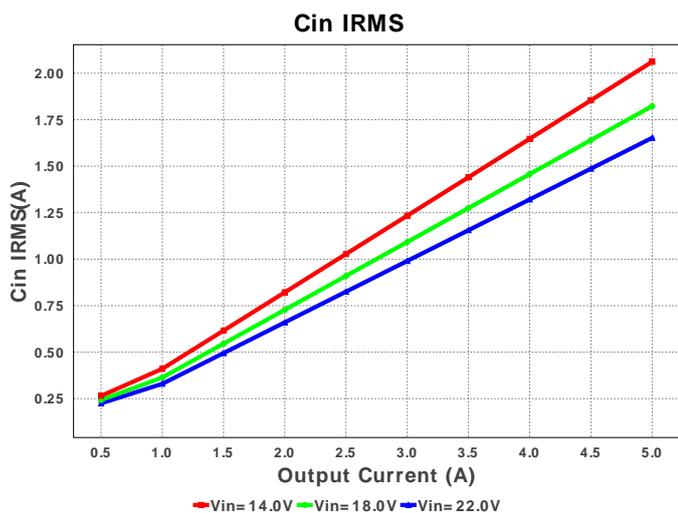
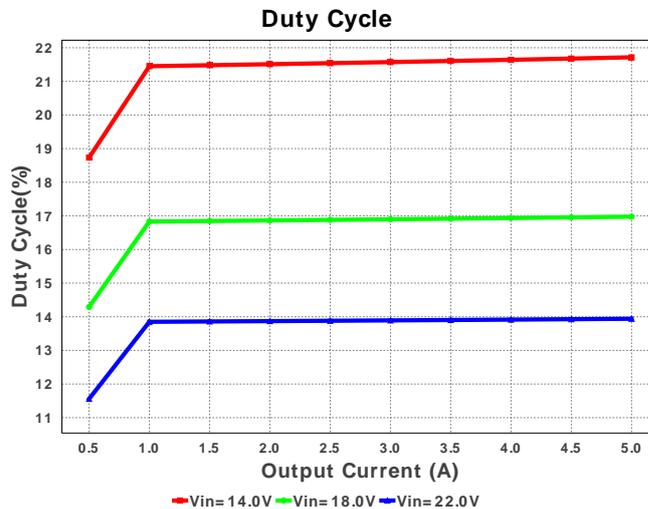
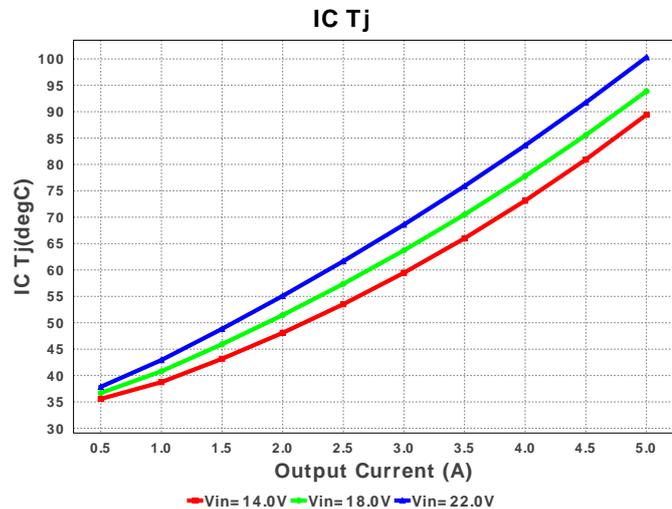








WEBENCH[®] Design Report







 Design : 4387439/1 TPS54531DDAR
 TPS54531DDAR 14.0V-22.0V to 2.50V @ 5.0A

Electrical BOM





#	Name	Manufacturer	Part Number	Properties	Qty	Price	Footprint
1.	Cboot	TDK	C1005X5R1A104K Series= X5R	Cap= 100.0 nF ESR= 20.413 mOhm VDC= 10.0 V IRMS= 0.0 A	1	\$0.01	0402 3 mm ²
2.	Ccomp	Yageo America	CC0805JRNPO9BN390 Series= C0G/NP0	Cap= 39.0 pF VDC= 50.0 V IRMS= 0.0 A	1	\$0.01	0805 7 mm ²
3.	Ccomp2	Yageo America	CC0805CRNP09BN4R0 Series= C0G/NP0	Cap= 4.0 pF VDC= 50.0 V IRMS= 0.0 A	1	\$0.01	0805 7 mm ²
4.	Cin	MuRata	GRM32ER71H475KA88L Series= X7R	Cap= 4.7 uF ESR= 2.0 mOhm VDC= 50.0 V IRMS= 5.35 A	2	\$0.29	1210 15 mm ²
5.	Cout	Panasonic	6SVPE220MW Series= 259	Cap= 220.0 uF ESR= 15.0 mOhm VDC= 6.3 V IRMS= 3.15 A	2	\$0.14	CAPSM_T_62_E61 53 mm ²
6.	Css	MuRata	GRM033R61A822KA01D Series= X5R	Cap= 8.2 nF VDC= 10.0 V IRMS= 0.0 A	1	\$0.01	0201 2 mm ²
7.	D1	Vishay-Semiconductor	MBRB1635PBF	VF@Io= 630.0 mV VRRM= 35.0 V	1	\$0.71	DDPAK 210 mm ²
8.	L1	Coilcraft	XAL5030-332MEB	L= 3.3 uH DCR= 21.2 mOhm	1	\$0.63	XAL5030 54 mm ²
9.	Rcomp	Vishay-Dale	CRCW0402215KFKED Series= CRCW..e3	Res= 215.0 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	0402 3 mm ²
10.	Rfbb	Vishay-Dale	CRCW04024K75FKED Series= CRCW..e3	Res= 4.75 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	0402 3 mm ²

#	Name	Manufacturer	Part Number	Properties	Qty	Price	Footprint
11.	Rfbt	Vishay-Dale	CRCW040210K2FKED Series= CRCW..e3	Res= 10.2 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	0402 3 mm ²
12.	U1	Texas Instruments	TPS54531DDAR	Switcher	1	\$0.75	 DDA0008E 57 mm ²

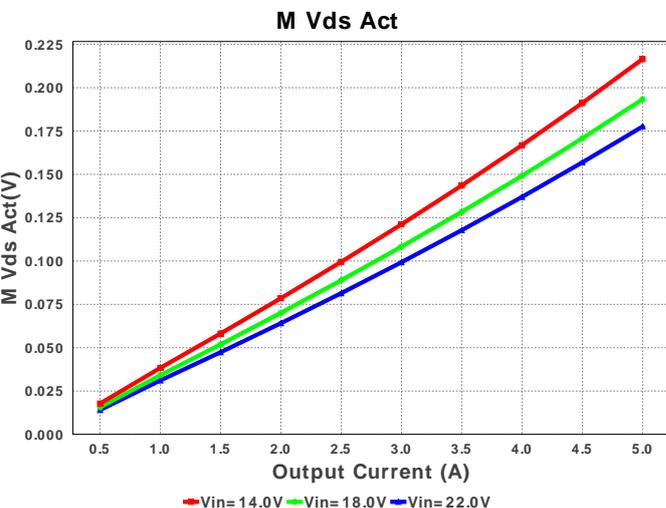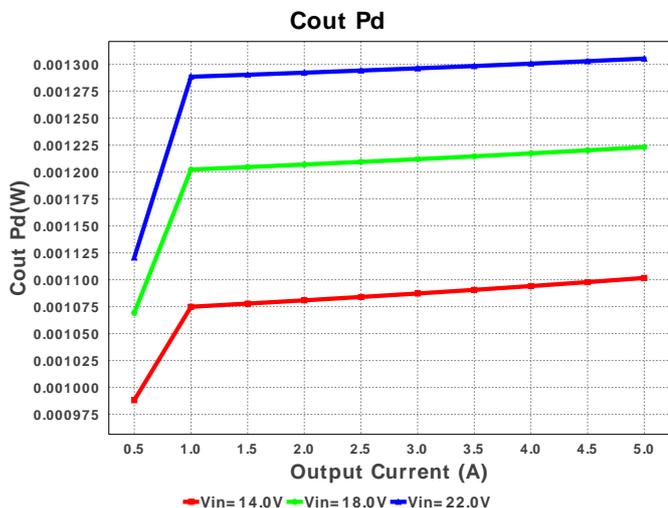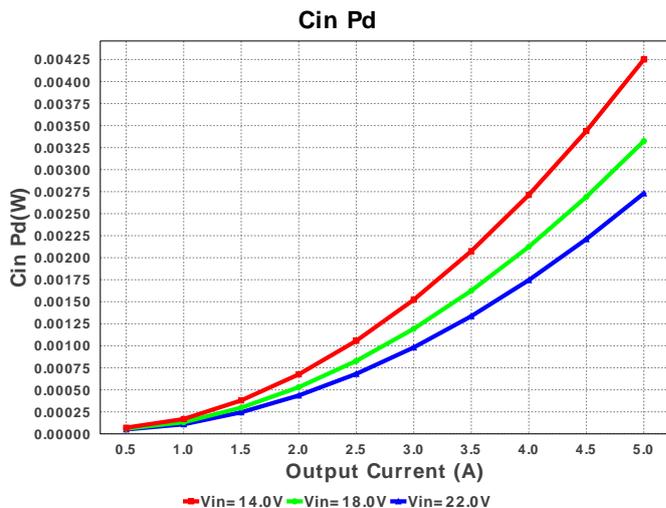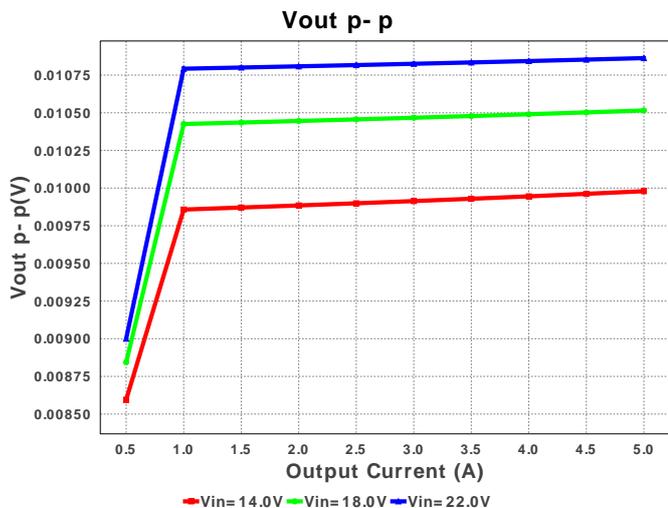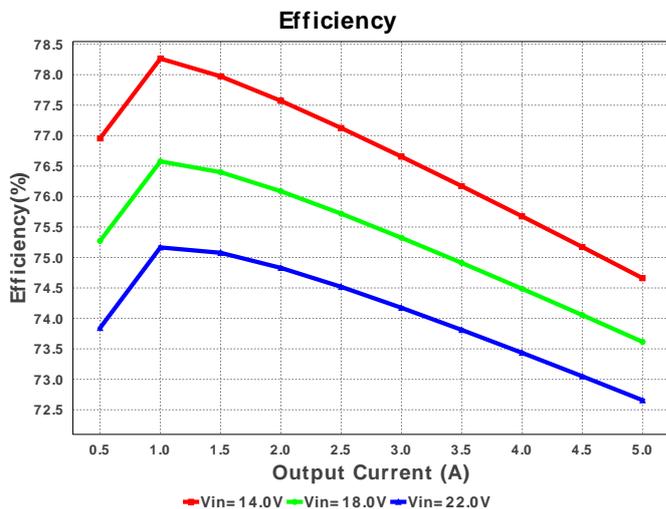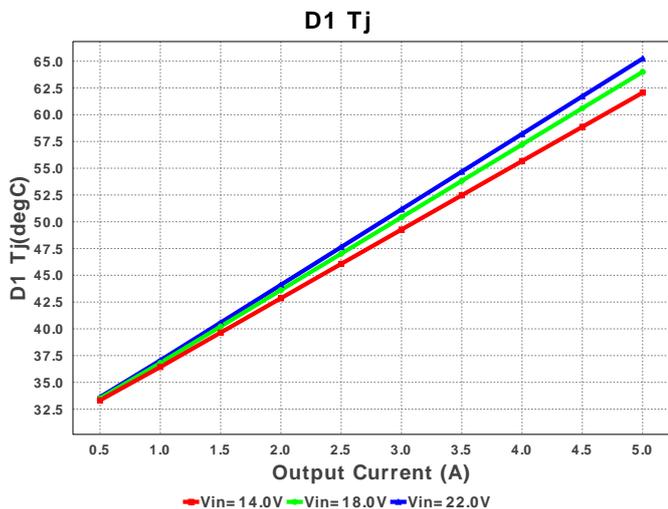

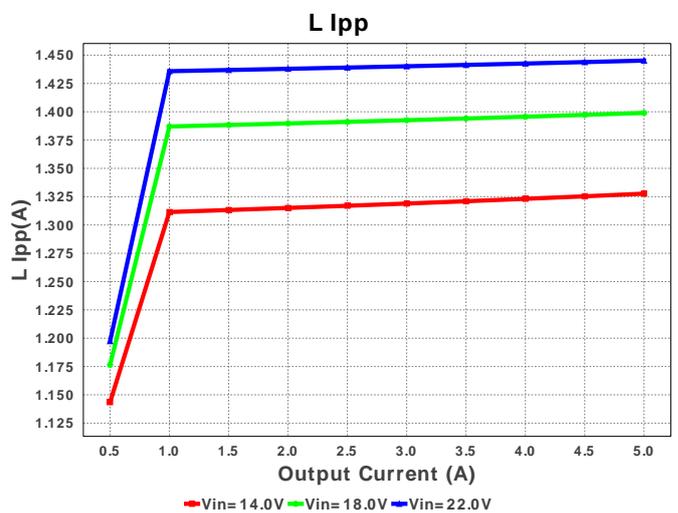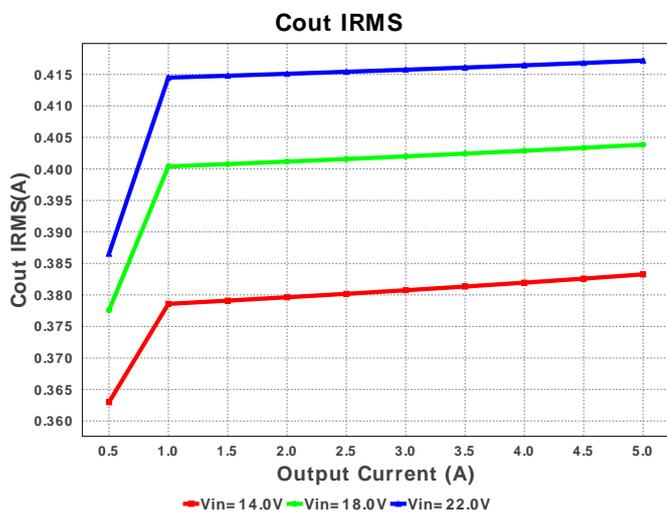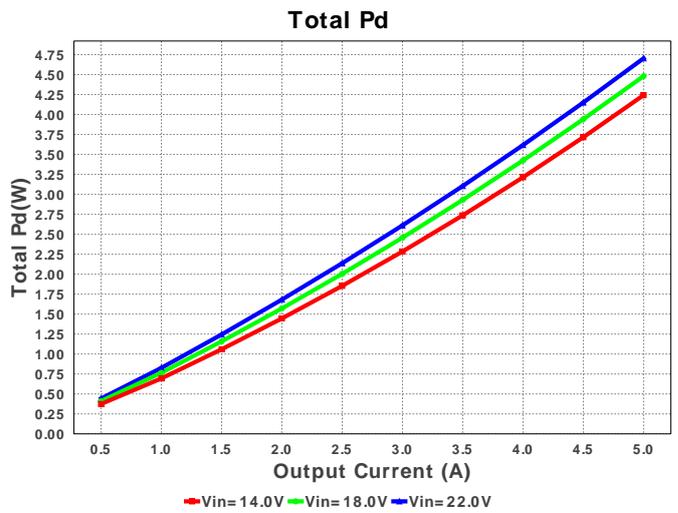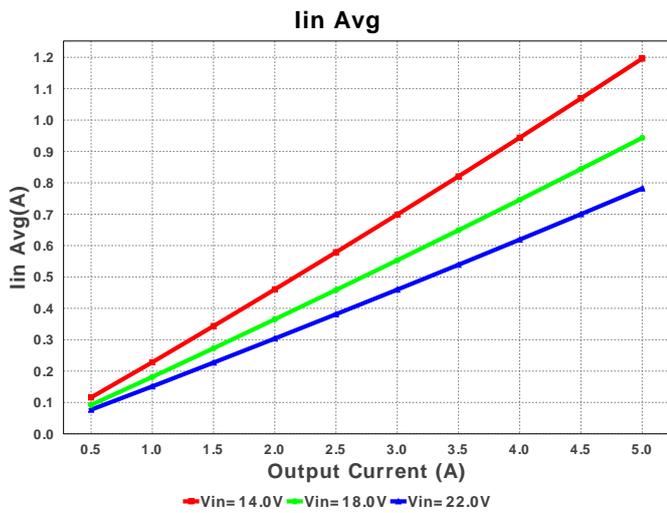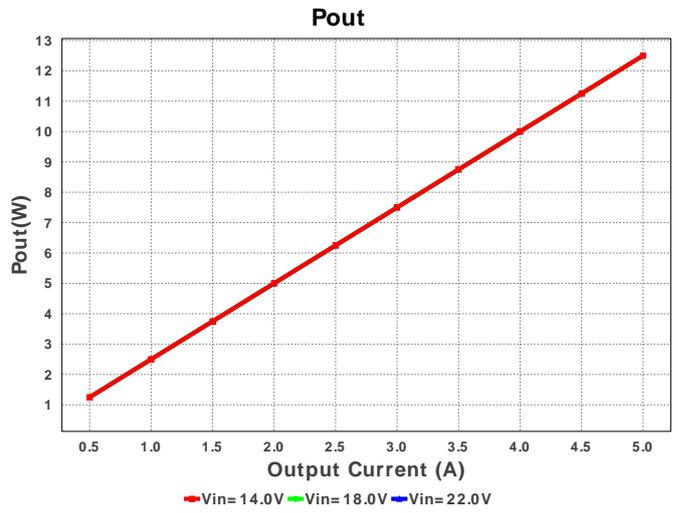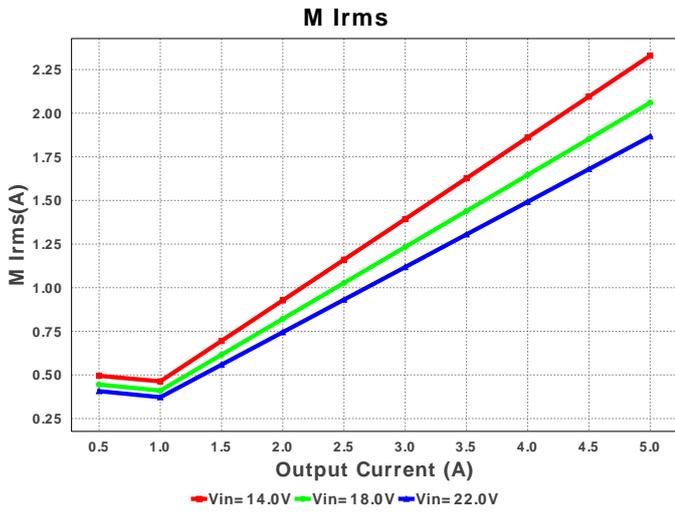



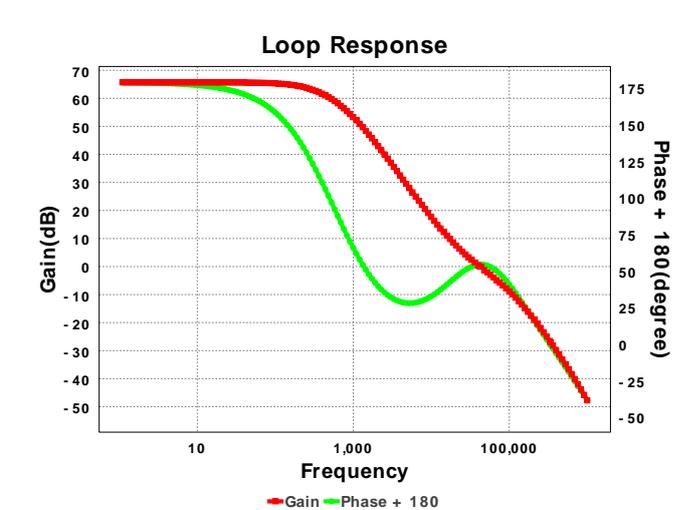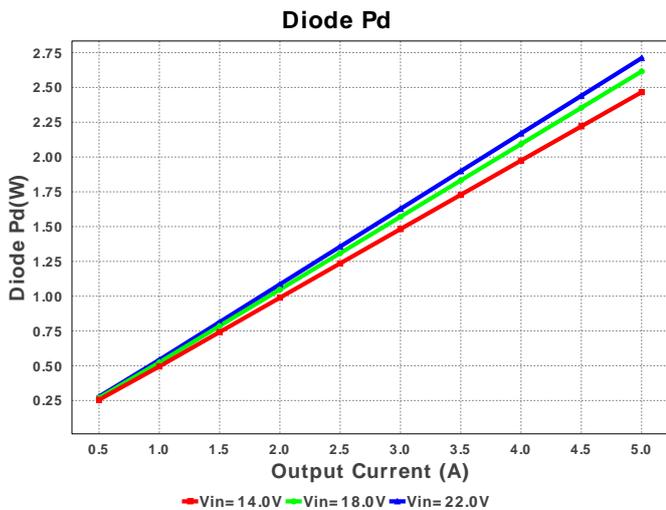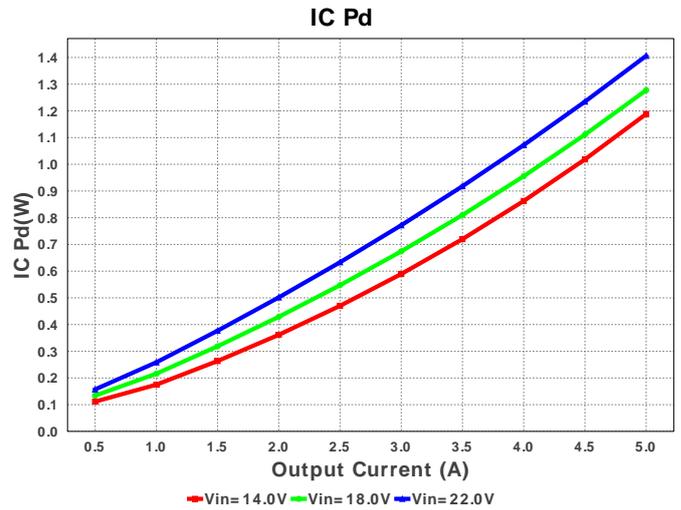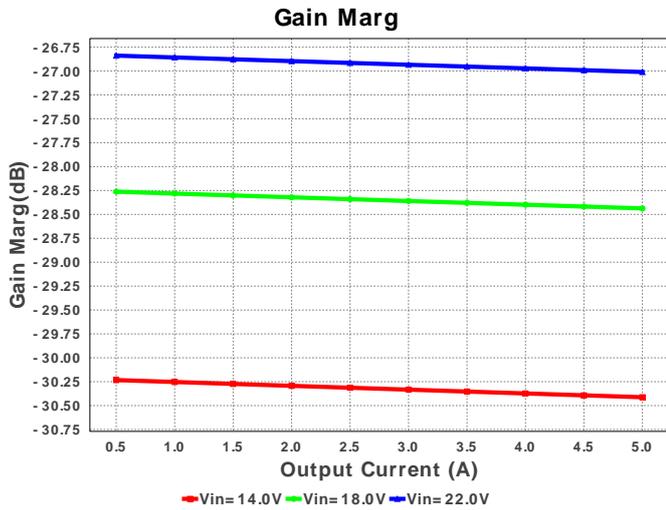

Operating Values

#	Name	Value	Category	Description
1.	Cin IRMS	1.652 A	Current	Input capacitor RMS ripple current
2.	Cout IRMS	417.193 mA	Current	Output capacitor RMS ripple current
3.	IC Ipk	5.723 A	Current	Peak switch current in IC
4.	Iin Avg	782.0 mA	Current	Average input current
5.	L Ipp	1.445 A	Current	Peak-to-peak inductor ripple current
6.	M Irms	1.867 A	Current	MOSFET RMS current
7.	BOM Count	14	General	Total Design BOM count
8.	FootPrint	485.0 mm ²	General	Total Foot Print Area of BOM components
9.	Frequency	570.0 kHz	General	Switching frequency
10.	M Vds Act	177.607 mV	General	Voltage drop across the MosFET
11.	Pout	12.5 W	General	Total output power
12.	Total BOM	\$3.02	General	Total BOM Cost
13.	D1 Tj	65.241 degC	Op_Point	D1 junction temperature
14.	Vout OP	2.5 V	Op_Point	Operational Output Voltage
15.	Cross Freq	42.058 kHz	Op_point	Bode plot crossover frequency
16.	Duty Cycle	13.941 %	Op_point	Duty cycle
17.	Efficiency	72.657 %	Op_point	Steady state efficiency
18.	Gain Marg	-27.01 dB	Op_point	Bode Plot Gain Margin
19.	IC Tj	100.308 degC	Op_point	IC junction temperature
20.	ICThetaJA	50.0 degC/W	Op_point	IC junction-to-ambient thermal resistance
21.	IOUT_OP	5.0 A	Op_point	Iout operating point
22.	Phase Marg	55.128 deg	Op_point	Bode Plot Phase Margin
23.	VIN_OP	22.0 V	Op_point	Vin operating point
24.	Vout p-p	10.863 mV	Op_point	Peak-to-peak output ripple voltage
25.	Cin Pd	2.73 mW	Power	Input capacitor power dissipation
26.	Cout Pd	1.305 mW	Power	Output capacitor power dissipation
27.	Diode Pd	2.711 W	Power	Diode power dissipation
28.	IC Pd	1.406 W	Power	IC power dissipation
29.	L Pd	583.0 mW	Power	Inductor power dissipation
30.	Total Pd	4.704 W	Power	Total Power Dissipation
31.	Low Freq Gain	65.688 dB	Unknown	Gain at 10Hz

Design Inputs

#	Name	Value	Description
1.	Iout	5.0	Maximum Output Current
2.	Iout1	5.0	Output Current #1
3.	VinMax	22.0	Maximum input voltage
4.	VinMin	14.0	Minimum input voltage
5.	Vout	2.5	Output Voltage
6.	Vout1	2.5	Output Voltage #1
7.	base_pn	TPS54531	Texas Instruments Base Part Number
8.	source	DC	Input Source Type
9.	ta	30.0	Ambient temperature

Design Assistance

1. TPS54531 Product Folder : <http://www.ti.com/product/TPS54531> : contains the data sheet and other resources.

Texas Instruments' WEBENCH simulation tools attempt to recreate the performance of a substantially equivalent physical implementation of the design. Simulations are created using Texas Instruments' published specifications as well as the published specifications of other device manufacturers. While Texas Instruments does update this information periodically, this information may not be current at the time the simulation is built. Texas Instruments does not warrant the accuracy or completeness of the specifications or any information contained therein. Texas Instruments does not warrant that any designs or recommended parts will meet the specifications you entered, will be suitable for your application or fit for any particular purpose, or will operate as shown in the simulation in a physical implementation. Texas Instruments does not warrant that the designs are production worthy.

You should completely validate and test your design implementation to confirm the system functionality for your application prior to production.

Use of Texas Instruments' WEBENCH simulation tools is subject to [Texas Instruments' Site Terms and Conditions of Use](#). Prototype boards based on WEBENCH created designs are provided AS IS without warranty of any kind for evaluation and testing purposes and are subject to the terms of the [Evaluation License Agreement](#).